 



Complete the waveform for the hardware design below

```
assign temp1 = a & b;
assign c = temp1;
assign d = a | b;
always@(posedge clk)
begin
  c<=d;
end
```

 **Solution:**



Write Verilog Program & TB for this circuit.




```
module program (clk, d, rst, y0;
input clk, d, rst;
output y;
reg y, n;
wire m;
assign m = d & (~y);
always@ (posedge clk or negedge rst)
begin
```


```
  if(~rst)
  begin
    n <= 0; y <= 0;
  end
  else
  begin
    n <= m; y <= n;
  end
end
endmodule
```

////////////////////////////////////
 
```
module program_tb;
reg clk, d, rst;
wire y;
program uut(clk, d, rst, y);
initial clk = 0;
always #10 clk = ~clk;
initial
begin
  rst = 0; d = 0;
  #16 rst = 1;
  #10 d = 1;
  #30 d = 0;
  #200 $stop;
end
endmodule
```



 Describe the following circuit in Verilog.



```
module decoder (e1, e2, e3, a, b, c, y);
input a, b, c, e1, e2, e3;
output [7:0] y;
wire m;
assign m = ~e1 & e2 & e3;
assign y[0] = ~((~c & ~b & ~a) & m);
```

```
assign y[1] = ~((~c & ~b & a) & m);
assign y[2] = ~((~c & b & ~a) & m);
assign y[3] = ~((~c & b & a) & m);
assign y[4] = ~((c & ~b & ~a) & m);
assign y[5] = ~((c & ~b & a) & m);
assign y[6] = ~((c & b & ~a) & m);
assign y[7] = ~((c & b & a) & m);
endmodule
```

////////////////////////////////////

```
module decoder_tb;
reg e1, e2, e3, a, b, c;
wire [7:0] y;
decoder uut(e1, e2, e3, a, b, c, y);
initial
```

```
begin
  {e1, e2, e3} = 3'b111;
  {c, b, a} = 3'b111;
  #10 {e1, e2, e3} = 3'b011;
```

```
{c, b, a} = 3'b000;
```

```
#10 {c, b, a} = 3'b001;
```

```
#10 {c, b, a} = 3'b010;
```

```
#10 {c, b, a} = 3'b011;
```

```
#10 {c, b, a} = 3'b100;
```


```
#10 {c, b, a} = 3'b101;
```

```
#10 {c, b, a} = 3'b110;
```

```
#10 {c, b, a} = 3'b111;
```

```
#50 $stop;
```

```
end
endmodule
```

 

Design 3-bit Ripple Carry Adder

```
module fulladder(a, b, cin, cout, s);
```

```
input a, b, cin;
```

```
output cout, s;
```

```
assign s = a ^ b ^ cin;
```

```
assign cout = ((a^b)&cin) | (a&b);
```

```
endmodule
```

////////////////////////////////////

```
module ripplecarryadder3(a, b, cin, cout, s);
```

```
input [2:0] a, b;
```

```
input cin;
```

```
output [2:0] s;
```

```
output cout;
```

```
wire [1:0] m;
```

```
fulladder g1(.a(a[0]), .b(b[0]), .cin(cin), .cout(m[0]), .s(s[0]));
```

```
fulladder g2(.a(a[1]), .b(b[1]), .cin(m[0]), .cout(m[1]), .s(s[1]));
```

```
fulladder g3(.a(a[2]), .b(b[2]), .cin(m[1]), .cout(s[2]));
```

```
endmodule
```

////////////////////////////////////

```
module ripplecarryadder3_tb;
```

```
reg [2:0] a, b;
```

```
reg cin;
```

```
wire[2:0] s;
```

```
wire cout;
```

```
ripplecarryadder3 uut(a, b, cin, cout, s);
```

```
initial
```

```
begin
```

```
  a = 0; b = 0; c = 0;
```

```
  #10 a = 4; b = 5;
```

```
  #10 a = 6; b = 6;
```

```
  #10 a = 0; b = 2; cin = 1;
```


```
  #10 a = 3; b = 3;
```

```
  #10 a = 5; b = 2;
```

```
  #20 $stop;
```

```
end
```

```
endmodule
```

 

Design 4-bit left shift registers in Verilog with serial data input and

serial data output.

```
module shift_L4(clk, din, dout);
```

```
input clk, din; output dout;
```

```
reg [3:0] q; assign dout = q[3];
```

```
always@(posedge clk)
```

```
begin
```

```
  //q <= { q[2:0], din };
```

```
  q[3] <= q[2];
```

```
  q[2] <= q[1];
```

```
  q[1] <= q[0];
```

```
  q[0] <= din;
```

```
end
```

```
endmodule
```

//Right shift//

```
module shift_R4(clk, din, dout);
```

```
input clk, din;
```

```
output dout;
```

```
reg [3:0] q;
```

```
assign dout = q[0];
```

```
always@(posedge clk)
```


```
begin
```

```
  q <= { din, q[3:1] };
```

```
end
```

```
endmodule
```

 Design the following finite state machine (mealy)



```
module fsm(clk, reset, a, y);
```

```
input clk, reset, a;
```

```
output y; reg y;
```

```
parameter s0 = 2'b00, s1=2'b01, s2=2'b10;
```

```
reg [1:0] cs, ns;
```

```
always@(posedge clk or posedge reset)
```

```
begin
```

```
  if(reset) cs <= s0;
```

```
  else cs <= ns;
```

```
end
```

```
always@(cs or a)
```

```
begin
```

```
  case(cs) s0: if(a) ns = s1;
```

```
  else ns = s0; s1: if(~a) ns = s2;
```

```
  else ns = s0; s2: if(a) ns = s2;
```

```
  else ns = s1; default: ns = s0;
```

```
  endcase
```

```
end
```

```
always@(cs or a)
```

```
begin
```

```
  case(cs) s0: y = 0;
```

```
  s1: if(a) y = 1; else y = 0;
```

```
  s2: y = 1;
```


```
  default: y = 0;
```

```
  endcase
```

```
end
```

```
endmodule
```

 Design the following finite state machine (moore)



```
module fsm ( clk, reset, a, y );
```

```
input clk, reset, a;
```

```
output [1:0] y;
```

```
reg [1:0] y;
```

```
parameter s0 = 3'b000, s1=3'b001, s2=3'b010, s3=3'b011,
```

```
s4=3'b100; reg [2:0] cs, ns;
```

```
always@(posedge clk or negedge reset)
```

```
begin
```

```
  if(~reset) cs <= s0;
```

```
  else cs <= ns;
```

```
end
```

```
always@(cs or a)
```

```
begin
```

```
  case(cs) s0: if(a) ns = s1;
```

```
  else ns = s0; s1: if(~a) ns = s2;
```

```
  else ns = s0; s2: if(a) ns = s3;
```

```
  else ns = s0; s3: if(a) ns = s4;
```

```
  else ns = s2; s4: if(a) ns = s1;
```

```
  else default:
```

```
  endcase
```

```
end
```

```
always@(cs)
```

```
begin
```

```
  ns = s2; ns = s0;
```

```
  case(cs)
```

```
  s0: y = 2'b00;
```

```
  s1: y = 2'b11;
```

```
  s2: y = 2'b01;
```

```
  s3: y = 2'b11;
```

```
  s4: y = 2'b10;
```

```
  default: y = 2'b00;
```

```
  endcase
```

```
end
```

```
endmodule
```

### Half Adder.v


```
module halfadder(sout,cout,a,b);
output sout,cout;
input a,b;
assign sout=a^b;
assign cout=(a&b);
endmodule
```

### Half Adder\_TB.v

```
module halfadder_tb; //test batch
reg ta, tb;
wire tcout, tsum;
halfadder u1 (.a(ta), .b(tb), .cout(tcout), .sum(tsum)); //name
association
initial
begin
    ta = 0; tb = 0;
    #10; ta = 0; tb = 1;
    #10;
    ta = 1; tb = 0;
    #10;
    ta = 1; tb = 1;
    #10 $stop;
end
endmodule
```

Inputs		Outputs	
A	B	C <sub>out</sub>	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

 Logic Equations:  
 $C_{out} = A \oplus B$   
 $Sum = A \oplus B$



### Full Adder.v


```
module fulladder(sout,cout,a,b,cin);
output sout,cout;
input a,b,cin;
assign sout=(a^b^cin);
assign cout=((a&b)|(a&cin)|(b&cin));
endmodule
```

### Full Adder\_TB.v

```
module fulladder_tb;
reg a, b, cin;
wire cout, sum;
fulladder u3(.a(a), .b(b), .cin(cin), .cout(cout), .sum(sum));
initial
begin
    a = 0; b = 0; cin = 0;
    #10; a = 0; b = 0; cin = 1;
    #10; a = 0; b = 1; cin = 0;
    #10; a = 0; b = 1; cin = 1;
    #10; a = 1; b = 0; cin = 0;
    #10; a = 1; b = 0; cin = 1;
    #10; a = 1; b = 1; cin = 0;
    #10; a = 1; b = 1; cin = 1;
    #10 $stop;
end
endmodule
```

Inputs			Outputs	
A	B	C <sub>in</sub>	C <sub>out</sub>	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 Logic Equations:  
 $Sum = A \oplus B \oplus C_{in}$   
 $C_{out} = (A \oplus B) C_{in} + A \oplus B$



### Multiply4bits.v

```
module multiply4bits(pro,a,b);
output [7:0]pro;
input [3:0]a;
input [3:0]b;
assign pro[0]=(a[0] & b[0]);
wire x1,x2,x3,x4,x5,x6,x7,x8,x9,x10,x11,x12,x13,x14,x15,x16,x17;
halfadder halfadder1(pro[1],x1,(a[1] & b[0]),(a[0] & b[1]));
fulladder fulladder2(x2,x3,a[1]&b[1],(a[0]&b[2]),x1);
fulladder fulladder3(x4,x5,(a[1]&b[2]),(a[0]&b[3]),x3);
halfadder halfadder4(x6,x7,(a[1]&b[3]),x5);
halfadder halfadder5(x8,x9,x10,x11,x12,(a[2]&b[0]));
fulladder fulladder6(x13,x14,x15,x16,x17,x12);
fulladder fulladder7(x9,x8,x7,(a[2]&b[3]),x17);
halfadder halfadder8(pro[3],x12,x14,(a[3]&b[0]));
fulladder fulladder9(x10,x9,(a[3]&b[2]),x11);
fulladder fulladder10(x13,x15,x16,x17,x14,x11);
endmodule
```

### Multiply4bits\_TB.v

```
module multiply4bits_tb;
reg [3:0]a;
reg [3:0]b;
wire [7:0]pro;
multiply4bits u1(.a(a), .b(b), .pro(pro));
initial
begin
    a = 4'b0000; b = 4'b0000;
    #10;
    a = 4'b0001; b = 4'b0001;
    #10;
    a = 4'b0010; b = 4'b0010;
    #10;
    a = 4'b0011; b = 4'b0011;
    #10;
    a = 4'b0100; b = 4'b0100;
    #10;
    a = 4'b0101; b = 4'b0101;
    #10;
    a = 4'b0110; b = 4'b0110;
    #10;
    a = 4'b0111; b = 4'b0111;
    #10;
    a = 4'b1000; b = 4'b1000;
    #10;
    a = 4'b1001; b = 4'b1001;
    #10;
    a = 4'b1010; b = 4'b1010;
    #10;
    a = 4'b1011; b = 4'b1011;
    #10;
    a = 4'b1100; b = 4'b1100;
    #10;
    a = 4'b1101; b = 4'b1101;
    #10;
    a = 4'b1110; b = 4'b1110;
    #10;
    a = 4'b1111; b = 4'b1111;
    #10; $stop;
end
endmodule
```

Inputs		Outputs
A[3:0]	B[3:0]	Pro[7:0]
0000	0000	00000000
0001	0001	00000001
0010	0010	00000100
0011	0011	00001001
0100	0100	00010000
0101	0101	00011001
0110	0110	00110001
0111	0111	00111001
1000	1000	01000000
1001	1001	01010001
1010	1010	01100100
1011	1011	01111001
1100	1100	10010000
1101	1101	10101001
1110	1110	11000100
1111	1111	11100001

Use Verilog to design a finite state machine to recognize the sequence 0110.

### Analysis:


S\_idle: does not detect anything  
S1: detect 0  
S2: detect 01  
S3: detect 011  
S4: detect 0110

### State Table:

Current State	A	Next state	Y
S_idle	0	S1	0
	1	S_idle	0
S1	0	S1	0
	1	S2	0
S2	0	S1	0
	1	S3	0
S3	0	S4	1
	1	S_idle	0
S4	0	S1	0
	1	S2	0

### Final Solution:

State Diagram:

 

```
module fsm_detector(reset, clk, a, y);
input reset, a, clk;
output y;
reg y;
parameter s_idle = 3'b000, s1=3'b001, s2=3'b010, s3=3'b011, s4=3'b100;
reg [2:0] cs, ns;
always@ (posedge clk or posedge reset)
begin
    if(reset) cs <= s_idle;
    else cs <= ns;
end
always@(cs or a)
begin
    case(cs)
        s_idle: if(a) ns = s_idle;
        else ns = s1;
        s1: if(a) ns = s2;
        else ns = s1;
        s2: if(a) ns = s3;
        else ns = s1;
        s3: if(~a) ns = s4;
        else ns = s_idle;
        s4: if(a) ns = s2;
        else ns = s1;
        default: ns = s_idle;
    endcase
end
always@(cs or a)
begin
    case(cs)
        s_idle: y = 0;
        s1: y=0;
        s2: y=0;
        s3: if(~a) y=1;
        else y=0;
        s4: y=0;
        default: y = 0;
    endcase
end
endmodule
```

### D-Flip-Flop

module dffa ( reset, clk, load, da, qa);

input reset, clk, load;

input [3:0] da;

output [3:0] qa;

reg [3:0] qa;

always@(posedge clk or posedge reset)

begin

if (reset)

qa <= 4'b0000;

else if (load)

qa <= da;

end

endmodule

`timescale 1ns / 1ps

module dffa\_tb;

// Inputs

reg reset;

reg clk;

reg load;

reg [3:0] da;

// Outputs

wire [3:0] qa;

// Instantiate the Unit Under Test (UUT)

dffa uut (

.reset(reset),

.clk(clk),

.load(load),

.da(da),

.qa(qa)

);

//continuous 20 sec clk

always

begin

clk = 1'b1;

#10;

clk = 1'b0;

#10;

end

initial begin

// Initialize Inputs

load = 1'b1;

da = 1'b1;

reset = 1'b0;

#20;

load = 1'b0;

da = 1'b0;

reset = 1'b0;

#20;

load = 1'b0;

da = 1'b1;

reset = 1'b1;

#20;

load = 1'b1;

da = 1'b1;

reset = 1'b0;

#20

// Wait 100 ns for global reset to finish

\$stop;

// Add stimulus here

endmodule