

**Started on** Wednesday, 14 December 2016, 10:11 AM

**State** Finished

**Completed on** Wednesday, 14 December 2016, 12:11 PM


**Time taken** 1 hour 59 mins

**Grade** 97.50 out of 100.00

**Question 1**

Correct

Mark 10.00 out of 10.00

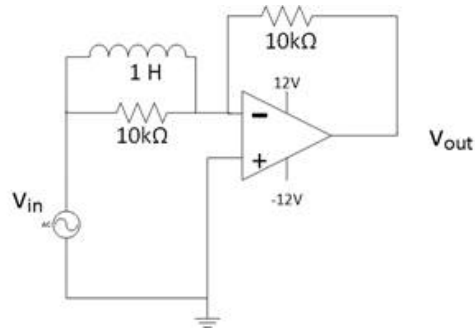

Q1k

Given  $V_{in} = 8 \cos(20,000t)$ .

What is the steady state output  $V_{out}$  ?

State your answer in the rectangular form Real + j Imaginary.

$V_{out} =$   ✓ + j  ✓ V


**Correct**

Marks for this submission: 10.00/10.00.

**Question 2**

Partially correct

Mark 12.50 out of 15.00

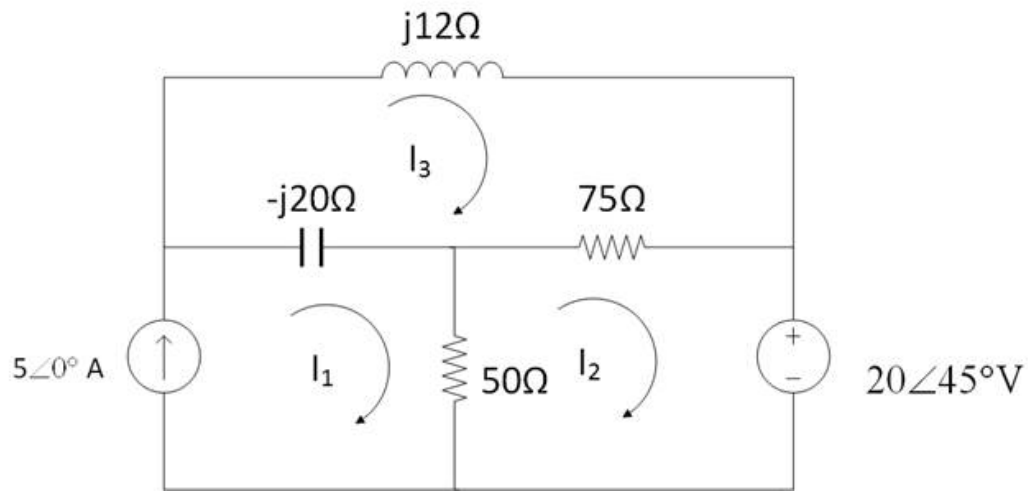

Q2d

Find the three mesh currents.

State your answer in the rectangular form Real + j Imaginary.

$$I_1 = 5 + j 0 \text{ Amps}$$


$$I_2 = 5.04 + j 1.2 \text{ Amps}$$

$$I_3 = 5.26 + j -2.21 \text{ Amps}$$

**Partially correct**Marks for this submission: 12.50/15.00. Accounting for previous tries, this gives **12.50/15.00**.**Question 3**

Correct

Mark 15.00 out of 15.00

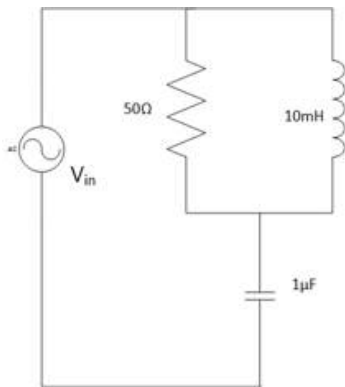

Q3a

$$\text{Given } V_{in} = 22 \cos(10,000 t)$$

Find the steady state phasor current through the 50 Ω (Ohm) resistor.

State your answer with the smallest appropriate positive angle.


$$I_{50\Omega} \text{ (polar form)} = \text{Magnitude } .22 \text{ Phase } 90^\circ \text{ (Degree) Amps}$$

**Correct**

Marks for this submission: 15.00/15.00.

**Question 4**

Correct

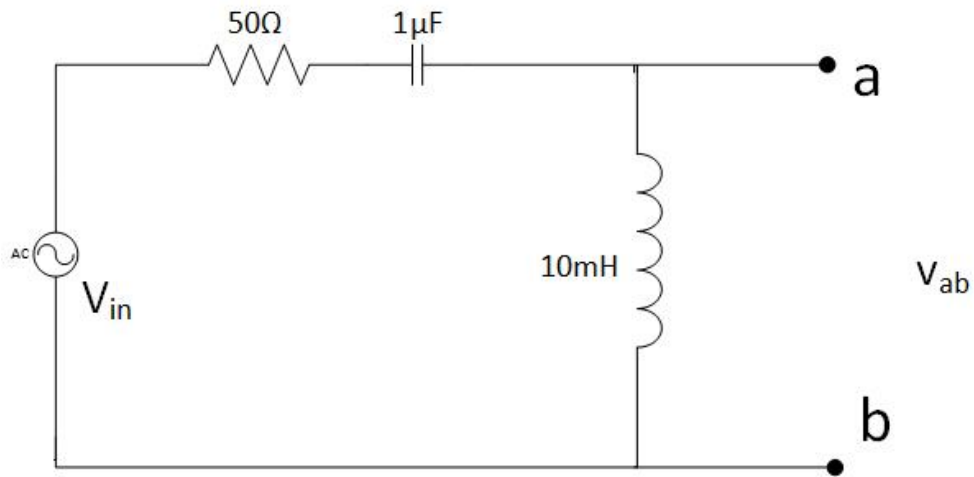Mark 15.00 out of  
15.00

Q4a

Given  $V_{in} = 22 \cos(10,000 t)$ 

Find the Thévenin phasor equivalent of this circuit.


 $Z_{Th}$  (rectangular form) =  ✓ + j  ✓  $\Omega$  (Ohm) $V_{Th}$  (rectangular form) =  ✓ + j  ✓ V**Correct**

Marks for this submission: 15.00/15.00.

**Question 5**

Correct

Mark 10.00 out of 10.00

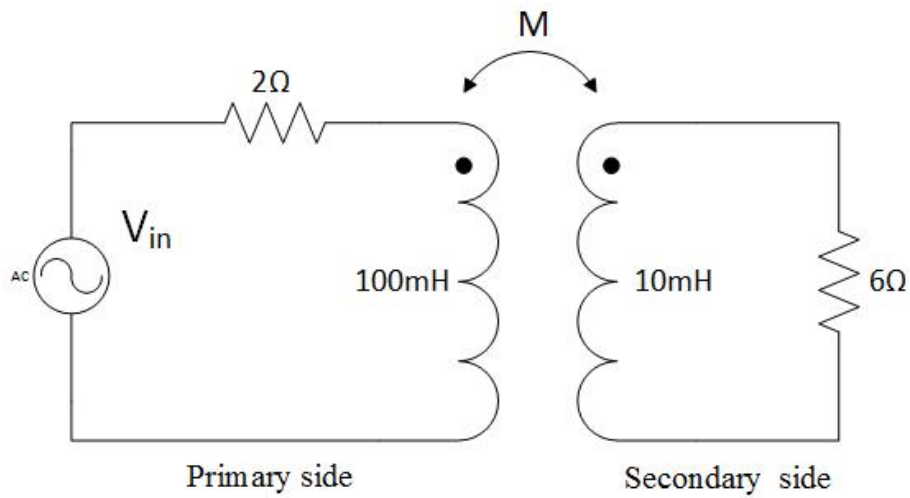

Q5b

Given  $V_{in} = 240 \cos(377t) \text{ V}_{\text{rms}}$  and the coefficient of coupling  $k = 0.8$

a) Find the mutual inductance between the two windings.

$M =$   ✓ mH (milli H)

b) Find the magnitude of the reflected impedance from the secondary side to the primary (source) side.

$|Z_r| =$   ✓  $\Omega$  (Ohms)

c) Find the current in the primary side.

State as positive current magnitude and smallest appropriate negative angle.

$|I_1| =$   ✓  $\text{A}_{\text{rms}}$       Angle  $I_1 =$   ✓  $^\circ$  (Degree)


**Correct**

Marks for this submission: 10.00/10.00.

**Question 6**

Correct

Mark 10.00 out of 10.00

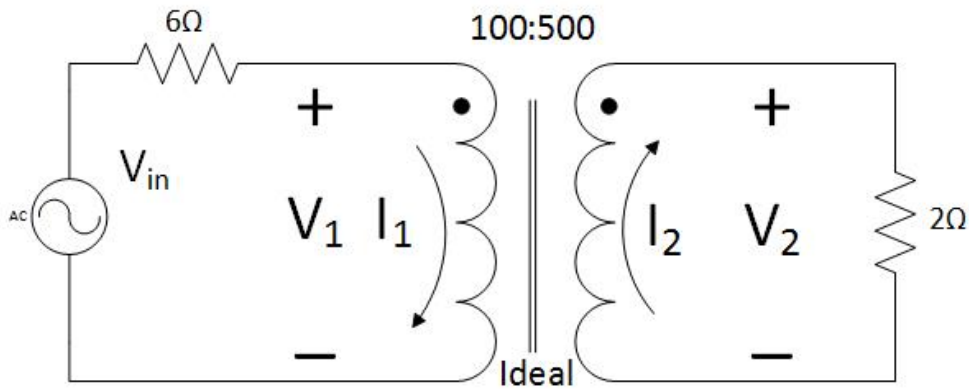

Q6d

Given: The transformer is ideal.

$$V_{in} = 120 \cos(377t) \text{ V}$$

a) Find the magnitude of the current  $I_1$ .  $|I_1| = 19.7 \text{ A}$  ✓

b) Find the magnitude of the voltage  $V_1$ .  $|V_1| = 1.57 \text{ V}$  ✓

**Correct**

Marks for this submission: 10.00/10.00.

**Question 7**

Correct

Mark 10.00 out of 10.00

Q7d No figure

A circuit has the following input voltage with the resulting current:

$$v = 100 \sin(377t + 10^\circ) \text{ V}_{\text{rms}}$$

$$i = 14 \cos(377t - 95^\circ) \text{ A}_{\text{rms}}$$

a) Find the average power absorbed by the circuit.  $P = 1358.75 \text{ W}$  ✓

b) Find the reactive power.  $Q = 362.35 \text{ VAR}$  ✓

c) Find the apparent power.  $|S| = 1400 \text{ VA}$  ✓

**Correct**

Marks for this submission: 10.00/10.00.

**Question 8**

Correct

Mark 5.00 out of 5.00

Q8c

A circuit has the following input voltage with the resulting current:

$$v = 120 \cos(377t + 25^\circ) \text{ V}_{\text{rms}}$$

$$i = 7 \cos(377t - 25^\circ) \text{ A}_{\text{rms}}$$

a) Find the power factor of this circuit. pf =  ✓

b) Is this a lagging or leading power factor?


 ✓**Correct**

Marks for this submission: 5.00/5.00.

**Question 9**

Correct

Mark 10.00 out of 10.00

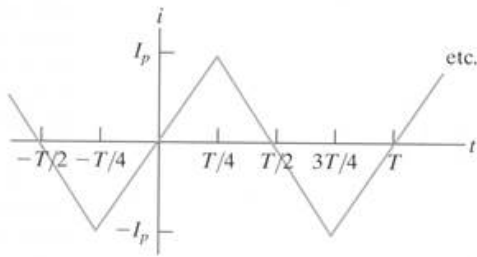

Q9c

The periodic triangular current has a peak value of 150 mA (milli Amp).

a) Find the rms value of the current.

$$I_{p,\text{rms}} = \text{86.6} \text{ mA}_{\text{rms}} \text{ (milli A}_{\text{rms}})$$

b) Find the average power that this current delivers to a 5 k $\Omega$  (kilo Ohm) resistor.

$$P_{\text{avg}} = \text{37.49} \text{ W}$$

**Correct**

Marks for this submission: 10.00/10.00.