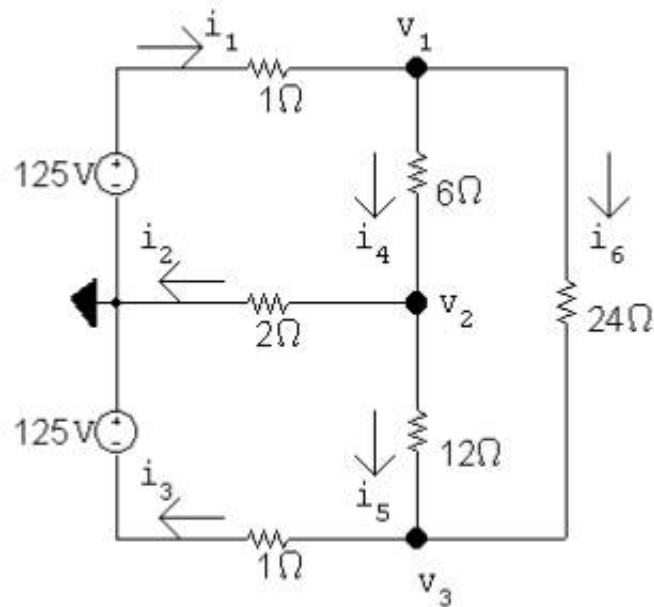


[Home](#) ► [Electrical Engineering](#) ► [Engr 17 F16 Tatro](#) ► [Exams and Quizzes](#) ► [Quiz 4 - Chap 4](#)

<b>Started on</b>	Wednesday, 5 October 2016, 12:43 PM
<b>State</b>	Finished
<b>Completed on</b>	Wednesday, 5 October 2016, 12:56 PM
<b>Time taken</b>	12 mins 52 secs
<b>Grade</b>	<b>100.00</b> out of 100.00

**Question 1**

Correct

Mark 100.00 out of  
100.00

Quiz 4c

Practice using the node-voltage method and ...

Find the three node voltages  $V_1$ ,  $V_2$  and  $V_3$ .

$$V_1 = 101.24 \text{ V}$$

$$V_2 = 10.66 \text{ V}$$

$$V_3 = -106.57 \text{ V}$$

**Numeric Answer**

$$V_1 = 101.2433 \text{ V}$$

$$V_2 = 10.6572 \text{ V}$$

$$V_3 = -106.5719 \text{ V}$$

**Correct**

Marks for this submission: 100.00/100.00.