
Started on Wednesday, 13 December 2017, 5:49 PM

State Finished

Completed on Wednesday, 13 December 2017, 7:03 PM

Time taken 1 hour 14 mins

Grade **43.00** out of 106.00 (**41**%)

Question 1

Correct

Mark 2.00 out of
2.00

Which of the following is true in modern bipolar junction transistors?

Select one:

- ☐ a. The base is kept narrow to minimize recombination in the base
- ☐ b. Carriers diffuse across the base and are collected by the collector
- ☐ c. The emitter doping is much higher than the base doping to minimize the number of carriers injected from the base into the emitter
- ☒ d. All of these ✓
- ☐ e. The minority carrier concentration in the base decreases almost linearly from the emitter to the collector

The correct answer is: All of these

Correct

Marks for this submission: 2.00/2.00.

Question 2

Correct

Mark 1.00 out of 2.00

Which of the following is true for an NPN BJT operating in the forward-active region ?

Select one:

- ☒ a. All of these ✓
- ☐ b. The collector current consists primarily of electrons injected from the emitter into the base
- ☐ c. The emitter current consists primarily of electrons injected from the emitter into the base
- ☐ d. Some base current flows to replace holes which are lost as electrons diffusing across the base recombine
- ☐ e. The base current consists primarily of holes injected from the base into the emitter

The correct answer is: All of these

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 3

Correct

Mark 1.00 out of 2.00

An NPN BJT operating in the saturation region has :

Select one:

- ☐ a. None of these
- ☒ b. $V_{be} > 0$ and $V_{bc} > 0$ ✓
- ☐ c. $V_{be} > 0$ and $V_{bc} < 0$
- ☐ d. $V_{be} < 0$ and $V_{bc} < 0$
- ☐ e. $V_{be} < 0$ and $V_{bc} > 0$

The correct answer is: $V_{be} > 0$ and $V_{bc} > 0$

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 4

Correct

Mark 1.00 out of 2.00

For a BJT operating in saturation, which of the following is true?

Select one:

- ☐ a. The collector current increases linearly as the base current is increased
- ☐ b. The base-collector junction can be forward biased by about 200mV before the collector current starts to decrease
- ☐ c. The common-emitter current gain, β , is much larger than in the forward-active region
- ☒ d. The output resistance, r_o , is much smaller than in the forward-active region ✓
- ☐ e. All of these

The correct answer is: The output resistance, r_o , is much smaller than in the forward-active region

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 5

Correct

Mark 1.00 out of 2.00

As $|V_{ce}|$ increases for a BJT in the forward active region, “base-width modulation” causes :

Select one:

- ☐ a. The width of the base to increase
- ☐ b. The output resistance, r_o , to increase
- ☒ c. The width of the base-collector depletion region to increase ✓
- ☐ d. The collector current for the BJT to decrease
- ☐ e. None of these

The correct answer is: The width of the base-collector depletion region to increase

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 6

Correct

Mark 1.00 out of 2.00

If an NPN BJT at 75°C with a constant collector current of 100μA has a V_{be} voltage of 770mV, then what will V_{be} be for this same BJT at 50°C ?

Select one:

- ☐ a. 720mV
- ☐ b. 620mV
- ☐ c. None of these
- ☐ d. 670mV
- ☒ e. 820mV ✓

The correct answer is: 820mV

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **1.00/2.00**.

Question 7

Correct

Mark 2.00 out of 2.00

For a BJT common-collector amplifier, which of the following is true ?

Select one:

- ☐ a. The output signal is measured at the collector
- ☐ b. The base is used by both the input and output ports
- ☒ c. The same circuit topologies are used for both NPNs and PNPs ✓
- ☐ d. The input signal is applied to the emitter
- ☐ e. All of these

The correct answer is: The same circuit topologies are used for both NPNs and PNPs

Correct

Marks for this submission: 2.00/2.00.

Question 8

Correct

Mark 2.00 out of
2.00

For a BJT common-collector amplifier, which of the following is true ?

Select one:

- ☐ a. The base is used by both the input and output ports
- ☒ b. The output signal is measured at the emitter ✓
- ☐ c. All of these
- ☐ d. Different circuit topologies are used for NPNs than for PNPs
- ☐ e. The input signal is applied to the collector

The correct answer is: The output signal is measured at the emitter

Correct

Marks for this submission: 2.00/2.00.

Question 9

Correct

Mark 2.00 out of
2.00

For a MOS common-gate amplifier, which of the following is true ?

Select one:

- ☐ a. All of these
- ☒ b. The input resistance is typically low ✓
- ☐ c. The output resistance is typically low
- ☐ d. The voltage gain is typically low
- ☐ e. The voltage gain is negative

The correct answer is: The input resistance is typically low

Correct

Marks for this submission: 2.00/2.00.

Question 10

Correct

Mark 2.00 out of
2.00

For a MOS common-gate amplifier, which of the following is true ?

Select one:

- ☐ a. The voltage gain is negative
- ☐ b. All of these
- ☐ c. The output resistance is typically low
- ☐ d. The input resistance is typically high
- ☒ e. The voltage gain is typically high ✓

The correct answer is: The voltage gain is typically high

Correct

Marks for this submission: 2.00/2.00.

Question 11

Correct

Mark 2.00 out of
2.00

The saturation current for a bipolar transistor is inversely proportional to the area of the emitter.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00.

Question 12

Correct

Mark 0.00 out of
2.00

As the base width of a BJT increases, the common-base current gain α of the transistor will increase.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **0.00/2.00**.

Question 13

Correct

Mark 2.00 out of
2.00

To keep the base current small for a PNP BJT in the forward-active region, the base must be narrow in order to minimize the number of holes which recombine as they diffuse across the base.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

Correct

Marks for this submission: 2.00/2.00.

Question 14

Correct

Mark 0.00 out of
2.00

In the forward-active region the base current of a PNP BJT consists of electrons injected from the base into the emitter and holes which recombine in the base.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **0.00/2.00**.

Question 15

Correct

Mark 0.00 out of
2.00

When finding the resistance “looking into” a node, all independent current sources should be replaced with open circuits.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **0.00/2.00**.

Question 16

Correct

Mark 2.00 out of
2.00

Ideally, the output resistance for a transresistance amplifier would be zero.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

Correct

Marks for this submission: 2.00/2.00.

Question 17

Correct

Mark 0.00 out of
2.00

A common-base BJT amplifier and a common-emitter BJT amplifier which use the same transistors, bias currents, and resistor sizes will have the same gain except the common-emitter amplifier gain will be negative.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **0.00/2.00**.

Question 18

Correct

Mark 0.00 out of
2.00

For an emitter-follower BJT amplifier, the input is applied to the emitter and the output is measured at the collector.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00. Accounting for previous tries, this gives **0.00/2.00**.

Question 19

Correct

Mark 2.00 out of
2.00

For a common-gate MOS amplifier, the input is applied to the gate and the output is measured at the drain.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00.

Question 20

Correct

Mark 2.00 out of
2.00

The maximum possible gain for a common-source MOSFET amplifier is 1.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 2.00/2.00.

Question 21

Correct

Mark 6.00 out of
6.00

What is the open-circuit voltage gain, μ_f , in V/V for an NPN BJT operating in the forward-active region at 27°C with $I_c = 756\mu\text{A}$? Use: $\beta = 127$, $V_A = 75\text{V}$ and $V_t = kT/q = 26\text{mV}$.

Answer: 

The correct answer is: 2884.62

Correct

Marks for this submission: 6.00/6.00.

Question 22

Not answered

Mark 0.00 out of
6.00

What is the device transconductance, g_m , in mA/V for an NMOS FET operating in saturation with $I_d = 200\mu\text{A}$? Use: $W/L = 50$ and $k'_n = 100\mu\text{A/V}^2$. Neglect the effects of channel-length modulation and body effect.

Answer: 


The correct answer is: 1.41

Question 23

Correct

Mark 6.00 out of 6.00

For the BJT bias circuit shown, what is the emitter voltage, V_E , in volts? Use $V_{CC} = 8V$, $V_{EE} = -7V$, $V_B = -2.6V$, $R_C = 4.9k\Omega$, and $R_E = 5.9k\Omega$. Assume that the transistor is in the forward-active region, with $\beta = 48$ and $|V_{BE(on)}| = 0.7V$. Neglect the effects of base-width modulation.

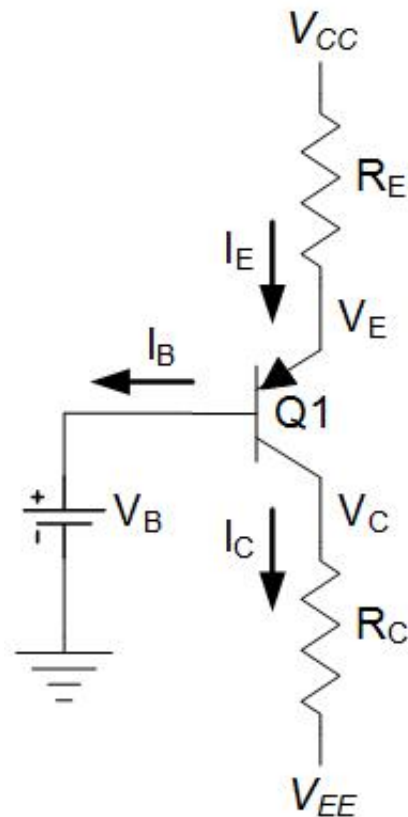

Answer: -1.9



The correct answer is: -1.9

Correct


Marks for this submission: 6.00/6.00.

Question 24

Correct

Mark 6.00 out of 6.00

For the MOSFET bias circuit shown, what is the source current, I_S , in milliamps? Assume that the transistor is in the saturation region, and use: $V_{DD} = 11V$, $R_{G1} = 41.7k\Omega$, $R_{G2} = 59.8k\Omega$, $R_D = 1.0k\Omega$, $R_S = 8.2k\Omega$, $V_t = -0.7V$, and $|V_{on}| = 0.18$. (Remember that $|V_{on}| = |V_{ov}| = |V_{GS}| - |V_t|$) Neglect the effect of channel-length modulation and body effect.

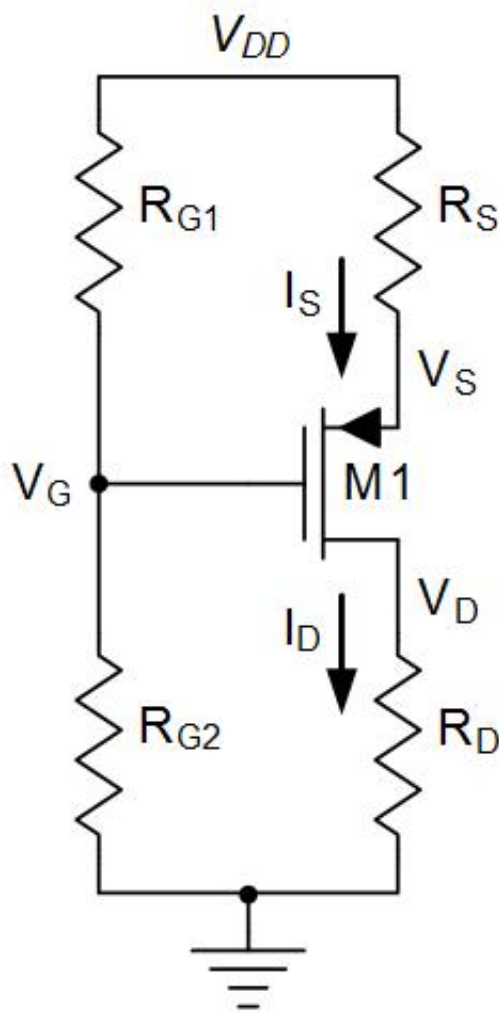

Answer: .444



The correct answer is: 0.44

Correct


Marks for this submission: 6.00/6.00.

Question 25

Incorrect

Mark 0.00 out of
6.00

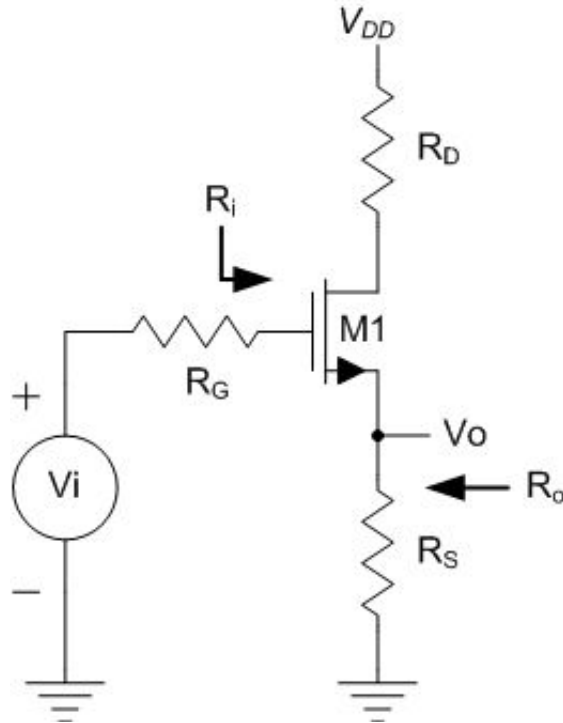What is the low frequency voltage gain for the amplifier shown at 27° C with $R_D = 16.5\text{k}\Omega$, $R_S = 0.6\text{k}\Omega$ and $R_G = 3.9\text{k}\Omega$? Use: $W/L = 17$, $I_D = 328\mu\text{A}$, $V_{TN} = 0.5\text{V}$, $k'_n = 100\mu\text{A/V}^2$. Neglect the effect of channel-length modulation and body effect.



Answer: 0.24



The correct answer is: 0.388

Incorrect

Marks for this submission: 0.00/6.00.


Question 26

Not answered

Mark 0.00 out of

6.00

What is the low frequency voltage gain for the amplifier shown at 27°C with $R_c = 24.3\text{k}\Omega$, $R_e = 0.1\text{k}\Omega$ and $R_b = 0.5\text{k}\Omega$? Use: $I_c = 305\mu\text{A}$, $\beta = 32$, and $V_t = kT/q = 26\text{mV}$. Neglect the effect of base-width modulation.

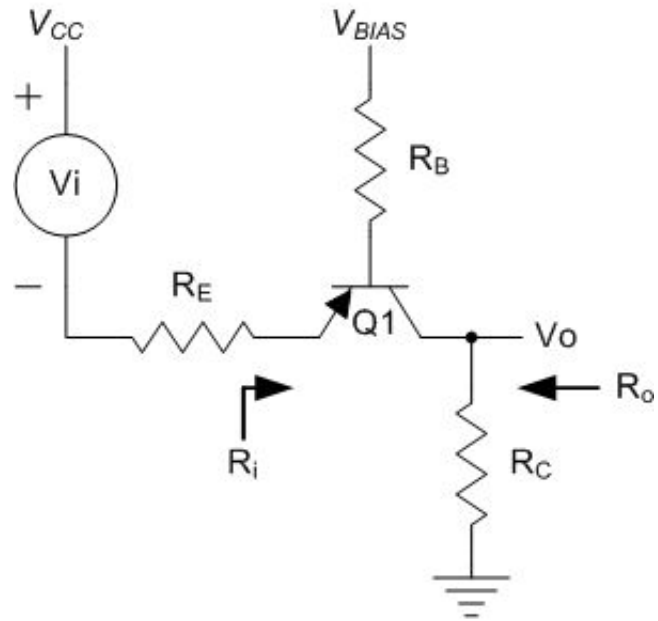Answer: ✗

The correct answer is: 119.12


Question 27

Not answered

Mark 0.00 out of

6.00

What is the low frequency input resistance, R_i , in Ω for the amplifier shown at 27°C with $R_d = 15.6\text{k}\Omega$, $R_s = 0.4\text{k}\Omega$ and $R_g = 4.8\text{k}\Omega$? Use: $W/L = 53$, $I_d = 248\mu\text{A}$, $V_{TP} = -0.5\text{V}$, $k'_n = 40\mu\text{A/V}^2$. Neglect the effect of channel-length modulation

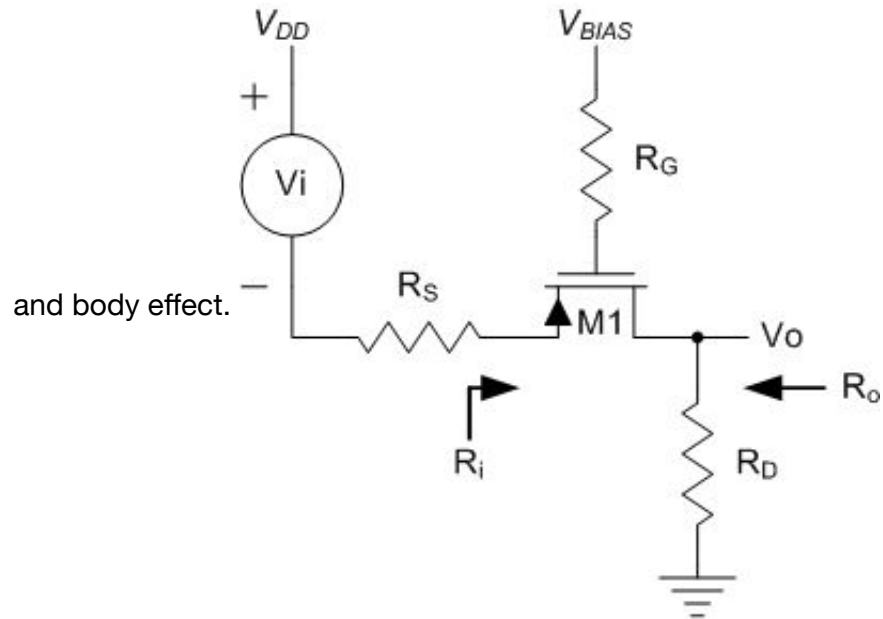Answer: ✗

The correct answer is: 975.2


Question 28

Not answered

Mark 0.00 out of

6.00

What is the low frequency input resistance, R_i , in $k\Omega$ for the amplifier shown at 27°C with $R_c = 47.0k\Omega$, $R_e = 0.6k\Omega$ and $R_b = 0.5k\Omega$? Use: $I_c = 282\mu\text{A}$, $\beta = 20$, and $V_t = kT/q = 26\text{mV}$. Neglect the effect of base-width modulation.

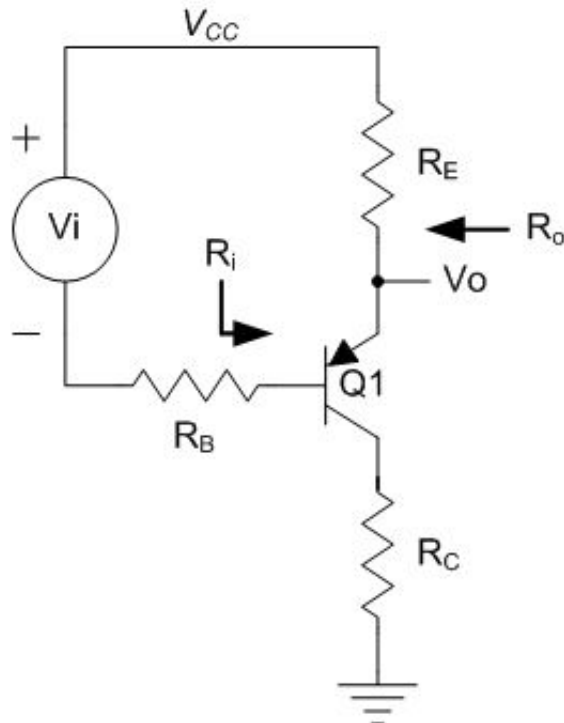Answer: ✗

The correct answer is: 14.4


Question 29

Not answered

Mark 0.00 out of

6.00

What is the low frequency output resistance, R_o , in $k\Omega$ for the amplifier shown at 27°C with $R_c = 79.3k\Omega$, $R_e = 0.1k\Omega$ and $R_b = 0.6k\Omega$? Use: $I_c = 270\mu\text{A}$, $\beta = 41$, $V_A = 10\text{V}$, and $V_t = kT/q = 26\text{mV}$. Use the "short-cut approach" discussed in

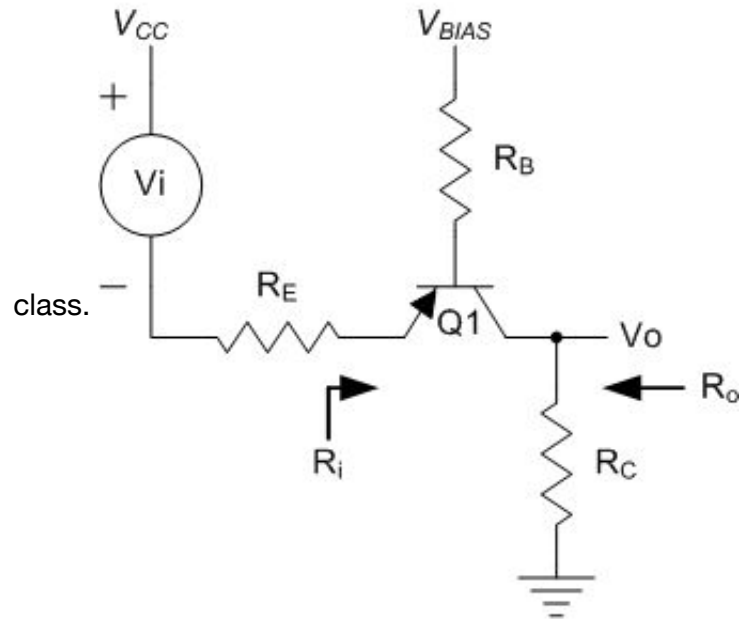Answer: ✗

The correct answer is: 38.7


Question 30

Not answered

Mark 0.00 out of

6.00

What is the low frequency output resistance, R_o , in $k\Omega$ for the amplifier shown at 27°C with $R_d = 98.5k\Omega$, $R_s = 0.9k\Omega$ and $R_g = 3.8k\Omega$. Use: $W/L = 16$, $I_d = 520\mu\text{A}$, $V_{TP} = -0.5\text{V}$, $k'_p = 40\mu\text{A/V}^2$, $\lambda = 0.10$. Neglect body effect.

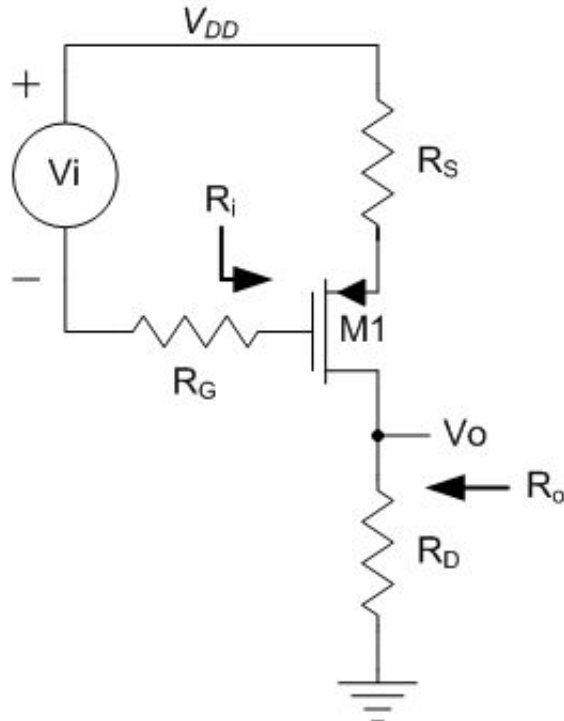Answer: ✗

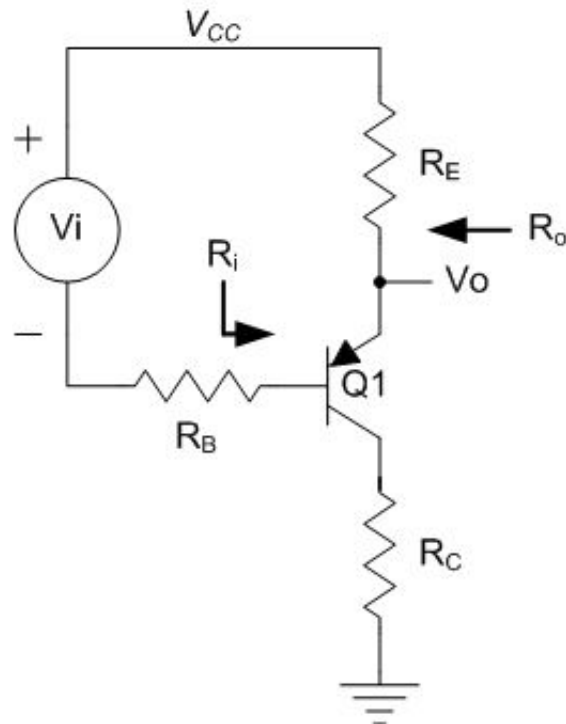
The correct answer is: 24.9

Question 31

Not answered

Mark 0.00 out of
6.00

Estimate the maximum low frequency voltage gain for the amplifier shown at 27°C with $R_C = 43.3\text{k}\Omega$, $R_E = 2.9\text{k}\Omega$ and $R_B = 0.4\text{k}\Omega$.

Answer: ✖

The correct answer is: 1.000