

Started on Wednesday, 5 April 2017, 11:01 AM**State** Finished**Completed on** Wednesday, 5 April 2017, 11:48 AM**Time taken** 47 mins 6 secs**Grade** 96.67 out of 100.00**Question 1**

Correct

Mark 5.00 out of 5.00

Q1c

Find the Laplace Transform of $\left\{ \frac{d}{dt}[e^{-at} \sin(\omega t)] \right\} \Leftrightarrow$

Select one:

- ☒ a. $\frac{s\omega}{(s+a)^2 + \omega^2}$ ✓
- ☐ b. $\frac{\omega^2}{(s+a)^2 + \omega^2}$
- ☐ c. $\frac{2sa}{(s+a)^2 + \omega^2}$
- ☐ d. $\frac{-s^2}{(s+a)^2 + \omega^2}$

Your answer is correct.

$$\frac{s\omega}{(s+a)^2 + \omega^2}$$

The correct answer is: $\frac{s\omega}{(s+a)^2 + \omega^2}$ **Correct**

Marks for this submission: 5.00/5.00.

Question 2

Correct

Mark 15.00 out of 15.00

Q2d

Given

$$F(s) = \frac{400}{(s+4)(s^2+4s+5)} = \frac{400}{(s+4)(s+2-j)(s+2+j)}$$

Find the partial fraction expansion of F(s) and then use the Laplace transform tables to find f(t).

$$f(t) = [80 e^{-4t} + 178.8 e^{-2t} \cos(1t + -116^\circ)] u(t)$$

$$f(t) = [80e^{-4t} + 178.8854e^{-2t} \cos(t - 116.57^\circ)] u(t)$$

Correct

Marks for this submission: 15.00/15.00.

Question 3

Correct

Mark 10.00 out of 10.00

Q3b

Given: $F(s) = \frac{10(s^2+40)}{(s+8)(s^2+12s+136)}$ which has an inverse transform f(t).

a) Find the initial value of f(t = 0).

$$f(t=0) = 10$$

b) Find the final value of f(t → ∞)

$$f(t \rightarrow \infty) = 0$$

Numeric Answer

a) f(t = 0) = 10

b) f(t → ∞) = 0


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 6.67 out of 10.00

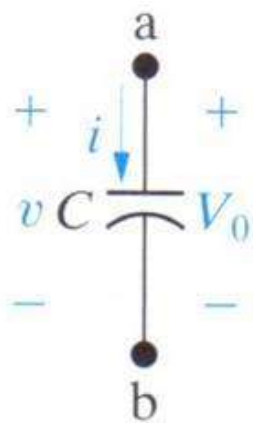

Q4a

Given: This capacitor has a value of $1\ \mu\text{F}$ (micro F) and has an initial voltage of $15\ \text{V}$ at $t = 0^-$.

Identify the Frequency Domain parallel form of the capacitor

Select one:

- ☐ a. $V = \frac{1}{s(1 \times 10^{-6})} + \frac{15}{s}$
- ☒ b. $I = s(1 \times 10^{-6})V - 15 \times 10^{-6}$ ✓
- ☐ c. $I = s(1 \times 10^{-3})V - 15 \times 10^{-3}$
- ☐ d. $V = \frac{1}{s(1 \times 10^{-3})} + \frac{15}{s}$

Your answer is correct.

$$I = s(1 \times 10^{-6})V - 15 \times 10^{-6}$$

The correct answer is: $I = s(1 \times 10^{-6})V - 15 \times 10^{-6}$


Correct

Marks for this submission: 10.00/10.00. Accounting for previous tries, this gives **6.67/10.00**.

Question 5

Correct

Mark 15.00 out of 15.00

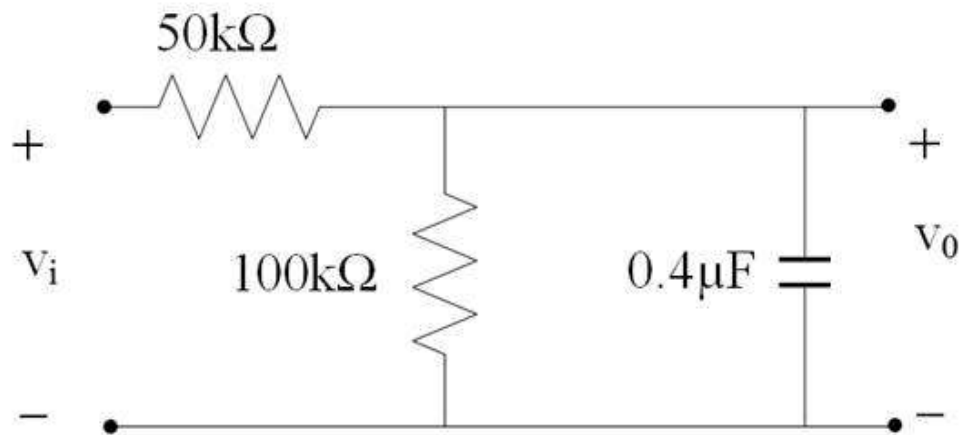

Q5a

Find the s domain transfer function $H(s) = V_0/V_i$ for this circuit.

$$H(s) = \boxed{50} / (s + \boxed{75})$$

$$H(s) = \frac{50}{s+75}$$


Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 15.00 out of 15.00

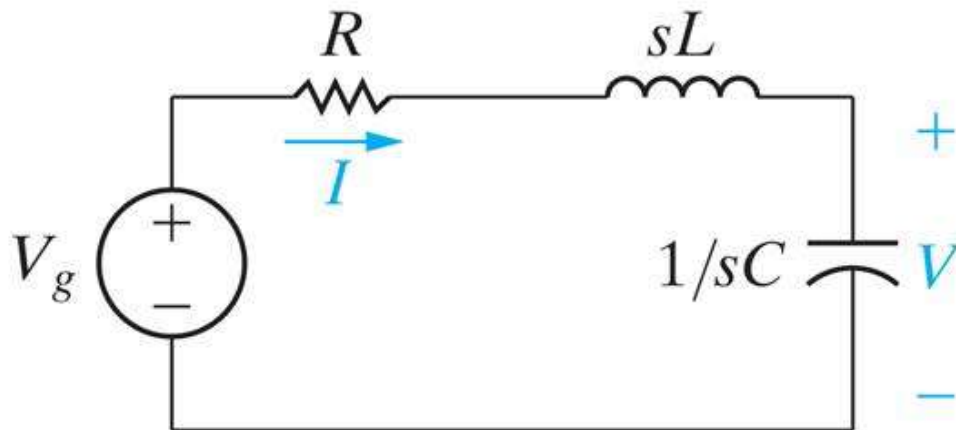

Q6a

Given: There is no energy stored in this circuit prior to $t = 0$.The voltage source $V_g = 10V$ for $t \geq 0^+$. $R = 125 \Omega$ (Ohm) $L = 1 \text{ H}$ $C = 1 \text{ mF}$ (milli F)Find defined voltage V in the s domain.

$$V(s) = \boxed{10000} / [s(s^2 + \boxed{125} s + \boxed{1000})]$$

$$V(s) = \frac{10,000}{s(s^2 + 125s + 1,000)}$$

Correct

Marks for this submission: 15.00/15.00.

Question 7

Correct

Mark 15.00 out of 15.00

Q7e

Given:
$$F(s) = \frac{2(5s+11)}{s^2+14s+625} = \frac{2(5s+11)}{(s+7-j24)(s+7+j24)}$$

Find the partial fraction expansion of this transfer function.

$$F(s) = \left[5 \right] \checkmark \text{ at Angle } \left[11.31 \right] \checkmark / (s + 7 - j24)$$

$$+ \left[5 \right] \checkmark \text{ at Angle } \left[-11.31 \right] \checkmark / (s + 7 + j24)$$

State the angle in each case as a positive angle.

$$F(s) = \frac{2(5s+11)}{s^2+14s+625} = \frac{5.0990 \angle 11.31^\circ}{s+7-j24} + \frac{5.0990 \angle [?][?]-11.31^\circ}{s+7+j24}$$


Correct

Marks for this submission: 15.00/15.00.

Question 8

Correct

Mark 15.00 out of 15.00

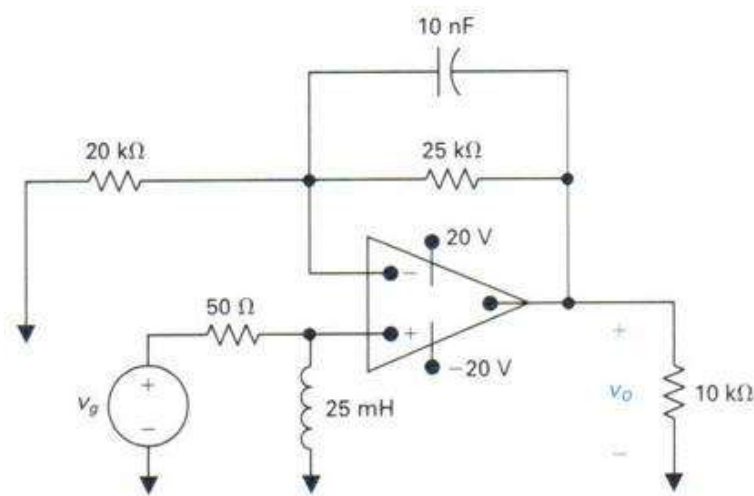

Q8c

Given: The opamp is ideal.

$$H(s) = \frac{V_o}{V_g} = \frac{s(s+9,000)}{(s+2,000)(s+4,000)}$$

Find the steady-state response when the input $v_g(t) = 12 \cos(10,000 t)$ V.

$$v_o(t)_{\text{steady-state}} = \left[14.7 \right] \checkmark \cos \left(10000 \right] \checkmark t + \left[-8.8 \right] \checkmark ^\circ \right] u(t) \text{ V}$$

Numeric Answer

$$v_o(t)_{\text{steady-state}} = 14.6980 \cos(10,000 t - 8.86^\circ) u(t) \text{ V}$$

Correct

Marks for this submission: 15.00/15.00.

