

Started on Wednesday, 14 September 2016, 11:02 AM

State Finished

Completed on Wednesday, 14 September 2016, 11:42 AM


Time taken 39 mins 33 secs

Grade 83.33 out of 100.00

Question 1

Correct

Mark 40.00 out of
40.00

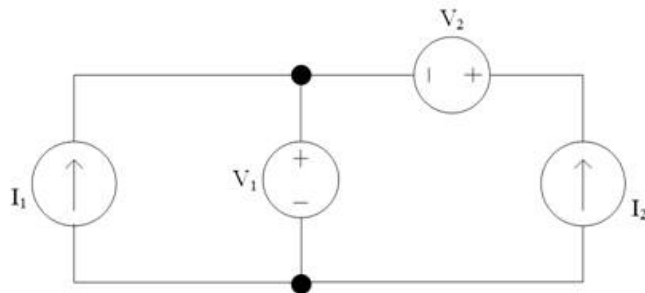

Quiz 2-1

Given: $I_1 = 11$ Amps $V_1 = 117$ Volts $I_2 = 11$ Amps $V_2 = 15$ Volts

What is the current through the voltage source V_1 ?

Answer: ✓


Calculated

The correct answer is: 22.00

Question 2

Correct

Mark 43.33 out of 60.00

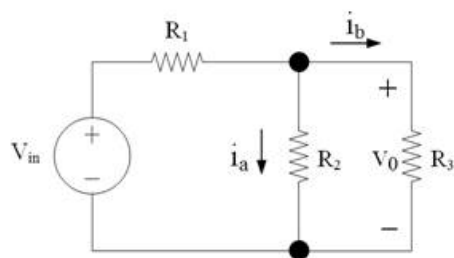

Quiz 2-2b

Given: $V_{in} = 60$ Volts $R_1 = 4 \Omega$ (Ohm) $R_2 = 20 \Omega$ (Ohm) $R_3 = 80 \Omega$ (Ohm)a) Find the value of i_a . $i_a = 2.4$ ✓ Ab) Find the value of v_0 . $v_0 = 48$ ✓ V

c) Find the power dissipated in each resistor.

 $P_{R1} = 36$ ✓ W $P_{R2} = 115.2$ ✓ W $P_{R3} = 28.8$ ✓ Wd) Find the power delivered by the V_{in} source. $P_{V_{in}} = -180$ ✓ W

Remember: “-” = Delivering “+” = Absorbing

Numeric Answera) $i_a = 2.40$ Ab) $v_0 = 48.0$ Vc) $P_{R1} = 36.0$ W $P_{R2} = 115.20$ W $P_{R3} = 28.80$ Wd) $P_{V_{in}} = -180.0$ W