

Started on Monday, 13 May 2019, 10:10 AM

State Finished

Completed on Monday, 13 May 2019, 11:42 AM


Time taken 1 hour 32 mins

Grade 92.00 out of 100.00

Question 1

Correct

Mark 9.00 out of 9.00

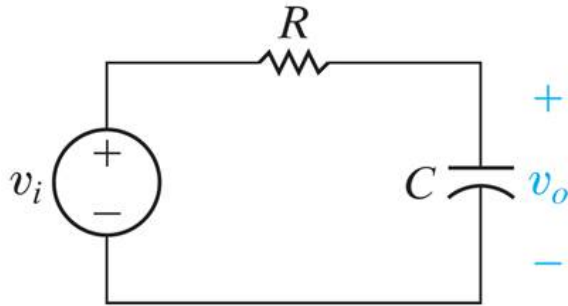

Q1a

Given: $C = 250 \text{ nF}$ (nano F) $R = 5 \text{ k}\Omega$ (kilo Ohm)a) Write the parameters of the transfer function $H(s)$.

$$H(s) = V_o / V_i = 800 / (s + 800)$$

b) Calculate the cutoff frequency ω_c in rad/sec and f_c in Hz.

$$\omega_c = 800 \text{ rad/sec} \quad f_c = 127.3 \text{ Hz}$$

c) State the phase angle of the output voltage when fully in the passband region where $\omega \ll \omega_c$.

$$\theta(\text{pass band}) = 0^\circ$$

d) State the phase angle of the output voltage at the corner frequency ω_c .

$$\theta(\omega_c) = -45^\circ$$

e) State the phase angle of the output voltage when fully in the stopband region where $\omega \gg \omega_c$.

$$\theta(\text{stop band}) = -90^\circ$$

f) Identify the filter type of this circuit.

Filter Type = Low Pass

Numeric Answer

a) $H(s) = 800 / (s + 800)$ b) $\omega_c = 800 \text{ rad/sec}$ $f_c = 127.3240 \text{ Hz}$ c) $\theta(\text{pass band}) = 0^\circ$ d) $\theta(\omega_c) = -45^\circ$ e) $\theta(\text{stop band}) = -90^\circ$

f) Filter Type = Low Pass


Correct

Marks for this submission: 9.00/9.00.

Question 2

Correct

Mark 9.00 out of 9.00

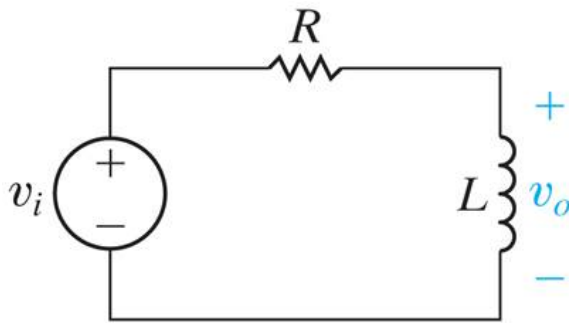

Q2e

Given: $L = 67 \text{ mH}$ (milli H) $R = 353 \Omega$ (Ohm)a) Write the parameters of the transfer function $H(s)$.

$$H(s) = V_o / V_i = s / (s + \boxed{5268.7}) \quad \checkmark$$

b) Calculate the cutoff frequency ω_c in rad/sec and f_c in Hz.

$$\omega_c = \boxed{5268.7} \quad \checkmark \text{ rad/sec} \quad f_c = \boxed{838.54} \quad \checkmark \text{ Hz}$$

c) State the phase angle of the output voltage when fully in the passband region where $\omega \gg \omega_c$.

$$\theta(\text{pass band}) = \boxed{0} \quad \checkmark \text{ }^\circ \text{ (Degrees)}$$

d) State the phase angle of the output voltage at the corner frequency $\omega = \omega_c$.

$$\theta(\omega_c) = \boxed{45} \quad \checkmark \text{ }^\circ \text{ (Degrees)}$$

e) State the phase angle of the output voltage when fully in the stopband region where $\omega \ll \omega_c$.

$$\theta(\text{stop band}) = \boxed{90} \quad \checkmark \text{ }^\circ \text{ (Degrees)}$$

f) Identify the filter type of this circuit.

Filter Type = High Pass ▼ ✓**Numeric Answer**a) $H(s) = s / (s + 5,268.6567)$ b) $\omega_c = 5,268.6567 \text{ rad/sec}$ $f_c = 838.5328 \text{ Hz}$ c) $\theta(\text{pass band}) = 0^\circ$ d) $\theta(\omega_c) = 45^\circ$ e) $\theta(\text{stop band}) = 90^\circ$

f) Filter Type = High Pass


Correct

Marks for this submission: 9.00/9.00.

Question 3

Correct

Mark 9.00 out of 9.00

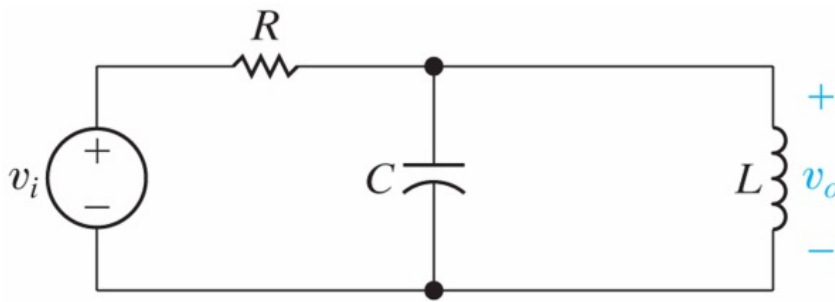

Q3Pb

Given: $R = 160 \, \Omega$ (Ohm) $C = 5 \, \mu\text{F}$ (micro F) $L = 100 \, \mu\text{H}$ (micro H)a) Find the resonant frequency ω_0 .

$$\omega_0 = 44721.36 \, \checkmark \text{ rad/sec}$$

b) Find the lower half-power frequency ω_{c1} .

$$\omega_{c1} = 44096 \, \checkmark \text{ rad/sec}$$

c) Find the upper half-power frequency ω_{c2} .

$$\omega_{c2} = 45346 \, \checkmark \text{ rad/sec}$$

d) Find the bandwidth β (Beta).

$$\beta = 1250 \, \checkmark \text{ rad/sec}$$

e) Find the quality factor Q.

$$Q = 35.77 \, \checkmark$$

f) Identify the filter type of this circuit.

Filter Type = Band Pass \checkmark **Numeric Answer**a) $\omega_0 = 44,721.3595 \text{ rad/sec}$ b) $\omega_{c1} = 44,100.7267 \text{ rad/sec}$ c) $\omega_{c2} = 45,350.7267 \text{ rad/sec}$ d) $\beta = 1,250 \text{ rad/sec}$ e) $Q = 35.7771$

f) Filter Type = Band Pass


Correct

Marks for this submission: 9.00/9.00.

Question 4

Correct

Mark 9.00 out of 9.00

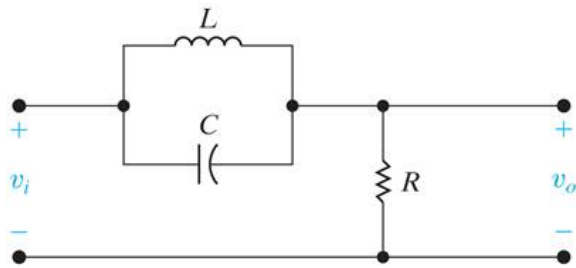

Q4Pb

Given: $R = 750 \, \Omega$ (Ohm) $C = 20 \, \text{nF}$ (nano F) $L = 150 \, \mu\text{H}$ (micro H)a) Calculate ω_0 .

$$\omega_0 = 577.35 \, \text{krad/sec (kilo rad/sec)}$$

b) Calculate f_0 .

$$f_0 = 91.888 \, \text{kHz (kilo Hz)}$$

c) Find ω_{c1} .

$$\omega_{c1} = 544.997 \, \text{krad/sec (kilo rad/sec)}$$

d) Find ω_{c2} .

$$\omega_{c2} = 611.645 \, \text{krad/sec (kilo rad/sec)}$$

e) Find β (Beta).

$$\beta = 66.66 \, \text{krad/sec (kilo rad/sec)}$$

f) Find Q.

$$Q = 8.66$$

g) Identify the filter type of this circuit.

Filter Type = Band Reject

Numeric Answera) $\omega_0 = 577.3503 \, \text{krad/sec}$ b) $f_0 = 91.8881 \, \text{kHz}$ c) $\omega_{c1} = 544.9784 \, \text{krad/sec}$ d) $\omega_{c2} = 611.6451 \, \text{krad/sec}$ e) $\beta = 66.6667 \, \text{krad/sec}$ f) $\beta = 8.6603$

g) Filter Type = Band Reject


Correct

Marks for this submission: 9.00/9.00.

Question 5

Correct

Mark 9.00 out of 9.00

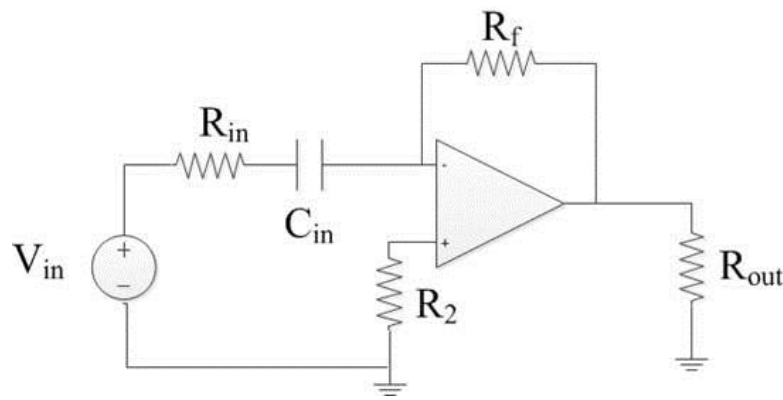

Q5a

Given: $V_{in} = 15 \cos(2,000t)$ Volts $R_{in} = 10 \text{ k}\Omega$ (kilo Ohm) $C_{in} = 0.1 \text{ }\mu\text{F}$ (micro F) $R_f = 10 \text{ k}\Omega$ (kilo Ohm) $R_{out} = 1 \text{ k}\Omega$ (kilo Ohm) $R_2 = 10 \text{ }\Omega$ (Ohm)

The opamp has power input rails at +15V and -15V.

Find the steady-state output voltage v_{out} which is the voltage across the resistor R_{out} .
 $v_{out} =$
 ✓
 $\cos(2,000 t +$
 ✓
 $^\circ \text{ (Degrees) Volts}$

State the voltage magnitude as positive and state the phase angle as a positive angle (counterclockwise from the origin) in the correct quadrant.


Numeric Answer $v_{out} = 13.4164 \cos(2,000 t + 206.57^\circ)$ Volts**Correct**

Marks for this submission: 9.00/9.00.

Question 6

Correct

Mark 9.00 out of 9.00

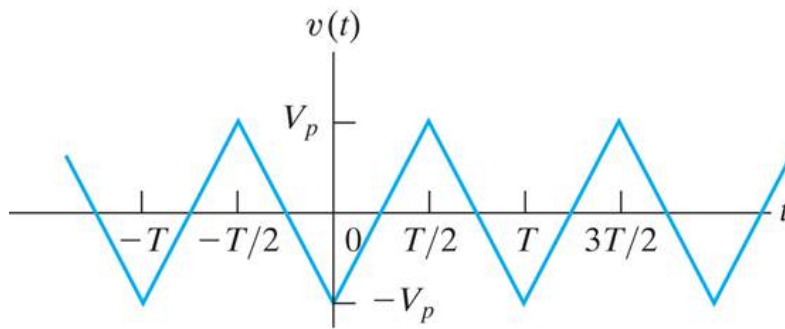

Q6b

Given: The Fourier coefficients for this waveform are

$$a_v = 0 \text{ V} \quad a_n = -8V_p / (n\pi)^2 \text{ Volts for } n \text{ odd} \quad b_n = 0 \text{ V}$$

$$V_p = 50 \text{ V} \quad T = 5 \text{ ms (milli sec)}$$

Write the following terms of this waveform's Fourier series.

a) What is the average value?

$$\text{Avg} = \boxed{0} \text{ Volts}$$

Answers for the next two questions are in the order of magnitude, identify cosine or sine and the frequency of the sinusoid in radians/sec.

b) Write the expression for $n = 1$.

$$v_1(t) = \boxed{-40.53} \text{ cosine } \boxed{1256.64} \text{ t Volts}$$

c) Write the expression for $n = 5$.

$$v_5(t) = \boxed{-1.62} \text{ cosine } \boxed{6283} \text{ t Volts}$$

Numeric Answera) $a_v = 0$ Voltsb) For $n = 1$, $v(t) = -400/(1*\pi)^2 \sin(1*400\pi t) = -40.5284 \cos(1,256.6371 t) \text{ V}$ c) For $n = 5$, $v_5(t) = -400/(5*\pi)^2 \sin(5*400\pi t) = -1.6211 \cos(6,283.1853 t) \text{ V}$ **Correct**

Marks for this submission: 9.00/9.00.

Question 7

Correct

Mark 9.00 out of
9.00

Q7b

Given the “normal” trigonometric form of the Fourier series coefficients for a waveform are

$$a_{\text{avg}} = \text{zero} \quad a_n = -5/n^2 \quad b_n = 15/n$$

Determine the coefficients for the Alternative trigonometric form of the Fourier series in the polar form

$$a_n - jb_n = A_n \angle -\theta_n \quad (\text{Magnitude } A_n \text{ at angle } -\theta_n)$$

a) For the first term in the summation where $n = 1$:

$$A_1 = \boxed{15.81} \checkmark \text{ Volts}$$

$$-\theta_1 \text{ (Theta 1)} = \boxed{-108.5} \checkmark ^\circ \text{ (Degrees, angle CW from origin)}$$

b) For the second term in the summation where $n = 2$:

$$A_2 = \boxed{7.6} \checkmark \text{ Volts}$$

$$-\theta_2 \text{ (Theta 2)} = \boxed{-99.47} \checkmark ^\circ \text{ (Degrees, angle CW from origin)}$$

c) For the third term in the summation where $n = 3$:

$$A_3 = \boxed{5.02} \checkmark \text{ Volts}$$

$$-\theta_3 \text{ (Theta 3)} = \boxed{-96.35} \checkmark ^\circ \text{ (Degrees, angle CW from origin)}$$

CW = Clock-wise

Note that the angle also includes the “-” sign as shown in the polar form.

Numeric Answer

$$\text{a) } A_1 = 15.8114 \text{ Volts} \quad -\theta_1 = -108.4349^\circ$$

$$\text{b) } A_2 = 7.6035 \text{ Volts} \quad -\theta_2 = -99.4623^\circ$$

$$\text{c) } A_3 = 5.0308 \text{ Volts} \quad -\theta_3 = -96.3402^\circ$$


Correct

Marks for this submission: 9.00/9.00.

Question 8

Correct

Mark 9.00 out of 9.00

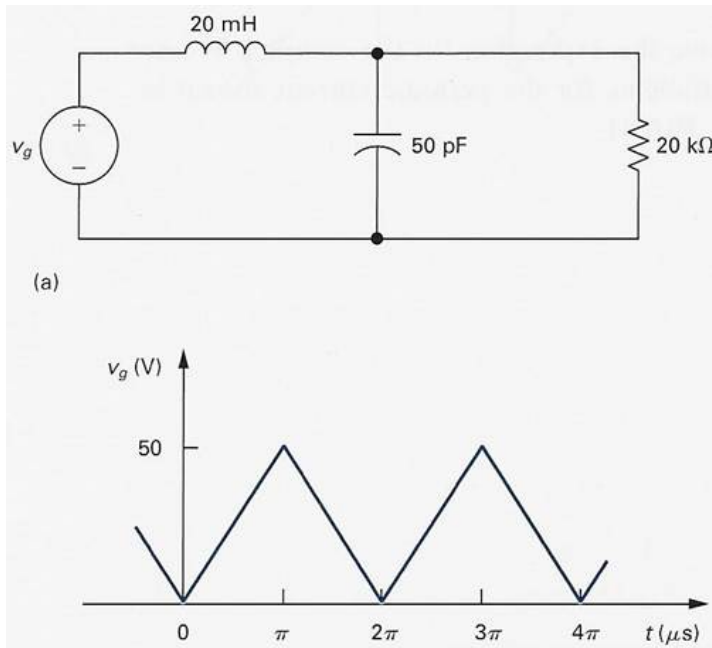

Q8

The triangular-wave voltage source is applied to this circuit.

The Fourier series of this input waveform is

$$v(t) = 25 - \frac{200}{\pi^2} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \cos(n\omega_0 t)$$

The s domain transfer function of the circuit is

$$H(s) = \frac{10^{12}}{s^2 + s10^6 + 10^{12}}$$

The desired output is the voltage across the $20\text{ k}\Omega$ (kilo Ohm) resistor.

a) Determine the steady-state output voltage for $n = 1$ written as polar phasor.

$v_{1,20W,\text{steady-state}}(t)$ = Magnitude ✓ at angle ✓ ° (Degrees) Volts (negative magnitude and negative angle)

b) Determine the steady-state output voltage for $n = 5$ written as polar phasor.

$v_{5,20W,\text{steady-state}}(t)$ = Magnitude ✓ at angle ✓ ° (Degrees) Volts (negative magnitude and positive angle)

c) Determine an estimate of the time varying power across the $20\text{ k}\Omega$ (kilo Ohm) resistor based on the voltage from $n = 1$ term only.

$P_{20W,\text{steady-state}}$ = ✓ mW (milli W)

Numeric Answer

a) $v_{1,20W,\text{steady-state}}(t) = -20.2642$ at angle -90° V

b) $v_{5,20W,\text{steady-state}}(t) = -0.1654$ at angle 11.77° V


c) $P_{20W,\text{steady-state}} = 10.266$ mW

Correct

Marks for this submission: 9.00/9.00.

Question 9

Correct

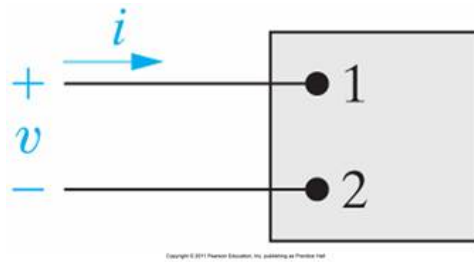Mark 9.00 out of
9.00

Q9e

The voltage and current at terminals of this network are

$$v(t) = 55 + 120 \cos(300t + 45^\circ) + 40 \sin(900t) \text{ Volts}$$

$$i(t) = 35 + 18 \sin(300t + 75^\circ) + 8 \cos(900t - 15^\circ) \text{ Amps}$$

a) What is the average power at terminals?

$$P = \boxed{2506} \checkmark \text{ W}$$

b) What is the rms value of the voltage of this truncated series?

$$V_{\text{rms}} = \boxed{105} \checkmark V_{\text{rms}}$$

c) What is the rms value of the current of this truncated series?

$$I_{\text{rms}} = \boxed{37.67} \checkmark A_{\text{rms}}$$

Numeric Answer

$$\text{a) } P = 2,506.4110 \text{ W}$$

$$\text{b) } V_{\text{rms}} = 105.00 V_{\text{rms}}$$

$$\text{c) } I_{\text{rms}} = 37.6696 I_{\text{rms}}$$

Correct

Marks for this submission: 9.00/9.00.

Question 10

Correct

Mark 9.00 out of
9.00

Q10c

Given
$$H(s) = \frac{(45,000)(s+200)}{(s+2,000)(s+9,000)}$$

a) What is the zero of this function in the form $s + z_1$?

$$z_1 = \boxed{200} \checkmark$$

b) What are the two poles of this function in the form $s + p_{1,2}$?

$$p_1 = \boxed{2000} \checkmark \text{ (positive lower value)}$$

$$p_2 = \boxed{9000} \checkmark \text{ (positive higher value)}$$

c) What is the *gain K* in dB after putting this function in *Standard Form*?

$$K = \boxed{-6} \checkmark \text{ dB}$$

For the following use the Bode diagram straight-line approximation conventions (do not plot the function)d) Find the magnitude of this transfer function at $\omega = 2,000$ rad/sec.

$$|H(j\omega = 2,000 \text{ rad/sec})| = \boxed{13.87} \checkmark \text{ dB}$$

e) Find the phase angle at $\omega = 2,000$ rad/sec

$$\theta(j\omega = 2,000 \text{ rad/sec}) = \boxed{45} \checkmark ^\circ \text{ (Degrees)}$$

a) $z_1 = 200$ b) $p_1 = 2,000$ $p_2 = 9,000$

c) K in dB = -6.0206 dB

d) $|H(j\omega = 2,000 \text{ rad/sec})| = 14$ dBe) $\theta(j\omega = 200 \text{ rad/sec}) = 45^\circ$ **Correct**

Marks for this submission: 9.00/9.00.

Question 11

Complete

Mark 2.00 out of
10.00

You created a hand-drawn Bode Diagram of a given transfer function in-class on May 6th. That in-class work has been manually graded. The instructor will enter your score here after you have completed this online exam.

Comment:

◀ Quiz 12 - Chapter 16

Jump to... ▼

Using Matlab at Sac State ►