

**Started on** Wednesday, 10 April 2019, 11:37 AM

**State** Finished

**Completed on** Wednesday, 10 April 2019, 11:38 AM


**Time taken** 33 secs

**Grade** 100.00 out of 100.00

### Question 1

Correct

Mark 20.00 out of 20.00

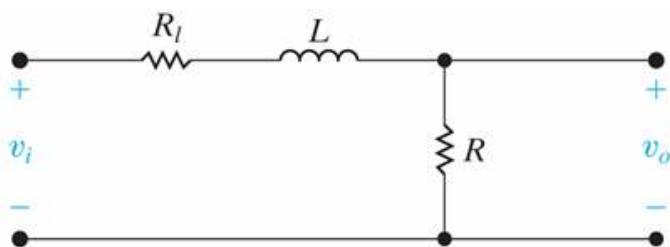

P14.3\_9ed

A resistor  $R_l$  is added in series with the inductor in this circuit.

Given:  $R_l = 75 \, \Omega$  (Ohm)  $L = 10 \, \text{mH}$  (mill H)  $R = 127 \, \Omega$  (Ohm)

a) Find the s domain transfer function  $H(s) = V_o/V_i$ .

$$H(s) = \frac{12700}{s + 20200}$$

b) At what frequency will the magnitude of  $H(j\omega)$  be maximum?

$$\omega_{H,\max} = 0 \, \text{rad/sec}$$

c) What is maximum value of the magnitude of  $H(j\omega)$ ?

$$H(j\omega)_{\max} = 0.628$$

d) At what frequency will the magnitude of  $H(j\omega)$  equal its maximum value divided by square root of 2?

$$\omega_{H,\max,\sqrt{2}} = 20200 \, \text{rad/sec}$$

e) Find  $\omega_c$  (omega\_c)

$$\omega_c = 20200 \, \text{rad/sec}$$

Now examine the transfer function magnitude and phase as the frequency varies.

f) Find  $H(j\omega = 0)$  in polar form..

$$H(j\omega = 0) = \text{Mag } 0.628 \text{ at angle } 0^\circ \text{ (Degrees)}$$

g) Find  $H(j\omega = 0.3\omega_c)$  in polar form.

$$H(j\omega = 0.3\omega_c) = \text{Mag } 0.602 \text{ at angle } -16.7^\circ \text{ (Degrees)}$$

h) Find  $H(j\omega = \omega_c)$  in polar form.

$$H(j\omega = \omega_c) = \text{Mag } 0.44 \text{ at angle } -45^\circ \text{ (Degrees)}$$

i) Find  $H(j\omega = 3\omega_c)$  in polar form.

$$H(j\omega = 3\omega_c) = \text{Mag } 0.198 \text{ at angle } -72^\circ \text{ (Degrees)}$$


**Correct**

Marks for this submission: 20.00/20.00.

**Question 2**

Correct

Mark 20.00 out of 20.00

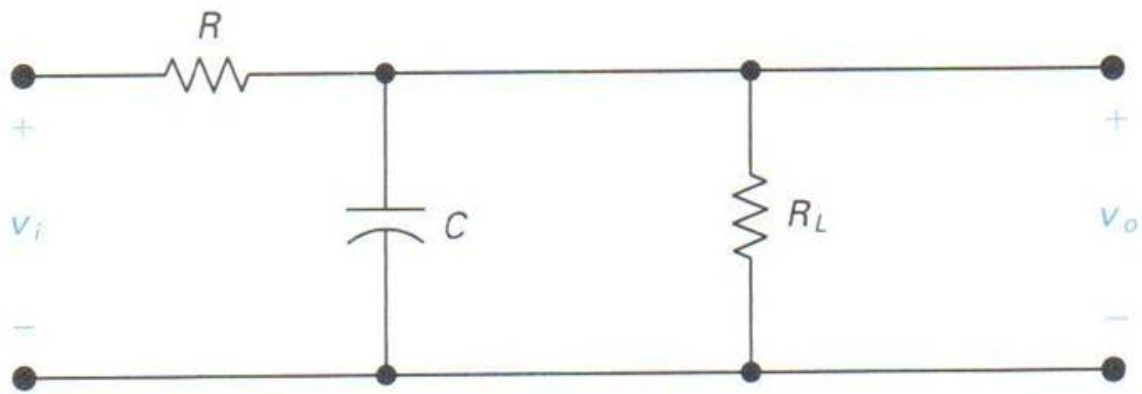

P14.3\_6ed

A resistor  $R_L$  is connected in parallel with the capacitor in this circuit. The circuit thus becomes a loaded low-pass filter.

Given:  $R = 20 \text{ k}\Omega$  (kilo Ohm)  $C = 4 \text{ nF}$   $R_L = 300 \text{ k}\Omega$  (kilo Ohm)

a) Find the s domain transfer function  $H(s) = V_o/V_i$ .

$$H(s) = \boxed{12500} \checkmark / (s + \boxed{13333} \checkmark)$$

b) Find  $\omega_c$  (omega\_c)

$$\omega_c = \boxed{13333} \checkmark \text{ rad/sec}$$

Now examine the transfer function magnitude and phase as the frequency varies.

c) Find  $H(j0)$

$$H(j0) = \boxed{.9375} \checkmark$$

d) Find  $H(j\omega_c)$  i.e. evaluate  $H(j\omega)$  at  $\omega = \omega_c$

$$H(j\omega_c) = \text{Mag } \boxed{.66} \checkmark \text{ Angle } \boxed{-45} \checkmark$$

e) Find  $H(j0.2\omega_c)$  i.e. evaluate  $H(j\omega)$  at  $\omega = 0.2 \omega_c$

$$H(j0.2\omega_c) = \text{Mag } \boxed{.91} \checkmark \text{ Angle } \boxed{-11.3} \checkmark$$

f) Find  $H(j8\omega_c)$  i.e. evaluate  $H(j\omega)$  at  $\omega = 8\omega_c$

$$H(j8\omega_c) = \text{Mag } \boxed{.116} \checkmark \text{ Angle } \boxed{-83} \checkmark$$


**Correct**

Marks for this submission: 20.00/20.00.

### Question 3

Correct

Mark 20.00 out of 20.00

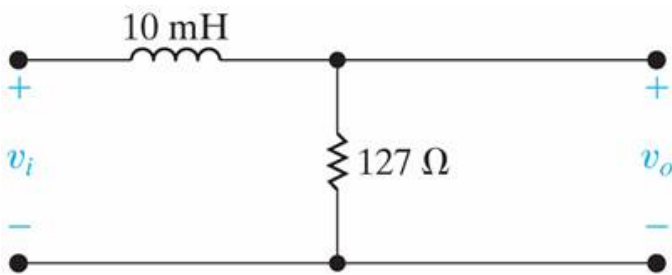

P14.1\_9ed

a) Find the cutoff frequency in hertz.

$$f_c = 2022 \text{ Hz}$$

b) Find  $H(j\omega = 0)$  in polar form.

$$H(j\omega = 0) = \text{Mag } 1 \text{ at angle } 0^\circ \text{ (Degrees)}$$

Now examine the output magnitude and phase as the input frequency varies.

c) Find  $H(j\omega = 0.2\omega_c)$  in polar form..

$$H(j\omega = 0.2\omega_c) = \text{Mag } .98 \text{ at angle } -11.3^\circ \text{ (Degrees)}$$

d) Find  $H(j\omega = \omega_c)$  in polar form.

$$H(j\omega = \omega_c) = \text{Mag } .707 \text{ at angle } -45^\circ \text{ (Degrees)}$$

e) Find  $H(j\omega = 5\omega_c)$  in polar form.

$$H(j\omega = 5\omega_c) = \text{Mag } .196 \text{ at angle } -78.7^\circ \text{ (Degrees)}$$

Now given  $v_i(t) = 10 \cos(\omega t)$  V. Write the steady-state expression for  $v_o$  for:

f)  $\omega = 0.2\omega_c$

$$v_o(t) = 9.8 \cos(2540 t + -11.3^\circ) \text{ Volts}$$

g)  $\omega = \omega_c$

$$v_o(t) = 7.07 \cos(12700 t + -45^\circ) \text{ Volts}$$

h)  $\omega = 5\omega_c$

$$v_o(t) = 1.96 \cos(63500 t + -79^\circ) \text{ Volts}$$


Correct

Marks for this submission: 20.00/20.00.

**Question 4**

Correct

Mark 20.00 out of 20.00

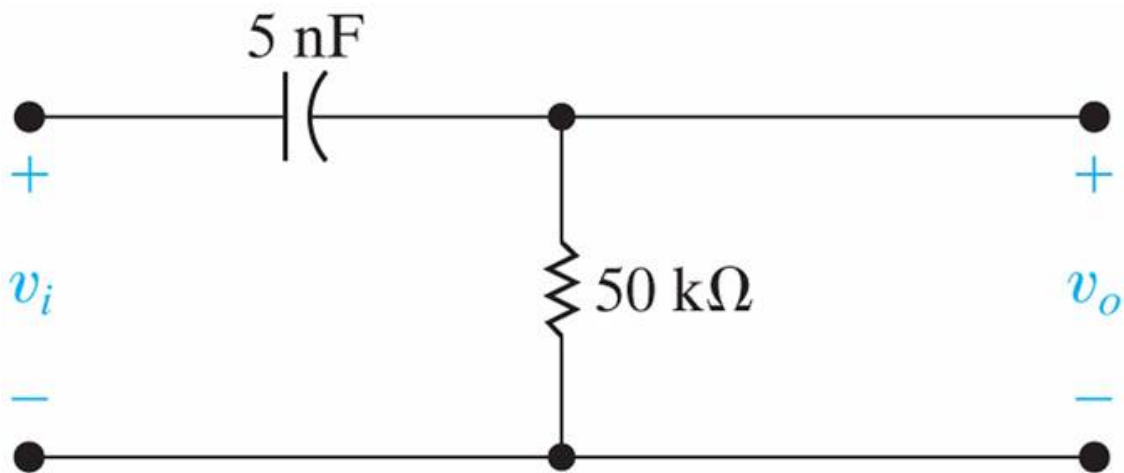

P14.10\_9ed

a) Find the cutoff frequency  $f_c$  for this high-pass filter.

$$f_c = 636.6 \text{ Hz}$$

b) Find the  $H(j\omega)$  for

$$H(j\omega = \omega_c) = 0.707 \text{ at angle } 45^\circ \text{ (degrees)}$$

$$H(j\omega = 0.2\omega_c) = 0.196 \text{ at angle } 79^\circ$$

$$H(j\omega = 5\omega_c) = 0.98 \text{ at angle } 11.3^\circ$$

c) If  $v_i(t) = 500 \cos(\omega t)$  mV (milli V), write the steady-state output voltage  $v_o(t)$  for

$$\text{For } \omega = \omega_c, \quad v_o(t) = 353 \cos(\omega t + 45^\circ) \text{ mV (milli V)}$$

$$\text{For } \omega = 0.2\omega_c, \quad v_o(t) = 98 \cos(\omega t + 78.69^\circ) \text{ mV (milli V)}$$

$$\text{For } \omega = 5\omega_c, \quad v_o(t) = 490 \cos(\omega t + 11.3^\circ) \text{ mV (milli V)}$$


**Correct**

Marks for this submission: 20.00/20.00.

# Question 5

Correct

Mark 20.00 out of 20.00

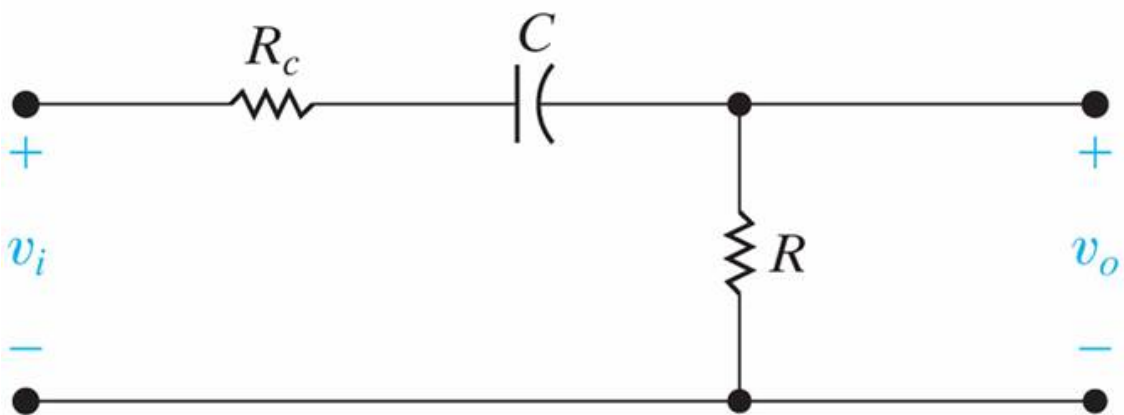

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P14.11\_9ed

Given:  $R_c = 12.5 \text{ k}\Omega$  (kilo Ohm)  $C = 5 \text{ nF}$   $R = 50 \text{ k}\Omega$  (kilo Ohm)

a) Find the cutoff frequency  $f_c$  for this high-pass filter.

$f_c = 509 \text{ Hz}$

b) Find the  $H(j\omega)$  for

$H(j\omega = \omega_c) = .56$  at angle  $45^\circ$  (degrees)

$H(j\omega = 0.2\omega_c) = .157$  at angle  $79^\circ$

$H(j\omega = 5\omega_c) = .78$  at angle  $11.4^\circ$

c) If  $v_i(t) = 500 \cos(\omega t) \text{ mV}$  (milli V), write the steady-state output voltage  $v_o(t)$  for

For  $\omega = \omega_c$ ,  $v_o(t) = 282 \cos(\omega t + 45^\circ) \text{ mV}$  (milli V)

For  $\omega = 0.2\omega_c$ ,  $v_o(t) = 78.4 \cos(\omega t + 79^\circ) \text{ mV}$  (milli V)

For  $\omega = 5\omega_c$ ,  $v_o(t) = 392 \cos(\omega t + 11.31^\circ) \text{ mV}$  (milli V)

Correct

Marks for this submission: 20.00/20.00.

◀ Homework 10 - Bode Diagrams

Jump to...

Homework 12 - Chapter 14 ▶