

Started on Wednesday, 15 March 2017, 11:58 AM

State Finished

Completed on Wednesday, 15 March 2017, 12:18 PM


Time taken 20 mins 4 secs

Grade 100.00 out of 100.00

Question 1

Correct

Mark 100.00 out of 100.00

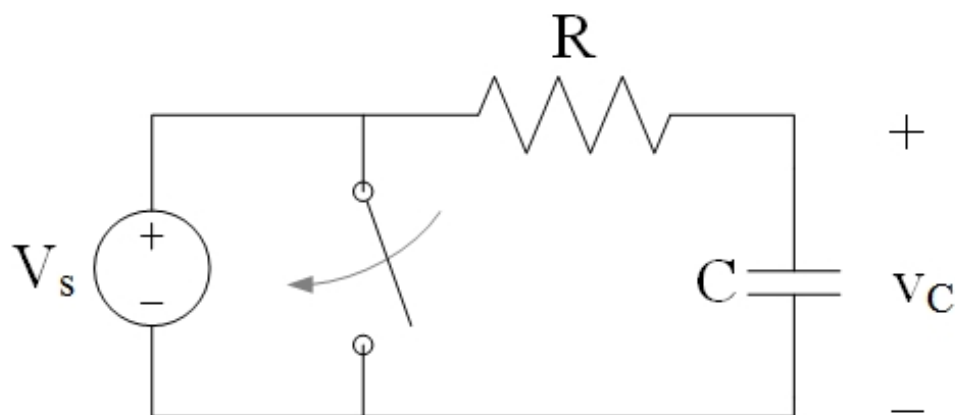

Quiz 6e

Given: After a long time the switch closes at $t = 0$.

$V_s = 6 \text{ V}$ $R = 1 \text{ k}\Omega$ (kilo Ohm) $C = 500 \text{ nF}$ (nano F)

a) Determine the initial voltage across the capacitor.

$$v_C(t = 0) = \boxed{6} \checkmark \text{ V}$$

b) Find the time domain voltage $v_C(t)$ across the capacitor for $t \geq 0^+$.

$$v_C(t \geq 0) = \boxed{6} \checkmark \exp(\boxed{-2000} \checkmark t) \text{ Volts}$$

Correct

Marks for this submission: 100.00/100.00.