

Home ► My courses ► EEE117-2017S-Tatro ► Homework ► Homework 13 - Chapter 15 and 16

Started on Sunday, 30 April 2017, 9:16 PM

State Finished

Completed on Monday, 1 May 2017, 12:06 AM


Time taken 2 hours 49 mins

Grade 100.00 out of 100.00

Question 1

Correct

Mark 13.00 out of 13.00

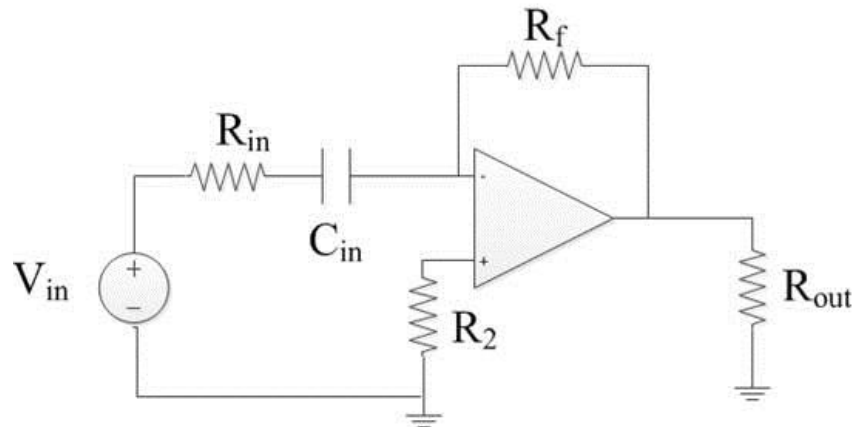

P15.1T

Given: $R_{in} = 10 \text{ k}\Omega$ (kilo Ohm) $C_{in} = 0.1 \text{ }\mu\text{F}$ (micro F) $R_2 = 10 \text{ }\Omega$ (Ohm)

$R_{out} = 1 \text{ k}\Omega$ (kilo Ohm) $R_f = 10 \text{ k}\Omega$ (kilo Ohm)

$V_{in} = 20 \cos(\omega t)$ Volts

The opamp is not ideal and can only deliver up to 15 mA at the output.

The opamp has power input rails at +15V and -15V.

Determine the radian frequency ω where the opamp just begins saturation.

$$\omega_{\text{saturation}} = 1138.9 \quad \checkmark$$

rad/sec

After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.

$$\omega_{\text{saturation}} = 1,133.8934 \text{ rad/sec}$$


Correct

Marks for this submission: 13.00/13.00.

Question 2

Correct

Mark 14.00 out of 14.00

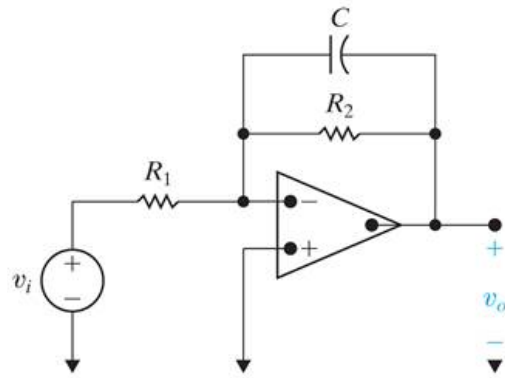

P15.1_10ed

Given: $R_1 = ?? \, \Omega$ (Ohm) $C_{in} = 750 \, \text{nF}$ (nano F) $R_2 = ?? \, \Omega$ (Ohm)

Assume the opamp is ideal.

Design a low-pass filter with a passband gain of 10 dB and a cutoff frequency of 1 kHz.

$$R_1 = \boxed{67.16} \checkmark$$

 Ω (Ohm)

$$R_2 = \boxed{212.21} \checkmark$$

 Ω (Ohm)

After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.

$$R_1 = 212.2066 \, \Omega$$

$$R_2 = 67.1056 \, \Omega$$


Correct

Marks for this submission: 14.00/14.00.

Question 3

Correct

Mark 14.00 out of 14.00

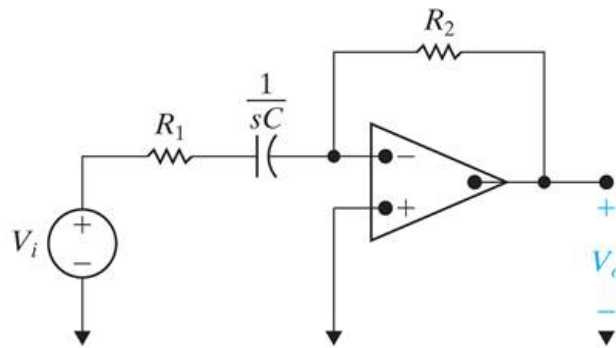

P15.11_10ed

Given: $R_1 = 159 \, \Omega$ (Ohm) $C_{in} = 250 \, \text{nF}$ (nano F) $R_2 = 1,273 \, \Omega$ (Ohm)

Assume the opamp is ideal.

The input to this high-pass filter is $v_i(t) = 2.5 \cos(\omega t)$ Volts.

The opamp has power input rails at +20V and -20V.

For the steady-state condition and letting the output voltage magnitude be negative:

a) Find the output voltage when the input frequency $\omega = \omega_c$. ($\omega = \text{omega}$)

$$v_o(t) = -14.15 \quad \checkmark$$

$$\cos(8000 \quad \checkmark \pi t + 45 \quad \checkmark^\circ) \text{ (Degrees) Volts}$$

b) Find the output voltage when the input frequency $\omega = 0.125 \, \omega_c$.

$$v_o(t) = -2.48 \quad \checkmark$$

$$\cos(1000 \quad \checkmark \pi t + 82.8 \quad \checkmark^\circ) \text{ (Degrees) Volts}$$

c) Find the output voltage when the input frequency $\omega = 8 \, \omega_c$.

$$v_o(t) = -19.8 \quad \checkmark$$

$$\cos(64000 \quad \checkmark \pi t + 7.12 \quad \checkmark^\circ) \text{ (Degrees) Volts}$$

After you get a numeric answer, create a PSpice simulation and compare your answer with the simulation results.

$$\text{a) } v_o(t) = -14.1533 \cos(8,008\pi t + 45^\circ) \text{ V}$$

$$\text{b) } v_o(t) = -2.4827 \cos(1,001\pi t + 82.87^\circ) \text{ V}$$

$$\text{c) } v_o(t) = -19.8612 \cos(64,062.3670\pi t + 7.13^\circ) \text{ V}$$


Correct

Marks for this submission: 14.00/14.00.

Question 4

Correct

Mark 14.00 out of 14.00

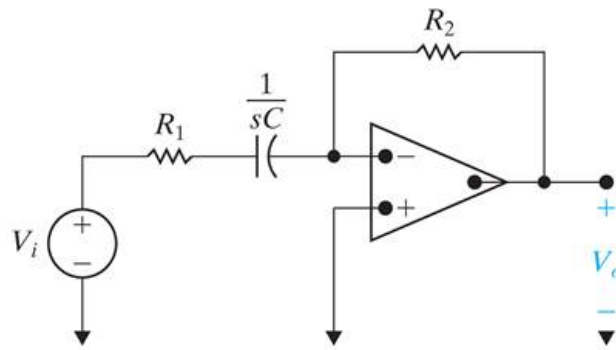

P15.8_10ed

Given: $R_1 = ?? \, \Omega$ (Ohm) $C_{in} = 3.9 \, \text{nF}$ (nano F) $R_2 = ?? \, \Omega$ (Ohm)

Assume the opamp is ideal.

Design a high-pass filter with a passband gain of 14 dB and a cutoff frequency of 8 kHz.

 $R_1 = 5100$ ✓ Ω (Ohm) $R_2 = 25550$ ✓ Ω (Ohm)

After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.


 $R_1 = 5,101.120 \, \Omega$ $R_2 = 25,566.1621 \, \Omega$ **Correct**

Marks for this submission: 14.00/14.00.

Question 5

Correct

Mark 15.00 out of 15.00

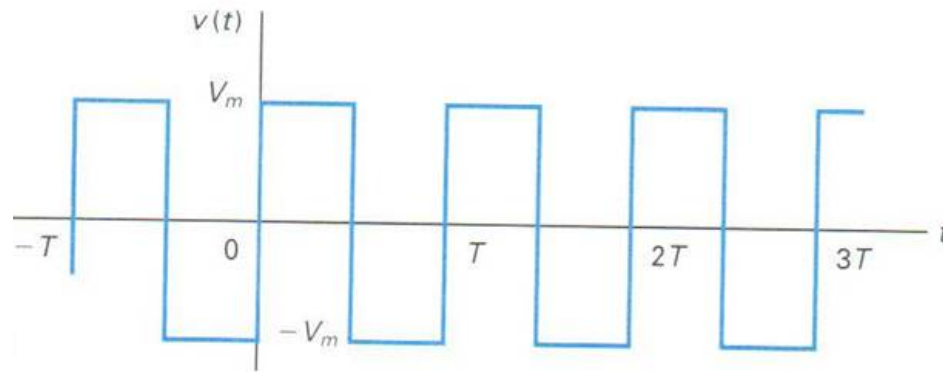

AP16.5_10ed

Find the Fourier series coefficients for this periodic waveform.

a) Find a_v .

$$a_v = \boxed{0} \checkmark$$

b) Find a_k .

$$a_k = \boxed{0} \checkmark$$

c) Find b_k .

$$b_k = \boxed{4} \checkmark$$


 $V_m / \pi k$ for k Odd ☒ \checkmark
a) $a_v = 0$ b) $a_k = 0$
 c) $b_k = \frac{4V_m}{\pi k}$ for k odd
Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 15.00 out of 15.00

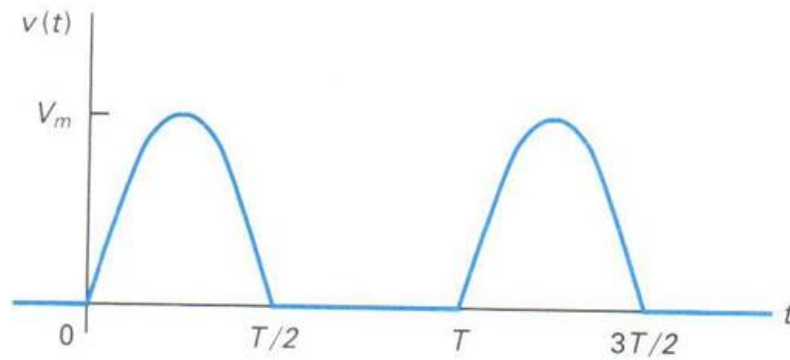

P16.03c_6ed

Find the Fourier series coefficients for this periodic waveform which is a half-wave rectified sine wave where $v(t) = V_m \sin(2\pi t/T)$ for $0 \leq t \leq T/2$.

Also given $V_m = 12$ V.

a) Find a_v .

$$a_v = \boxed{3.8} \checkmark$$

Volts

b) Find a_k .

$$a_k = \boxed{7.64} \checkmark$$

/ $(1 - k^2)$ Volts for all even

c) Find b_k .

$$b_k = \boxed{0} \checkmark$$

for k even and for k odd > 1 .

$$b_1 = \boxed{6} \checkmark$$

$\sin(\omega_0 t)$ Volts

a) $a_v = 3.8197$ V

$$b) a_{k, \text{even}} = \frac{2V_m}{\pi} \left[\frac{1}{1-k^2} \right] = 7.6394 \left[\frac{1}{1-k^2} \right] V$$

c) $b_k = 0$ for k even and odd (for $k > 1$)

$$b_1 = (12V/2) \sin(\omega_0 t) = 6 \sin(\omega_0 t) \text{ Volts}$$


Correct

Marks for this submission: 15.00/15.00.

Question 7

Correct

Mark 15.00 out of 15.00

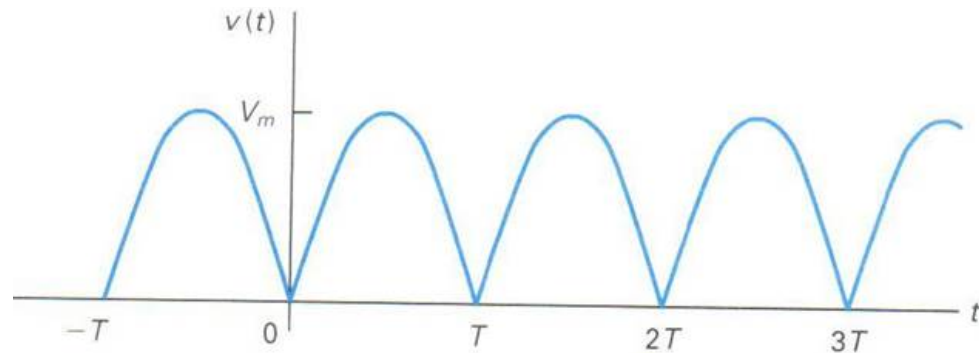

P16.03b_6ed

Find the Fourier series coefficients for this periodic waveform which is a full-wave rectified sine wave where $v(t) = V_m \sin(\pi t/T)$ for $0 \leq t \leq T$.

a) Find a_v .

$$a_v = \boxed{2} \checkmark$$

 V_m / π b) Find a_k .

$$a_k = \boxed{4} \checkmark$$

 $V_m / [\pi (1 - \boxed{4} \checkmark k^2)]$ for all k
c) Find b_k .

$$b_k = \boxed{0} \checkmark$$

a) $a_v = 2 V_m / \pi$

$$b) \ a_k = \frac{4 V_m}{\pi (1 - 4 k^2)}$$

c) $b_k = 0$ **Correct**

Marks for this submission: 15.00/15.00.