

Started on Friday, 14 April 2017, 2:59 PM

State Finished

Completed on Wednesday, 26 April 2017, 1:20 PM


Time taken 11 days 22 hours

Grade 100.00 out of 100.00

Question 1

Correct

Mark 13.00 out of 13.00

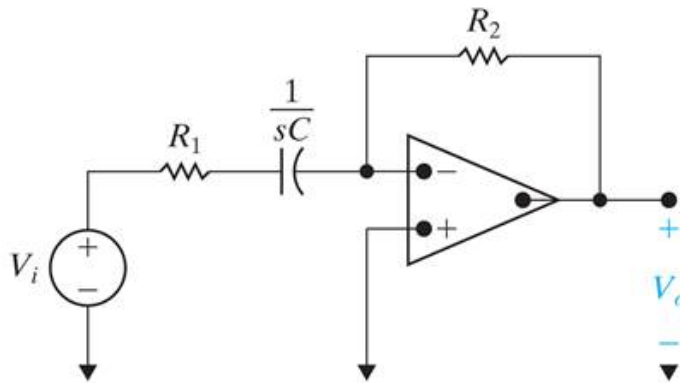

P15.11_10ed

Given: $R_1 = 159 \, \Omega$ (Ohm) $C_{in} = 250 \, \text{nF}$ (nano F) $R_2 = 1,273 \, \Omega$ (Ohm)

Assume the opamp is ideal.

The input to this high-pass filter is $v_i(t) = 2.5 \cos(\omega t)$ Volts.

The opamp has power input rails at +20V and -20V.

For the steady-state condition and letting the output voltage magnitude be negative:

a) Find the output voltage when the input frequency $\omega = \omega_c$. ($\omega = \text{omega}$)

$$v_o(t) = -14.15 \checkmark \cos(8000 \checkmark \pi t + 45 \checkmark^\circ) \text{ (Degrees) Volts}$$

b) Find the output voltage when the input frequency $\omega = 0.125 \omega_c$.

$$v_o(t) = -2.48 \checkmark \cos(1000 \checkmark \pi t + 82.87 \checkmark^\circ) \text{ (Degrees) Volts}$$

c) Find the output voltage when the input frequency $\omega = 8 \omega_c$.

$$v_o(t) = -19.85 \checkmark \cos(64000 \checkmark \pi t + 7.13 \checkmark^\circ) \text{ (Degrees) Volts}$$


After you get a numeric answer, create a PSpice simulation and compare your answer with the simulation results.

Correct

Marks for this submission: 13.00/13.00.

Question 2

Correct

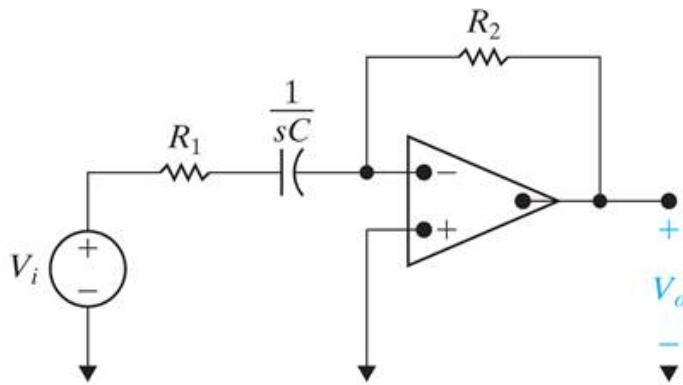Mark 14.00 out of
14.00

P15.8_10ed

Given: $R_1 = ?? \, \Omega$ (Ohm) $C_{in} = 3.9 \, \text{nF}$ (nano F) $R_2 = ?? \, \Omega$ (Ohm)

Assume the opamp is ideal.

Design a high-pass filter with a passband gain of 14 dB and a cutoff frequency of 8 kHz.

 $R_1 =$ $\checkmark \, \Omega$ (Ohm) $R_2 =$ $\checkmark \, \Omega$ (Ohm)


After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.

Correct

Marks for this submission: 14.00/14.00.

Question 3

Correct

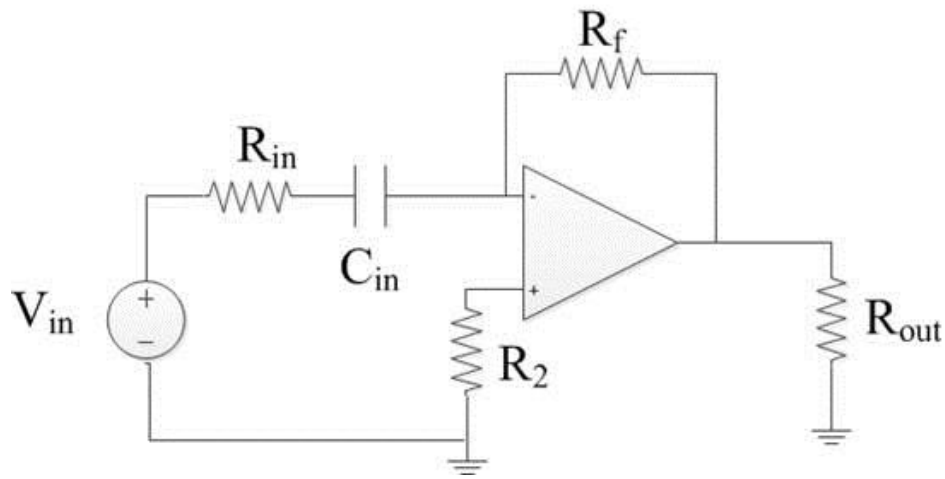Mark 14.00 out of
14.00

P15.1T

Given: $R_{in} = 10 \text{ k}\Omega$ (kilo Ohm) $C_{in} = 0.1 \text{ }\mu\text{F}$ (micro F) $R_2 = 10 \text{ }\Omega$ (Ohm) $R_{out} = 1 \text{ k}\Omega$ (kilo Ohm) $R_f = 10 \text{ k}\Omega$ (kilo Ohm) $V_{in} = 20 \cos(\omega t)$ Volts

The opamp is not ideal and can only deliver up to 15 mA at the output.

The opamp has power input rails at +15V and -15V.

Determine the radian frequency ω where the opamp just begins saturation.

$$\omega_{\text{saturation}} = 1138.9 \text{ rad/sec}$$


After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.

Correct

Marks for this submission: 14.00/14.00.

Question 4

Correct

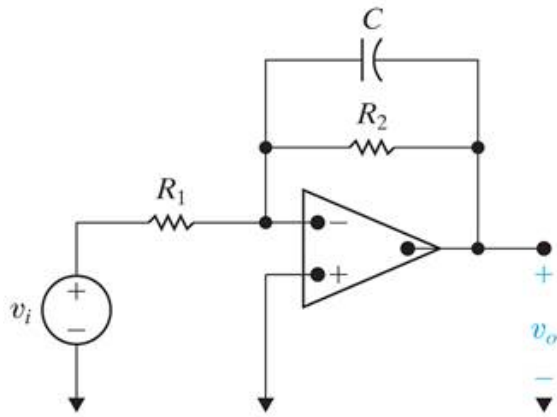Mark 14.00 out of
14.00

P15.1_10ed

Given: $R_1 = ?? \, \Omega$ (Ohm) $C_{in} = 750 \, \text{nF}$ (nano F) $R_2 = ?? \, \Omega$ (Ohm)

Assume the opamp is ideal.

Design a low-pass filter with a passband gain of 10 dB and a cutoff frequency of 1 kHz.

$$R_1 = \boxed{67.16} \, \checkmark \, \Omega \text{ (Ohm)}$$

$$R_2 = \boxed{212.21} \, \checkmark \, \Omega \text{ (Ohm)}$$


After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.

Correct

Marks for this submission: 14.00/14.00.

Question 5

Correct

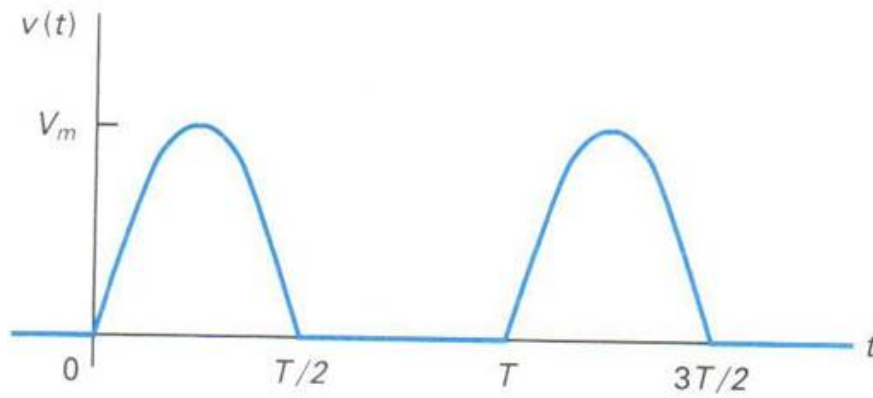Mark 15.00 out of
15.00

P16.03c_6ed

Find the Fourier series coefficients for this periodic waveform which is a half-wave rectified sine wave where $v(t) = V_m \sin(2\pi t/T)$ for $0 \leq t \leq T/2$.

Also given $V_m = 12 \text{ V}$.

a) Find a_v .

$a_v =$ ✓ Volts

b) Find a_k .

$a_k =$ ✓ / $(1 - k^2)$ Volts for all even

c) Find b_k .

$b_k =$ ✓ for k even and for k odd > 1 .


$b_1 =$ ✓ $\sin(\omega_0 t)$ Volts

Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

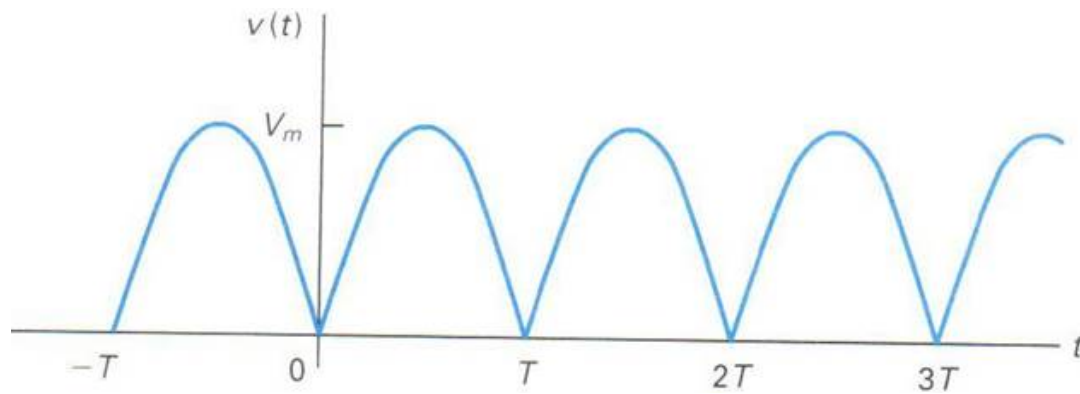Mark 15.00 out of
15.00

P16.03b_6ed

Find the Fourier series coefficients for this periodic waveform which is a full-wave rectified sine wave where $v(t) = V_m \sin(\pi t/T)$ for $0 \leq t \leq T$.

a) Find a_v .

$$a_v = \boxed{2} \checkmark V_m / \pi$$

b) Find a_k .

$$a_k = \boxed{4} \checkmark V_m / [\pi (1 - \boxed{4} \checkmark k^2)] \text{ for all } k$$

c) Find b_k .


$$b_k = \boxed{0} \checkmark$$

Correct

Marks for this submission: 15.00/15.00.

Question 7

Correct

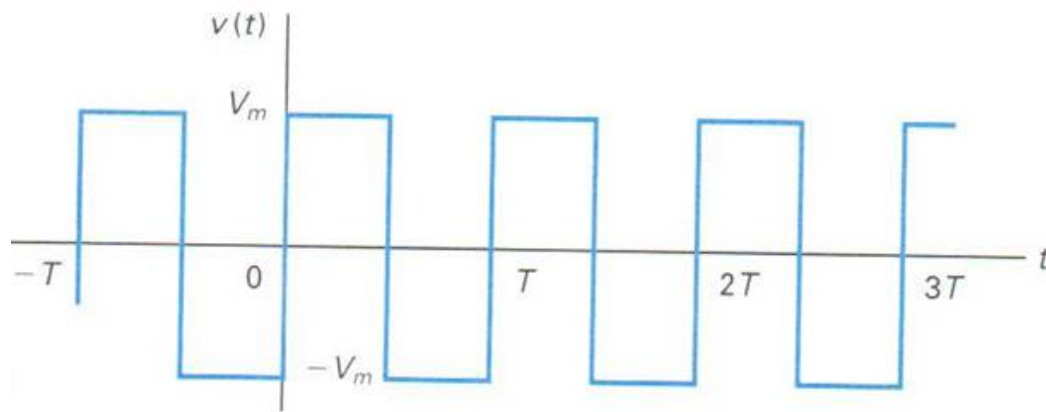Mark 15.00 out of
15.00

AP16.5_10ed

Find the Fourier series coefficients for this periodic waveform.

a) Find a_v .

$$a_v = 0$$

b) Find a_k .

$$a_k = 0$$

c) Find b_k .

$$b_k = 4 \checkmark V_m / \pi k \quad \text{for } k \text{ Odd} \checkmark$$

Correct

Marks for this submission: 15.00/15.00.