

Started on Sunday, 2 April 2017, 5:07 PM

State Finished

Completed on Sunday, 2 April 2017, 5:07 PM


Time taken 8 secs

Grade 90.92 out of 100.00

Question 1

Partially correct

Mark 2.50 out of 10.00

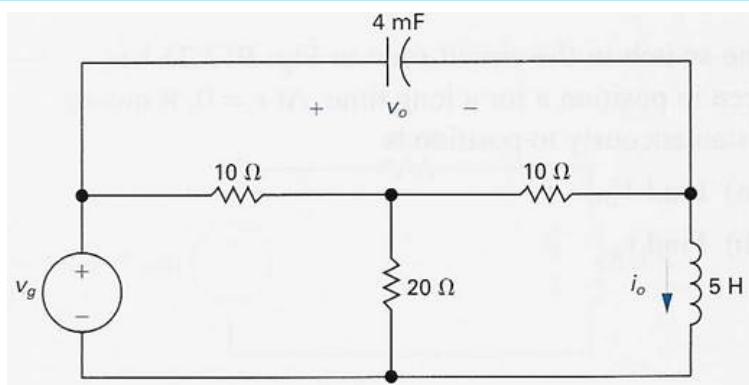

P13.27b_6ed

There is no energy stored in this circuit for $t < 0$.

Given that $v_g(t) = 75 u(t)$ for $t \geq 0$.

a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the current $i_o(t)$.

$$I_0(s) = \boxed{-2.3} \times / [s (s + \boxed{-0.8503} \times)]$$

b) Find the time domain $i_o(t)$.

$$i_o(t) = \boxed{2.99} \checkmark [1 - \exp(\boxed{0.8503} \times t)] u(t) \text{ A}$$

$$I_0 = \frac{15}{s(s+5)}$$

$$i_0(t) = 3[1 - e^{-5t}]u(t) \text{ Amps}$$


Partially correct

Marks for this submission: 2.50/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

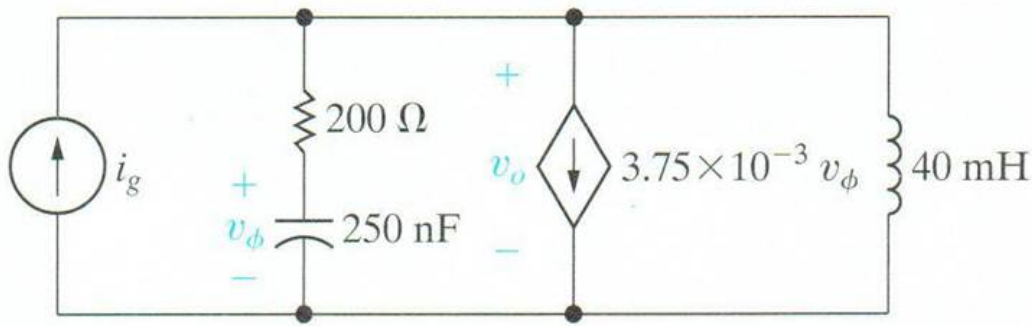

P13.17_7ed

Given: No energy is stored in this circuit for $t < 0$ and $i_g = 5 \text{ mA}$ for $t \geq 0$.

a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the voltage $v_o(t)$.

$$V(s) = (s + 20000) / (s + 10000)^2$$

b) Find the inverse transform to find the time domain $v_o(t)$.

$$v_o(t) = [10000 t \exp(-10000 t) + \exp(-10000 t)] u(t) \text{ V}$$

$$V_0(s) = \frac{s+20,000}{(s+10,000)^2}$$

$$v_0(t) = [10,000 t e^{-10,000 t} + e^{-10,000 t}] u(t) \text{ Volts}$$


Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

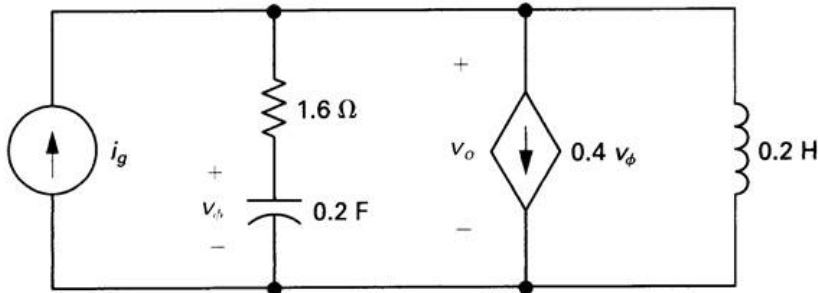

P13.11_6ed

There is no energy stored in the circuit at $t = 0$.

Find $v_o(t)$ if $i_g(t) = 15 u(t) \text{ A}$.

$$v_o(t) = [-45 t \exp(-5 t) + 24 \exp(-5 t)] u(t) \text{ V}$$

$$v_0(t) = [-45 t e^{-5 t} + 24 e^{-5 t}] u(t) \text{ V}$$


Correct

Marks for this submission: 10.00/10.00.

Question 4

Partially correct

Mark 8.42 out of 10.00

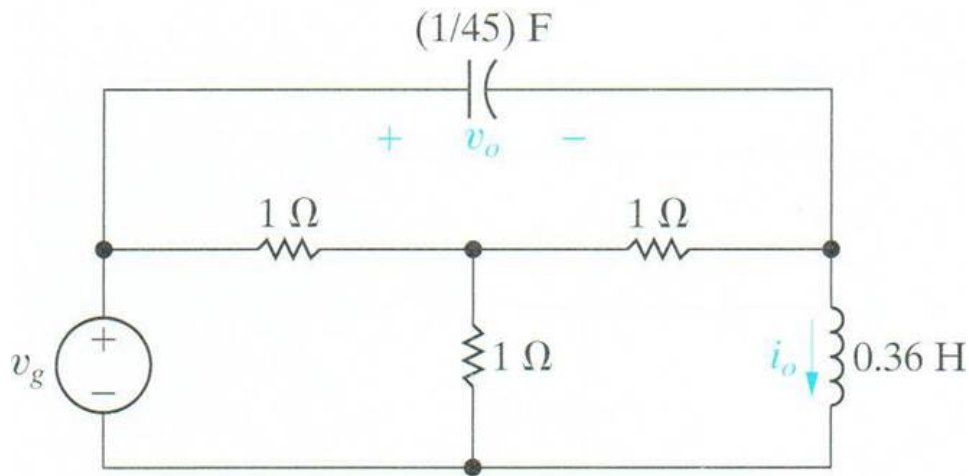

P13.28_7ed

Given: No energy is stored in this circuit for $t < 0$ and $v_g(t) = 54 \text{ V}$ for $t \geq 0$.

a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the voltage $v_o(t)$ and $i_o(t)$.

$$V_o(s) = \frac{449.982 \times (54 \times s + -5)}{(s + 5)(s + 25)}$$

$$I_o(s) = \frac{150}{(s + 15)(s + 5)(s + 25)}$$

b) Find the inverse transform to find the time domain $v_o(t)$ and $i_o(t)$.

$$v_o(t) = [54 + -27 \exp(-5t) + -27 \exp(-25t)] u(t) \text{ V}$$

$$i_o(t) = [18 + -15 \exp(-5t) + -3 \exp(-25t)] u(t) \text{ A}$$

$$V_o = \frac{270(3s+25)}{s(s+5)(s+25)} \quad I_o = \frac{150(s+15)}{s(s+5)(s+25)}$$

$$v_o(t) = [54 - 27e^{-5t} - 27e^{-25t}] u(t) \text{ V}$$

$$i_o(t) = [18 - 15e^{-5t} - 3e^{-25t}] u(t) \text{ A}$$


Partially correct

Marks for this submission: 8.42/10.00. Accounting for previous tries, this gives 8.42/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

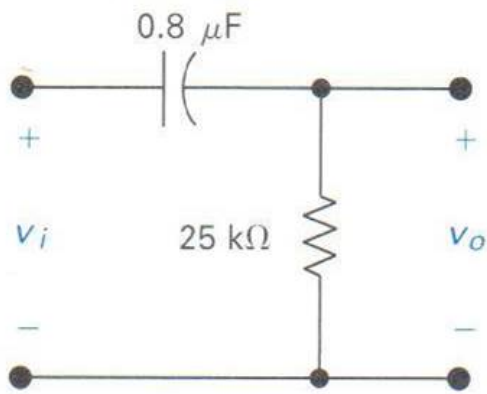

P13.49b_6ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = s / (s + 50) \quad \checkmark$$

$$H(s) = \frac{s}{s+50}$$


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

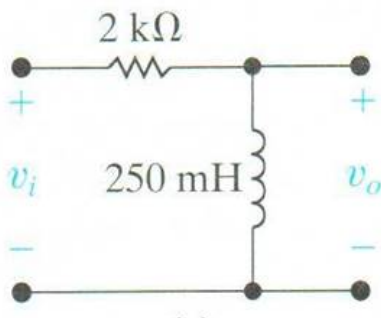

P13.49c_7ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = s / (s + 8000) \quad \checkmark$$

$$H(s) = \frac{s}{s+8,000}$$


Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

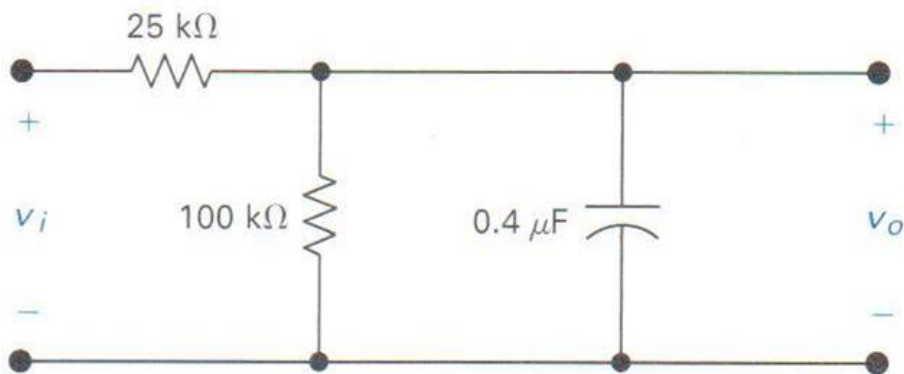

P13.49e_6ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = \frac{100}{s + 125}$$

$$H(s) = \frac{100}{s + 125}$$


Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

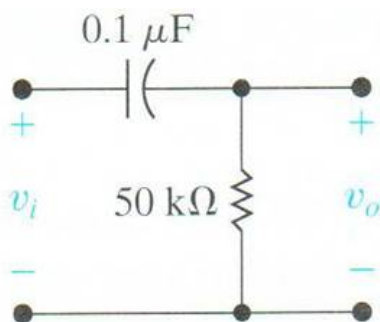

P13.49b_7ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = \frac{s}{s + 200}$$

$$H(s) = \frac{s}{s + 200}$$


Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

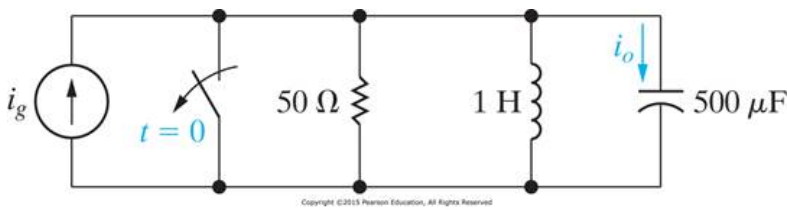

P13.56_10ed

There is no energy stored in this circuit at the time the switch is opened. The sinusoidal current source is generating the signal $25 \cos(200t)$ mA (milli Amp). The desired response signal is the current $i_o(t)$.

a) Find the s domain transfer function $H(s) = I_o/I_g$ for this circuit.

$$H(s) = s^2 / (s^2 + \boxed{40} s + \boxed{2000})$$

b) Find the s domain form for $I_o(s)$.

$$I_o(s) = \boxed{0.025} s^3 / (\text{There are four factors in the denominator – list each one separately})$$

$$\text{Factor 1: } s + 20 - j \boxed{40}$$

$$\text{Factor 2: } s + 20 + j \boxed{40}$$

$$\text{Factor 3: } s + 0 - j \boxed{200}$$

$$\text{Factor 4: } s + 0 + j \boxed{200}$$

c) Find the time domain form $i_o(t)$.

$$i_o(t) = [\boxed{1.44} \exp(\boxed{-20} t) \cos(\boxed{40} t + \boxed{-97.94}^\circ) + \boxed{25.76} \cos(\boxed{200} t + \boxed{11.98}^\circ)] u(t) \text{ mA (milli A)}$$

$$H(s) = \frac{I_o}{I_g} = \frac{s^2}{s^2 + 40s + 2,000}$$

$$I_o = \frac{0.025s^3}{(s+20-j40)(s+20+j40)(s+0-j200)(s+0+j200)}$$

$$i_o(t) = [1.4395e^{-20t} \cos(40t - 97.94^\circ) + 25.7514 \cos(200t + 11.89^\circ)] u(t) \text{ mA}$$


Correct

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of 10.00

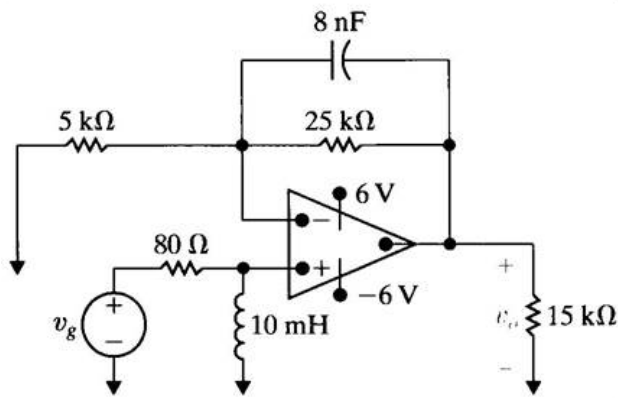

P13.78_7ed and P13.77_10ed

You may assume the opamp is ideal.

a) Find the s domain transfer function $H(s) = V_0/V_g$ for this circuit.

$$H(s) = s * (s + 30000) / [(s + 5,000) * (s + 8000)]$$

b) Find the time domain $v_0(t)$ if $v_g(t) = 600 u(t)$ mV (milli V).

$$v_0(t) = [5 e^{-5,000t} + -4.4 \exp(-8000t)] u(t) \text{ V}$$

c) Find the steady-state express for $v_0(t)$ if $v_g(t) = 2 \cos(10,000 t)$ V.

$$v_0(t)_{\text{steady-state}} = [4.42 \cos(10000t - 6.34^\circ)] u(t) \text{ V}$$

$$H(s) = \frac{s(s+30,000)}{(s+5,000)(s+8,000)}$$

$$v_0(t) = [5e^{-5,000t} - 4.4e^{-8,000t}] u(t) \text{ Volts}$$

$$v_0(t)_{\text{steady-state}} = 4.4172 \cos(10,000t - 6.34^\circ) u(t) \text{ Volts}$$

Correct

Marks for this submission: 10.00/10.00.