

**Started on** Monday, 24 October 2016, 12:13 PM

**State** Finished

**Completed on** Monday, 24 October 2016, 12:14 PM


**Time taken** 1 min 15 secs

**Grade** 100.00 out of 100.00

**Question 1**

Correct

Mark 10.00 out of 10.00

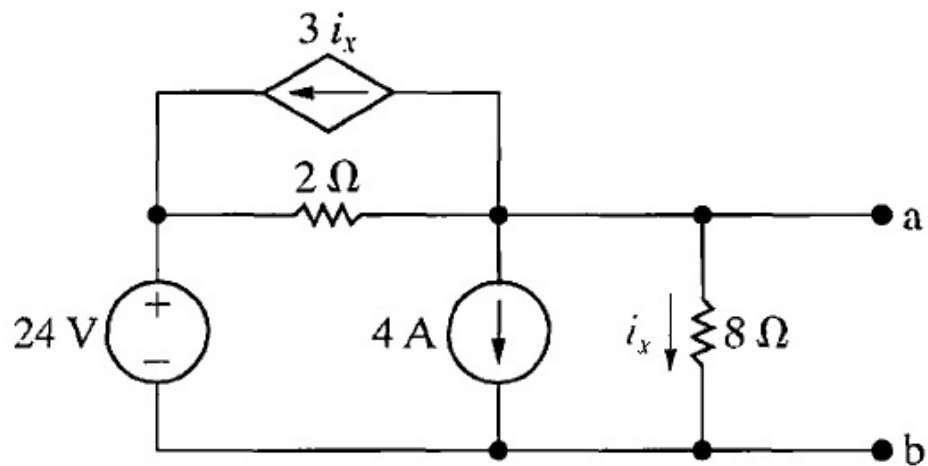

AP4.19\_9ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown

$V_{Th} =$    $\checkmark$  V


$R_{Th} =$    $\checkmark$  Ω (Ohm)

**Correct**

Marks for this submission: 10.00/10.00.

**Question 2**

Correct

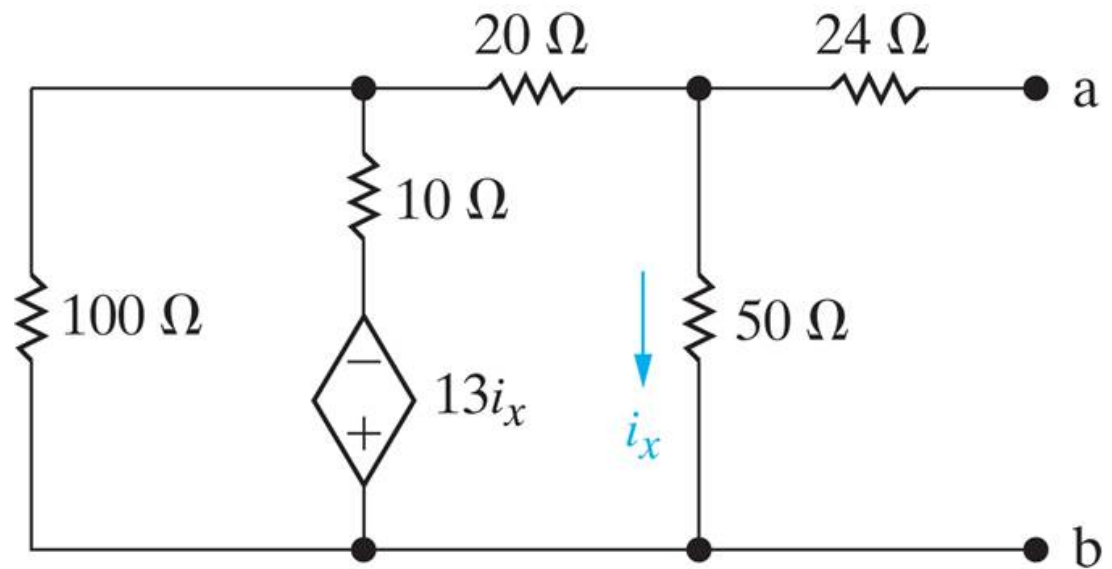Mark 10.00 out of  
10.00

P4.80\_10ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown.

Hint: Note that there are no independent sources in this circuit! You will have to provide an excitation to get a response.

$$V_{Th} = 0 \text{ V}$$


$$R_{Th} = 40 \text{ } \Omega \text{ (Ohm)}$$

**Correct**

Marks for this submission: 10.00/10.00.

**Question 3**

Correct

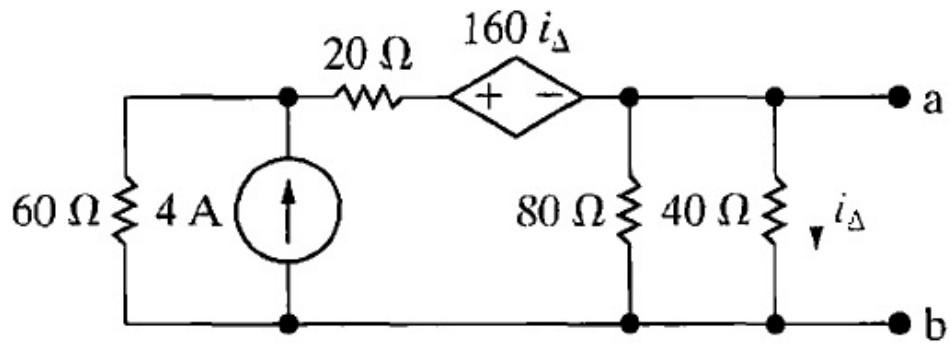Mark 10.00 out of  
10.00

AP4.20\_9ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown.

Hint: Define the voltage at the left-most node as  $v$ , and write two nodal equations with  $V_{Th}$  as the right node voltage.

$$V_{Th} = 30 \text{ V}$$


$$R_{Th} = 10 \text{ } \Omega \text{ (Ohm)}$$

**Correct**

Marks for this submission: 10.00/10.00.

**Question 4**

Correct

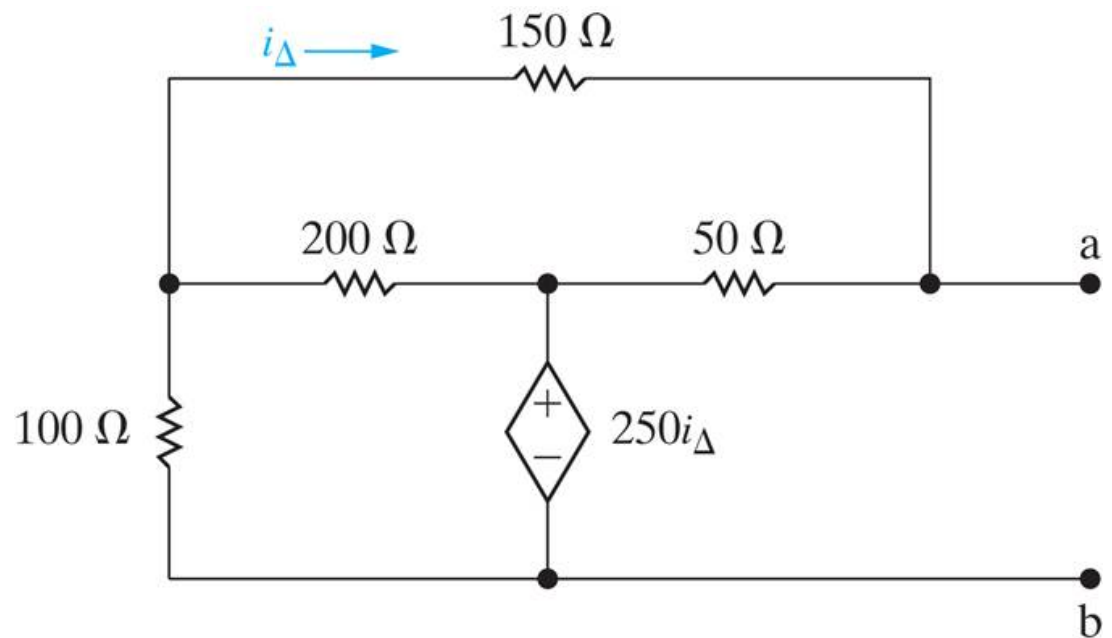Mark 10.00 out of  
10.00

Copyright ©2015 Pearson Education, All Rights Reserved

P4.79\_10ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown.

Hint: Note that there are no independent sources in this circuit! You will have to provide an excitation to get a response.

$$V_{Th} = 0 \text{ V}$$

$$R_{Th} = 15.38 \text{ } \Omega \text{ (Ohm)}$$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 5**

Correct

Mark 10.00 out of 10.00

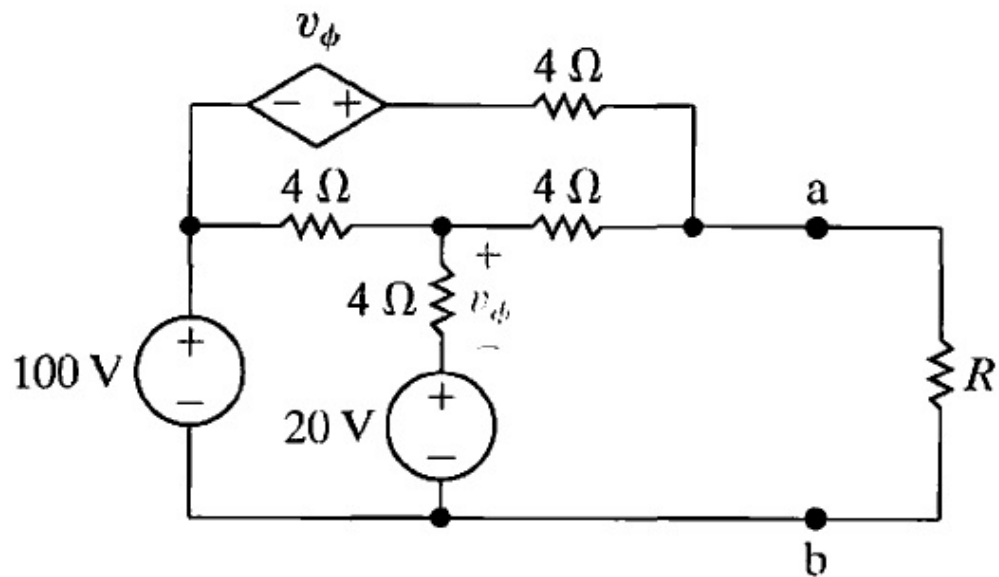

AP4.21\_9ed

a) Find the value of  $R$  that enable the circuit to deliver maximum power to the terminals a,b

$$R = 3 \checkmark \Omega \text{ (Ohm)}$$

b) Find the maximum power delivered to  $R$

$$P_R = 1200 \checkmark \text{ W}$$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 6**

Correct

Mark 10.00 out of 10.00

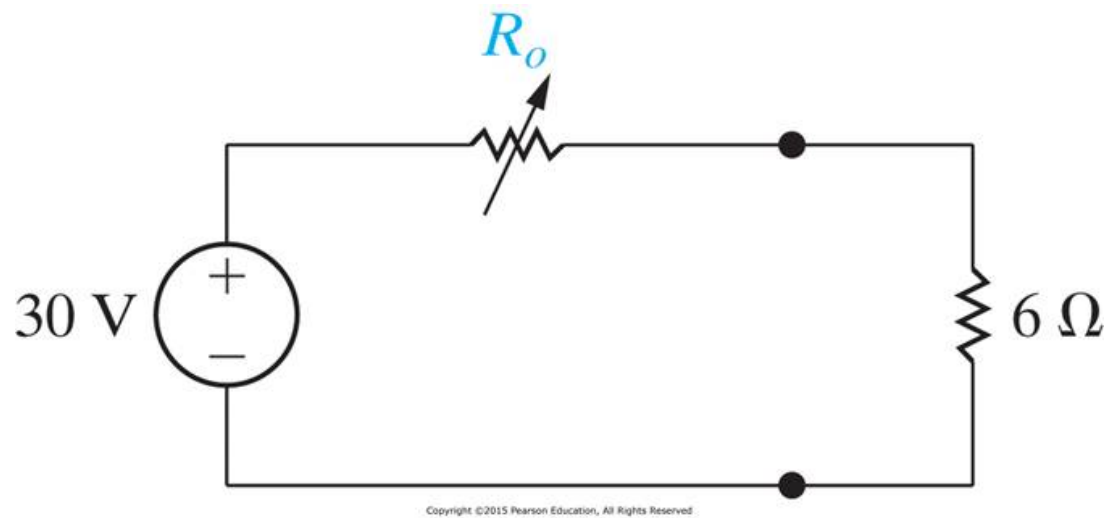

P4.85\_10ed

a) Find the value of the variable resistor  $R_o$  in the circuit that will result in maximum power dissipation in the  $6\ \Omega$  (Ohm) resistor.  $0 \leq R_o \leq \infty$

$$R_o = \boxed{0} \checkmark \Omega \text{ (Ohm)}$$

b) Find the maximum power that can be delivered to the  $6\ \Omega$  (Ohm) resistor.


$$P_{\max} = \boxed{150} \checkmark \text{ W}$$

**Correct**

Marks for this submission: 10.00/10.00.

**Question 7**

Correct

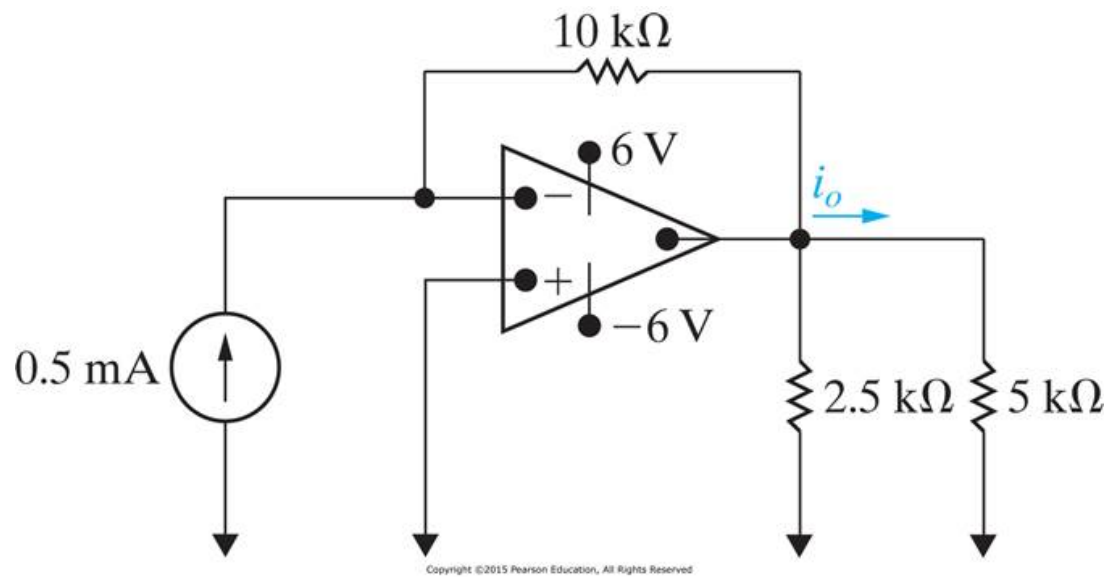Mark 10.00 out of  
10.00

P5.05\_10ed

Assume the op amp is ideal.

Find current  $i_o$  which flows through the 5k  $\Omega$  resistor.


$$i_o = \boxed{-1} \checkmark \text{ mA (milli Amp)}$$

**Correct**

Marks for this submission: 10.00/10.00.

**Question 8**

Correct

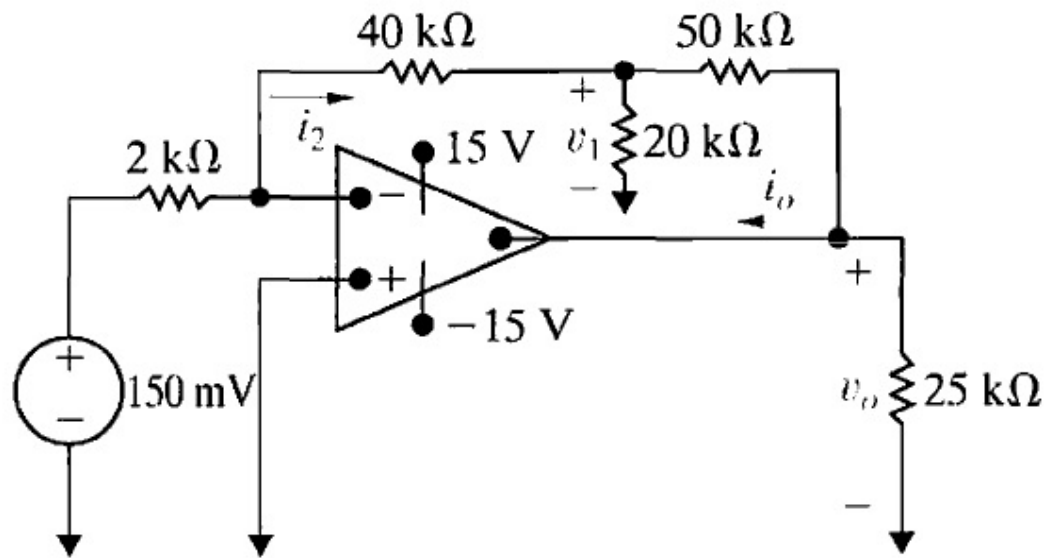Mark 10.00 out of  
10.00

P5.06\_9ed

Assume the op amp is ideal.

Calculate  $v_1$ ,  $v_O$ ,  $i_2$ , and  $i_O$ .

$$v_1 = -3 \text{ V}$$

$$v_O = -14.25 \text{ V}$$

$$i_2 = 75 \text{ } \mu\text{A (micro Amp)}$$

$$i_O = 795 \text{ } \mu\text{A (micro Amp)}$$


**Correct**

Marks for this submission: 10.00/10.00.



**Question 9**

Correct

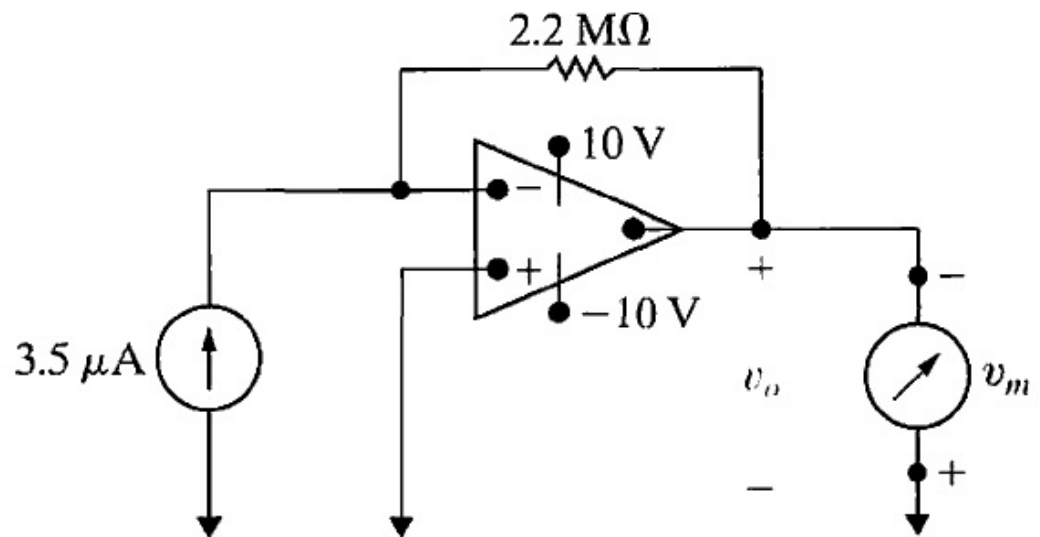Mark 10.00 out of  
10.00

P5.07\_10ed

Assume the op amp is ideal.

A voltmeter capable of a full-scale reading of 10 V is used to measure the output in the circuit in the figure below. What is the reading of the voltmeter?


$$v_m = 7.7 \text{ V}$$

**Correct**

Marks for this submission: 10.00/10.00.


**Question 10**

Correct

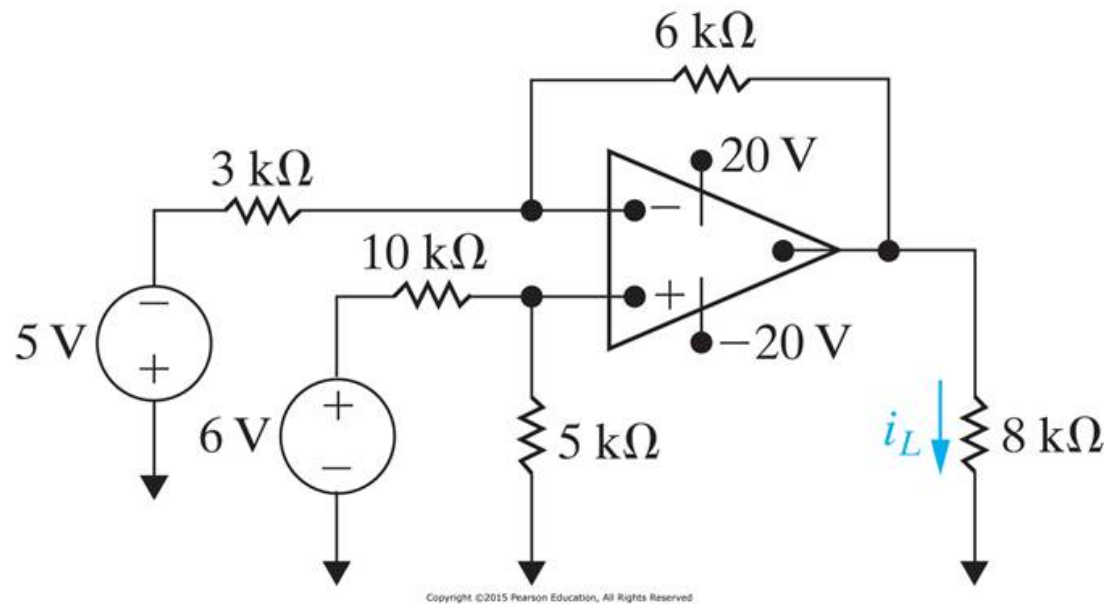Mark 10.00 out of  
10.00

P5.03\_10ed

Assume the op amp is ideal.

Find  $i_L$  in this circuit.  $i_L =$    mA (milli Amps)**Correct**

Marks for this submission: 10.00/10.00.