

Home ► My courses ► **EEE117-2019S-Sec1** ► Homework ►
Homework 3 - Chapter 10

Started on	Wednesday, 6 February 2019, 11:38 AM
-------------------	--------------------------------------

State	Finished
--------------	----------

Completed on	Wednesday, 6 February 2019, 11:39 AM
---------------------	--------------------------------------


Time taken	44 secs
-------------------	---------

Grade	100.00 out of 100.00
--------------	-----------------------------

Question 1

Correct

Mark 10.00 out of 10.00

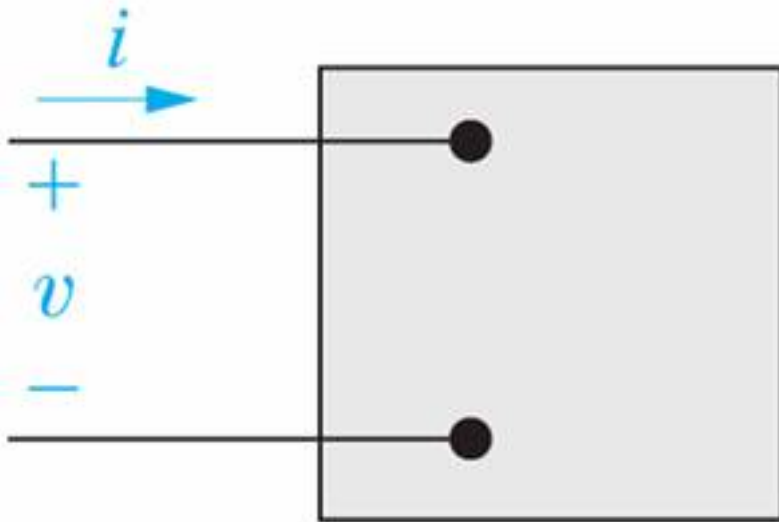

P10.01d_9ed

For the following set of values, calculate P , Q and state whether the circuit inside the box is absorbing or delivering (1) average power and (2) magnetizing vars.

d) $v = 200 \sin(\omega t + 250^\circ) \text{ V}$ $i = 5 \cos(\omega t + 40^\circ) \text{ A}$

$P =$ ✓ W ▼ ✓ Watts

$Q =$ ✓ VARs ▼ ✓ VARs


Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

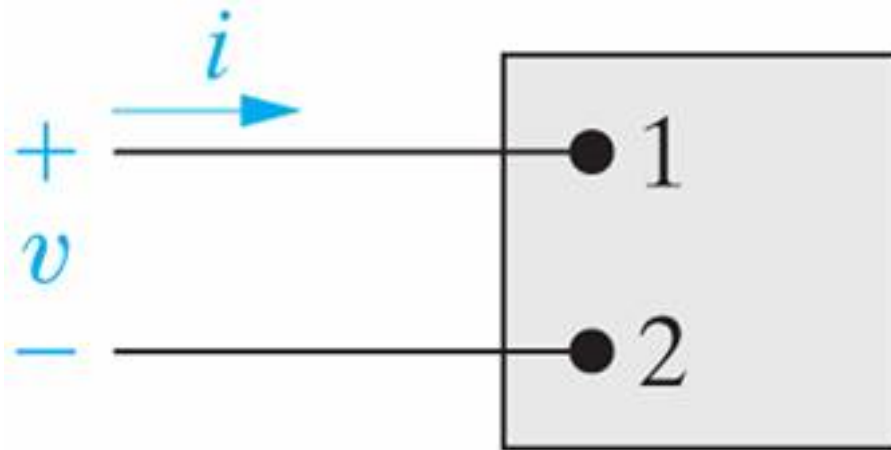

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P10.01b_6ed

Calculate P and Q of the following voltage and current. State whether the element is absorbing or delivering average power and magnetizing VARs.

$$v = 75 \cos(\omega t - 15^\circ) \text{ V}$$

$$i = 16 \cos(\omega t + 60^\circ) \text{ A}$$

P = ✓ W ▼ ✓ Watts

Q = ✓ VAR ▼ ✓ VARs


Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

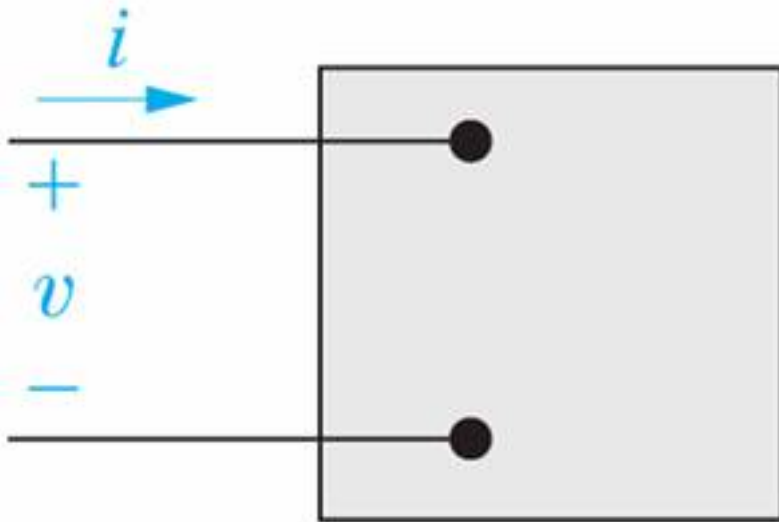

P10.01c_9ed

For the following set of values, calculate P , Q and state whether the circuit inside the box is absorbing or delivering (1) average power and (2) magnetizing vars.

c) $v = 400 \cos(\omega t + 30^\circ) \text{ V}$ $i = 10 \sin(\omega t + 240^\circ) \text{ A}$

$P =$ ✓ W ▼ ✓ Watts

$Q =$ ✓ VARs ▼ ✓ VARs


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

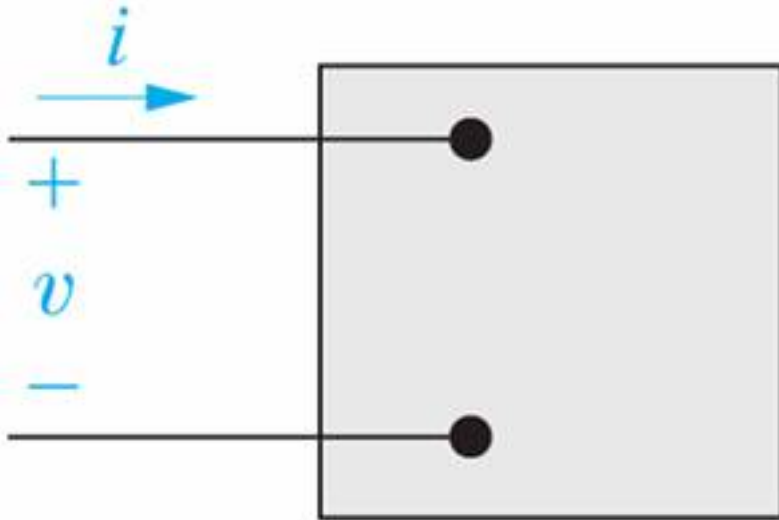

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P10.01b_9ed

For the following set of values, calculate P , Q and state whether the circuit inside the box is absorbing or delivering (1) average power and (2) magnetizing vars.

b) $v = 40 \cos(\omega t - 15^\circ) \text{ V}$ $i = 20 \cos(\omega t + 60^\circ) \text{ A}$

$P =$ ✓ W ▼ ✓ Watts

$Q =$ ✓ VARs ▼ ✓ VARs


Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

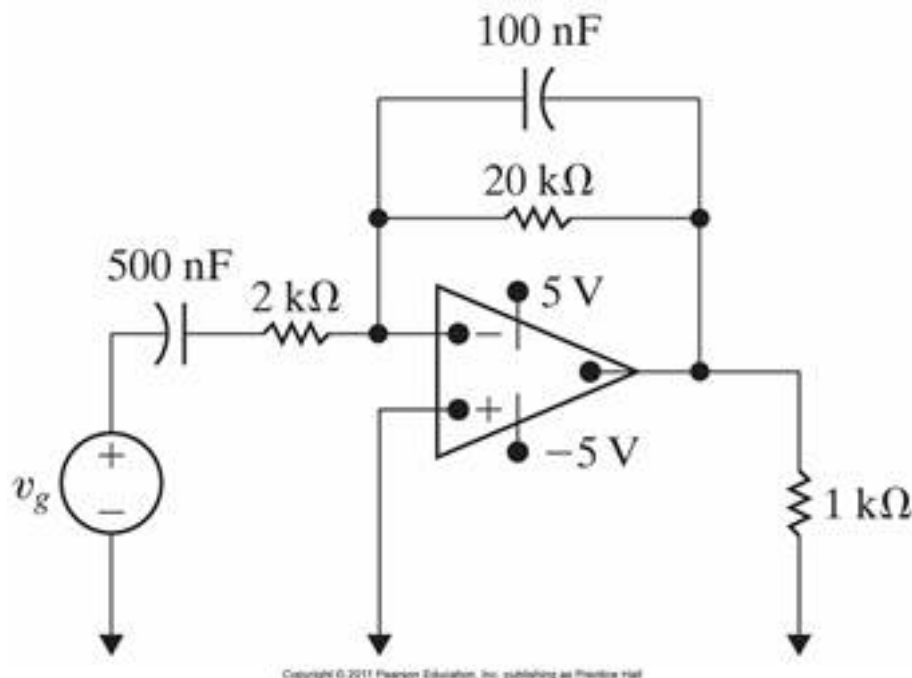


P10.07_9ed

The opamp is ideal.

$$v_g = \cos(1,000 t) \text{ V}$$

Calculate the average power dissipated by the $1\text{ k}\Omega$ (kilo Ohm) resistor.

$P_{\text{avg}, 1\text{k}\Omega} =$  mW (milli Watt) “+” = absorbed “-” = delivered


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct


Mark 10.00 out of 10.00

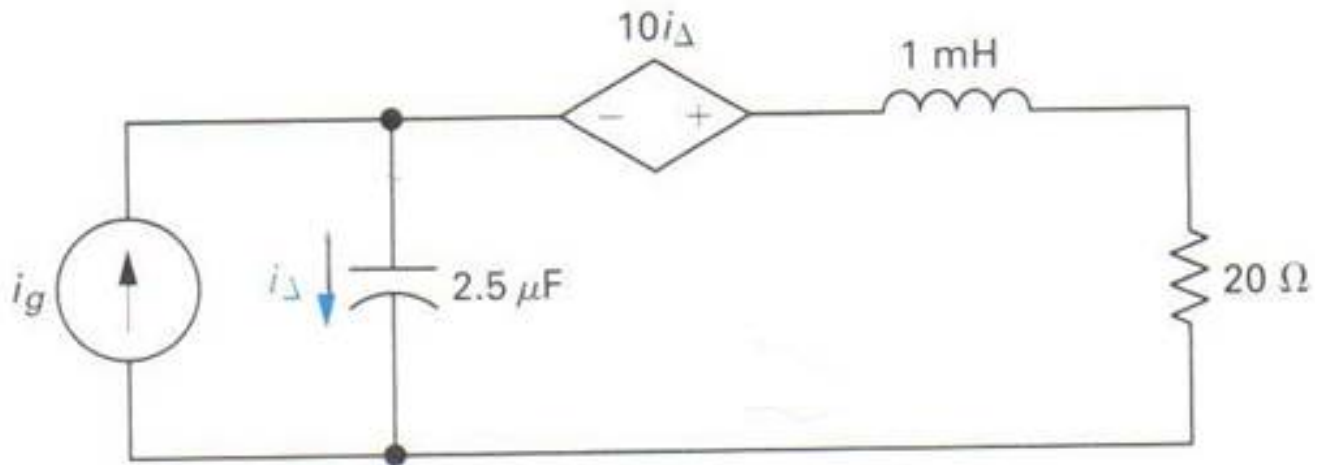

P10.9_6ed

Given: $i_g = 15 \cos(10,000 t) \text{ A}$

Find the average power absorbed by the 20Ω (Ohm) resistor.

$P_{\text{avg}, 20\Omega} =$  W “+” = absorbed and “-” = delivered

Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

P10.11a_9ed

A personal computer with a monitor and keyboard voltage and current are:

$$v(t) = 115 \cos(2\pi 60 + 0^\circ) \text{ V}_{\text{rms}} \quad i(t) = 0.5 \cos(2\pi 60 - 25^\circ) \text{ Arms}$$

Calculate the real power absorbed by the computer system.

$$P_{\text{computer}} = \boxed{52} \checkmark \text{ W} \quad \text{"+" = absorbed} \quad \text{"-" = delivered}$$


Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

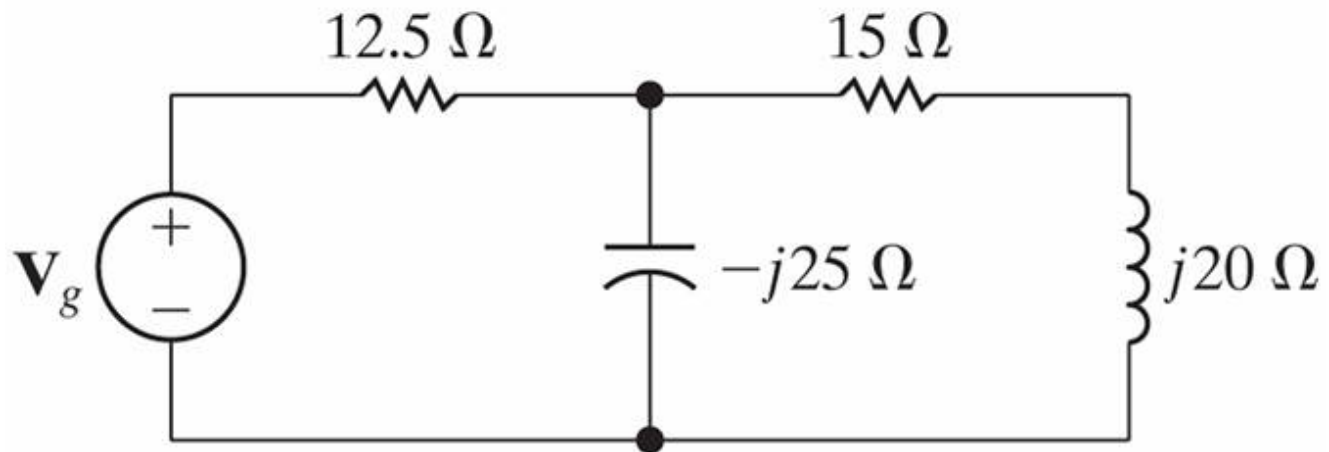

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P10.16_9ed

The voltage V_g is 240 at angle 0° V_{rms} (240 V_{rms} at angle zero degrees)

a) Find the average and reactive power for the voltage source V_g .

$$S_g = \boxed{-1084} \checkmark + j \boxed{271} \checkmark \text{ VA}$$

b) Is the voltage source absorbing or delivering average power?

Watts

c) Is the voltage source absorbing or delivering magnetizing VARs?

VARs

d) Find the average and reactive powers associated with each element in this circuit.

$$P_{12.5\Omega} = \boxed{271} \checkmark \text{ W}$$

$$Q_{-j25\Omega} = \boxed{-1355} \checkmark \text{ VAR}$$

$$P_{15\Omega} = \boxed{813} \checkmark \text{ W}$$

$$Q_{j20\Omega} = \boxed{1084} \checkmark \text{ VAR}$$


Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

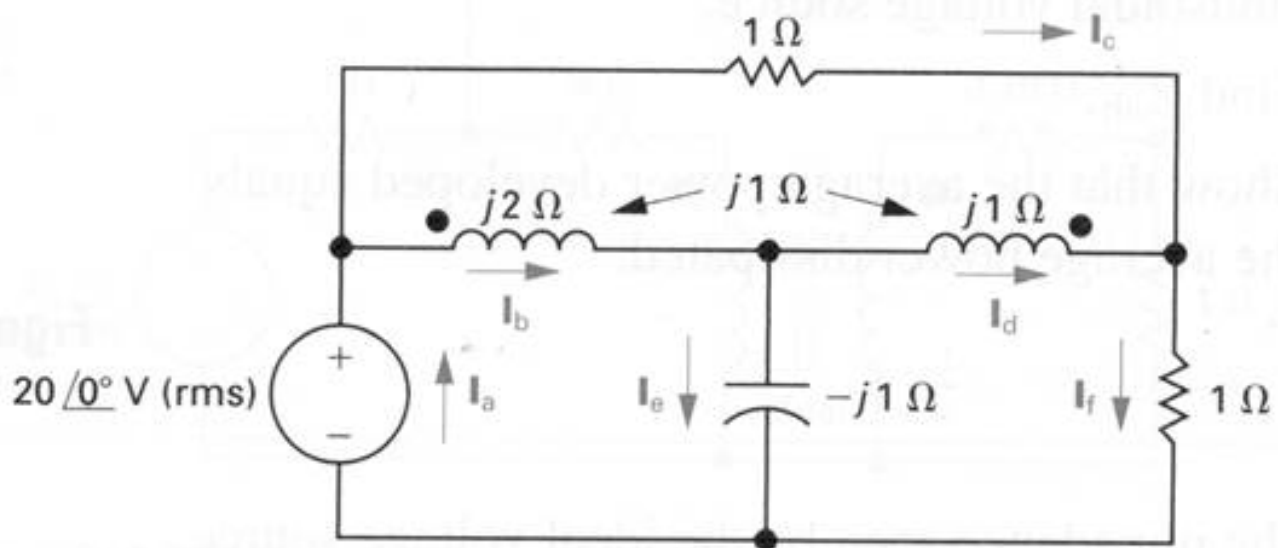

P10.48_6ed

Mesh analysis in a mutually inductive circuit.

a) Find the six phasor branch currents.

$$\mathbf{I}_a = 20 + j(-20) \text{ A}_{\text{rms}}$$

$$\mathbf{I}_b = 0 + j(-20) \text{ A}_{\text{rms}}$$

$$\mathbf{I}_c = 20 + j0 \text{ A}_{\text{rms}}$$

$$\mathbf{I}_d = -20 + j0 \text{ A}_{\text{rms}}$$

$$\mathbf{I}_e = 20 + j(-20) \text{ A}_{\text{rms}}$$

$$\mathbf{I}_f = 0 + j0 \text{ A}_{\text{rms}}$$

b) Find the complex power in each of the six branches.

$$\mathbf{S}_a = -400 + j(-400) \text{ VA}$$

$$S_b = \boxed{-400} \checkmark + j \boxed{800} \checkmark \text{ VA}$$

$$S_c = \boxed{400} \checkmark + j \boxed{0} \checkmark \text{ VA}$$

$$S_d = \boxed{400} \checkmark + j \boxed{400} \checkmark \text{ VA}$$

$$S_e = \boxed{0} \checkmark + j \boxed{-800} \checkmark \text{ VA}$$

$$S_f = \boxed{0} \checkmark + j \boxed{0} \checkmark \text{ VA}$$


Correct

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of 10.00

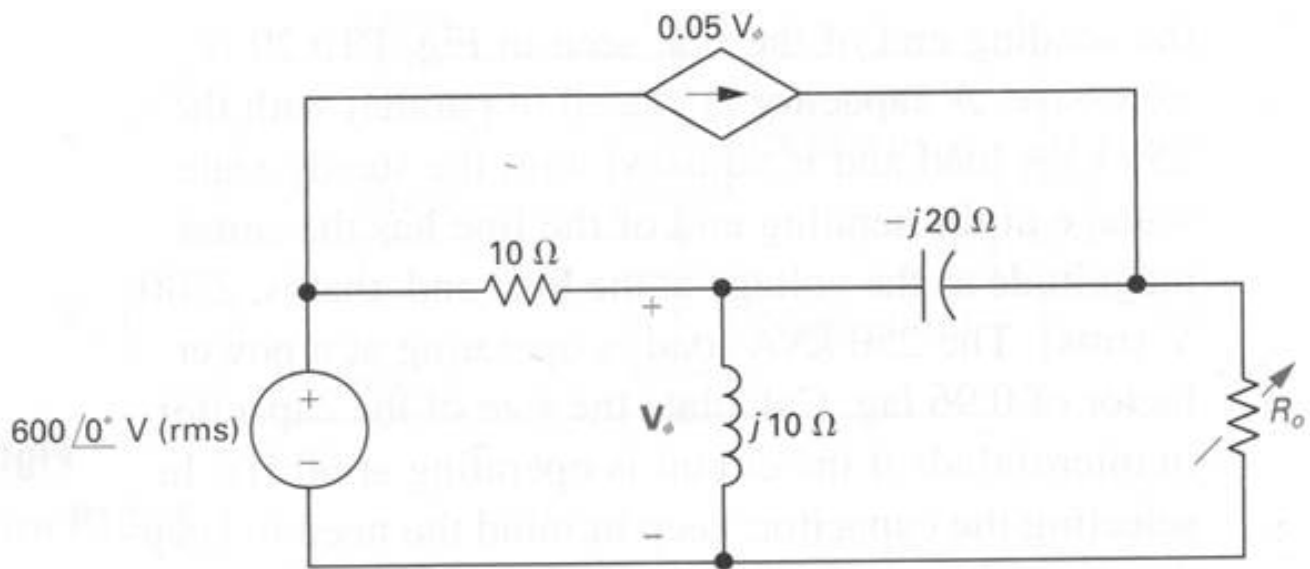

P10.33_6ed

The variable resistor R_0 in this circuit is adjusted until maximum average power is delivered to R_0 .

a) What is the value of R_0 in Ohms?

$$R_0 = \boxed{20} \checkmark \Omega \text{ (Ohm)}$$

b) Calculate the average power delivered to R_0 in this maximum average power condition.

$$P_{R0} = \boxed{9000} \checkmark \text{ W}$$

c) If R_0 is replaced with variable impedance Z_0 , what is the maximum average power that can be delivered to Z_0 ?

$$P_{Z0} = \boxed{12000} \checkmark \text{ W}$$

Correct

Marks for this submission: 10.00/10.00.

◀ Homework 2 - Chapter 9

Jump to...



Homework 4 - Chapter 11 ▶