

Home ► My courses ► 174-185-Sum19 ► Quizzes ►
Homework 0 Quiz

Started on Wednesday, 10 July 2019, 8:58 PM

State Finished

Completed on Wednesday, 10 July 2019, 9:00 PM

Time taken 2 mins 33 secs

Grade **38.00** out of 38.00 (**100%**)

Question 1

Correct

Mark 2.00 out of 2.00

1,200mV is equal to:

Select one:

- ☒ a. 1.2v ✓
- ☐ b. 12v
- ☐ c. 0.0012v
- ☐ d. 0.12v

The correct answer is: 1.2v

Question 2

Correct

Mark 2.00 out of 2.00

1mA is equal to:

Select one:

- ☐ a. 0.01A
- ☐ b. 0.1A
- ☐ c. 0.00001A
- ☒ d. 0.001A ✓

The correct answer is: 0.001A

Question 3

Correct

Mark 2.00 out of 2.00

A 10k resistor in parallel with 10k produces:

Select one:

- ☐ a. 10k
- ☒ b. 5k ✓
- ☐ c. 20k
- ☐ d. Cannot be determined

The correct answer is: 5k

Question 4

Correct

Mark 2.00 out of 2.00

A DC voltage . . .

Select one:

- ☒ a. remains constant ✓
- ☐ b. rises and falls
- ☐ c. is a sinewave
- ☐ d. is an audio waveform

The correct answer is: remains constant

Question 5

Correct

Mark 2.00 out of 2.00

A red-red-red-gold resistor in series with an orange-orange-orange-gold resistor produces:

Select one:

- ☐ a. 5k5 ohms
- ☒ b. 35,200 ohms ✓
- ☐ c. 55k ohms
- ☐ d. None of the above

The correct answer is: 35,200 ohms

Question 6

Correct

Mark 2.00 out of 2.00

Choose the set that has 4 resistors in ascending order.

Select one:

- ☐ a. 4k7 10k 47R 330k
- ☐ b. 22R 270k 2k2 1M
- ☒ c. 3R3 4R7 22R 5k6 ✓
- ☐ d. 100R 10k 1M 3k3

The correct answer is: 3R3 4R7 22R 5k6

Question 7

Correct

Mark 2.00 out of 2.00

For the AND gate, what is the output when both inputs are HIGH:

Select one:

- ☐ a. Can be HIGH or LOW
- ☐ b. Cannot be determined
- ☐ c. LOW
- ☒ d. HIGH ✓

The correct answer is: HIGH

Question 8

Correct

Mark 2.00 out of 2.00

For the XOR gate, what is the output when both inputs are HIGH:

Select one:

- ☒ a. LOW ✓
- ☐ b. HIGH
- ☐ c. Cannot be determined
- ☐ d. Can be HIGH or LOW

The correct answer is: LOW

Question 9

Correct

Mark 2.00 out of 2.00

If a 10k resistor is placed across a 10v supply, the current will be:

Select one:

- ☐ a. 0.01mA
- ☐ b. 10mA
- ☐ c. 0.1mA
- ☒ d. 1mA ✓

The correct answer is: 1mA

Question 10

Correct

Mark 2.00 out of 2.00

If two resistors are placed in series, is the final resistance:

Select one:

- ☒ a. Higher ✓
- ☐ b. Lower
- ☐ c. The same
- ☐ d. Cannot be determined

The correct answer is: Higher

Question 11

Correct

Mark 2.00 out of 2.00

The current requirement of a LED is:

Select one:

- ☐ a. 1.7mA
- ☐ b. 25mA
- ☐ c. 65mA
- ☒ d. Between 3 and 35mA ✓

The correct answer is: Between 3 and 35mA

Question 12

Correct

Mark 2.00 out of 2.00

To obtain a higher value of resistance, resistors are connected in:

Select one:

- ☐ a. Reverse
- ☒ b. Series ✓
- ☐ c. Forward
- ☐ d. Parallel

The correct answer is: Series

Question 13

Correct

Mark 2.00 out of 2.00

Using the color code below, determine the value of each of the resistors. Hint: You may want to use Lab 0 Appendix B for the resistor color code. Color code : red, orange, red

Select one:

- ☐ a. 3200 ohms
- ☐ b. 320 ohms
- ☐ c. 230 ohms
- ☒ d. 2300 ohms ✓

The correct answer is: 2300 ohms

Question 14

Correct

Mark 2.00 out of 2.00

Using the color code below, determine the value of each of the resistors. Hint: You may want to use Lab0 Appendix B for the resistor color code. Color code : brown, black, orange

Select one:

- ☒ a. 10 K ohms ✓
- ☐ b. 1 K ohms
- ☐ c. 100 K ohms
- ☐ d. 100 ohms

The correct answer is: 10 K ohms

Question 15

Correct

Mark 2.00 out of 2.00

Using the color code below, determine the value of each of the resistors. Hint: You may want to use Lab0 Appendix B for the resistor color code. Color code : orange, orange, orange

Select one:

- ☐ a. 330 K ohms
- ☒ b. 33 K ohms ✓
- ☐ c. 330 ohms
- ☐ d. 3.3 K ohms

The correct answer is: 33 K ohms

Question 16

Correct

Mark 2.00 out of 2.00

Using the color code below, determine the value of each of the resistors. Hint: You may want to use Lab0 Appendix B for the resistor color code. Color code : brown, black, green

Select one:

- ☐ a. 10 K ohms
- ☐ b. 1 K ohms
- ☒ c. 1 M ohms ✓
- ☐ d. 100 K ohms

The correct answer is: 1 M ohms

Question 17

Correct

Mark 2.00 out of 2.00

Using the color code below, determine the value of each of the resistors. Hint: You may want to use Lab0 Appendix B for the resistor color code. Color code : red-red-red-gold

Select one:

- ☒ a. 2.2 K ohms 5% ✓
- ☐ b. 2.2 K ohms 10%
- ☐ c. 2.2 K ohms 2%
- ☐ d. 2.2 K ohms 1%

The correct answer is: 2.2 K ohms 5%

Question 18

Correct

Mark 2.00 out of 2.00

What does the acronym LED mean?

Select one:

- ☐ a. Light Emitting Display
- ☐ b. Low Energy Display
- ☒ c. Light Emitting Diode ✓
- ☐ d. Light Emitting Detector

The correct answer is: Light Emitting Diode

Question 19

Correct

Mark 2.00 out of 2.00

What is the approximate characteristic voltage that develops across A red LED?

Select one:

- ☒ a. 1.7 V ✓
- ☐ b. 0.6 V
- ☐ c. 5 V
- ☐ d. 3.4 V

The correct answer is: 1.7 V

◀ Lab Assessment

Jump to...



Homework 1 Quiz ►