

Home ► Electrical Engineering ► Engr 17 F16 Tatro ► Exams and Quizzes ►
Exam 2 - Section 1 - Chapters 4, 5 and 6

Started on	Wednesday, 2 November 2016, 11:55 AM
-------------------	--------------------------------------

State	Finished
--------------	----------

Completed on	Wednesday, 2 November 2016, 12:55 PM
---------------------	--------------------------------------


Time taken	59 mins 42 secs
-------------------	-----------------

Grade	82.50 out of 100.00
--------------	----------------------------

Question 1

Partially correct

Mark 7.50 out of 15.00

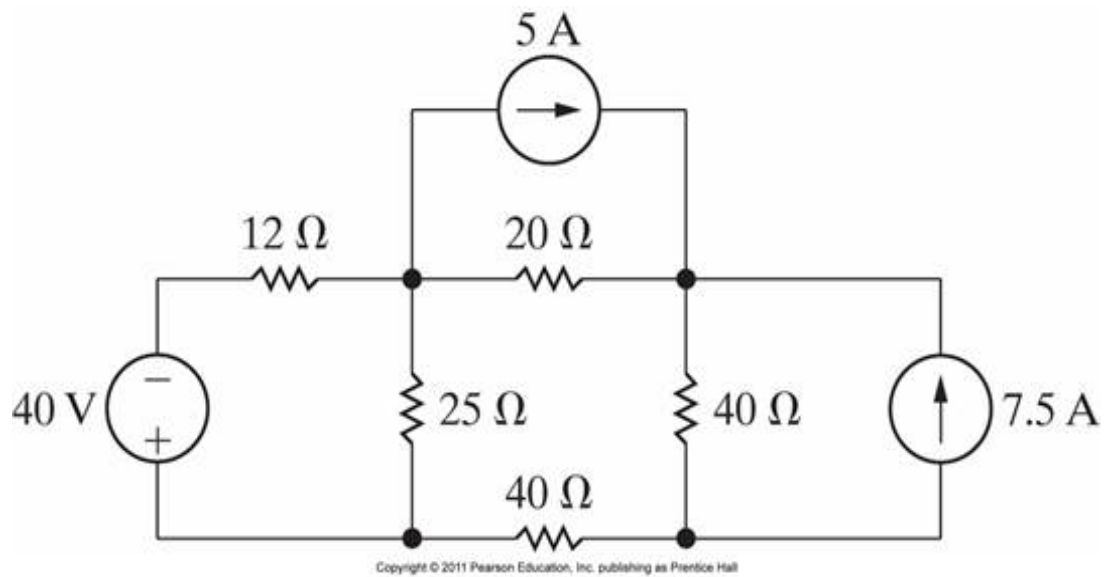

Q1d

a) Find the voltage across the 7.5A current source.

$$V_{7.5A} = -122 \text{ Volts}$$

b) Find the voltage across the 25 Ω (Ohm) resistor.

$$V_{25\Omega} = -10 \text{ Volts}$$

Numeric Answer

$$V_{7.5A} = 216V$$

$$V_{25\Omega} = -10V$$


Partially correct

Marks for this submission: 7.50/15.00.

Question 2

Correct

Mark 15.00 out of 15.00

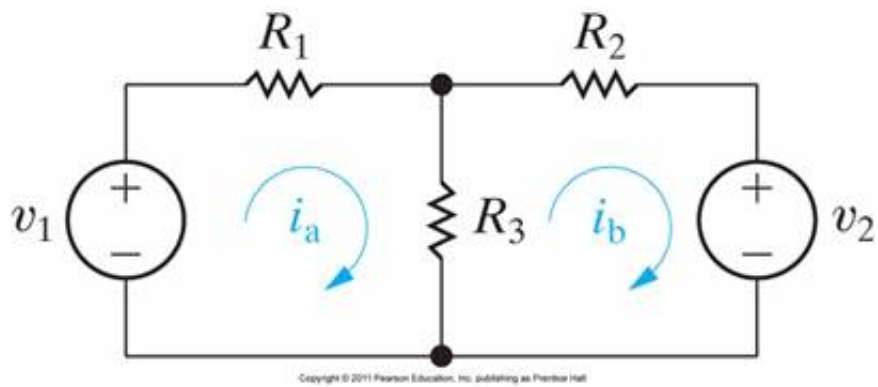

Q2j

Given:

$$v_1 = 21 \text{ Volts}$$

$$v_2 = 28 \text{ Volts}$$

$$R_1 = 10 \, \Omega \text{ (Ohms)}$$

$$R_2 = 40 \, \Omega \text{ (Ohms)}$$

$$R_3 = 80 \, \Omega \text{ (Ohms)}$$

Find the currents i_a and i_b .

$$i_a = 63.6 \text{ mA (milli Amp)}$$

$$i_b = -190.9 \text{ mA (milli Amp)}$$

Numeric Answer

$$i_a = 63.636 \text{ mA}$$


$$i_b = -190.909 \text{ mA}$$

Correct

Marks for this submission: 15.00/15.00.

Question 3

Correct

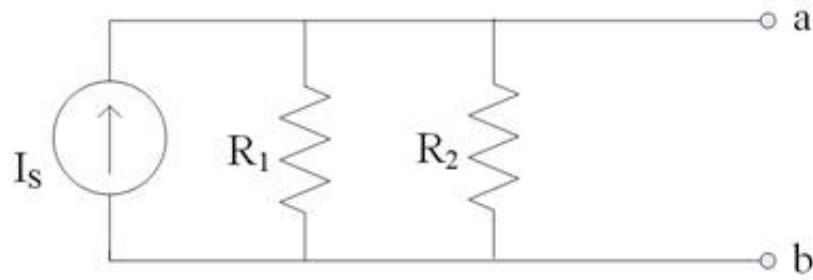Mark 10.00 out of
10.00

Q3f

Given: $I_s = 10 \text{ A}$ $R_1 = 10 \Omega$ (Ohms) $R_2 = 40 \Omega$ (Ohms)

Perform a source transformation and find the voltage transform equivalent.

this circuit.

$$V_{transform} = 80 \checkmark \text{ V}$$

$$R_{transform} = 8 \checkmark \Omega \text{ (Ohm)}$$

Numeric Answer

$$V_{transform} = 80 \text{ V}$$


$$R_{transform} = 8 \Omega \text{ (Ohm)}$$

Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

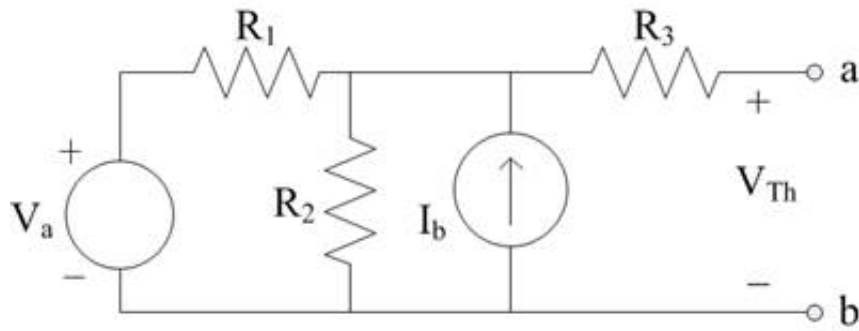Mark 15.00 out of
15.00

Q4b

Given:

$V_a = 10 \text{ Volts}$

$I_b = 3 \text{ Amps}$

$R_1 = 20 \, \Omega \text{ (Ohm)}$

$R_2 = 20 \, \Omega \text{ (Ohm)}$

$R_3 = 10 \, \Omega \text{ (Ohm)}$

a) Find the Thévenin equivalent voltage V_{Th} .

$V_{Th} = 35 \text{ Volts}$

b) Find the Thévenin equivalent resistance R_{Th} .

$R_{Th} = 20 \, \Omega \text{ (Ohms)}$

Numeric Answer

a) $V_{Th} = 35.0 \text{ Volts}$


b) $R_{Th} = 20.0 \, \Omega \text{ (Ohms)}$

Correct

Marks for this submission: 15.00/15.00.

Question 5

Correct

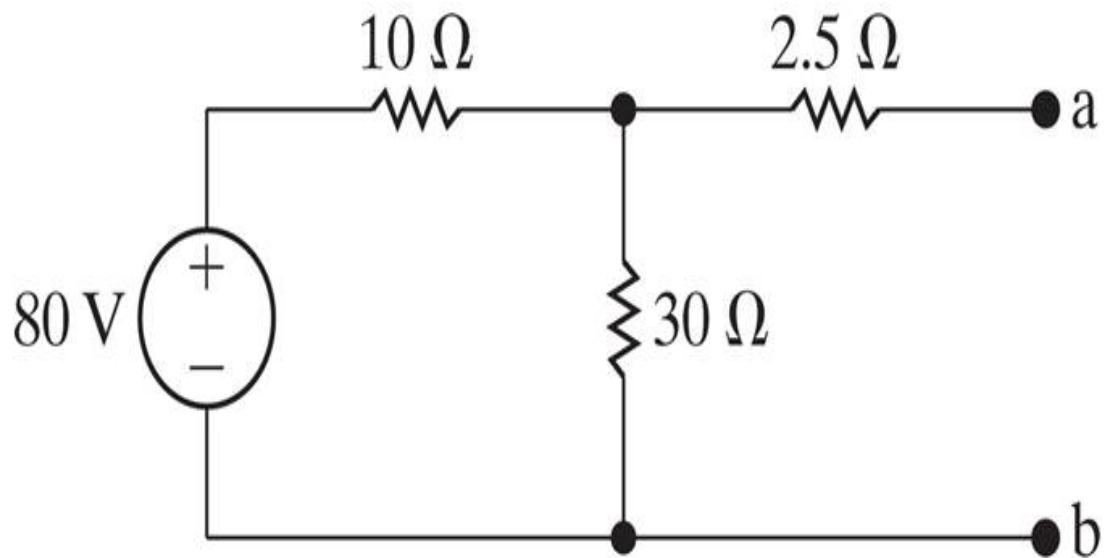Mark 15.00 out of
15.00

Copyright ©2015 Pearson Education, All Rights Reserved

Q5b

Find the Norton equivalent circuit with respect to terminals ab.

$$I_N = 6 \text{ A}$$

$$R_{Th} = 10 \text{ } \Omega \text{ (Ohm)}$$

Numeric Answer

$$I_N = 6 \text{ A}$$

$$R_{Th} = 10 \text{ } \Omega \text{ (Ohm)}$$


Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 10.00 out of 10.00

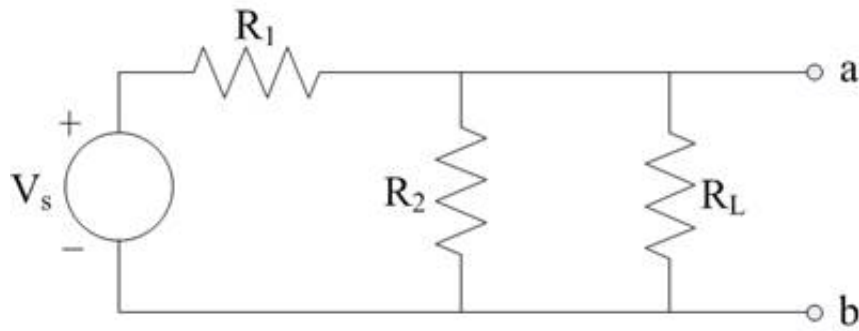

Q6j

Given:

$$V_s = 40 \text{ Volts} \quad R_1 = 140 \, \Omega \text{ (Ohm)} \quad R_2 = 84 \, \Omega \text{ (Ohm)}$$

a) Find the value of R_L that results in maximum power being transferred to R_L .

$$R_{L, \text{max power}} = 52.5 \, \Omega \text{ (Ohms)}$$

b) Find the maximum power that can be delivered to R_L .

$$P_{RL, \text{max power}} = 1.07 \text{ Watts}$$

Numeric Answer

$$\text{a) } R_{L, \text{max power}} = 52.50 \, \Omega \text{ (Ohms)}$$

$$\text{b) } P_{RL, \text{max power}} = 1.071 \text{ Watts}$$

Correct


Marks for this submission: 10.00/10.00.

Question 7

Not answered

Mark 0.00 out of

5.00

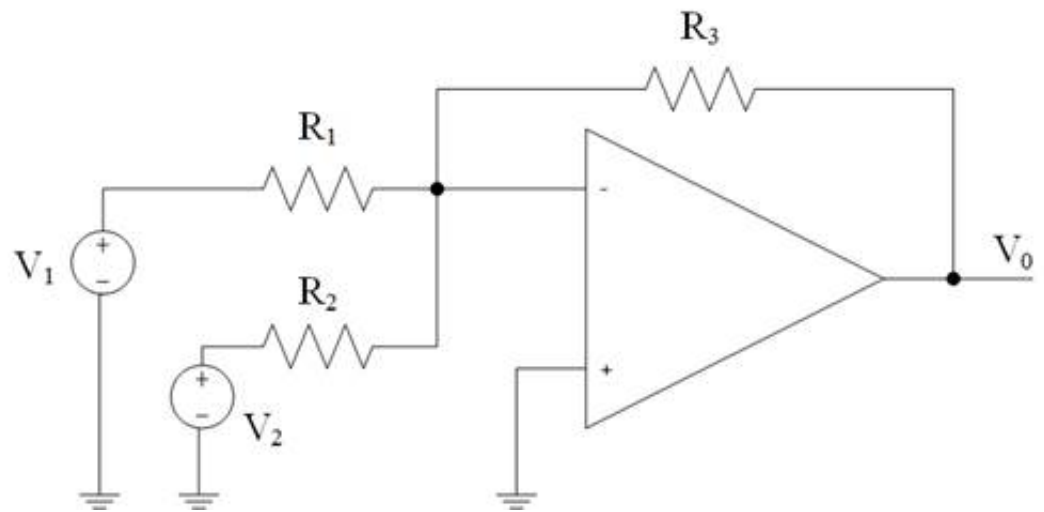

Q7j

Assume that the operational amplifier is ideal.

The opamp has two power inputs (not shown) of $+V_{cc} = +15V$ and $-V_{cc} = -15V$.

Given: $V_1 = 10$ Volts $V_2 = 10$ Volts

$R_1 = 2$ k Ω (kilo Ohm) $R_2 = 3$ k Ω (kilo Ohm) $R_3 = 1.5$ k Ω (kilo Ohm)

Determine the voltage v_{out} .


$v_{out} =$ \times Volts

Numeric Answer

$v_{out} = -12.5$ Volts

Question 8

Incorrect

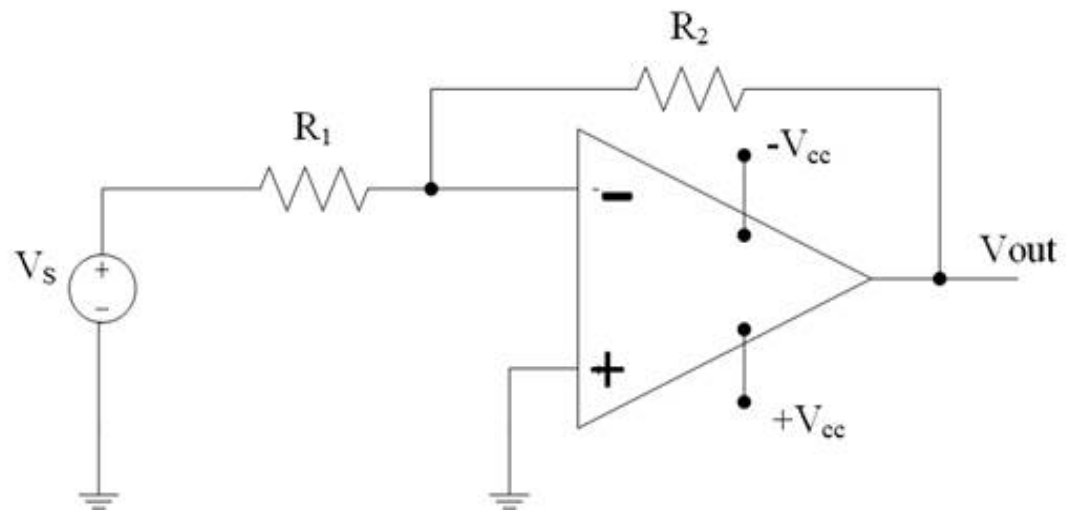Mark 0.00 out of
5.00

Q8c


Assume that the operational amplifier is ideal.

The opamp has two power inputs $+V_{cc} = +15\text{V}$ and $-V_{cc} = -15\text{V}$.Given: $V_s = -3.0\text{ Volts}$
(kilo Ohm) $R_1 = 47\text{ k}\Omega$ (kilo Ohm) $R_2 = 270\text{ k}\Omega$ Determine the voltage V_{out} . $V_{out} = -17.23$ ✗ Volts**Numeric Answer** $v_{out} = 15.0\text{ Volts}$ **Incorrect**

Marks for this submission: 0.00/5.00.

Question 9

Correct

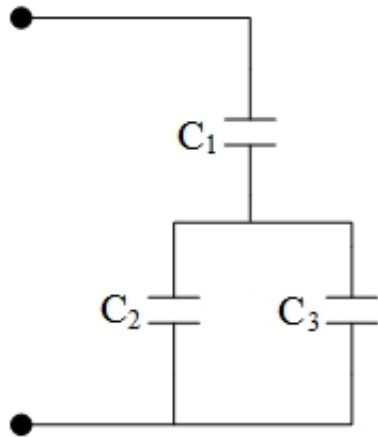Mark 5.00 out of
5.00

Q9e

Given:

$$C_1 = 10 \mu\text{F (micro F)} \quad C_2 = 6 \mu\text{F (micro F)} \quad C_3 = 4 \mu\text{F (micro F)}$$

Find the equivalent capacitance C_{Eq} .

$$C_{\text{Eq}} = 5 \mu\text{F (micro F)}$$

Numeric Answer


$$C_{\text{Eq}} = 5.0 \mu\text{F (micro F)}$$

Correct

Marks for this submission: 5.00/5.00.

Question 10

Correct

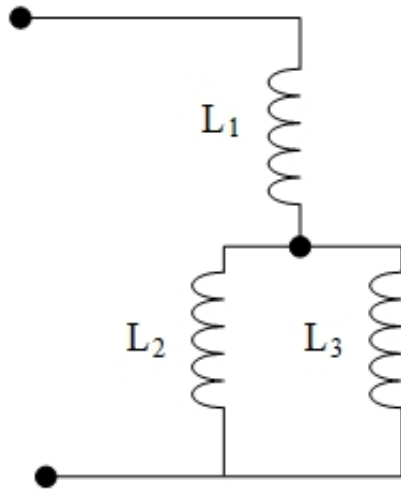Mark 5.00 out of
5.00

Q10h

Given:

$$L_1 = 1 \text{ mH (milli H)} \quad L_2 = 4 \text{ mH (milli H)} \quad L_3 = 7 \text{ mH (milli H)}$$

Find the equivalent inductance L_{Eq} .

$$L_{\text{Eq}} = \boxed{3.55} \checkmark \text{ mH (milli H)}$$

Numeric Answer

$$L_{\text{Eq}} = 3.5455 \text{ mH}$$

Correct

Marks for this submission: 5.00/5.00.