

Started on Wednesday, 6 March 2019, 7:41 PM

State Finished

Completed on Wednesday, 6 March 2019, 7:44 PM


Time taken 2 mins 43 secs

Grade 100.00 out of 100.00

## Question 1

Correct

Mark 100.00 out of 100.00

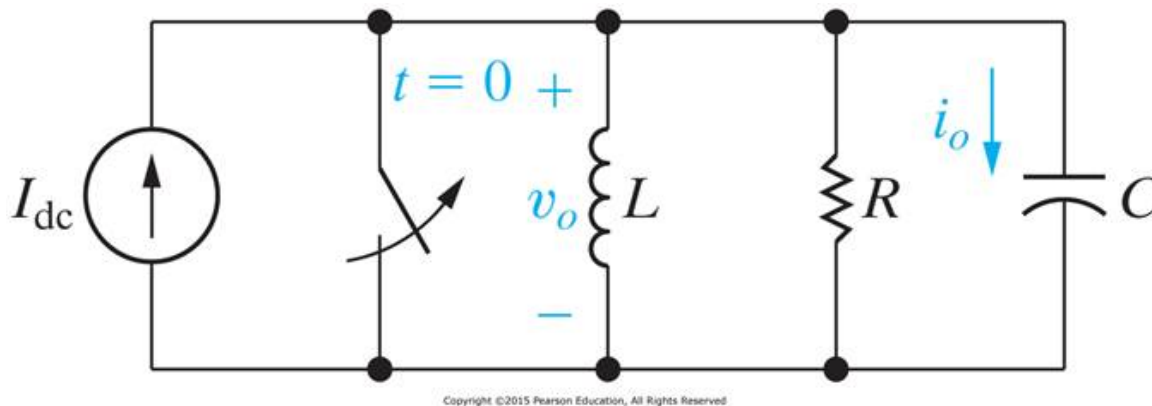

## Quiz 5a

The circuit parameters for this circuit are

 $R = 20 \, \Omega$  (Ohm)    $L = 50 \, \text{mH}$  (milli H)    $C = 20 \, \mu\text{F}$  (micro F)    $I_{dc} = 75 \, \text{mA}$  (milli A)

Also given 
$$V_0(s) = \frac{\frac{I_{dc}}{C}}{s^2 + s\frac{1}{RC} + \frac{1}{LC}}$$

Find the time domain voltage  $v_0(t)$  for  $t \geq 0$ . (t equal to or greater than zero)

$v_0(t) = [ \text{2.5} \checkmark \exp[ \text{-500} \checkmark t ] + \text{-2.5} \checkmark \exp[ \text{-2000} \checkmark t ] ]$   
u(t) V

Answer is in the form  $v_0(t) = [A e^{Bt} + C e^{Dt}] u(t)$  V and where  $|B|$  is less than  $|D|$ 

$$v_0(t) = [2.5 e^{-500t} - 2.5 e^{-2000t}] u(t) \text{ V}$$

Correct

Marks for this submission: 100.00/100.00.