

Sam Lee  
CPE 166 –03  
Advanced Logic Design Lab  
Wednesday: 5PM -7:50 PM  
Lecture Professor: Jing Pang  
Lab Professor: Eric Carmi  
Lab #4 Report

---

Contents	
Introduction .....	3
Part 1: Microprocessor Data Path Design .....	3
Design Purpose .....	3
Engineering Data: .....	3
Source Code .....	7
Simulation Waveforms .....	12
Results Discussion.....	14
Part 2: Microprocessor Control Path Design .....	15
Design Purpose .....	15
Engineering Data .....	15
Source Code .....	16
Simulation Waveforms .....	18
Results Discussion.....	18
Part 3: Final 4-Bit Microprocessor Design .....	18
Design Purpose .....	19
Engineering Data .....	19
Source Code .....	20
User Constraint File.....	27
Results Discussion.....	28
Conclusion.....	29

## Introduction

A microprocessor is a computer processor that incorporates the functions of a central processing unit on a single integrated circuit (IC). The microprocessor is a multipurpose, clock driven, register based, digital integrated circuit that accepts binary data as input, processes it according to instructions stored in its memory, and provides results as output. Microprocessors contain both combinational logic and sequential digital logic. Microprocessors operate on numbers and symbols represented in the binary number system. For this lab we needed to build a simplified microprocessor in which it would take roughly 6 inputs and would output a value. Specifically, M0, M1, M2 and Cin inputs, one input switch SW1 and also a clock input. The SW1 switch serves as asynchronous reset function. The design needed to implement the following logic equation:  $R2 = M0 + (\text{not } M1) + \text{Cin}$ . Once everything was set up; the final step would be to download the design onto the NEXYS 4DDR board to view the results.

## Part 1: Microprocessor Data Path Design

### Design Purpose:

The purpose of this lab was to design a simplified version a microprocessor using VHDL in which would take in 6 inputs: M0, M1, M2, Cin, SW1, and Clk and one output: dout. The design should implement the following logical equation if it is successful:  $R2 = M0 + (\text{not } M1) + \text{Cin}$ . The logic '1' on "SW1" switch will force the controller to enter its first state. After "SW1" becomes logic '0', the finite state machine will proceed forward automatically into the next state after the rising edge of the clock. To summarize it all up, The LED display will be on if the final R2 result is '1' and will be off if final result R2 is '0'.

### Engineering Data:

In simple terms, we can think of the microprocessor design for this lab as being two distinct blocks. One block will be the data path block which is responsible for processing all of the arithmetic that is needed for each distinct input. The second block will be the finite state machine; and it will be responsible for controlling the state of the circuit. As explained before, the logic value '1' will kickstart the controller into entering its first state. Once the logic value from SW1 goes back to '0' it will automatically continue into its next state; until the final value is calculated. Figure 1 shows the detailed datapath circuit broken down into different circuit elements.

The detailed data path circuit is shown in Figure 4-2.


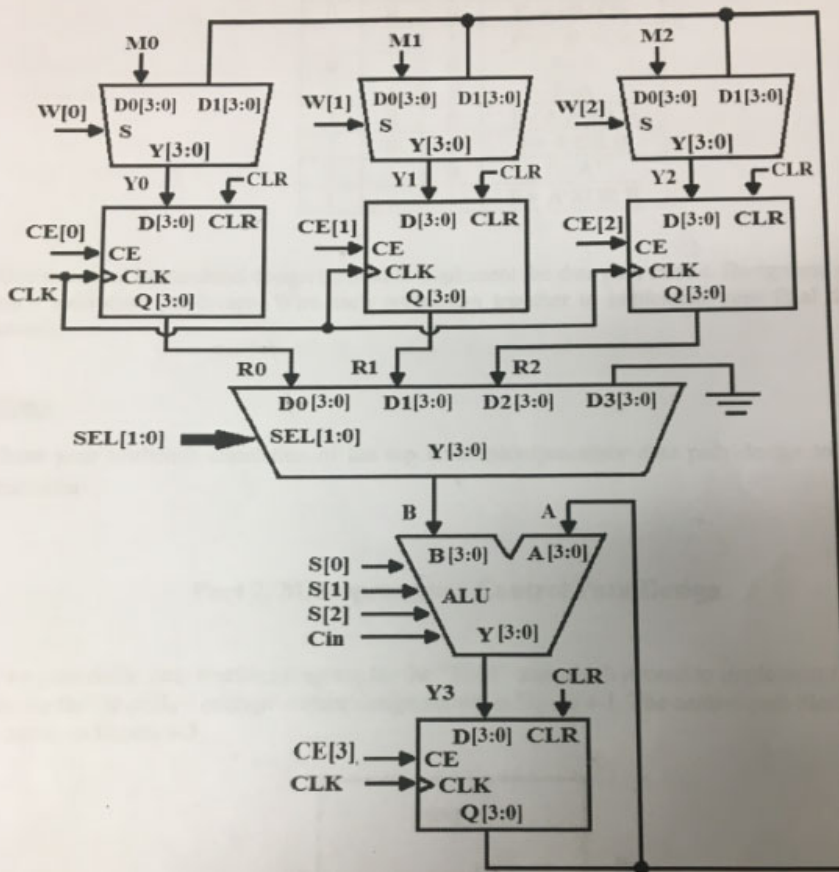


Figure 4-2. Simplified microprocessor data path circuit

Figure 1: A simplified microprocessor data path circuit.

A D flip flop tracks the input, making transitions with match those of the input D. The D stands for “data”; this flip-flop stores the value that is on the data line. It can be thought of as a basic memory cell. A D flip-flop can be made from a set/reset flip-flop by tying the set to the reset through an inverter. The result may be clocked.

Figure 2: D flip-flop truth table and circuit diagram

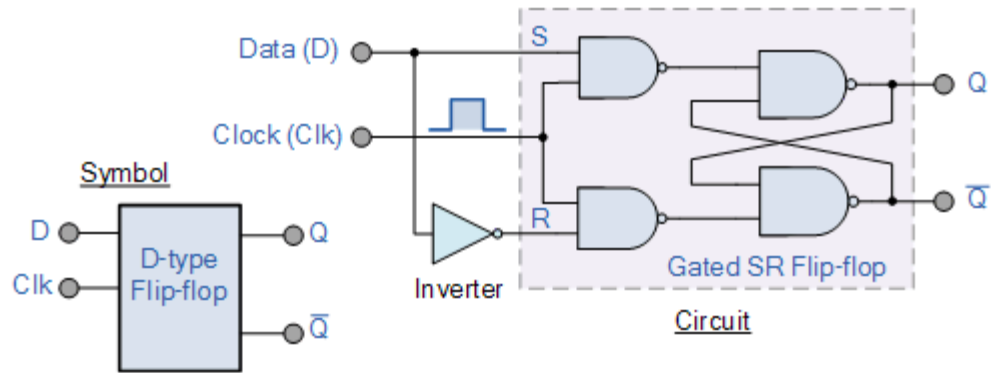


Clk	D	Q		Description
$\downarrow \gg 0$	X	Q	$\bar{Q}$	Memory no change
$\uparrow \gg 1$	0	0	1	Reset Q $\gg$ 0
$\uparrow \gg 1$	1	1	0	Set Q $\gg$ 1

MUX 2to1 and MUX 4to1:

A multiplexer or mux is a common digital circuit used to mix a lot of signals into just one. If you want multiple sources of data to share a single, common data line, you'd use a multiplexer to run them into that line. Multiplexers come in all sorts of shapes and sizes, but they're all made out of logic gates. Every multiplexer has at least one select line, which is used to select which input signal gets relayed to the output. In a 2-to-1 multiplexer, there's just one select line. More inputs means more select lines: a 4-to-1 multiplexer would have 2 select lines, an 8-to-1 has 3, and so on.

Figure 3: MUX 2to1 and MUX 4to1 Schematic and Truth Table

Select Data Inputs		Output
$S_1$	$S_0$	Y
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

 



---

$I_0$	$I_1$	$I_2$	$I_3$	$S_1$	$S_0$	$Y$
$d_0$	$d_1$	$d_2$	$d_3$	0	0	$d_0$
$d_0$	$d_1$	$d_2$	$d_3$	0	1	$d_1$
$d_0$	$d_1$	$d_2$	$d_3$	1	0	$d_2$
$d_0$	$d_1$	$d_2$	$d_3$	1	1	$d_3$

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

---

 

#### ALU:

An arithmetic logic unit (ALU) is a digital circuit used to perform arithmetic and logic operations. It represents the fundamental building block of the central processing unit (CPU) of a computer. Modern CPUs contain very powerful and complex ALUs. In addition to ALUs, modern CPUs contain a control unit (CU). Most of the operations of a CPU are performed by one or more ALUs, which load data from input registers. A register is a small amount of storage available as part of a CPU. The control unit tells the ALU what operation to perform on that data, and the ALU stores the result in an output register. The control unit moves the data between

these registers, the ALU, and memory. An ALU performs basic arithmetic and logic operations. Examples of arithmetic operations are addition, subtraction, multiplication, and division. Examples of logic operations are comparisons of values such as NOT, AND, and OR.

Figure 4: ALU Schematic and Truth Table

 


Table 4-1. ALU truth table

S[2]	S[1]	S[0]	ALU Output F
0	0	0	$F = A + B + \text{Cin}$
0	0	1	$F = A + B' + \text{Cin}$
0	1	0	$F = B$
0	1	1	$F = A$
1	0	0	$F = A \text{ AND } B$
1	0	1	$F = A \text{ OR } B$
1	1	0	$F = A'$
1	1	1	$F = A \text{ XOR } B$

Source Code:

D Flip Flop Verilog and Testbench Code:

```

`timescale 1ns / 1ns
module dff (clk, clr, d, q, ce);
  input[3:0] d;
  input clk, ce, clr;

  output reg[3:0] q;

  always@(posedge clr or posedge clk)
  begin
    if(clr) q <= 0;
    else if(ce) q <= d;
  end

```

```
endmodule
```

```
`timescale 1ns / 1ns
module dff_tb;

reg[3:0] d;
reg clk, clr, ce;

wire[3:0] q;

dff u1(clk, clr, d, q, ce);

initial clk = 0;
always #10 clk = ~clk;

initial begin
  clr = 1; d = 1; ce = 1;
  #20 clr = 0;
  #20 ce = 0;
  #40 $stop;
end
```

```
endmodule
```

MUX 2to1 and MUX 4to1 Verilog and Testbench Code:

```
`timescale 1ns / 1ps
module mux2to1(d0, d1, s, y);
  input[3:0] d0, d1;
  input s;
  output reg[3:0] y;

  always@(d0 or d1 or s) begin
    if(s) y = d1;
    else y = d0;
  end
end
```

```
endmodule
```

```
`timescale 1ns / 1ns
module mux2to1_tb;

reg[3:0] d0, d1;
reg s;
wire[3:0] y;

mux2to1 u1(d0, d1, s, y);
```



```

initial begin
    d1 = 0; d0 = 0; s = 0;
    #10 d1 = 0; d0 = 0; s = 1;
    #10 d1 = 0; d0 = 1; s = 0;
    #10 d1 = 0; d0 = 1; s = 1;
    #10 d1 = 1; d0 = 0; s = 0;
    #10 d1 = 1; d0 = 0; s = 1;
    #10 d1 = 1; d0 = 1; s = 0;
    #10 d1 = 1; d0 = 1; s = 1;
    #10 $stop;
end
endmodule

`timescale 1ns / 1ps
module mux4to1(d0, d1, d2, d3, sel, y);
    input[3:0] d0,d1,d2,d3;
    input[1:0] sel;
    output reg[3:0] y;

    always @(d0 or d1 or d2 or d3 or sel) begin
        case (sel)
            2'b00: y = d0;
            2'b01: y = d1;
            2'b10: y = d2;
            2'b11: y = d3;
        endcase
    end
endmodule

`timescale 1ns / 1ns
module mux4to1_tb;

    reg[3:0] d0, d1, d2, d3;
    reg[1:0] sel;
    wire[3:0] y;

    mux_4to1 u1(d0, d1, d2, d3, sel, y);

    initial begin
        d0 = 0; d1 = 1; d2 = 2; d3 = 3; sel = 2'b00;
        #10 d0 = 0; d1 = 1; d2 = 2; d3 = 3; sel = 2'b01;
        #10 d0 = 0; d1 = 1; d2 = 2; d3 = 3; sel = 2'b10;
        #10 d0 = 0; d1 = 1; d2 = 2; d3 = 3; sel = 2'b11;
        #10 $stop;
    end
end

```

endmodule

ALU Verilog and Testbench Code:

```
`timescale 1ns / 1ps
module alu(a, b, s, cin, y);
input[3:0] a, b;
input[2:0] s;
input cin;

output reg[3:0] y;

always@(a or b or s or cin or y) begin
    case(s)
        3'b000: y = a + b + cin;
        3'b001: y = a + ~b + cin;
        3'b010: y = b;
        3'b011: y = a;
        3'b100: y = a & b;
        3'b101: y = a | b;
        3'b110: y = ~a;
        3'b111: y = a ^ b;
    endcase
end
endmodule
```

```
`timescale 1ns / 1ns
```

```
module alu_tb;
```

```
reg[3:0] a, b;
```

```
reg[2:0] s;
```

```
reg cin;
```

```
wire[3:0] y;
```

```
alu u1(a, b, s, cin, y);
```

```
initial begin
```

```
    s = 0; a = 1; b = 2; cin = 1;
```

```
    #10 s = 1; a = 1; b = 0; cin = 1;
```

```
    #10 s = 2; a = 1; b = 0; cin = 1;
```

```
    #10 s = 3; a = 1; b = 0; cin = 1;
```

```
    #10 s = 4; a = 1; b = 0; cin = 1;
```

```
    #10 s = 5; a = 1; b = 0; cin = 1;
```

```
    #10 s = 6; a = 1; b = 0; cin = 1;
```

```
    #10 s = 7; a = 1; b = 0; cin = 1;
```

```
    #10 $stop;
```

end

endmodule

Datapath Verilog and Testbench Code:

```
`timescale 1ns / 1ps
module datapath(m0, m1, m2, cin, clr, w, ce, sel, s, clk, r0, r1, r2);
    input clk, clr, cin;
    input[3:0] m0,m1,m2,ce;
    input[2:0] w, s;
    input[1:0] sel;
    output[3:0] r0, r1, r2;

    wire [3:0] y0, y1, y2, y3, a, b;

    mux2to1 g1(.d0(m0),.d1(a),.s(w[0]),.y(y0));
    mux2to1 g2(.d0(m1),.d1(a),.s(w[1]),.y(y1));
    mux2to1 g3(.d0(m2),.d1(a),.s(w[2]),.y(y2));

    dff d1(.clk(clk),.clr(clr),.ce(ce[0]),.d(y0),.q(r0));
    dff d2(.clk(clk),.clr(clr),.ce(ce[1]),.d(y1),.q(r1));
    dff d3(.clk(clk),.clr(clr),.ce(ce[2]),.d(y2),.q(r2));
    dff d4(.clk(clk),.clr(clr),.ce(ce[3]),.d(y3),.q(a));

    mux4to1 g4(.d0(r0),.d1(r1),.d2(r2),.d3(4'b0000),.sel(sel),.y(b));

    alu a1(.a(a),.b(b),.s(s),.cin(cin),.y(y3));
endmodule

`timescale 1ns / 1ps
module datapath_tb;
    reg[3:0] m0, m1, m2, ce;
    reg[2:0] w, s;
    reg[1:0] sel;
    reg clk, clr, cin;
    wire [3:0] r0, r1, r2;

    datapath uut(m0, m1, m2, cin, clr, w, ce, sel, s, clk, r0, r1, r2);

    initial begin
        clr = 1'b1; w = 3'b000; ce = 4'b0000; sel = 2'b00; s = 3'b000; clk = 1'b0; m2 = 4'b0000;
        m0 = 4'b0101; m1 = 4'b0011;
        cin = 1;
    end
    always #1 clk = ~clk;
```

```

initial begin
    #8; clr = 1'b0;
    #2; ce = 4'b0011; sel = 2'b00; s = 3'b010;
    #2; ce = 4'b1011;
    #2; ce = 4'b0011; sel = 2'b01; s = 3'b001;
    #2; ce = 4'b1000;
    #2; ce = 4'b0100; w = 3'b100;
    #2; w = 3'b000; ce = 4'b0000; sel = 2'b00; s = 3'b000;
    #8; $stop;
end
endmodule

```

Simulation Waveforms:

Figure 5: This figure is the simulation of the D flip flop.

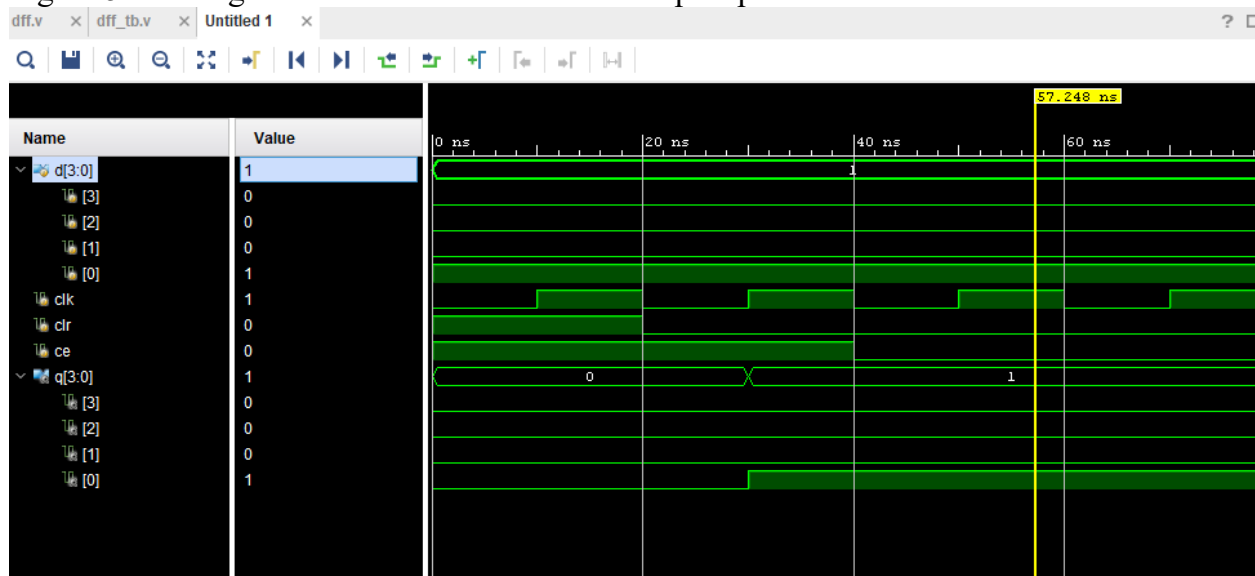


Figure 6: This figure is the simulation of the MUX 2to1 and MUX 4to1.

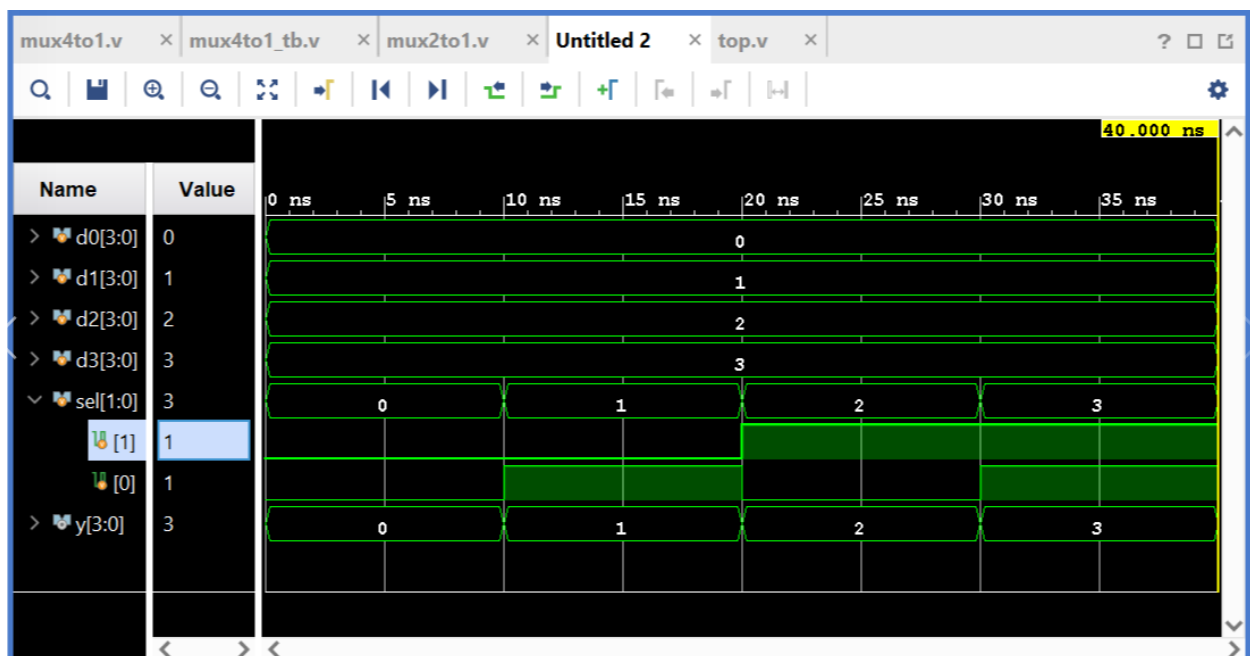
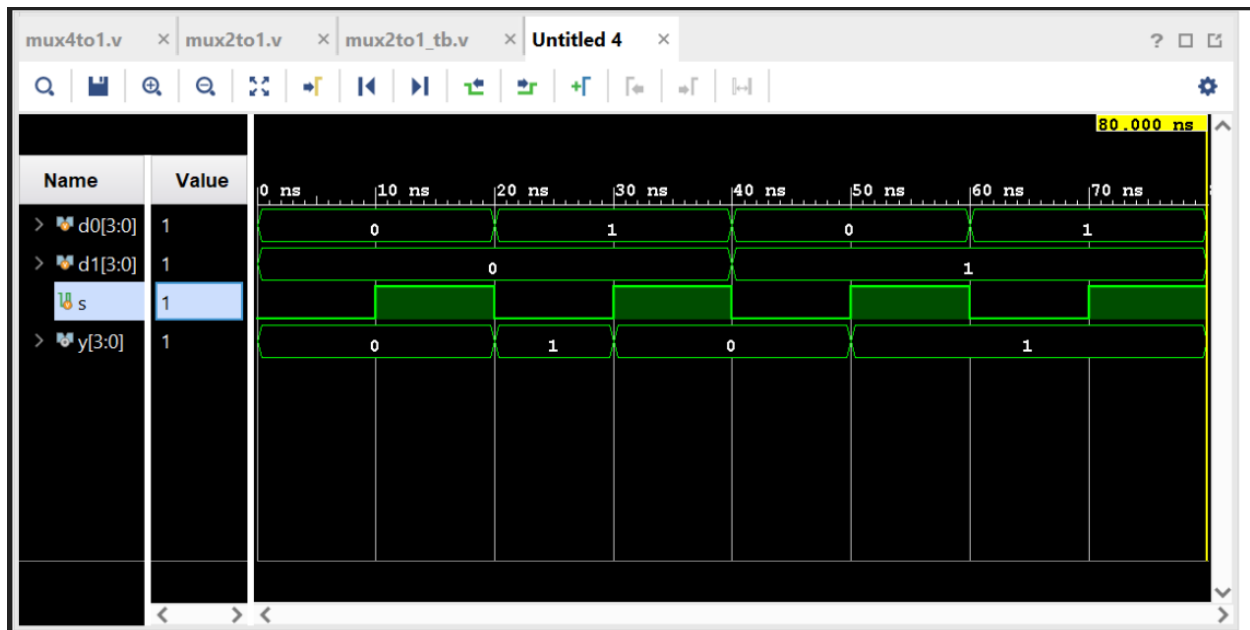


Figure 7: This figure is the simulation of the ALU.


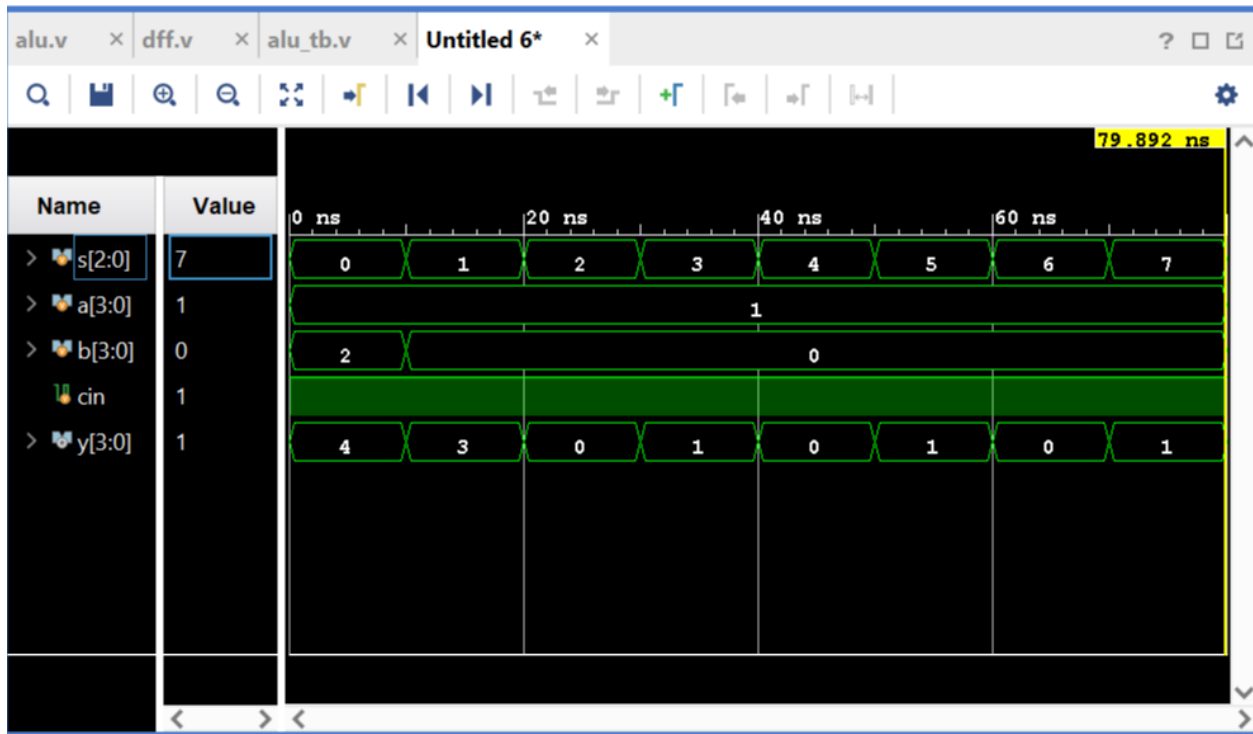


Figure 8: This figure is the simulation of the Datapath.

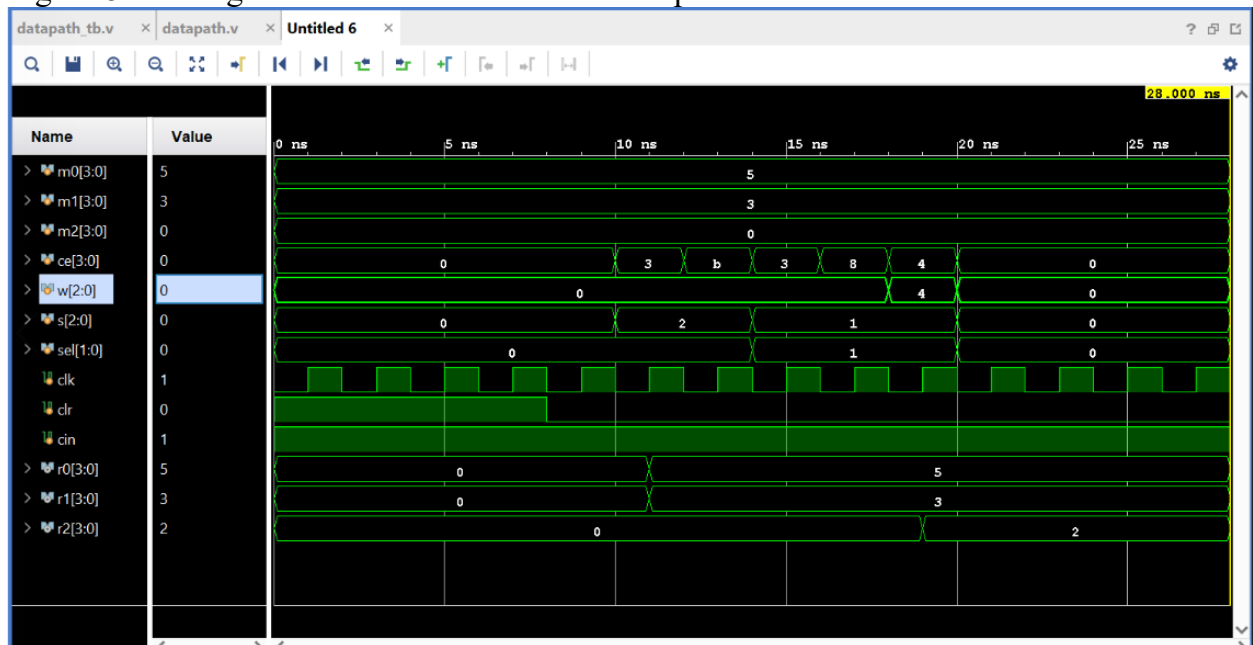

#### Results Discussion:

Part 1 had most of the work for this lab but it was mostly easy work because we had most of the components from previous parts of the lab, making it work together and making sure it worked together properly was the tricky part. The MUX selects properly, the flip flops store data properly, and the ALU does all of the calculations properly. The data path waveform shows the simplified processor doing the  $R2 = M0 + (\text{not } M1) + \text{Cin}$  calculation, and getting

the timing to calculate that properly was a bit tricky but after some time we got it done no problems.

## Part 2: Microprocessor Control Path Design

### Design Purpose:

Once the data path module is built, we can proceed to building the finite state machine. We will design this FSM based on the conditions set. Figure 9 shows the block diagram of the finite state machine with its outputs.

### Engineering Data:

A finite state machine is a computation model that can be implemented with hardware or software and can be used to simulate sequential logic and some computer programs. This particular finite state machine controls all of the inputs to the other modules. The state machine has 5 states: reset state, initial loading state,  $F = B$  (pass through) state,  $F = A + \text{not } B + C_{in}$  state, load R2 and enable/loop state. The FSM is just a Moore FSM, each state going directly into another without any consideration for input.

Figure 9: This is the schematic for the FSM block diagram.


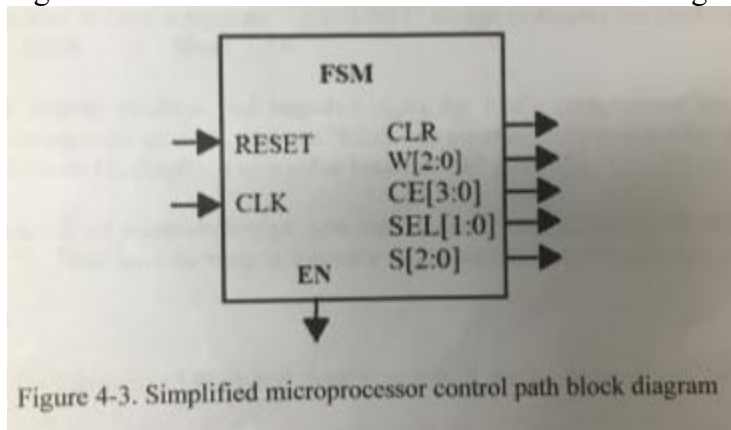


Figure 10: This is the drawing of the FSM that was implemented in order for the simulation to work.

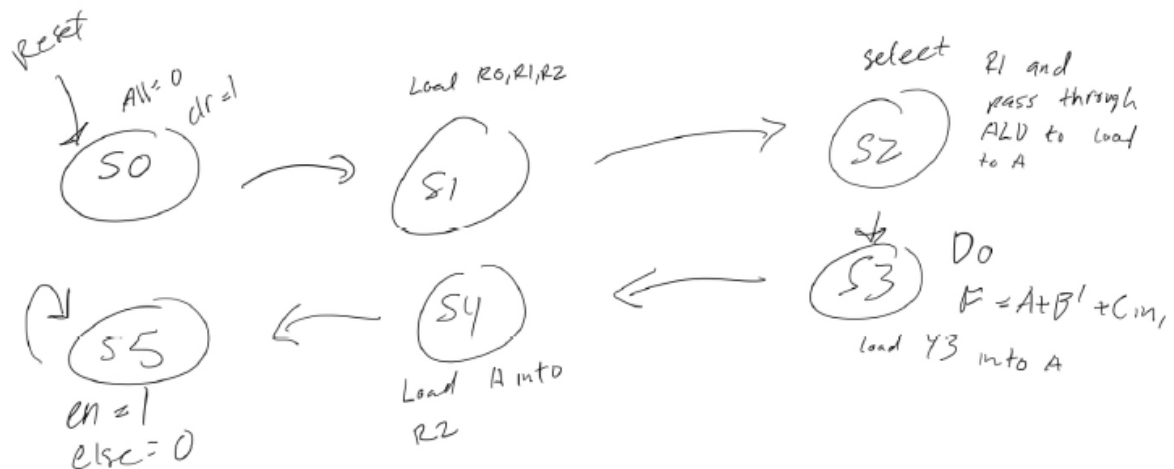

Source Code:

FSM Verilog and Testbench Code:

```
`timescale 1ns / 1ps
module FSM(clk, reset, en, clr, w, ce, sel, s);
    input clk, reset;
    output reg en, clr;
    output reg [2:0] w, s;
    output reg [1:0] sel;
    output reg [3:0] ce;

    reg [2:0] cs, ns;
    parameter s0=0, s1=1, s2=2, s3=3, s4=4, s5=5;

    always@(posedge clk or posedge reset) begin

        if( reset ) begin
            cs <= s0;
        end else begin
            cs <= ns;
        end

    end

    always@(cs) begin

        case(cs)
            s0 : begin
                clr = 1'b1;
                en = 1'b0;
                w = 3'b000;
                s = 3'b000;
                sel = 2'b00;
                ce = 4'b0000;
                ns <= s1;
            end

            s1 : begin
                clr = 1'b0;
                en = 1'b0;
                w = 3'b101;
                s = 3'b000;
                sel = 2'b00;
                ce = 4'b0111;
                ns <= s2;
            end

        endcase

    end

end
```



```

s2 : begin
    clr = 1'b0;
    en = 1'b0;
    w = 3'b100;
    s = 3'b010;
    sel = 2'b11;
    ce = 4'b1000;
    ns <= s3;
end

s3 : begin
    clr = 1'b0;
    en = 1'b0;
    w = 3'b100;
    s = 3'b001;
    sel = 2'b10;
    ce = 4'b1000;
    ns <= s4;
end

s4 : begin
    clr = 1'b0;
    en = 1'b0;
    w = 3'b000;
    s = 3'b000;
    sel = 2'b00;
    ce = 4'b0100;
    ns <= s5;
end

s5 : begin
    clr = 1'b0;
    en = 1'b1;
    w = 3'b000;
    s = 3'b000;
    sel = 2'b00;
    ce = 4'b0000;
    ns <= s5;
end
default : ns = s0;

endcase
end

`timescale 1ns / 1ps

```

```

module FSM_tb();
reg clk, reset;
wire clr;
wire [1:0] sel;
wire [2:0] w, s;
wire [3:0] ce;

FSM uut(clk, reset, clr, ce, w, s, sel);


always
begin
#5 clk = ~clk;
end

initial
begin
clk = 0;
#2 reset = 1;
#10 reset = 0;
#150
$stop;
end
endmodule

```

#### Simulation Waveforms:

Figure 11: Below is the simulation for the finite state machine that was implements for the microprocessor design.

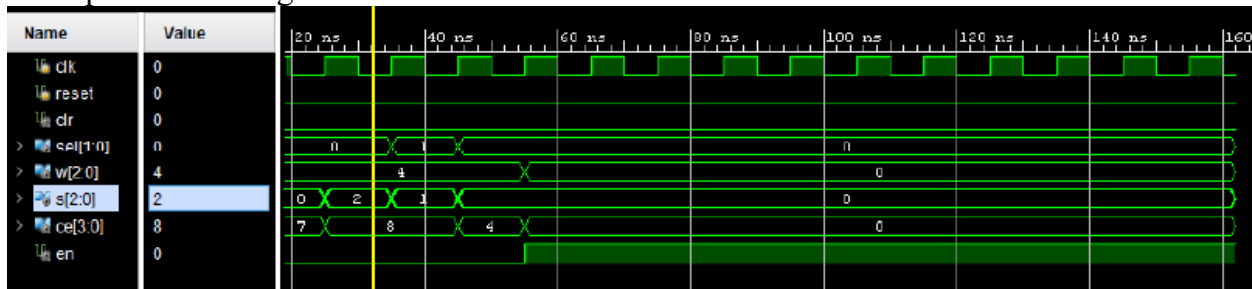

#### Results Discussion:

The FSM works as expected. Even though it took a bit to create, everything works properly: the FSM controls the inputs of the data path to load and do the ALU calculations, and turns on the EN on the last state, continuously staying on the last state. One of the hardest part of just implementing correctly to show the correct inputs and outputs.

#### Part 3: Final 4-Bit Microprocessor Design

##### Design Purpose:


For this part of the lab, it requires to implement the top level design with the seven segment display along with the datapath and finite state machine and implement all of the concepts from part 1 and part 2 for this lab. The final result should be able to display the result using the

switches on the FPGA board.

Engineering Data:

For the display to happen we to had create three instances: FSM, datapath, and seg7unit, that were part of the top design.

Figure 13: This figure is the block diagram for the whole design.

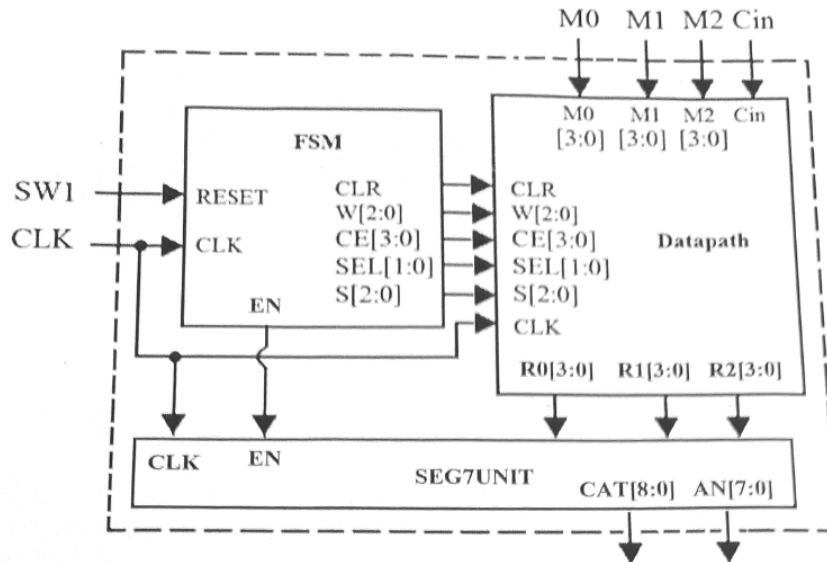

The 7-segment display consists of seven LEDs arranged in a rectangular fashion as shown. Each of the seven LEDs is called a segment because when illuminated the segment forms part of a numerical digit to be displayed.

Figure 14: This figure is a common anode seven segment display device.

 


Figure 15: This figure below is the 8-digit seven segment displays on the NEXXYS4 DDR

FPGA board.

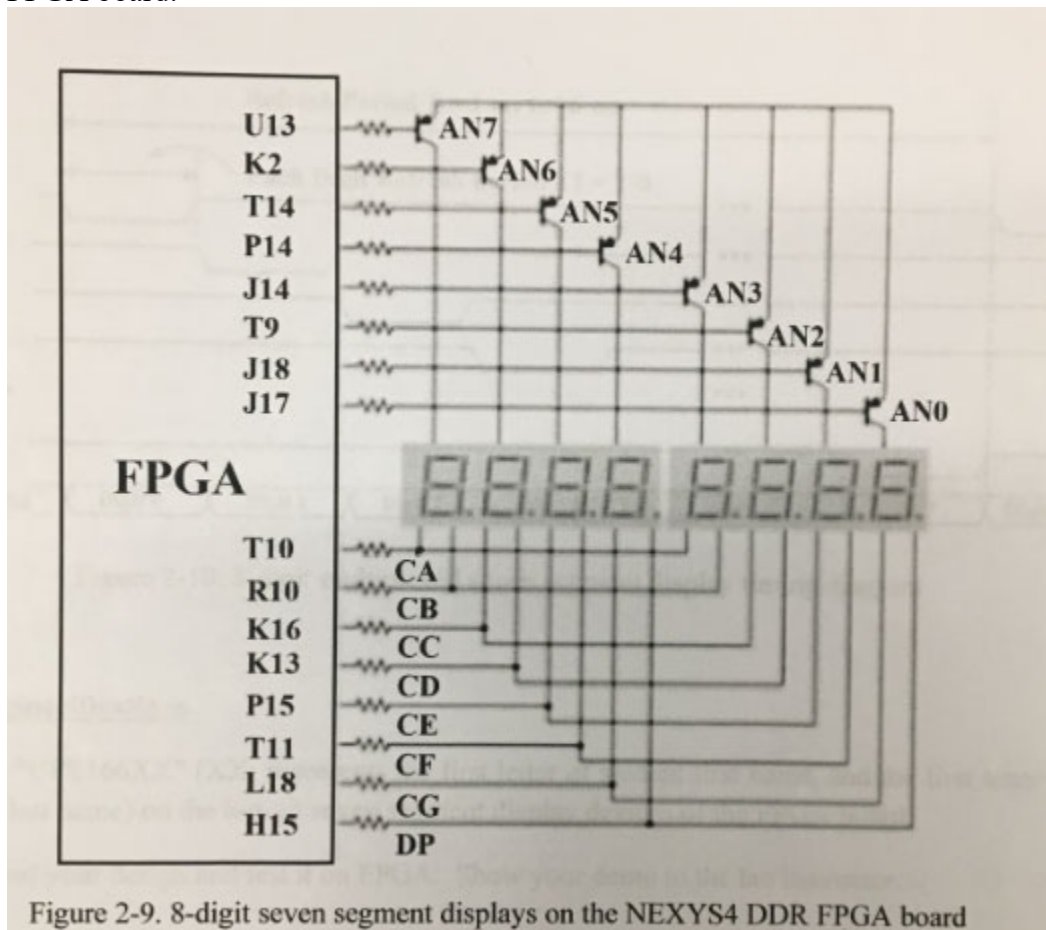


Figure 2-9. 8-digit seven segment displays on the NEXYS4 DDR FPGA board

Figure 16: This figure is the seven segment display.

Source Code:

TOP Verilog and Testbench Code:

```
`timescale 1ns / 1ps
```

```
module TOP( clk, reset, m0, m1, m2, cin, seg, dig);
```

```
    input clk, cin, reset;
```

```
    input [3:0] m0, m1, m2;
```

```
    wire [3:0] r0, r1, r2;
```

```
    output [7:0] seg, dig;
```

```
    wire [2:0] w, s;
```

```
    wire [1:0] sel;
```

```
    wire [3:0] ce;
```

```
    wire clr;
```

```
    wire en;
```

```
    reg sign2, sign1, sign0;
```

```
    reg [3:0] num2, num1;
```

```
    wire [3:0] num0;
```

```
//Twos complement controller for m0 and m1.
always@(m0 or m1) begin
```

```
    if( m0[3] == 1'b1 ) begin
        sign2 = 1'b1;
    end else begin
        sign2 = 1'b0;
    end
```

```
    if( m1[3] == 1'b1 ) begin
        sign1 = 1'b1;
    end else begin
        sign1 = 1'b0;
    end
```

```
case( m0 )
```

```
    4'b0000 : num2 = 4'b0000;
    4'b0001 : num2 = 4'b0001;
    4'b0010 : num2 = 4'b0010;
    4'b0011 : num2 = 4'b0011;
    4'b0100 : num2 = 4'b0100;
    4'b0101 : num2 = 4'b0101;
    4'b0110 : num2 = 4'b0110;
    4'b0111 : num2 = 4'b0111;
    4'b1000 : num2 = 4'b1000;
    4'b1001 : num2 = 4'b0111;
    4'b1010 : num2 = 4'b0110;
    4'b1011 : num2 = 4'b0101;
    4'b1100 : num2 = 4'b0100;
    4'b1101 : num2 = 4'b0011;
    4'b1110 : num2 = 4'b0010;
    4'b1111 : num2 = 4'b0001;
    default : num2 = 4'b1111;
endcase
```

```
case( m1 )
```

```
    4'b0000 : num1 = 4'b0000;
    4'b0001 : num1 = 4'b0001;
    4'b0010 : num1 = 4'b0010;
    4'b0011 : num1 = 4'b0011;
    4'b0100 : num1 = 4'b0100;
    4'b0101 : num1 = 4'b0101;
    4'b0110 : num1 = 4'b0110;
```

```

        4'b0111 : num1 = 4'b0111;
        4'b1000 : num1 = 4'b1000;
        4'b1001 : num1 = 4'b0111;
        4'b1010 : num1 = 4'b0110;
        4'b1011 : num1 = 4'b0101;
        4'b1100 : num1 = 4'b0100;
        4'b1101 : num1 = 4'b0011;
        4'b1110 : num1 = 4'b0010;
        4'b1111 : num1 = 4'b0001;
        default : num1 = 4'b1111;
    endcase

end

FSM fsm1(clk, reset, en, clr, w, ce, sel, s);

Datapath datapath1(clk, clr, w, ce, sel, s, m0, m1, m2, cin, r0, r1, r2);

assign num0 = r2;

Seg7Unit segdig( clk, sign2, sign1, sign0, num2, num1, num0, seg, dig);
endmodule

`timescale 1ns / 1ns
module top_tb;
// Inputs
    reg reset,clk, cin;
    reg [3:0] m0,m1,m2;

    // Outputs
    wire [3:0] R0,R1,R2;
    wire [8:0] cat;
    wire [7:0] an;

/*
    module top(da, db, dout, clk, rst, start);
*/
    // Instantiate the Unit Under Test (UUT)
    // module Top( clk, reset, m0, m1, m2, cin, seg, dig);
    Top uut(clk, reset, m0, m1, m2, cin, seg, dig);
//Top uut(reset, clk, m0, m1, m2, cin, cat,an);
    initial clk = 0;
    always #5 clk = ~clk;
    initial begin
        reset = 0;

```

```

        #10;
        m0 = 4'b1000;
    m1 = 4'b1001;
    m2 = 4'b1011;
    cin = 1;
    reset = 0;
        #100;

        reset = 1; #10;

        #10;
    m0 = 1;
    m1 = 1;
    m2 = 1;
    cin = 1;
    reset = 0;

        #10; $stop;

    end

endmodule

```

Seg7Unit Verilog Code:

```
module Seg7Unit( clk, sign2, sign1, sign0, num2, num1, num0, seg, dig);
```

```

input    clk;
input sign2, sign1, sign0;
input [3:0] num2, num1, num0;
output [7:0] seg;
output [7:0] dig;

```

```
parameter N = 18;
```

```

reg [N-1:0] count;
reg [3:0] dd;
reg [7:0] seg;
reg [7:0] an;

```

```

always @ (posedge clk)
begin
    count <= count + 1;

    case(count[N-1:N-3])
    3'b000 :
        begin

```

```
    dd = 4'd7;  
    an = 8'b11111110;  
end
```

```
3'b001:  
begin  
    dd = 4'd6;  
    an = 8'b11111101;  
end
```

```
3'b010:  
begin  
    dd = 4'd5;  
    an = 8'b11111011;  
end
```

```
3'b011:  
begin  
    dd = 4'd4;  
    an = 8'b11110111;  
end
```

```
3'b100 :  
begin  
    dd = 4'd3;  
    an = 8'b11101111;  
end
```

```
3'b101:  
begin  
    dd = 4'd2;  
    an = 8'b11011111;  
end
```

```
3'b110:  
begin  
    dd = 4'd1;  
    an = 8'b10111111;  
end
```

```
3'b111:  
begin  
    dd = 4'd0;  
    an = 8'b01111111;  
end  
endcase
```



```

end
assign dig = an;

always @( dd)
begin
seg[7] = 1'b1;
case(dd)
4'd0 : begin
    if( sign2 == 1'b1) begin
        seg[6:0] = 7'b0111111; //to display F
    end else begin
        seg[6:0] = 7'b1111111;
    end
end
4'd1 : begin
    case( num2 )
        4'b0000 : seg[6:0] = 7'b1000000; //0
        4'b0001 : seg[6:0] = 7'b1111001; //1
        4'b0010 : seg[6:0] = 7'b0100100; //2
        4'b0011 : seg[6:0] = 7'b0110000; //3
        4'b0100 : seg[6:0] = 7'b0011001; //4
        4'b0101 : seg[6:0] = 7'b0010010; //5
        4'b0110 : seg[6:0] = 7'b0000010; //6
        4'b0111 : seg[6:0] = 7'b1111000; //7
        4'b1000 : seg[6:0] = 7'b0000000; //8
        4'b1001 : seg[6:0] = 7'b0011000; //9
        4'b1010 : seg[6:0] = 7'b0001000; //A
        4'b1011 : seg[6:0] = 7'b0000011; //b
        4'b1100 : seg[6:0] = 7'b1000110; //c
        4'b1101 : seg[6:0] = 7'b0100001; //d
        4'b1110 : seg[6:0] = 7'b0000110; //E
        4'b1111 : seg[6:0] = 7'b0001110; //F
        default : seg[6:0] = 7'b1111111;
    endcase
end
4'd3 : begin
    if( sign1 == 1'b1) begin
        seg[6:0] = 7'b0111111; //to display F
    end else begin
        seg[6:0] = 7'b1111111;
    end
end
4'd4 : begin
    case( num1 )

```

```

    4'b0000 : seg[6:0] = 7'b1000000; //0
    4'b0001 : seg[6:0] = 7'b1111001; //1
    4'b0010 : seg[6:0] = 7'b0100100; //2
    4'b0011 : seg[6:0] = 7'b0110000; //3
    4'b0100 : seg[6:0] = 7'b0011001; //4
    4'b0101 : seg[6:0] = 7'b0010010; //5
    4'b0110 : seg[6:0] = 7'b0000010; //6
    4'b0111 : seg[6:0] = 7'b1111000; //7
    4'b1000 : seg[6:0] = 7'b0000000; //8
    4'b1001 : seg[6:0] = 7'b0011000; //9
    4'b1010 : seg[6:0] = 7'b0001000; //A
    4'b1011 : seg[6:0] = 7'b0000011; //b
    4'b1100 : seg[6:0] = 7'b1000110; //c
    4'b1101 : seg[6:0] = 7'b0100001; //d
    4'b1110 : seg[6:0] = 7'b0000110; //E
    4'b1111 : seg[6:0] = 7'b0001110; //F
    default : seg[6:0] = 7'b1111111;
endcase
end
4'd6 : begin
    if( sign0 == 1'b1) begin
        seg[6:0] = 7'b0111111; //to display F
    end else begin
        seg[6:0] = 7'b1111111;
    end
end
4'd7 : begin
    case( num0 )
        4'b0000 : seg[6:0] = 7'b1000000; //0
        4'b0001 : seg[6:0] = 7'b1111001; //1
        4'b0010 : seg[6:0] = 7'b0100100; //2
        4'b0011 : seg[6:0] = 7'b0110000; //3
        4'b0100 : seg[6:0] = 7'b0011001; //4
        4'b0101 : seg[6:0] = 7'b0010010; //5
        4'b0110 : seg[6:0] = 7'b0000010; //6
        4'b0111 : seg[6:0] = 7'b1111000; //7
        4'b1000 : seg[6:0] = 7'b0000000; //8
        4'b1001 : seg[6:0] = 7'b0011000; //9
        4'b1010 : seg[6:0] = 7'b0001000; //A
        4'b1011 : seg[6:0] = 7'b0000011; //b
        4'b1100 : seg[6:0] = 7'b1000110; //c
        4'b1101 : seg[6:0] = 7'b0100001; //d
        4'b1110 : seg[6:0] = 7'b0000110; //E
        4'b1111 : seg[6:0] = 7'b0001110; //F
        default : seg[6:0] = 7'b1111111;
    endcase
end

```

```

    end
    default : seg[6:0] = 7'b1111111; //blank
endcase

```

User Constraints File:

## Clock signal

```

set_property -dict { PACKAGE_PIN E3  IOSTANDARD LVCMOS33 } [get_ports {clk}];
#IO_L12P_T1_MRCC_35 Sch=clk100mhz
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {clk}];

```

##Switches

#m1

```

set_property -dict { PACKAGE_PIN J15  IOSTANDARD LVCMOS33 } [get_ports { m0[0]
}]; #IO_L24N_T3_RS0_15 Sch=sw[0]
set_property -dict { PACKAGE_PIN L16  IOSTANDARD LVCMOS33 } [get_ports { m0[1]
}]; #IO_L3N_T0_DQS_EMCCLK_14 Sch=sw[1]
set_property -dict { PACKAGE_PIN M13  IOSTANDARD LVCMOS33 } [get_ports { m0[2]
}]; #IO_L6N_T0_D08_VREF_14 Sch=sw[2]
set_property -dict { PACKAGE_PIN R15  IOSTANDARD LVCMOS33 } [get_ports { m0[3]
}]; #IO_L13N_T2_MRCC_14 Sch=sw[3]

```

#m0

```

set_property -dict { PACKAGE_PIN R17  IOSTANDARD LVCMOS33 } [get_ports { m1[0]
}]; #IO_L12N_T1_MRCC_14 Sch=sw[4]
set_property -dict { PACKAGE_PIN T18  IOSTANDARD LVCMOS33 } [get_ports { m1[1]
}]; #IO_L7N_T1_D10_14 Sch=sw[5]
set_property -dict { PACKAGE_PIN U18  IOSTANDARD LVCMOS33 } [get_ports { m1[2]
}]; #IO_L17N_T2_A13_D29_14 Sch=sw[6]
set_property -dict { PACKAGE_PIN R13  IOSTANDARD LVCMOS33 } [get_ports { m1[3]
}]; #IO_L5N_T0_D07_14 Sch=sw[7]

```

#m2

```

set_property -dict { PACKAGE_PIN T8   IOSTANDARD LVCMOS18 } [get_ports { m2[8] }];
#IO_L24N_T3_34 Sch=sw[8]
set_property -dict { PACKAGE_PIN U8   IOSTANDARD LVCMOS18 } [get_ports { m2[9]
}]; #IO_25_34 Sch=sw[9]
set_property -dict { PACKAGE_PIN R16  IOSTANDARD LVCMOS33 } [get_ports { m2[10]
}]; #IO_L15P_T2_DQS_RDWR_B_14 Sch=sw[10]
set_property -dict { PACKAGE_PIN T13  IOSTANDARD LVCMOS33 } [get_ports { m2[11]
}]; #IO_L23P_T3_A03_D19_14 Sch=sw[11]

```

#cin

```

set_property -dict { PACKAGE_PIN U11  IOSTANDARD LVCMOS33 } [get_ports { cin }];
#IO_L24P_T3_35 Sch=sw[12]

```

```

#reset
set_property -dict { PACKAGE_PIN V10  IOSTANDARD LVCMOS33 } [get_ports { sw1 }];
#IO_L21P_T3_DQS_14 Sch=sw[15]

##7 segment display
set_property -dict { PACKAGE_PIN T10  IOSTANDARD LVCMOS33 } [get_ports { seg[0]
}]; #IO_L24N_T3_A00_D16_14 Sch=ca
set_property -dict { PACKAGE_PIN R10  IOSTANDARD LVCMOS33 } [get_ports { seg[1]
}]; #IO_25_14 Sch=cb
set_property -dict { PACKAGE_PIN K16  IOSTANDARD LVCMOS33 } [get_ports { seg[2]
}]; #IO_25_15 Sch=cc
set_property -dict { PACKAGE_PIN K13  IOSTANDARD LVCMOS33 } [get_ports { seg[3]
}]; #IO_L17P_T2_A26_15 Sch=cd
set_property -dict { PACKAGE_PIN P15  IOSTANDARD LVCMOS33 } [get_ports { seg[4]
}]; #IO_L13P_T2_MRCC_14 Sch=ce
set_property -dict { PACKAGE_PIN T11  IOSTANDARD LVCMOS33 } [get_ports { seg[5]
}]; #IO_L19P_T3_A10_D26_14 Sch=cf
set_property -dict { PACKAGE_PIN L18  IOSTANDARD LVCMOS33 } [get_ports { seg[6]
}]; #IO_L4P_T0_D04_14 Sch=cg
set_property -dict { PACKAGE_PIN H15  IOSTANDARD LVCMOS33 } [get_ports { seg[7]
}]; #IO_L19N_T3_A21_VREF_15 Sch=dp

set_property -dict { PACKAGE_PIN J17  IOSTANDARD LVCMOS33 } [get_ports { dig[0]
}]; #IO_L23P_T3_FOE_B_15 Sch=an[0]
set_property -dict { PACKAGE_PIN J18  IOSTANDARD LVCMOS33 } [get_ports { dig[1]
}]; #IO_L23N_T3_FWE_B_15 Sch=an[1]
set_property -dict { PACKAGE_PIN T9   IOSTANDARD LVCMOS33 } [get_ports { dig[2] }];
#IO_L24P_T3_A01_D17_14 Sch=an[2]
set_property -dict { PACKAGE_PIN J14  IOSTANDARD LVCMOS33 } [get_ports { dig[3]
}]; #IO_L19P_T3_A22_15 Sch=an[3]
set_property -dict { PACKAGE_PIN P14  IOSTANDARD LVCMOS33 } [get_ports { dig[4]
}]; #IO_L8N_T1_D12_14 Sch=an[4]
set_property -dict { PACKAGE_PIN T14  IOSTANDARD LVCMOS33 } [get_ports { dig[5]
}]; #IO_L14P_T2_SRCC_14 Sch=an[5]
set_property -dict { PACKAGE_PIN K2   IOSTANDARD LVCMOS33 } [get_ports { dig[6]
}]; #IO_L23P_T3_35 Sch=an[6]
set_property -dict { PACKAGE_PIN U13  IOSTANDARD LVCMOS33 } [get_ports { dig[7]
}]; #IO_L23N_T3_A02_D18_14 Sch=an[7]


```

#### Results Discussion:

This part of the lab was the hardest part because of the calculation errors that we kept getting, everything integrated properly in the end. The values add just like we would expect from the given examples, exporting it onto the board worked without issues and our seven segment output with a two's complement representation of numbers works properly as well. The results above show  $M0 = 6$ ,  $M1 = -3$  (1101), and  $Cin = 1$  adding up to 9, just like the example in the lab

manual.

Figure 17: The figure is the final display of the design.

 

### Conclusion:

To conclude the main objective of this lab, which was to design a simple microprocessor that implemented the logic equation  $R2 = M0 + \text{not}(M1) + C_{in}$  was successfully created. The use of hierarchal design within the different modules was again used in order to link all modules together and create instances. It was again great practice for designing combinational and sequential circuits. Once the modules were built, using the NEXYS 4DDR, I was able to verify that the design was working correctly. Overall, the objectives for this lab were successfully completed.