

Started on Saturday, 26 November 2016, 4:40 PM

State Finished

Completed on Saturday, 26 November 2016, 4:40 PM

Time taken 9 secs

Grade 90.00 out of 100.00

Question 1

Correct

Mark 10.00 out of
10.00

CQ6.13

Given two inductors are magnetically coupled.

The coefficient of coupling $k = 0.56$

The self-inductances are:

$$L_1 = 4.3 \text{ H} \quad L_2 = 3.1 \text{ H}$$

Find the mutual inductance.

$$M = ?? \text{ H}$$

Answer:




Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

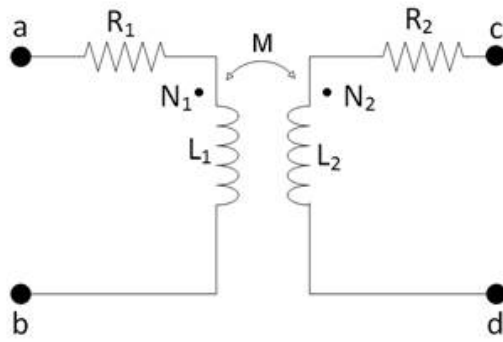

P6.39_6ed

Two magnetically coupled coils which have

$$L_1 = 196 \text{ mH} \quad L_2 = 4 \text{ mH} \quad M = 23.8 \text{ mH}$$

a) What is the coefficient of coupling k ?

$$k = \boxed{0.85} \checkmark$$

b) What is the largest possible value of M if the coupling was perfect?

$$M = \boxed{28} \checkmark \text{ mH}$$

c) Given that in this circuit $P_1 = P_2$, what is the turns ratio N_1/N_2 ?

$$N_1/N_2 = \boxed{7} \checkmark$$


Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

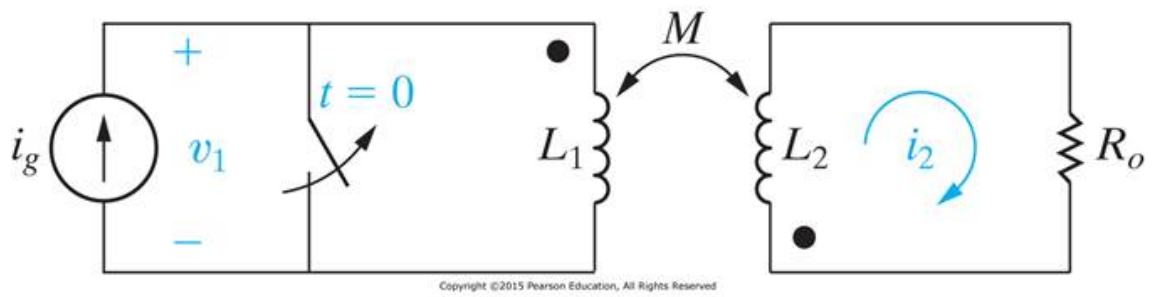

P6.39_10ed

Given: $L_1 = 5 \text{ H}$ $L_2 = 0.2 \text{ H}$ $M = 0.5 \text{ H}$ $R_o = 10 \Omega$ (Ohm)
 $i_g = -10 + e^{-10t} \text{ A for } t \geq 0$ $i_2 = 0.625e^{-10t} - 0.250e^{-50t} \text{ A for } t \geq 0$

There is no energy stored in this circuit at the time the switch is opened.

a) Find the voltage $v_1(t)$ at $t = 0^+$ sec just as the switch opens.

$$v_1(t = 0^+ \text{ sec}) = -46.875 \text{ V}$$

b) Find the voltage $v_1(t)$ at $t = 0.2$ sec after the switch opens.

$$v_1(t = 0.2 \text{ sec}) = -7.189 \text{ V}$$


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

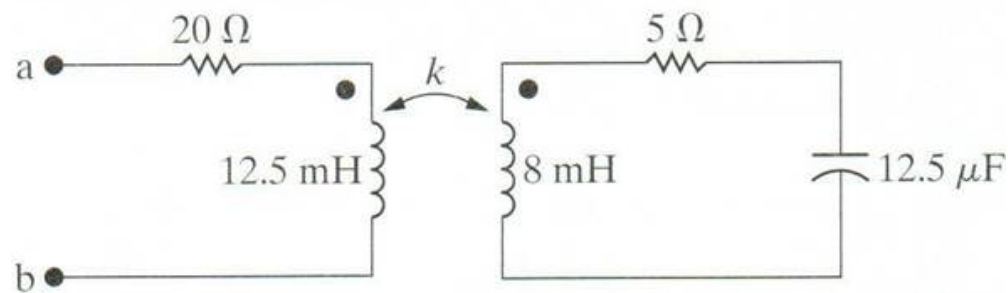

P9.69_7ed

Given driving source frequency = 4 krad/sec.

The coefficient of coupling k is adjusted so that Z_{ab} is purely resistive.

a) Find k for this condition.

$$k = 0.66$$

b) Find Z_{ab} for this condition.

$$Z_{ab} = 40.83 \Omega \text{ (Ohm)}$$


Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

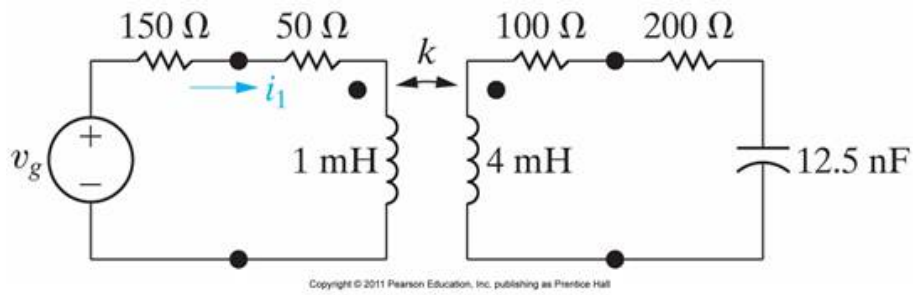

P9.76_9ed

The sinusoidal source is operating at 200 krad/sec (kilo rad/sec).

The coefficient of coupling k is adjusted until the peak amplitude of i_1 is maximum.

Given $v_g = 560 \cos(200,000t)$ V.

a) What is the value of k ? [Hint: Use reflected impedance which includes k and determine when Z_{in} is minimum which yields the max current]

$$k = 0.3536 \quad \checkmark$$

b) What is the peak amplitude of i_1 ?

$$|i_1| = 2 \quad \checkmark \text{ A}$$


Correct

Marks for this submission: 10.00/10.00.

Question 6

Incorrect

Mark 0.00 out of 10.00

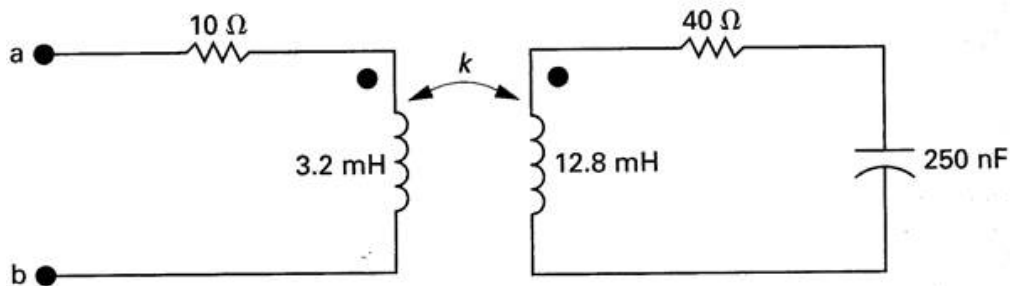

P9.63_6ed

Given driving source frequency = 25 krad/sec.

The coefficient of coupling k is adjusted so that Z_{ab} is purely resistive.

Find Z_{ab} for this condition.

$$Z_{ab} = 22.48 \quad \times \text{ } \Omega \text{ (Ohm)}$$


Incorrect

Marks for this submission: 0.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

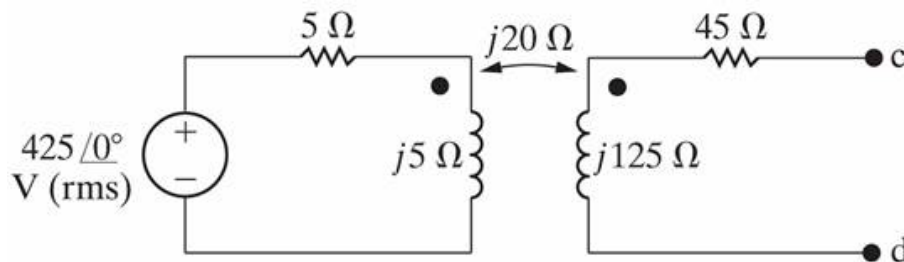

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P9.78_9ed

Find the Thevenin equivalent of this circuit w.r.t. terminals c,d.

$|Z_{Th}| = 120.21 \checkmark \Omega \text{ (Ohms)}$ $Z_{Th} \text{ angle} = 45 \checkmark^\circ \text{ (Degrees)}$

$|V_{Th}| = 1202.1 \checkmark \text{ Vrms}$ $V_{Th} \text{ angle} = 45 \checkmark^\circ \text{ (Degrees)}$

Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

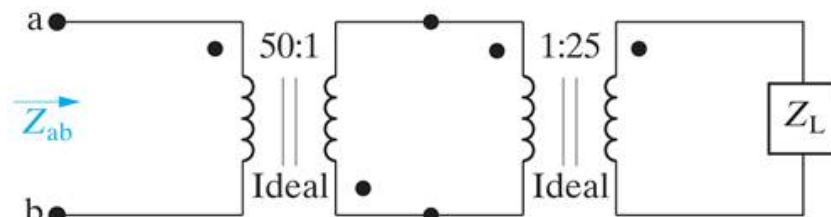


Figure: 09-58-55P9.77

Copyright © 2008 Pearson Prentice Hall, Inc.

P9.77_8ed

Given: $Z_L = 200 + j 150 \Omega$.

Find the impedance Z_{ab}

$Z_{ab} = \text{Magnitude } 1000 \checkmark \text{ at Angle } 36.87 \checkmark^\circ \text{ (Degrees)} \Omega \text{ (Ohm)}$


Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

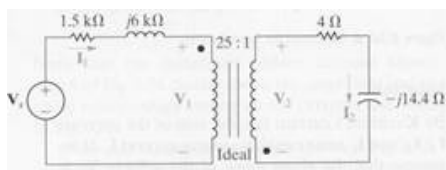

AP9.15_9ed

The source voltage is 25 at angle 0° kV (kilo Volts).

Find the amplitude and phase angle of V_2 and I_2 .

$|V_2| = 1868.15$ ✓ Volts

Phase angle $V_2 = 142.39$ ✓ $^\circ$ (Degrees)

$|I_2| = 125$ ✓ A

Phase angle $I_2 = 216.87$ ✓ $^\circ$ (Degrees)


Correct

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of 10.00

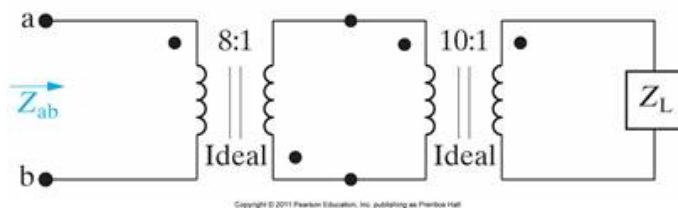

P9.83_6ed

Find the impedance Z_{ab} if $Z_L = 80$ at angle 60° Ω (Ohms).

$|Z_{ab}| = 512$ ✓ k Ω (kilo Ohm)

Z_{ab} angle = 60 ✓ $^\circ$ (Degrees)

Correct

Marks for this submission: 10.00/10.00.