

Started on Tuesday, 6 September 2016, 2:06 PM

State Finished

Completed on Tuesday, 6 September 2016, 3:29 PM

Time taken 1 hour 23 mins

Grade 100.00 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

SI-05

In a science fiction show, an hour is $\frac{1}{10}$ of a day and a minute is $\frac{1}{100}$ of an hour (Centons). How many Centons are in two days of this science fiction show?

2000 ✓ Centons

Question 2

Correct

Mark 10.00 out of 10.00

SI-04


A political rally in 1995 known as the "Million Man March" occurred on the National Mall. Assume the Washington DC subway was the sole means of transport. A subway train arrives every 1 minute (not really - just for this problem) and delivered 1,000 men each time. How long in minutes did it take for all the million men to arrive?

Arrival time period: 1000 ✓ minutes.

Question 3

Correct

Mark 10.00 out of 10.00

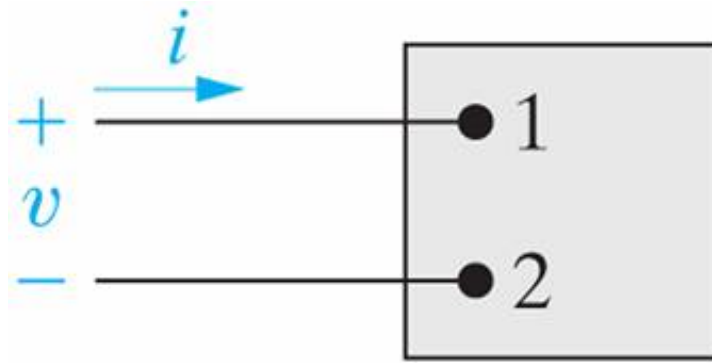

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P1.07_10ed

There is no charge at the upper terminal of the ideal element in the above figure for $t < 0$.

At $t = 0$ a current of $125 e^{-2,500t}$ mA enters the upper terminal and will accumulate at the upper terminal.

a) Be able to derive the expression for the charge that accumulates at the upper terminal for $t \geq 0$.

$$q(t) = 50 (1 - e^{-2,500t}) \mu\text{C} \text{ (micro Coulomb)}$$

b) Find the total charge that accumulates at the upper terminal, i.e. let $t \rightarrow \infty$.

$$q(t \rightarrow \infty) = 50(1 - e^{-(2500t)}) \mu\text{C} \text{ (micro Coulomb)}$$

c) If the current is abruptly stopped at $t = 0.5$ ms, how much charge has accumulated at the upper terminal?


$$q(t \rightarrow 0.5\text{ms}) = 35(1 - e^{-2500t}) \mu\text{C} \text{ (micro Coulomb)}$$

Coulomb)

Question 4

Correct

Mark 10.00 out of 10.00

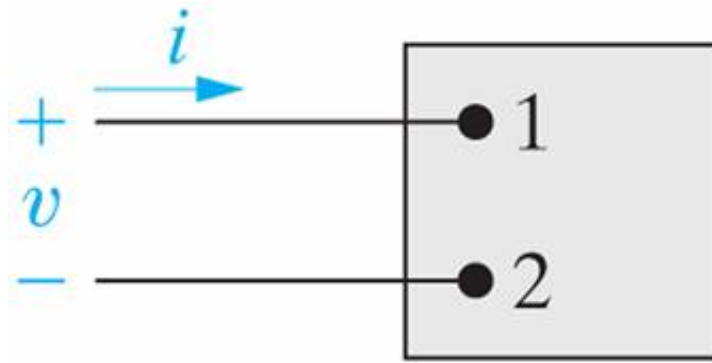

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P1.07_10ed

There is no charge at the upper terminal of the ideal element in the above figure for $t < 0$.

At $t = 0$ a current of $125 e^{-2,500t}$ mA enters the upper terminal and will accumulate at the upper terminal.

a) Be able to derive the expression for the charge that accumulates at the upper terminal for $t \geq 0$.

$$q(t) = 50 (1 - e^{-2,500t}) \mu\text{C} \text{ (micro Coulomb)}$$

b) Find the total charge that accumulates at the upper terminal, i.e. let $t \rightarrow \infty$.

$$q(t \rightarrow \infty) = 50(1 - e^{-(2500t)}) \mu\text{C} \text{ (micro Coulomb)}$$

c) If the current is abruptly stopped at $t = 0.5$ ms, how much charge has accumulated at the upper terminal?


$$q(t \rightarrow 0.5\text{ms}) = 35(1 - e^{-2500t}) \mu\text{C} \text{ (micro Coulomb)}$$

Coulomb)

Question 5

Correct

Mark 10.00 out of 10.00

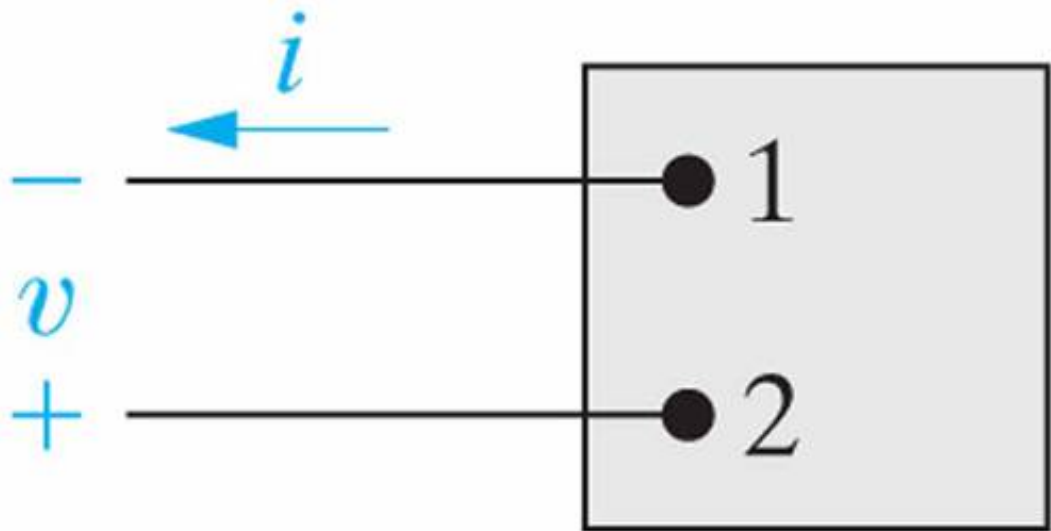

PSS-1

Select the correct expression for power at the terminals 1,2 of the figure.


Select one:

- ☒ A. $p = (+) v i$ ✓
- ☐ B. $p = (-) v i$

Question 6

Correct

Mark 10.00 out of 10.00

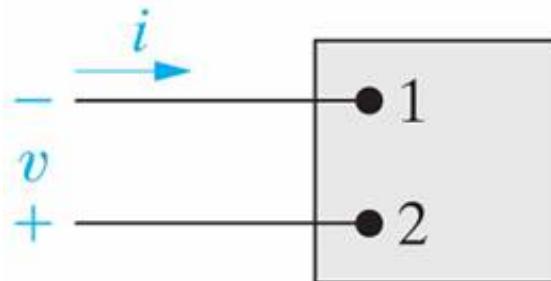

PSS-1

Select the correct expression for power at the terminals 1,2 of the figure.

Select one:

- ☐ A. $p = (+) v i$
- ☒ B. $p = (-) v i$ ✓

Question 7

Correct

Mark 10.00 out of 10.00

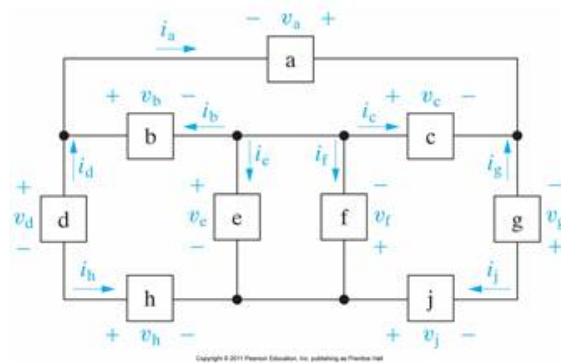


TABLE P1.30

Element	Voltage (V)	Current (mA)
a	1.6	80
b	2.6	60
c	-4.2	-50
d	1.2	20
e	1.8	30
f	-1.8	-40
g	-3.6	-30
h	3.2	-20
j	-2.4	30

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P1.30_9ed

To be valid, the total power delivered in a complete circuit MUST equal the power absorbed by the circuit.

$P_{abs} + P_{del} = \text{zero}$ In other words, all energy is accounted for.

Use the circuit diagram and table to prove the circuit obeys this conservation-of-energy principle.

$p_a = -128$ ✓ mW

$p_b = -156$ ✓ mW

$p_c = 210$ ✓ mW

$p_d = -24$ ✓ mW

$p_e = 54$ ✓ mW

$p_f = -72$ ✓ mW

$p_g = 108$ ✓ mW

$p_h = -64$ ✓ mW

$p_j = 72$ ✓ mW

Question 8

Correct

Mark 10.00 out of 10.00

P1.12_9ed

One 12V battery supplies 100 mA to a music player.


How much energy does the battery supply in 4 hours?

$w = 17280$ ✓ J

Question 9

Correct

Mark 10.00 out of 10.00

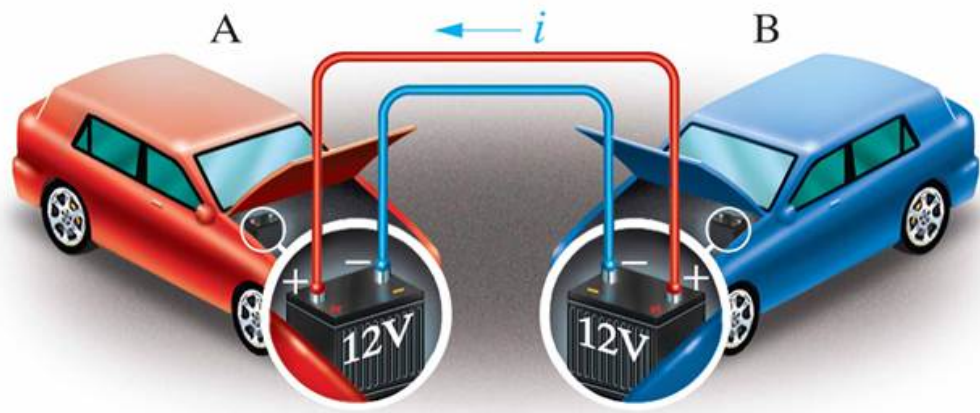

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P1.11a_9ed

You find out that your car's battery is dead. A friend "jumps" your battery as shown in the figure.

What is the color of your car? {Red} Red or Blue?

Select one:

- ☒ A. Red - Car A ✓
- ☐ B. Blue - Car B
- ☐ C. Not enough information shown.

Question 10

Correct

Mark 10.00 out of 10.00

P1.12_9ed

One 12V battery supplies 100 mA to a music player.

How much energy does the battery supply in 4 hours?

w = 17280 ✓ J