

Home ► My courses ► **EEE 108_f17** ► Chapter 1 - Signals and Amplifiers ►
Quiz 1b - Signals and Amplifiers

Started on Thursday, 14 September 2017, 4:43 PM

State Finished

Completed on Thursday, 14 September 2017, 10:43 PM

Time taken 5 hours 59 mins

Grade **10.0** out of 10.0 (**100%**)

Question 1

Correct

Mark 2.0 out of 2.0

What is the power dissipation in milliwatts for an amplifier which delivers a sinusoidal output voltage of 3.4 V_{peak} to a 0.8k Ω load while drawing a current of 11.1mA from two power supplies of VCC = +10V and VEE = -10V ? Neglect any power drawn from the input signal source.

Answer:



The correct answer is: 214.78


Correct

Marks for this submission: 2.0/2.0.

Question 2

Correct

Mark 2.0 out of 2.0

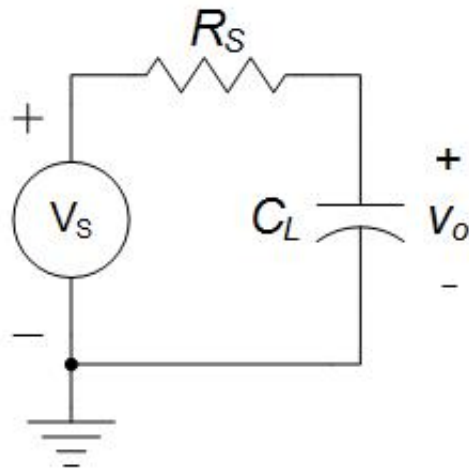

For the filter circuit shown, what is the pole frequency in MHz for the transfer function V_o/V_s ? Use $R_s = 4.5\text{k}\Omega$ and $C_L = 2.8\text{pF}$.

Answer: 12.63



The correct answer is: 12.63

Correct

Marks for this submission: 2.0/2.0.

Question 3

Correct

Mark 2.0 out of 2.0

For an amplifier with a single high frequency pole, which of the following is true?

Select one:

- ☐ a. At this pole frequency, the phase of the gain will be +45 degrees above the midband value
- ☒ b. Above this pole frequency, the magnitude of the gain will roll off at -20dB/decade as frequency increases ✓
- ☐ c. None of these
- ☐ d. Above this pole frequency, the phase of the gain will increase at +45 degrees/decade as frequency increases
- ☐ e. At this pole frequency, the magnitude of the gain will be +3dB above the midband value

The correct answer is: Above this pole frequency, the magnitude of the gain will roll off at -20dB/decade as frequency increases


Correct

Marks for this submission: 2.0/2.0.

Question 4

Correct

Mark 2.0 out of 2.0

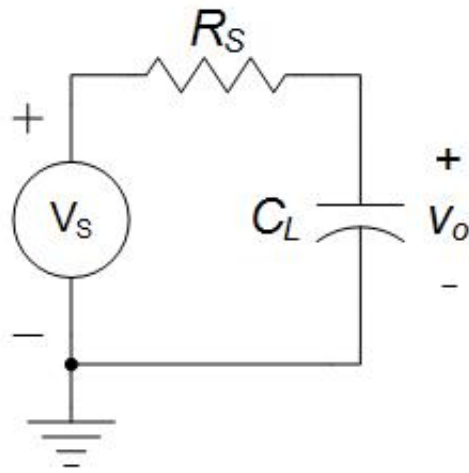

The circuit shown has a :

Select one:

- ☐ a. Impossible to determine
- ☐ b. None of these
- ☒ c. Low pass response ✓
- ☐ d. High pass response
- ☐ e. Bandpass response

The correct answer is: Low pass response

Correct

Marks for this submission: 2.0/2.0.

Question 5

Correct

Mark 2.0 out of 2.0

For an amplifier with a single-time constant high pass response, the magnitude of the gain decreases at -6dB/octave as the frequency is decreased below the corner frequency.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

Correct

Marks for this submission: 2.0/2.0.