

[Home](#) ► [Electrical Engineering](#) ► [Engr 17 F16 Tatro](#) ► [Exams and Quizzes](#) ► [Quiz 7 - Chap 4](#)

---

<b>Started on</b>	Wednesday, 26 October 2016, 11:23 AM
-------------------	--------------------------------------

---

<b>State</b>	Finished
--------------	----------

---

<b>Completed on</b>	Wednesday, 26 October 2016, 11:41 AM
---------------------	--------------------------------------

---

<b>Time taken</b>	17 mins 21 secs
-------------------	-----------------

---


<b>Grade</b>	<b>100.00</b> out of 100.00
--------------	-----------------------------

---

**Question 1**

Correct

Mark 100.00 out of 100.00

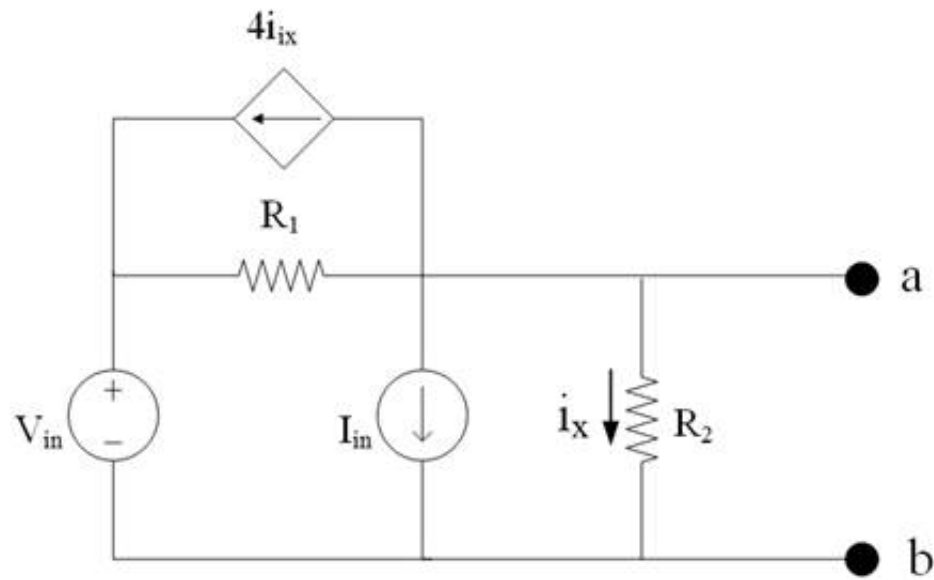

Quiz 7g

Given:  $V_{in} = 26 \text{ V}$     $I_{in} = 4 \text{ A}$     $R_1 = 2 \Omega$  (Ohms)    $R_2 = 7.5 \Omega$  (Ohms)

Find the Thévenin equivalent circuit with respect to the terminals ab.

$$V_{Th} = 7.712 \text{ V}$$

$$R_{TH} = 0.856 \Omega \text{ (Ohms)}$$

**Numeric Answer**

$$V_{Th} = 7.714 \text{ Volts}$$

$$R_{TH} = 0.857 \Omega \text{ (Ohms)}$$

**Correct**

Marks for this submission: 100.00/100.00.