

**Started on** Wednesday, 22 February 2017, 10:56 AM

**State** Finished

**Completed on** Wednesday, 22 February 2017, 11:54 AM

**Time taken** 58 mins 7 secs

**Grade** 100.00 out of 100.00

**Question 1**

Correct

Mark 15.00 out of 15.00

Q1c

Consider the sinusoidal voltage  $v(t) = 300 \cos(200 \pi t - 60^\circ) V_{\text{rms}}$ .

a) What is the maximum amplitude of the voltage?

$V_m =$   ✓ V

b) What is the frequency of  $v(t)$  in hertz?

$f =$   ✓ Hz

c) What is the frequency of  $v(t)$  in radians per second?

$\omega =$   ✓ rad/sec

d) What is the phase angle in radians?

$\phi \text{ (phi)} =$   ✓ radians

e) What is the period in milliseconds?

$T =$   ✓ ms (milli sec)

**Correct**

Marks for this submission: 15.00/15.00.

**Question 2**

Correct

Mark 5.00 out of 5.00

Q2b

Given:  $x(t) = 150 \cos(300t + 35^\circ) + 450 \cos(300t - 55^\circ)$

Use the concept of the phasor to combine this sinusoidal function into a single trigonometric expression in the form similar to  $x(t) = A \cos(\omega t + \theta^\circ)$ .

Magnitude A of  $x(t) =$   ✓

Angle  $\theta$  of  $x(t) =$   ✓° (Degree)


**Correct**

Marks for this submission: 5.00/5.00.

**Question 3**

Correct

Mark 15.00 out of 15.00

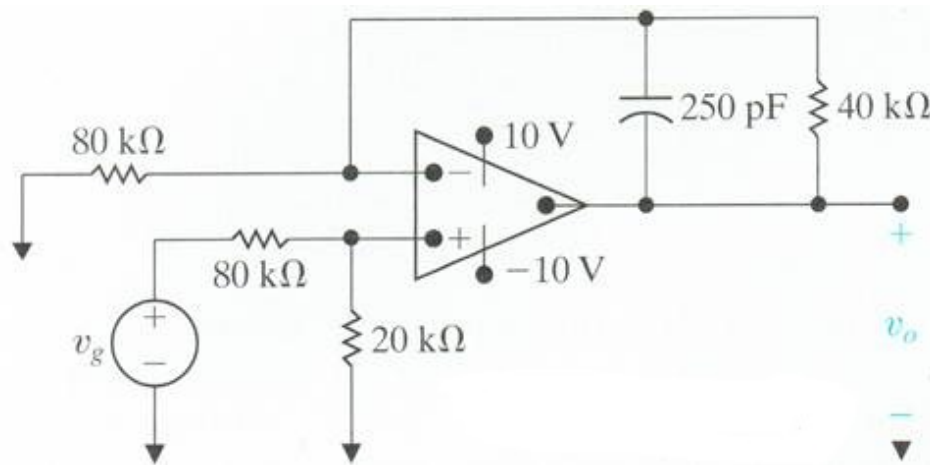

Q3d

Assume the operational amplifier is ideal.

Given  $v_g(t) = 38.0 \text{ V}$  (a constant voltage)

Find the steady-state output  $v_o(t)$ .

$v_o(t) =$   ✓ Volts


**Correct**

Marks for this submission: 15.00/15.00.

**Question 4**

Correct

Mark 10.00 out of 10.00

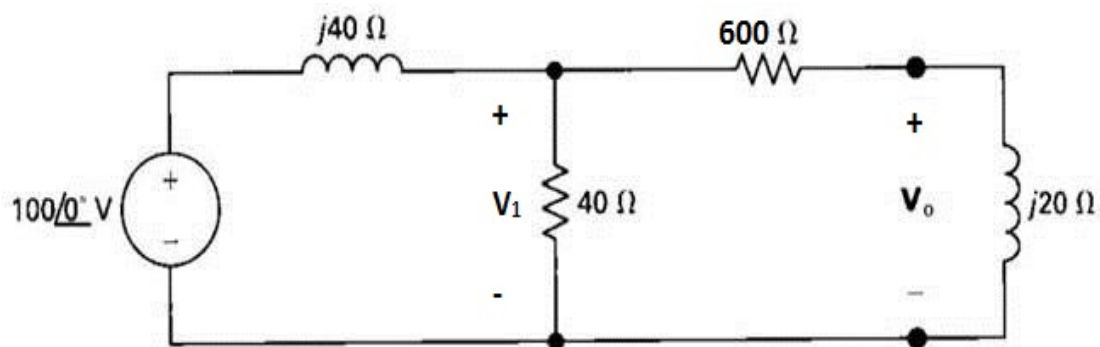

Q4c

Find the phasor voltages  $V_0$  and  $V_1$ . I suggest you use the Node Method.

$V_0 =$   ✓ at angle  ✓° (Degrees) Volts

$V_1 =$   ✓ at angle  ✓° (Degrees) Volts

Express your answer as a positive magnitude and then the angle in the appropriate quadrant.


**Correct**

Marks for this submission: 10.00/10.00.


**Question 5**

Correct

Mark 15.00 out of 15.00

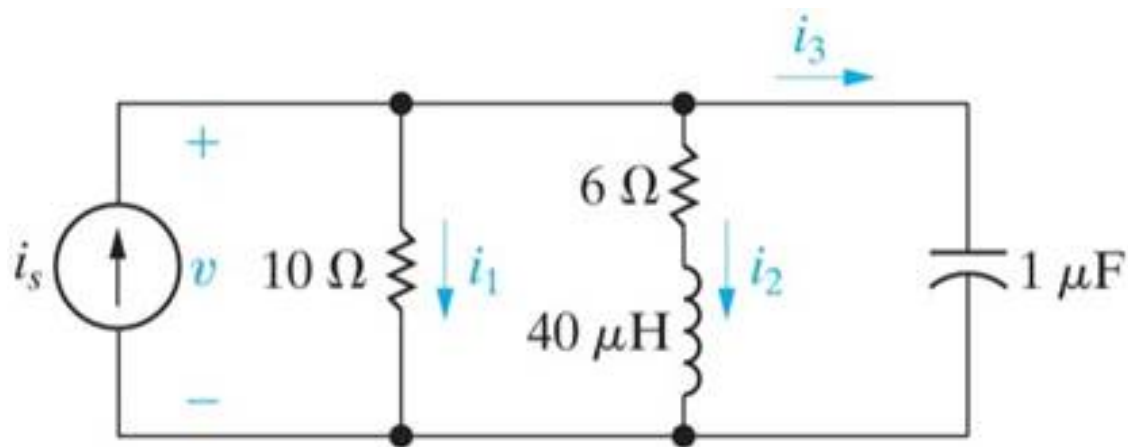

Q5b


Given  $i_s = 20 \cos(100,000 t + 6.12^\circ)$  AmpsThe equivalent admittance of the circuit is  $Y_{Eq} = 0.2166$  at angle  $6.12^\circ$  (Degrees) SiemensCalculate the average power absorbed/delivered by the  $6 \Omega$  (Ohm) resistor. $P_{6\Omega} =$    W “+” = absorbed “-” = delivered**Correct**

Marks for this submission: 15.00/15.00.

**Question 6**

Correct

Mark 10.00 out of 10.00

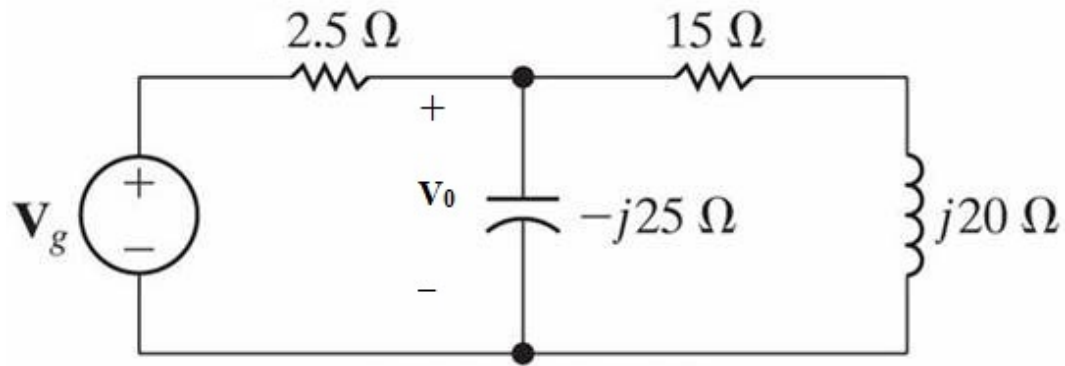

Q6d

Given:

The voltage source  $V_g = 160$  at angle  $0^\circ$   $V_{\text{rms}}$   
 and the voltage  $V_0 = 139.0763$  at angle  $4.40^\circ$   $V_{\text{rms}}$ .

Find the average and reactive power for the voltage source  $V_g$ .

$$S_g = \boxed{-273.0667} \checkmark + j \boxed{-136.533} \checkmark \text{ VA}$$

“+” = absorbed and “-” = delivered

**Correct**

Marks for this submission: 10.00/10.00.

**Question 7**

Correct

Mark 5.00 out of 5.00

Q7c

Given that a balanced three-phase set of voltages is in the positive phase sequence where

$$v_a = 170 \cos(\omega t + 23^\circ) \text{ V.}$$

Find the other two phase voltages.

$$v_b = \boxed{170} \checkmark \cos(\omega t + \boxed{-97} \checkmark^\circ) \text{ V}$$

$$v_c = \boxed{170} \checkmark \cos(\omega t + \boxed{143} \checkmark^\circ) \text{ V}$$


**Correct**

Marks for this submission: 5.00/5.00.

**Question 8**

Correct

Mark 15.00 out of 15.00

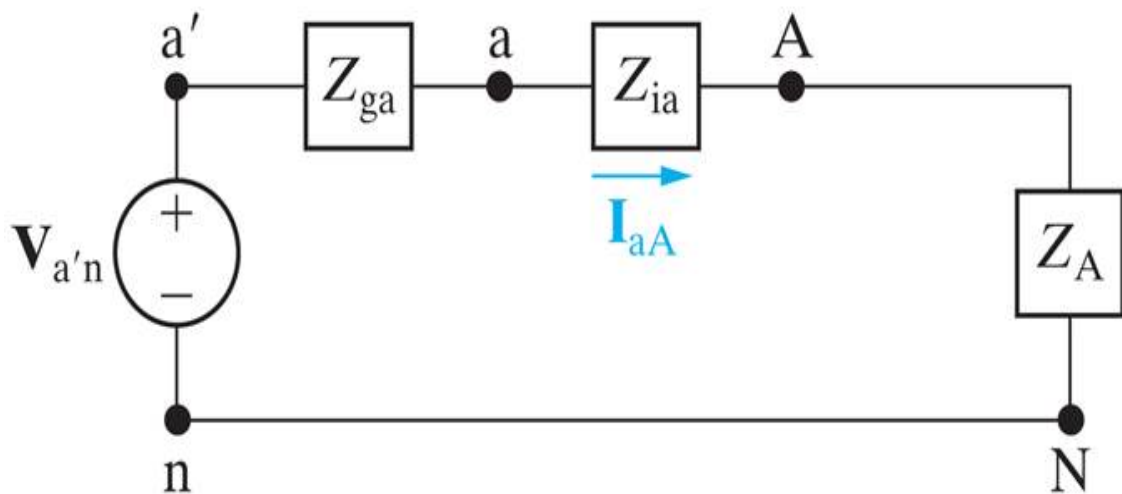

Q8a

Given:  $V_{a'n} = 120$  at angle  $0^\circ$   $V_{rms}$  in a balanced three phase system with a positive phase sequence.

The source and load are Y connected.

$$Z_{ga} = 1 + j15 \, \Omega \quad Z_{ia} = 19 + j5 \, \Omega \quad Z_A = 20 + j20 \, \Omega$$

Calculate the single phase equivalent line currents  $I_{aA}$ ,  $I_{bB}$  and  $I_{cC}$ .

$$I_{aA} = 2.121 \checkmark \text{ at angle } -45 \checkmark^\circ \text{ (Degrees) } A_{rms}$$

$$I_{bB} = 2.121 \checkmark \text{ at angle } -165 \checkmark^\circ \text{ (Degrees) } A_{rms}$$

$$I_{cC} = 2.121 \checkmark \text{ at angle } 75 \checkmark^\circ \text{ (Degrees) } A_{rms}$$

Calculate the line to line voltages  $V_{AB}$ ,  $V_{BC}$ , and  $V_{CA}$ .

$$V_{AB} = 103.92 \checkmark \text{ at angle } 30 \checkmark^\circ \text{ (Degrees) } V_{rms}$$

$$V_{BC} = 103.92 \checkmark \text{ at angle } -90 \checkmark^\circ \text{ (Degrees) } V_{rms}$$

$$V_{CA} = 103.92 \checkmark \text{ at angle } 150 \checkmark^\circ \text{ (Degrees) } V_{rms}$$

**Correct**

Marks for this submission: 15.00/15.00.

**Question 9**

Correct

Mark 10.00 out of  
10.00

Q9a

The total apparent power supplied in a balanced three-phase Y-D system is 3,600 VA. The source line to neutral voltage is 240 V<sub>rms</sub>. The line impedance is negligible and the power factor angle of the load is 35° lagging.

Determine the impedance of the load.

$$Z_{\Delta, \text{load}} = 39.32 \checkmark + j 27.5 \checkmark \Omega \text{ (Ohms)}$$

**Correct**

Marks for this submission: 10.00/10.00.