

Started on Wednesday, 19 April 2017, 11:08 AM

State Finished

Completed on Wednesday, 19 April 2017, 11:56 AM


Time taken 47 mins 49 secs

Grade 100.00 out of 100.00

Question 1

Correct

Mark 100.00 out of 100.00

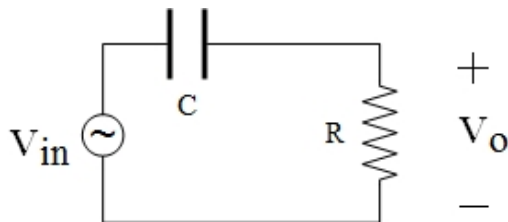

Quiz 9d

Given: $C = 12 \text{ nF}$ (nano F) $R = 125 \text{ k}\Omega$ (kilo Ohm)

a) Find the cutoff frequency f_c for this high-pass filter.

$f_c =$ \checkmark Hz

b) Find the $H(j\omega)$ for $H(j\omega = 0.2\omega_c)$.

$H(j\omega = 0.2\omega_c) =$ \checkmark at angle \checkmark° (Degrees)

c) Find the $H(j\omega)$ for $H(j\omega = \omega_c)$.

$H(j\omega = \omega_c) =$ \checkmark at angle \checkmark° (Degrees)

d) Find the $H(j\omega)$ for $H(j\omega = 5\omega_c)$.

$H(j\omega = 5\omega_c) =$ \checkmark at angle \checkmark° (Degrees)

Numeric Answer

a) $f_c = 106.1033 \text{ Hz}$

b) $H(j\omega = 0.2\omega_c) = 0.1961$ at angle 78.69°

c) $H(j\omega = \omega_c) = 0.7071$ at angle 45°

d) $H(j\omega = 5\omega_c) = 0.9806$ at angle 11.31°

Correct

Marks for this submission: 100.00/100.00.