

**Started on** Tuesday, 12 September 2017, 11:49 AM

**State** Finished

**Completed on** Tuesday, 12 September 2017, 11:51 AM


**Time taken** 2 mins 19 secs

**Grade** 2.0 out of 10.0 (20%)

**Question 1**

Not answered

Mark 0.0 out of 2.0

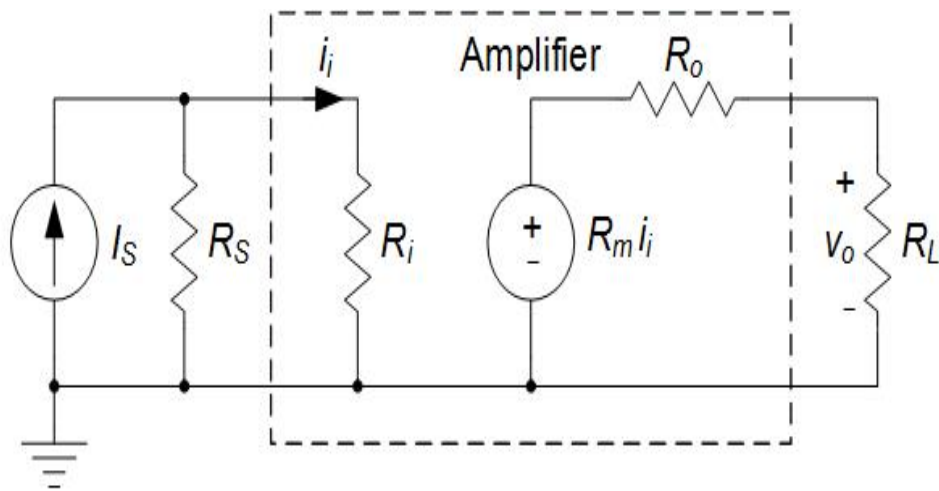

For the amplifier shown, what is the largest output resistance in  $k\Omega$  that can be used and still get at least 50.5 percent of the amplifier's open circuit output voltage =  $R_m i_i$  to appear across  $R_L$ ? Use  $R_L = 95.2k\Omega$ .

Answer:  ✖

The correct answer is: 93.31

**Question 2**

Correct

Mark 1.0 out of 2.0

Which of the following is true for a DC coupled amplifier with a single high frequency pole?

Select one:

- ☐ a. Below this pole frequency, the magnitude of the gain will be approximately constant
- ☒ b. All of these ✓
- ☐ c. Above this pole frequency, the magnitude of the gain will roll off at -20dB/decade as frequency increases
- ☐ d. At this pole frequency, the magnitude of the gain will be -3dB below the midband value
- ☐ e. At this pole frequency, the phase of the gain will be -45 degrees below the midband value

The correct answer is: All of these

**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **1.0/2.0**.

**Question 3**

Correct

Mark 0.0 out of 2.0

Transresistance amplifiers use a current input signal and a voltage output signal.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.


**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **0.0/2.0**.

**Question 4**

Correct

Mark 1.0 out of 2.0

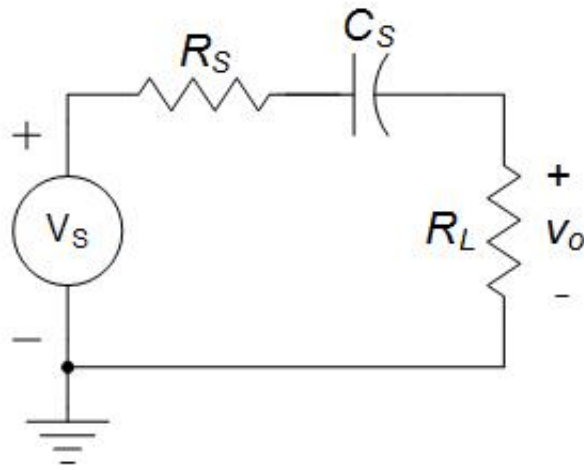

The circuit shown has a :

Select one:

- ☒ a. High pass response ✓
- ☐ b. None of these
- ☐ c. Impossible to determine
- ☐ d. Low pass response
- ☐ e. Bandpass response

The correct answer is: High pass response


**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **1.0/2.0**.

**Question 5**

Not answered

Mark 0.0 out of 2.0

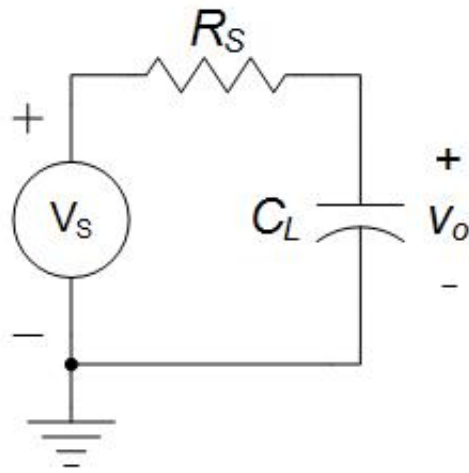

For the filter circuit shown, what is the phase in degrees of the transfer function  $V_o/V_s$  at a frequency of 5.8MHz? Use  $R_s = 6.6\text{k}\Omega$  and  $C_L = 5.3\text{pF}$ .

Answer:  ✗

The correct answer is: -51.887

**Started on** Tuesday, 12 September 2017, 11:52 AM

**State** Finished

**Completed on** Tuesday, 12 September 2017, 11:52 AM


**Time taken** 11 secs

**Grade** 0.0 out of 10.0 (0%)

**Question 1**

Not answered

Mark 0.0 out of 2.0

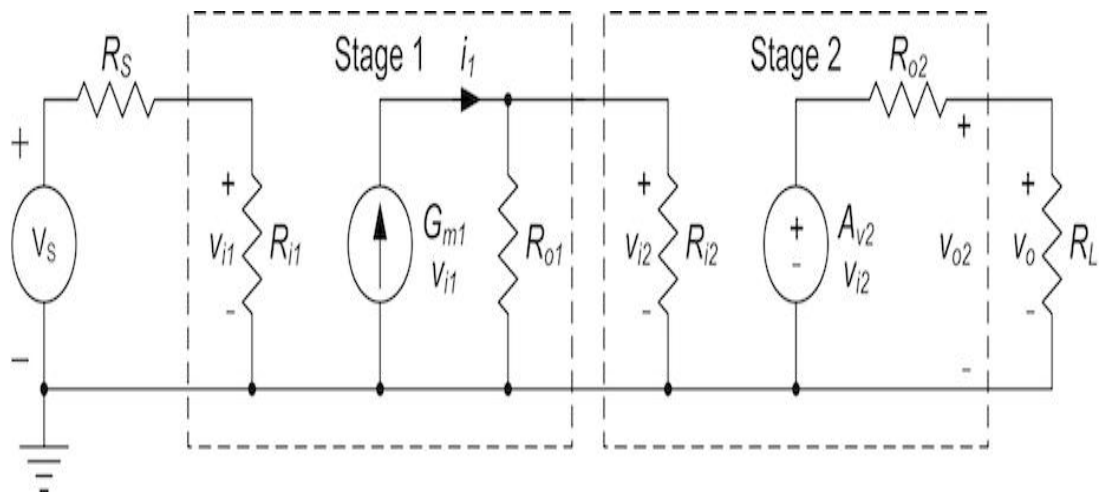

What is the value of the transconductance gain in mA/V for the 2-stage amplifier circuit shown? Use  $R_s = 4.8\text{k}\Omega$ ,  $R_{i1} = 35.5\text{k}\Omega$ ,  $R_{o1} = 35.4\text{k}\Omega$ ,  $G_{m1} = 35.9\text{ mA/V}$ ,  $R_{i2} = 36.6\text{k}\Omega$ ,  $R_{o2} = 19.5\text{k}\Omega$ ,  $A_{v2} = 90.8\text{ V/V}$  and  $R_L = 28.2\text{k}\Omega$ .

Answer:  ✖

The correct answer is: 1083.27

**Question 2**

Not answered

Mark 0.0 out of 2.0

The gain for a transresistance amplifier has units of :

Select one:

- ☐ a. Amps per Volt
- ☐ b. Amps per Amp
- ☐ c. None of these
- ☐ d. Volts per Amp
- ☐ e. Volts per Volt

The correct answer is: Volts per Amp

**Question 3**

Not answered

Mark 0.0 out of 2.0

A transconductance amplifier needs a high input resistance and a high output resistance.

Select one:


- ☐ True
- ☐ False

The correct answer is 'True'.

**Question 4**

Not answered

Mark 0.0 out of 2.0

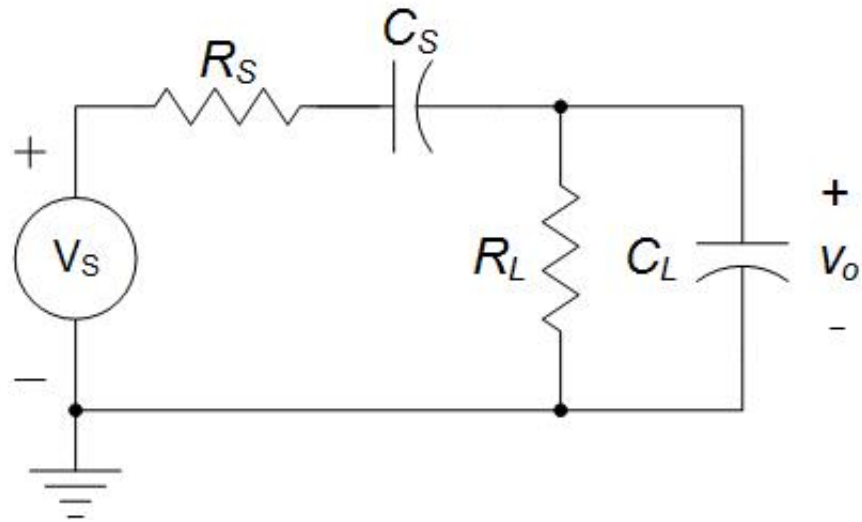

The circuit shown has a :

Select one:


- ☐ a. Bandpass response
- ☐ b. Low pass response
- ☐ c. None of these
- ☐ d. Impossible to determine
- ☐ e. High pass response

The correct answer is: Bandpass response

**Question 5**

Not answered

Mark 0.0 out of 2.0

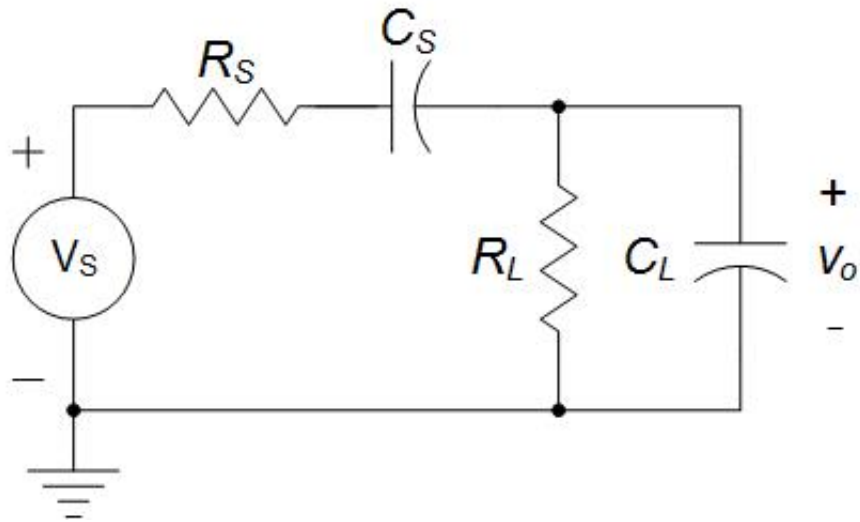

For the filter circuit shown, what is the magnitude of the transfer function  $V_o/V_s$  at midband frequencies? (Note: Midband refers to frequencies that are well above the low frequency pole and also well below the high frequency pole.) Use  $R_s = 2.1\text{k}\Omega$ ,  $R_L = 11.4\text{k}\Omega$ ,  $C_s = 382.8\text{pF}$  and  $C_L = 5.7\text{pF}$ .

Answer:  ✗

The correct answer is: 0.84



**Started on** Tuesday, 12 September 2017, 11:53 AM

**State** Finished

**Completed on** Tuesday, 12 September 2017, 11:55 AM


**Time taken** 2 mins 6 secs

**Grade** 2.0 out of 10.0 (20%)

**Question 1**

Incorrect

Mark 0.0 out of 2.0

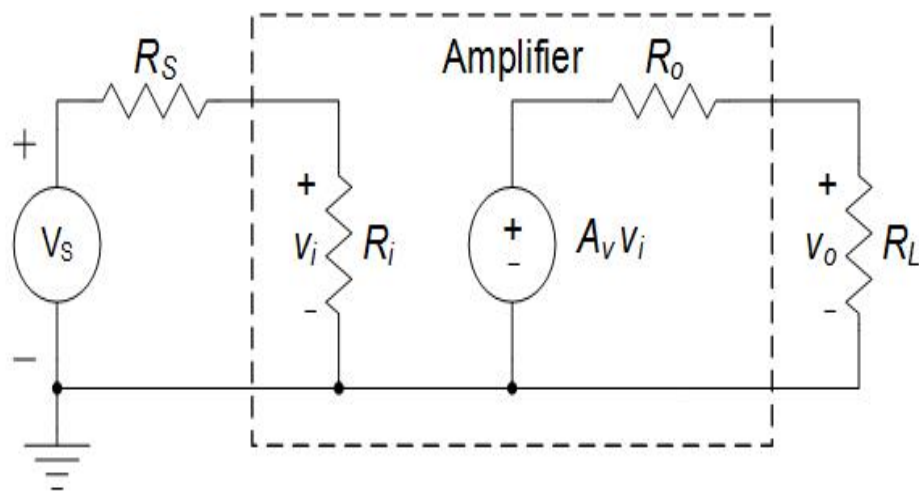

For the amplifier shown, what is the smallest input resistance in  $k\Omega$  that can be used without losing more than 41 percent of the source voltage across the source resistance? Use  $R_s = 8.2k\Omega$ .

Answer:  ✗

The correct answer is: 11.80

**Incorrect**

Marks for this submission: 0.0/2.0.

**Question 2**

Correct

Mark 1.0 out of 2.0

An amplifier which needs a low input resistance and a low output resistance is :

Select one:

- ☐ a. A voltage amplifier
- ☐ b. None of these
- ☐ c. A transconductance amplifier
- ☒ d. A transresistance amplifier ✓
- ☐ e. A current amplifier

The correct answer is: A transresistance amplifier

**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **1.0/2.0**.

**Question 3**

Correct

Mark 0.0 out of 2.0

Voltage amplifiers use a voltage input signal and a current output signal.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.


**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **0.0/2.0**.

**Question 4**

Correct

Mark 1.0 out of 2.0

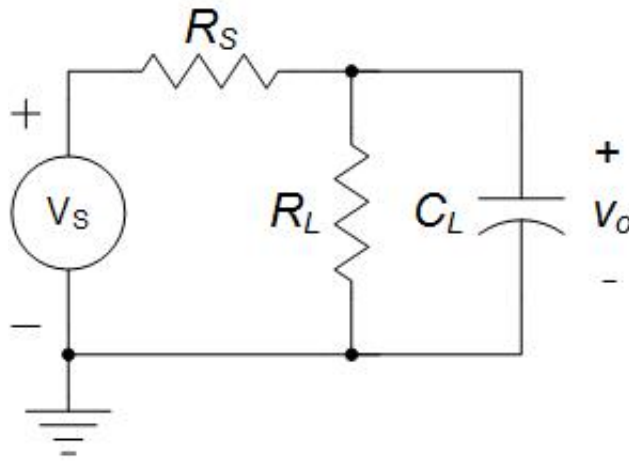

The circuit shown has a :

Select one:

- ☐ a. None of these
- ☐ b. High pass response
- ☐ c. Bandpass response
- ☒ d. Low pass response ✓
- ☐ e. Impossible to determine

The correct answer is: Low pass response


**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **1.0/2.0**.

**Question 5**

Not answered

Mark 0.0 out of 2.0

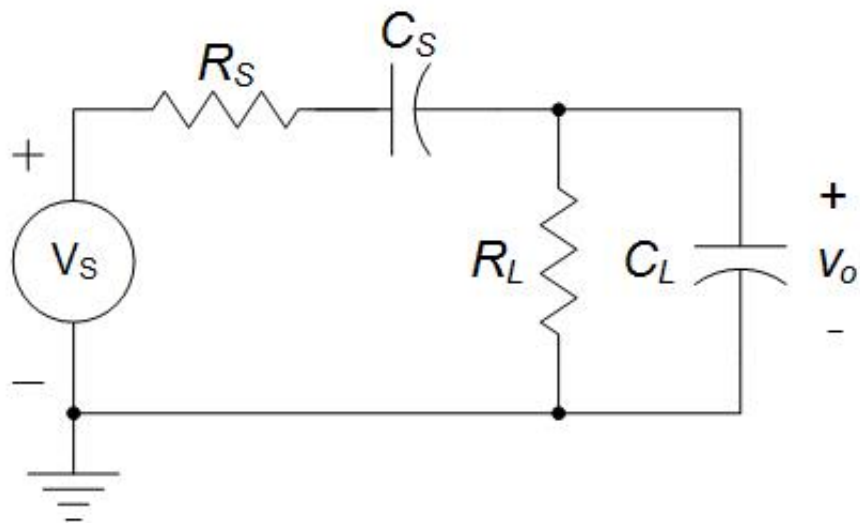

For the filter circuit shown, what is the frequency in kHz of the low frequency pole for the transfer function  $V_o/V_s$  ? Use  $R_s = 1.3\text{k}\Omega$ ,  $R_L = 11.7\text{k}\Omega$ ,  $C_s = 445.3\text{pF}$  and  $C_L = 2.2\text{pF}$ .

Answer:  ✖

The correct answer is: 27.49

**Started on** Tuesday, 12 September 2017, 11:58 AM

**State** Finished

**Completed on** Tuesday, 12 September 2017, 11:59 AM


**Time taken** 42 secs

**Grade** 0.0 out of 10.0 (0%)

**Question 1**

Not answered

Mark 0.0 out of 2.0

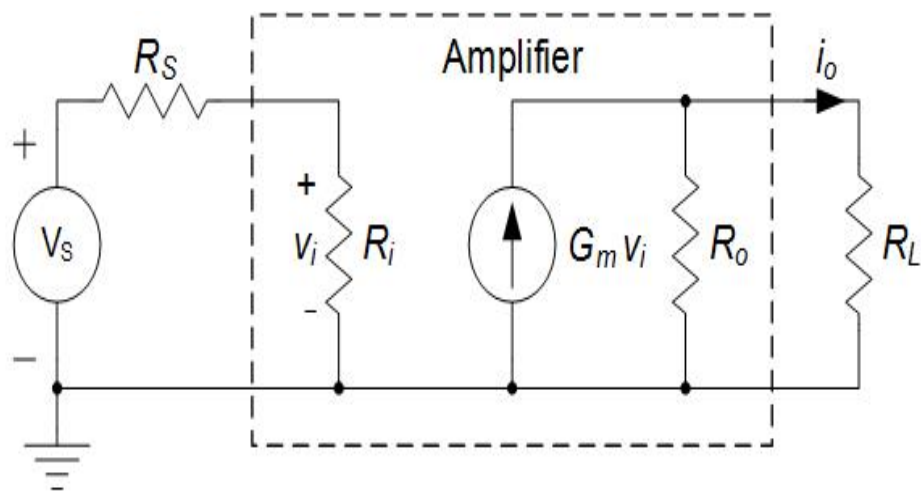

For the amplifier shown, what is the smallest input resistance in  $k\Omega$  that can be used without losing more than 13.2 percent of the source voltage across the source resistance? Use  $R_s = 15.4k\Omega$ .

Answer:  ✖

The correct answer is: 101.27

**Question 2**

Not answered

Mark 0.0 out of 2.0

The gain for a transconductance amplifier has units of :

Select one:

- ☐ a. Volts per Amp
- ☐ b. Amps per Amp
- ☐ c. Amps per Volt
- ☐ d. None of these
- ☐ e. Volts per Volt

The correct answer is: Amps per Volt

**Question 3**

Not answered

Mark 0.0 out of 2.0

If an amplifier needs a high input resistance and a high output resistance, then it is a current amplifier.

Select one:


- ☐ True
- ☐ False

The correct answer is 'False'.

**Question 4**

Not answered

Mark 0.0 out of 2.0

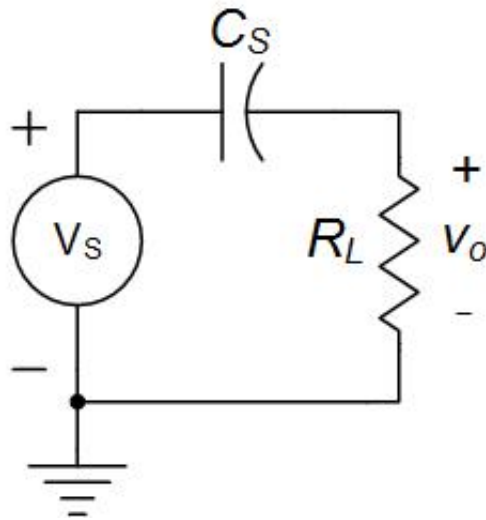

The circuit shown has a :

Select one:


- ☐ a. High pass response
- ☐ b. Low pass response
- ☐ c. Impossible to determine
- ☐ d. None of these
- ☐ e. Bandpass response

The correct answer is: High pass response

**Question 5**

Not answered

Mark 0.0 out of 2.0

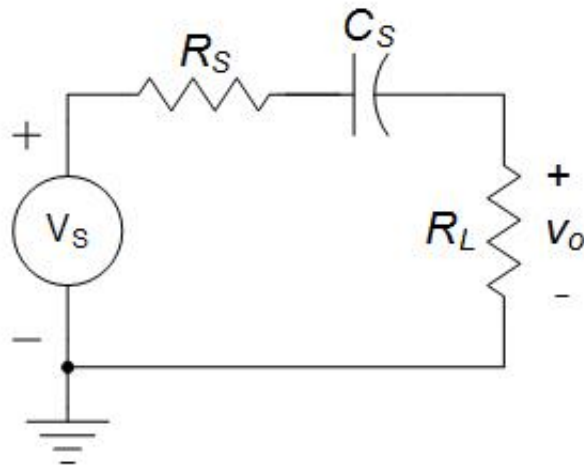

For the filter circuit shown, what is the pole frequency in MHz for the transfer function  $V_o/V_s$  ? Use  $R_s = 3.4\text{k}\Omega$ ,  $R_L = 18.8\text{k}\Omega$  and  $C_s = 5.4\text{pF}$ .

Answer:  ✗

The correct answer is: 1.33



**Started on** Tuesday, 12 September 2017, 12:08 PM

**State** Finished

**Completed on** Tuesday, 12 September 2017, 12:35 PM


**Time taken** 27 mins 1 sec

**Grade** 4.0 out of 10.0 (40%)

**Question 1**

Not answered

Mark 0.0 out of 2.0

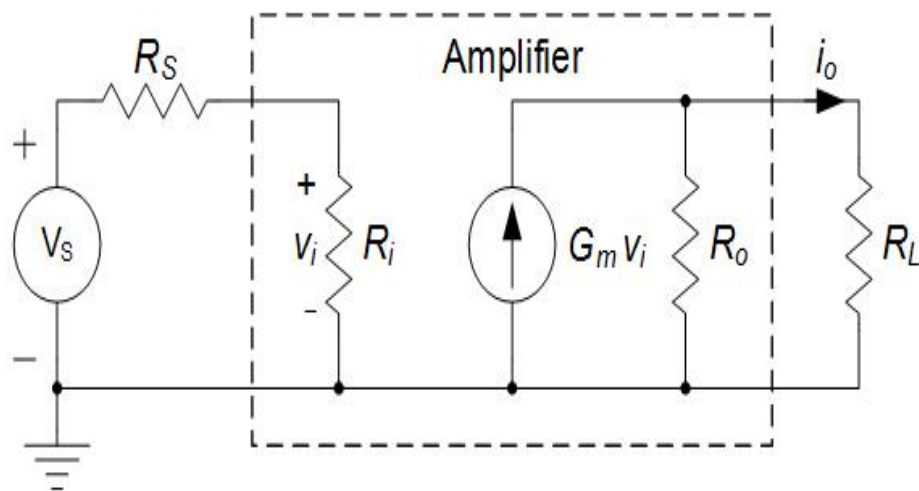

For the amplifier shown, what is the smallest output resistance in  $k\Omega$  that can be used and still get at least 57.4 percent of the amplifier's short circuit output current =  $G_m v_i$  to flow in  $R_L$ ? Use  $R_L = 91.6k\Omega$ .


Answer:  ✖

The correct answer is: 123.42

**Question 2**

Not answered

Mark 0.0 out of 2.0

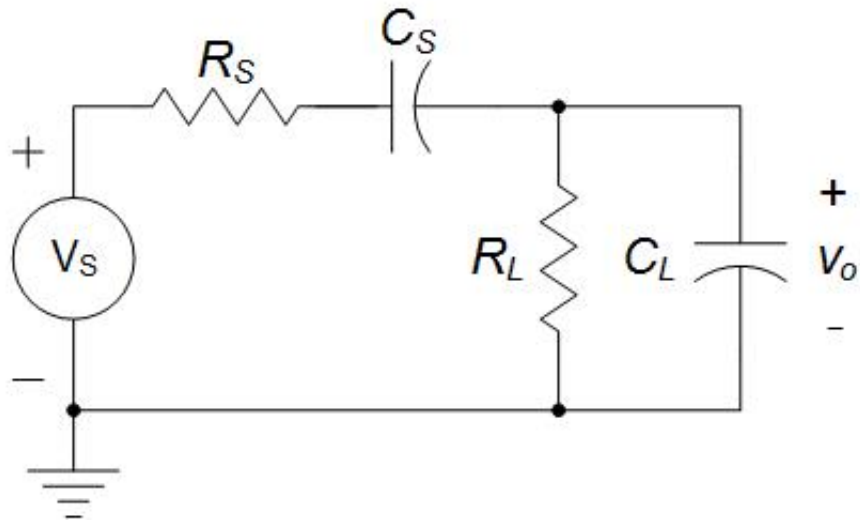

For the filter circuit shown, what is the frequency in MHz of the high frequency pole for the transfer function  $V_o/V_s$  ? Use  $R_s = 4.3\text{k}\Omega$ ,  $R_L = 9.6\text{k}\Omega$ ,  $C_s = 313.8\text{pF}$  and  $C_L = 2.5\text{pF}$ .

Answer:  ✗

The correct answer is: 21.44

**Question 3**

Correct

Mark 2.0 out of 2.0

For an amplifier with a single high frequency pole, which of the following is true?

Select one:

- ☐ a. At this pole frequency, the phase of the gain will be +45 degrees above the midband value
- ☐ b. At this pole frequency, the magnitude of the gain will be +3dB above the midband value
- ☐ c. All of these
- ☒ d. Above this pole frequency, the phase of the gain will roll off at -45 degrees/decade as frequency increases ✓
- ☐ e. Above this pole frequency, the magnitude of the gain will increase at +20dB/decade as frequency increases

The correct answer is: Above this pole frequency, the phase of the gain will roll off at -45 degrees/decade as frequency increases


**Correct**

Marks for this submission: 2.0/2.0.

**Question 4**

Correct

Mark 2.0 out of 2.0

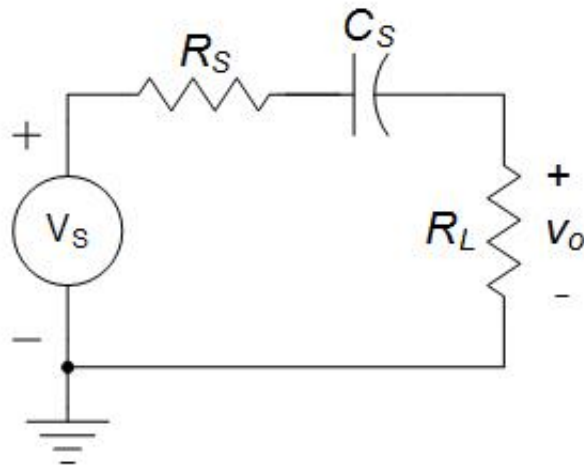

The circuit shown has a :

Select one:

- ☐ a. Bandpass response
- ☒ b. High pass response ✓
- ☐ c. None of these
- ☐ d. Low pass response
- ☐ e. Impossible to determine

The correct answer is: High pass response

**Correct**

Marks for this submission: 2.0/2.0.

**Question 5**

Correct

Mark 0.0 out of 2.0

The model for a transresistance amplifier uses a Thevenin's equivalent circuit at its output.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **0.0/2.0**.

**Started on** Thursday, 14 September 2017, 4:22 PM

**State** Finished

**Completed on** Thursday, 14 September 2017, 4:42 PM


**Time taken** 19 mins 49 secs

**Grade** 6.0 out of 10.0 (60%)

**Question 1**

Not answered

Mark 0.0 out of 2.0

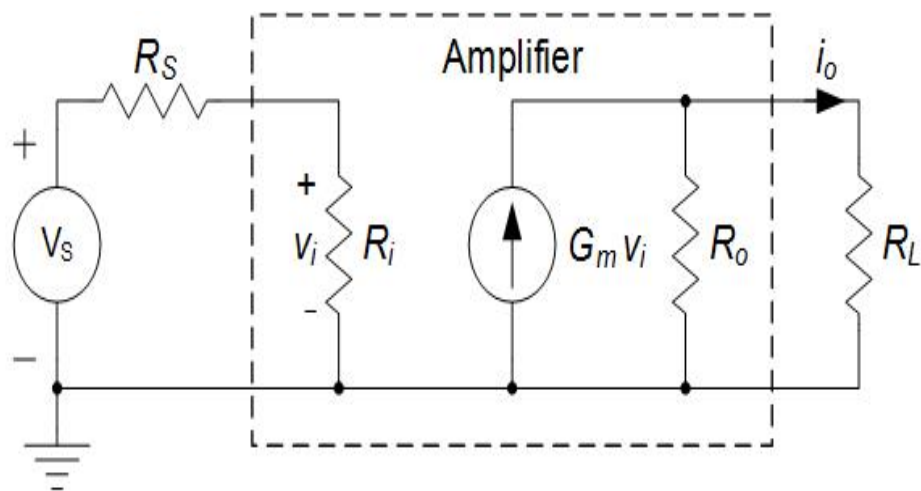

For the amplifier shown, what is the smallest output resistance in  $k\Omega$  that can be used without losing more than 37.4 percent of the amplifier's short circuit output current =  $G_m V_i$  in  $R_o$ ? Use  $R_L = 62.7k\Omega$ .


Answer:  ✖

The correct answer is: 104.95

**Question 2**

Incorrect

Mark 0.0 out of 2.0

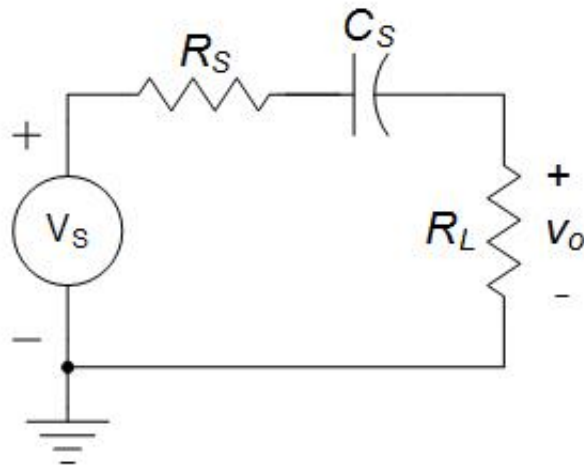

For the filter circuit shown, what is the pole frequency in MHz for the transfer function  $V_o/V_s$  ? Use  $R_s = 4.8\text{k}\Omega$ ,  $R_L = 18.2\text{k}\Omega$  and  $C_s = 4.4\text{pF}$ .

Answer:  ❌

The correct answer is: 1.57

**Incorrect**

Marks for this submission: 0.0/2.0.

**Question 3**

Correct

Mark 2.0 out of 2.0

Which of the following is true for a DC coupled amplifier with a single high frequency pole?

Select one:

- ☐ a. At this pole frequency, the magnitude of the gain will be +3dB above the midband value
- ☐ b. At this pole frequency, the phase of the gain will be +45 degrees above the midband value
- ☒ c. Below this pole frequency, the magnitude of the gain will be approximately constant ✓
- ☐ d. Below this pole frequency, the magnitude of the gain will roll off at -20dB/decade as frequency decreases
- ☐ e. None of these

The correct answer is: Below this pole frequency, the magnitude of the gain will be approximately constant


**Correct**

Marks for this submission: 2.0/2.0.

**Question 4**

Correct

Mark 2.0 out of 2.0

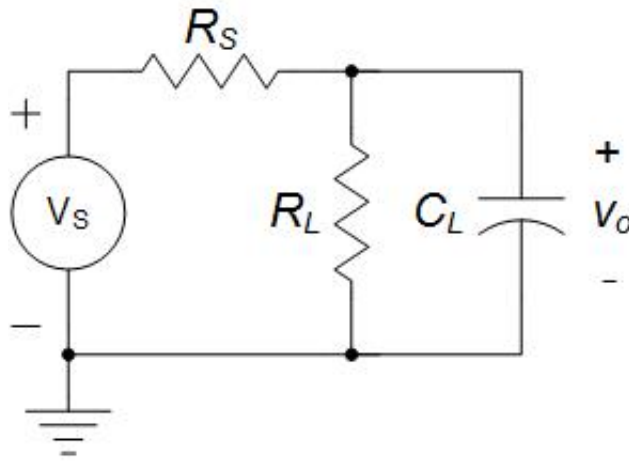

The circuit shown has a :

Select one:

- ☐ a. High pass response
- ☐ b. None of these
- ☐ c. Impossible to determine
- ☒ d. Low pass response ✓
- ☐ e. Bandpass response

The correct answer is: Low pass response

**Correct**

Marks for this submission: 2.0/2.0.

**Question 5**

Correct

Mark 2.0 out of 2.0

The model for a voltage amplifier uses a Norton's equivalent circuit at it's output.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

**Correct**

Marks for this submission: 2.0/2.0.



Home ► My courses ► **EEE 108\_f17** ► Chapter 1 - Signals and Amplifiers ►  
Quiz 1b - Signals and Amplifiers

---

**Started on** Tuesday, 12 September 2017, 12:36 PM

---

**State** Finished

---

**Completed on** Tuesday, 12 September 2017, 1:01 PM

---

**Time taken** 25 mins

---

**Grade** 5.0 out of 10.0 (50%)

**Question 1**

Not answered

Mark 0.0 out of 2.0

What is the power efficiency in percent for an amplifier which delivers a sinusoidal output voltage of 1.6 V<sub>peak</sub> to a 1.4kΩ load while drawing a current of 3.3mA from two power supplies of V<sub>CC</sub> = +5V and V<sub>EE</sub> = -0V ? Neglect any power drawn from the input signal source.

Answer:




The correct answer is: 5.54

**Question 2**

Incorrect

Mark 0.0 out of 2.0

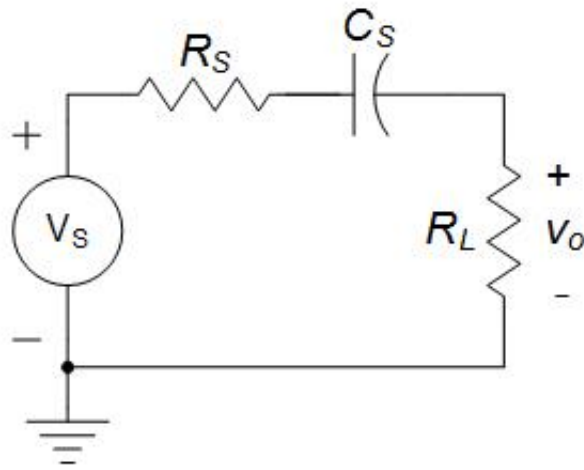

For the filter circuit shown, what is the phase in degrees of the transfer function  $V_o/V_s$  at a frequency of 5.4MHz? Use  $R_s = 4.0\text{k}\Omega$ ,  $R_L = 16.6\text{k}\Omega$  and  $C_s = 6.5\text{pF}$ .

Answer:  ❌

The correct answer is: 12.414

**Incorrect**

Marks for this submission: 0.0/2.0.

**Question 3**

Correct

Mark 1.0 out of 2.0

In order to minimize signal loss, a voltage amplifier needs :

Select one:

- ☐ a. A low input resistance and a low output resistance
- ☒ b. A high input resistance and a low output resistance ✓
- ☐ c. A high input resistance and a high output resistance
- ☐ d. None of these
- ☐ e. A low input resistance and a high output resistance

The correct answer is: A high input resistance and a low output resistance


**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **1.0/2.0**.

**Question 4**

Correct

Mark 2.0 out of 2.0

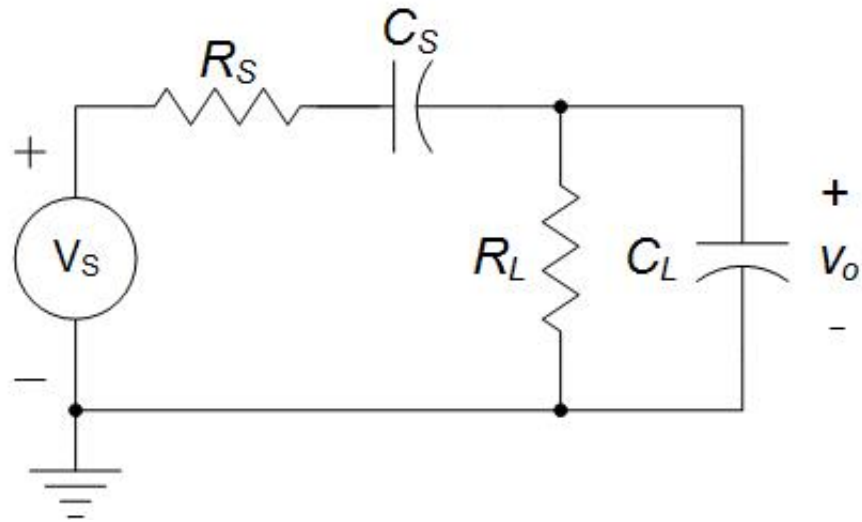

The circuit shown has a :

Select one:

- ☐ a. Impossible to determine
- ☐ b. Low pass response
- ☐ c. None of these
- ☐ d. High pass response
- ☒ e. Bandpass response ✓

The correct answer is: Bandpass response

**Correct**

Marks for this submission: 2.0/2.0.

**Question 5**

Correct

Mark 2.0 out of 2.0

The gain for a current amplifier has units of A/V.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

**Correct**

Marks for this submission: 2.0/2.0.

**Started on** Tuesday, 12 September 2017, 1:02 PM

**State** Finished

**Completed on** Thursday, 14 September 2017, 12:22 PM


**Time taken** 1 day 23 hours

**Grade** 3.0 out of 10.0 (30%)

**Question 1**

Not answered

Mark 0.0 out of 2.0

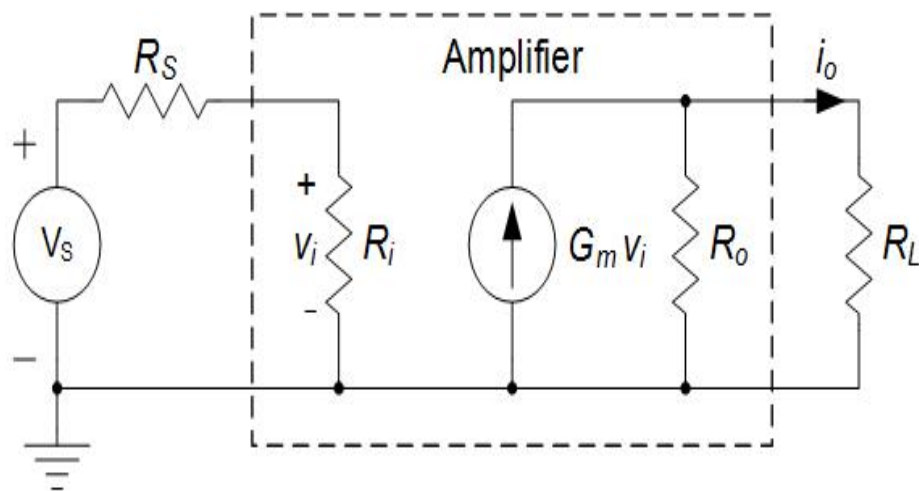

For the amplifier shown, what is the smallest input resistance in  $k\Omega$  that can be used without losing more than 11.8 percent of the source voltage across the source resistance? Use  $R_s = 19.9k\Omega$ .


Answer:  ✖

The correct answer is: 148.74

**Question 2**

Incorrect

Mark 0.0 out of 2.0

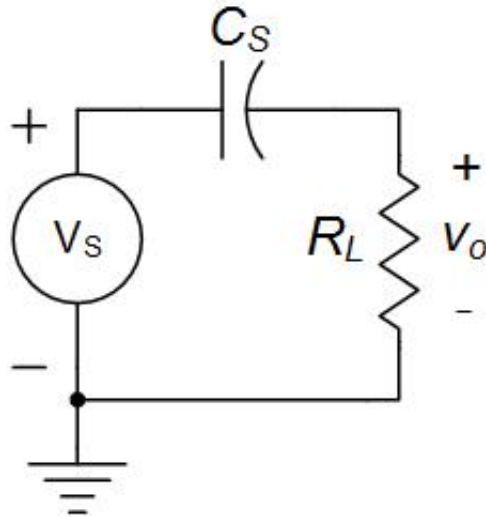

For the filter circuit shown, what is the magnitude of the transfer function  $V_o/V_s$  at a frequency of 7.6MHz? Use  $R_L = 8.1\text{k}\Omega$  and  $C_S = 3.1\text{pF}$ .

Answer: 1 ✖

The correct answer is: 0.768

**Incorrect**

Marks for this submission: 0.0/2.0.

**Question 3**

Correct

Mark 1.0 out of 2.0

If an amplifier needs a Thevenin's equivalent circuit to model its output, then it is :

Select one:

- ☐ a. None of these
- ☐ b. Either a current amplifier or a transresistance amplifier
- ☐ c. Either a current amplifier or a transconductance amplifier
- ☐ d. Either a voltage amplifier or a transconductance amplifier
- ☒ e. Either a voltage amplifier or a transresistance amplifier ✔

The correct answer is: Either a voltage amplifier or a transresistance amplifier


**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **1.0/2.0**.

**Question 4**

Correct

Mark 2.0 out of 2.0

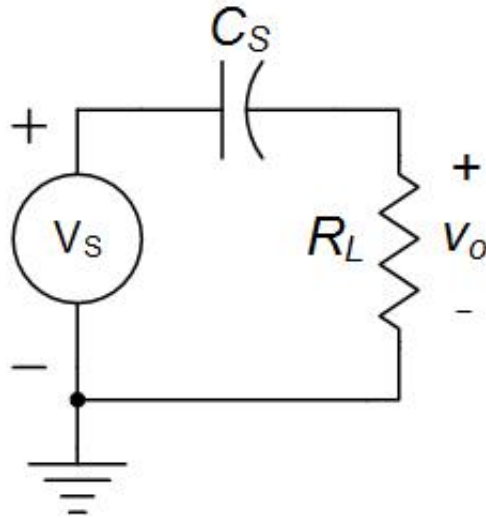

The circuit shown has a :

Select one:

- ☒ a. High pass response ✓
- ☐ b. Impossible to determine
- ☐ c. None of these
- ☐ d. Bandpass response
- ☐ e. Low pass response

The correct answer is: High pass response

**Correct**

Marks for this submission: 2.0/2.0.

**Question 5**

Correct

Mark 0.0 out of 2.0

For an AC coupled amplifier with a single high frequency pole, the phase of the gain approaches -90 degrees at frequencies well above the upper corner frequency.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **0.0/2.0**.

Home ► My courses ► **EEE 108\_f17** ► Practice Quizzes and Exams ►  
Practice Quiz 1b - Signals and Amplifiers

---

**Started on** Thursday, 14 September 2017, 12:47 PM

---

**State** Finished

---

**Completed on** Thursday, 14 September 2017, 12:48 PM

---

**Time taken** 57 secs

---

**Grade** 5.0 out of 10.0 (50%)

**Question 1**

Not answered

Mark 0.0 out of 2.0

What is the power dissipation in milliwatts for an amplifier which delivers a sinusoidal output voltage of 1.6 V<sub>peak</sub> to a 1.8k $\Omega$  load while drawing a current of 8.1mA from two power supplies of VCC = +5V and VEE = -5V ? Neglect any power drawn from the input signal source.

Answer:  

The correct answer is: 80.29

**Question 2**

Correct

Mark 1.0 out of 2.0

For an amplifier with a single low frequency pole, which of the following is true?

Select one:

- ☐ a. All of these
- ☐ b. At this pole frequency, the magnitude of the gain will be +3dB above the midband value
- ☐ c. At this pole frequency, the phase of the gain will be -45 degrees below the midband value
- ☒ d. Below this pole frequency, the magnitude of the gain will increase at +20dB/decade as frequency increases ✓
- ☐ e. Below this pole frequency, the phase of the gain will increase at +45 degrees/decade as frequency increases

The correct answer is: Below this pole frequency, the magnitude of the gain will increase at +20dB/decade as frequency increases

**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **1.0/2.0**.

**Question 3**

Correct

Mark 2.0 out of 2.0

For an AC coupled amplifier with a single high frequency pole, the phase of the gain approaches -90 degrees at frequencies well above the upper corner frequency.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.

**Correct**


Marks for this submission: 2.0/2.0.



**Question 4**

Correct

Mark 2.0 out of 2.0

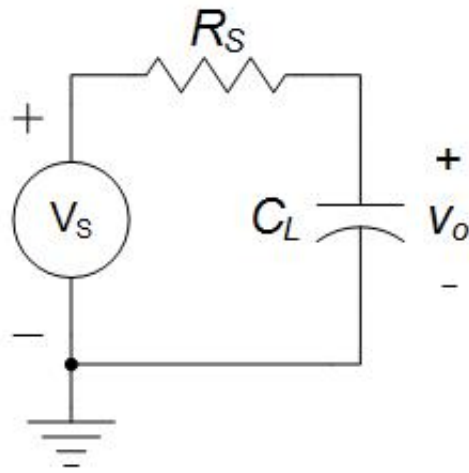

The circuit shown has a :

Select one:

- ☒ a. Low pass response ✓
- ☐ b. Bandpass response
- ☐ c. High pass response
- ☐ d. Impossible to determine
- ☐ e. None of these

The correct answer is: Low pass response


**Correct**

Marks for this submission: 2.0/2.0.

**Question 5**

Incorrect

Mark 0.0 out of 2.0

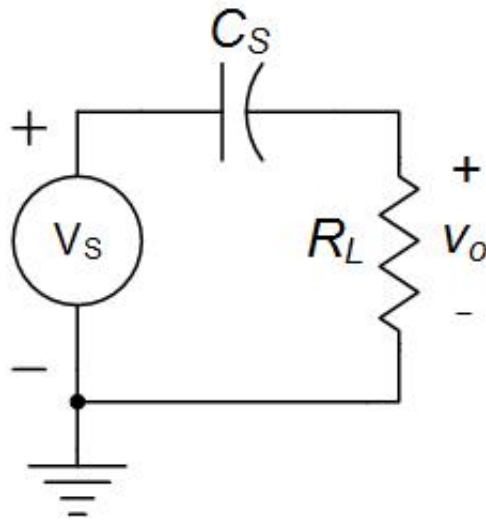

For the filter circuit shown, what is the magnitude of the transfer function  $V_o/V_s$  at a frequency of 8.0MHz? Use  $R_L = 5.9\text{k}\Omega$  and  $C_S = 6.7\text{pF}$ .

Answer: 1 ✖

The correct answer is: 0.893

**Incorrect**

Marks for this submission: 0.0/2.0.

**Started on** Thursday, 14 September 2017, 12:24 PM

**State** Finished

**Completed on** Thursday, 14 September 2017, 1:04 PM


**Time taken** 39 mins 49 secs

**Grade** 3.0 out of 10.0 (30%)

**Question 1**

Incorrect

Mark 0.0 out of 2.0

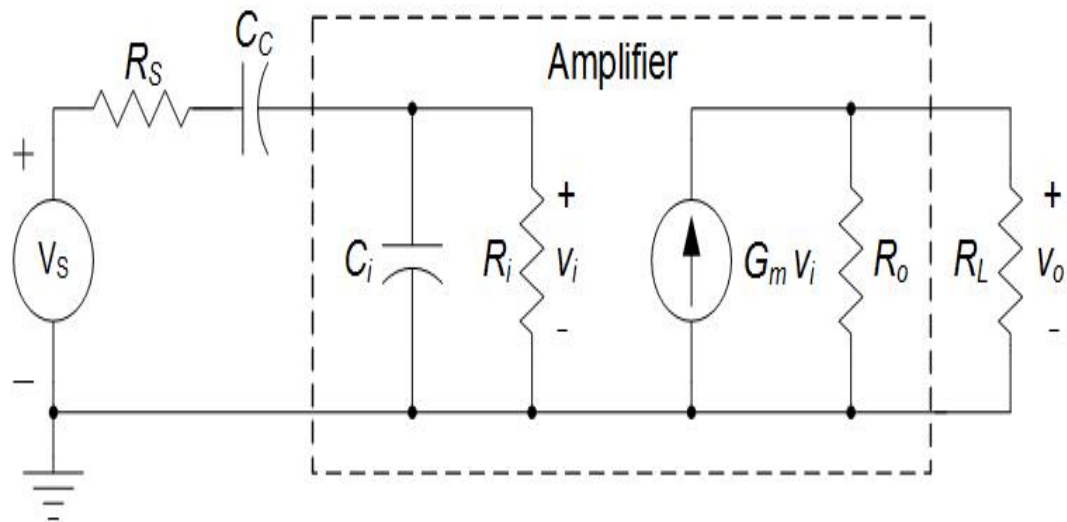

What is the value of the unity gain frequency in MHz for the amplifier shown? Use  $R_S = 1.8\text{k}\Omega$ ,  $R_i = 9.5\text{k}\Omega$ ,  $R_o = 34.5\text{k}\Omega$ ,  $R_L = 23.1\text{k}\Omega$ ,  $C_C = 338.1\text{pF}$ ,  $C_i = 5.5\text{pF}$  and  $G_m = 6.5\text{ mA/V}$ .

Answer: 737



The correct answer is: 1445.80


**Incorrect**

Marks for this submission: 0.0/2.0.

**Question 2**

Not answered

Mark 0.0 out of 2.0

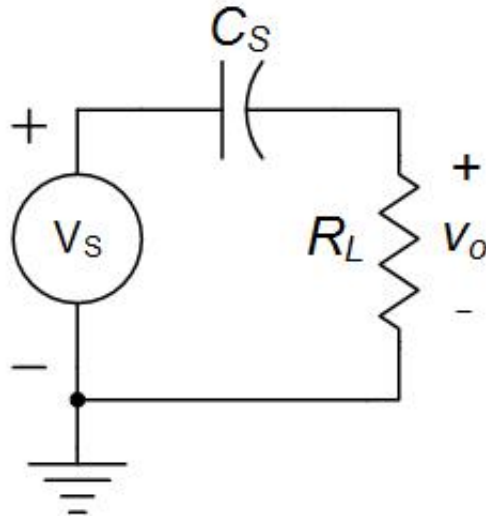

For the filter circuit shown, what is the phase in degrees of the transfer function  $V_O/V_S$  at a frequency of 17.9MHz? Use  $R_L = 1.3\text{k}\Omega$  and  $C_S = 8.8\text{pF}$ .

Answer:  ✖

The correct answer is: 37.85

**Question 3**

Correct

Mark 2.0 out of 2.0

Which of the following is true for an AC coupled amplifier with a single high frequency pole?

Select one:

- ☐ a. Below the upper corner frequency, the phase of the gain will decrease at -45 degrees/decade for one decade as frequency decreases
- ☐ b. Above the lower corner frequency, the magnitude of the gain will roll off at -20dB/decade as frequency increases
- ☐ c. Below the upper corner frequency, the magnitude of the gain will roll off at -20dB/decade as frequency decreases
- ☐ d. Above the lower corner frequency, the phase of the gain will increase at +45 degrees/decade for one decade as frequency increases
- ☒ e. None of these ✔

The correct answer is: None of these


**Correct**

Marks for this submission: 2.0/2.0.

**Question 4**

Correct

Mark 1.0 out of 2.0

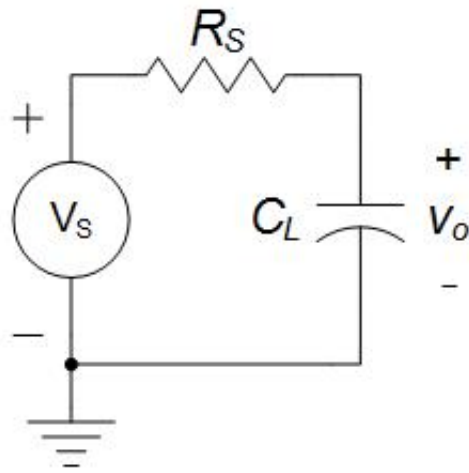

The circuit shown has a :

Select one:

- ☐ a. None of these
- ☒ b. Low pass response ✓
- ☐ c. Bandpass response
- ☐ d. High pass response
- ☐ e. Impossible to determine

The correct answer is: Low pass response

**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **1.0/2.0**.

**Question 5**

Correct

Mark 0.0 out of 2.0

A transconductance amplifier needs a high input resistance and a low output resistance.

Select one:

- ☐ True
- ☒ False ✓

The correct answer is 'False'.

**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **0.0/2.0**.

**Started on** Thursday, 14 September 2017, 3:19 PM

**State** Finished

**Completed on** Thursday, 14 September 2017, 3:21 PM


**Time taken** 2 mins 41 secs

**Grade** 1.0 out of 10.0 (10%)

**Question 1**

Incorrect

Mark 0.0 out of 2.0

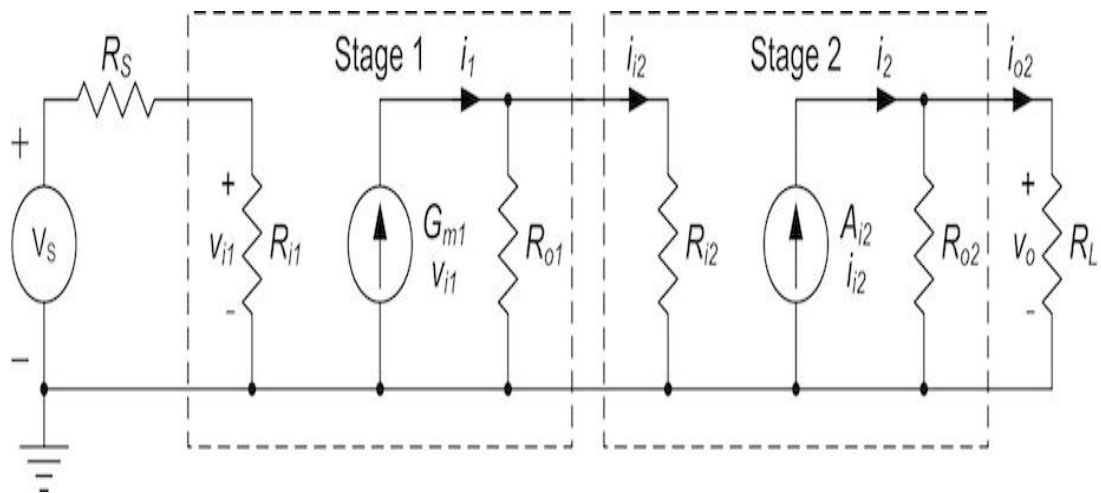

What is the value of the voltage gain in dB for the 2-stage amplifier circuit shown? Use  $R_S = 18.2\text{k}\Omega$ ,  $R_{i1} = 42.6\text{k}\Omega$ ,  $R_{o1} = 39.6\text{k}\Omega$ ,  $G_{m1} = 5.6\text{ mA/V}$ ,  $R_{i2} = 8.2\text{k}\Omega$ ,  $R_{o2} = 7.0\text{k}\Omega$ ,  $A_{i2} = 51.5\text{ A/A}$  and  $R_L = 17.5\text{k}\Omega$ .

Answer: 2



The correct answer is: 58.45

**Incorrect**

Marks for this submission: 0.0/2.0.

**Question 2**

Correct

Mark 0.0 out of 2.0

In order to minimize signal loss, a transresistance amplifier needs :

Select one:

- ☐ a. A high input resistance and a low output resistance
- ☐ b. None of these
- ☐ c. A low input resistance and a high output resistance
- ☒ d. A low input resistance and a low output resistance ✓
- ☐ e. A high input resistance and a high output resistance

The correct answer is: A low input resistance and a low output resistance

**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **0.0/2.0**.

**Question 3**

Correct

Mark 0.0 out of 2.0

For an amplifier with a single-time constant high pass response, the magnitude of the gain decreases at -6dB/octave as the frequency is decreased below the corner frequency.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.


**Correct**

Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **0.0/2.0**.

**Question 4**

Correct

Mark 1.0 out of 2.0

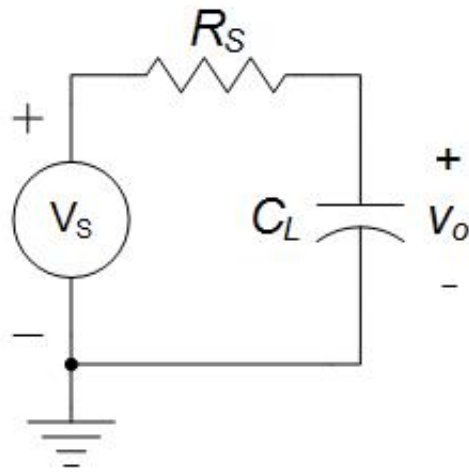

The circuit shown has a :

Select one:

- ☐ a. Impossible to determine
- ☐ b. Bandpass response
- ☐ c. High pass response
- ☐ d. None of these
- ☒ e. Low pass response ✓

The correct answer is: Low pass response

**Correct**


Marks for this submission: 2.0/2.0. Accounting for previous tries, this gives **1.0/2.0**.



**Question 5**

Incorrect

Mark 0.0 out of 2.0

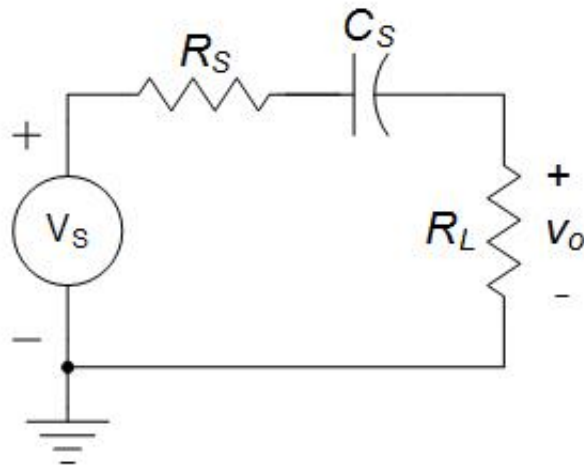

For the filter circuit shown, what is the phase in degrees of the transfer function  $V_o/V_s$  at a frequency of 2.4MHz? Use  $R_s = 5.3\text{k}\Omega$ ,  $R_L = 5.3\text{k}\Omega$  and  $C_s = 4.8\text{pF}$ .

Answer:  ❌

The correct answer is: 52.503

**Incorrect**

Marks for this submission: 0.0/2.0.