

**Started on** Thursday, 8 September 2016, 11:58 AM

**State** Finished

**Completed on** Thursday, 8 September 2016, 12:26 PM


**Time taken** 28 mins 20 secs

**Grade** 100.00 out of 100.00

**Question 1**

Correct

Mark 10.00 out of 10.00

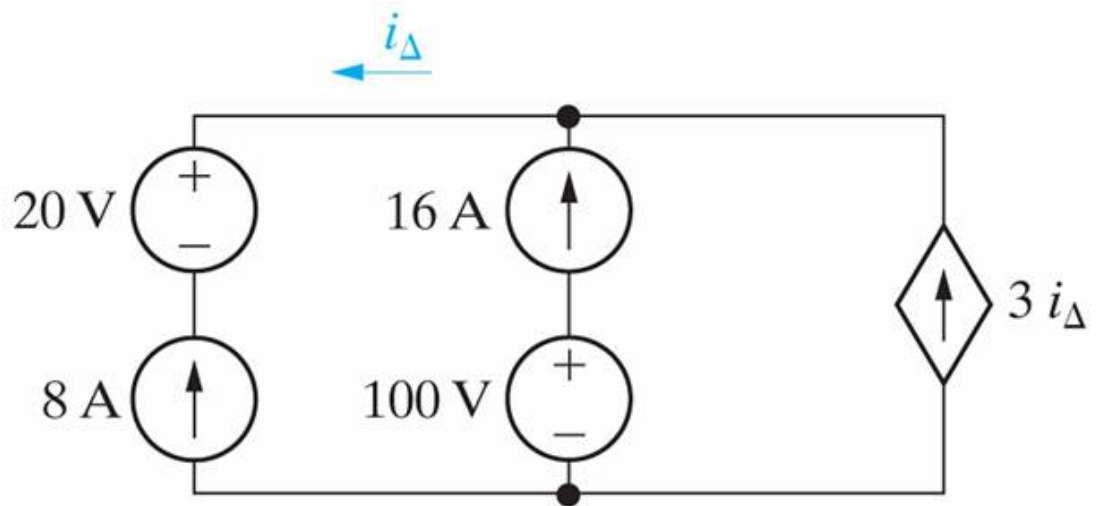

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P2.09a\_9ed

What is the current  $i_{\Delta}$  (i delta)?  $i_{\Delta} = ??$  A

Answer:



**Numeric Answer**

$i_D = -8$  A

The correct answer is: -8


**Correct**

Marks for this submission: 10.00/10.00.

**Question 2**

Correct

Mark 10.00 out of 10.00

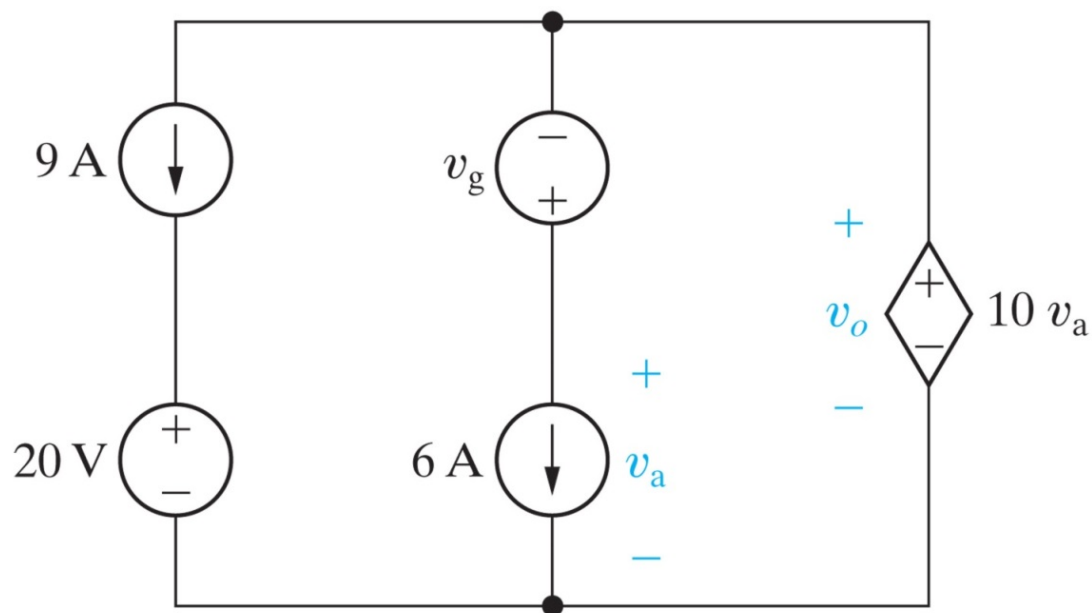

P2.10\_10ed

Given that  $v_o = 5$  Volts.Find the total power developed in the circuit.  $P_{\text{delivered}} = ??$  W

“+” = absorbed and “-” = delivered

Answer: 

Numeric Answer

 $P_{\text{del}} = -210$  W delivered

The correct answer is: -210

**Correct**

Marks for this submission: 10.00/10.00.

**Question 3**

Correct

Mark 10.00 out of 10.00

C3

An independent source  influenced by any other current or voltage in the circuit.

An independent source is not influenced by any other source.


**Correct**

Marks for this submission: 10.00/10.00.

**Question 4**

Correct

Mark 10.00 out of 10.00

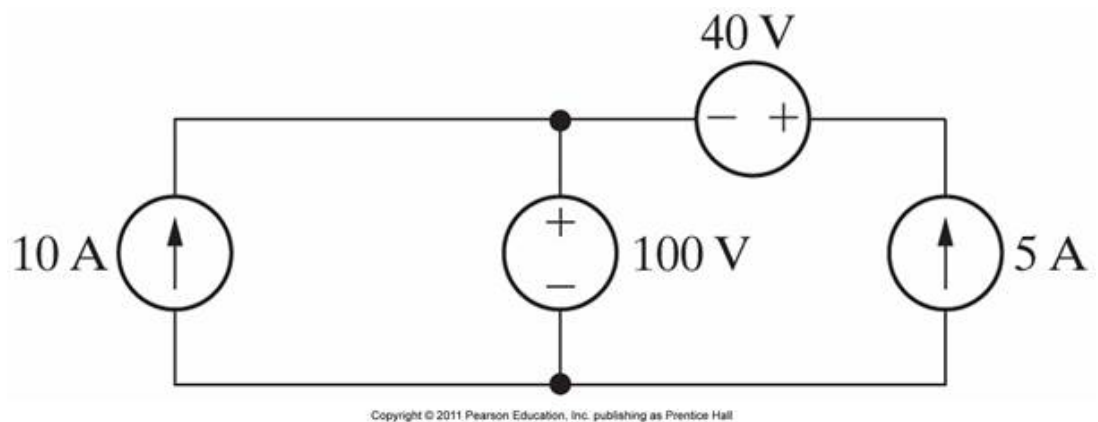

P2.04a\_9ed

What is the current in the 100 V source?

 $I_{100V} =$ Answer: **Numeric Answer** $I_{100V} = 15 \text{ A}$ 


The correct answer is: 15

**Correct**

Marks for this submission: 10.00/10.00.

**Question 5**

Correct

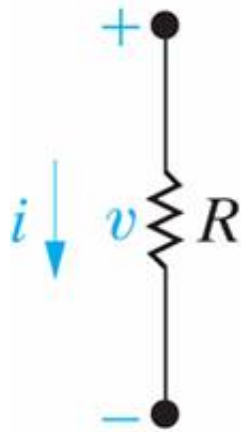Mark 10.00 out of  
10.00

CQ2.03

Given:  $v = -43$  Volts       $R = 19 \, \Omega$  (Ohm)Find the unknown current  $i$ .     $i = ??$  AmpsAnswer: 

Calculated question.

The correct answer is: -2.2632

**Correct**

Marks for this submission: 10.00/10.00.

**Question 6**

Correct

Mark 10.00 out of  
10.00

C4

A resistor is a passive circuit element. Resistors can only (absorb/deliver) power.

Answer: Resistor can only absorb power.


The correct answer is: absorb

**Correct**

Marks for this submission: 10.00/10.00.

**Question 7**

Correct

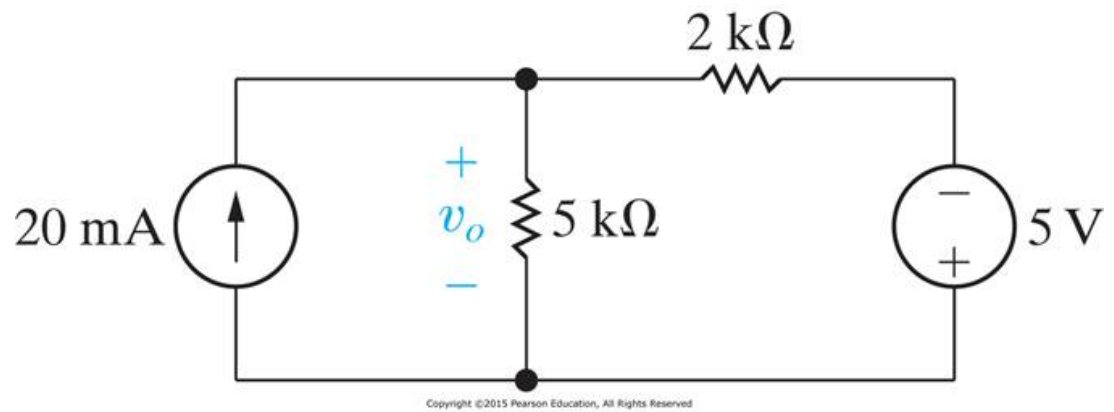Mark 10.00 out of  
10.00

P2.17\_10ed

Find  $v_o$  using Kirchhoff's Laws and Ohm's Law.  $v_o = ??$  VAnswer: **Numeric Answer**

$$v_o = 25 \text{ V}$$


The correct answer is: 25

**Correct**

Marks for this submission: 10.00/10.00.

**Question 8**

Correct

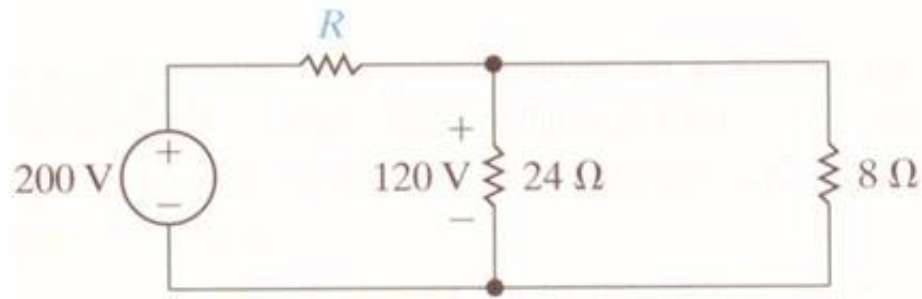Mark 10.00 out of  
10.00

AP2.06\_9ed

Use Ohm's Law and Kirchhoff's laws to find the value of  $R$  in this circuit.  $R =$   
??  $\Omega$  (Ohm)

Answer: 4

**Numeric Answer** $R = 4.0\ \Omega$  (Ohm)


The correct answer is: 4

**Correct**

Marks for this submission: 10.00/10.00.

**Question 9**

Correct

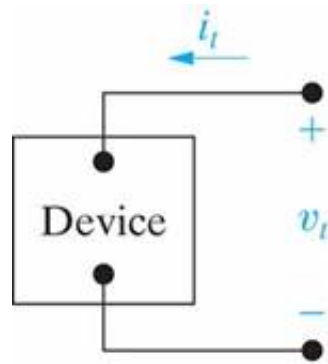Mark 10.00 out of  
10.00

(a)

$v_t$ (V)	$i_t$ (A)
100	0
120	4
140	8
160	12
180	16

(b)

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P2.14\_9ed

The voltage and current were measured at the terminals of the device as shown in the table (b).

What is the value of the current source and resistor known to make up the device?

Current Source  $i =$   ✓ A


Resistor  $R =$   ✓  $\Omega$  (Ohm)

**Numeric Answer**Current Source  $i = 20$  AResistor  $R = 5$   $\Omega$  (Ohm)**Correct**

Marks for this submission: 10.00/10.00.

**Question 10**

Correct

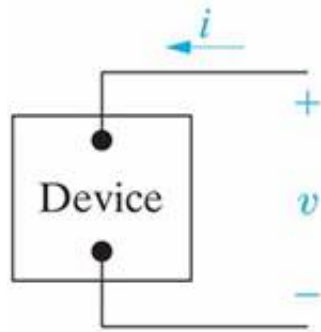Mark 10.00 out of  
10.00

(a)

$i$ (mA)	$v$ (V)
-4	-108
-2	-54
2	54
4	108
6	162

(b)

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall.

P2.11\_9ed

The terminal voltage and terminal current were measured on the device in Figure (a) and recorded in table (b).

Use the values in the table to construct a circuit model for the device consisting of a single resistor  $R = ?? \text{ k}\Omega$  (kilo Ohm).

Answer: 27

**Numeric Answer** $R = 27 \text{ kW}$  (kilo Ohm)

The correct answer is: 27

**Correct**

Marks for this submission: 10.00/10.00.