

**Started on** Monday, 12 September 2016, 12:17 AM

**State** Finished

**Completed on** Monday, 12 September 2016, 1:48 AM


**Time taken** 1 hour 30 mins

**Grade** 100.00 out of 100.00

**Question 1**

Correct

Mark 10.00 out of 10.00

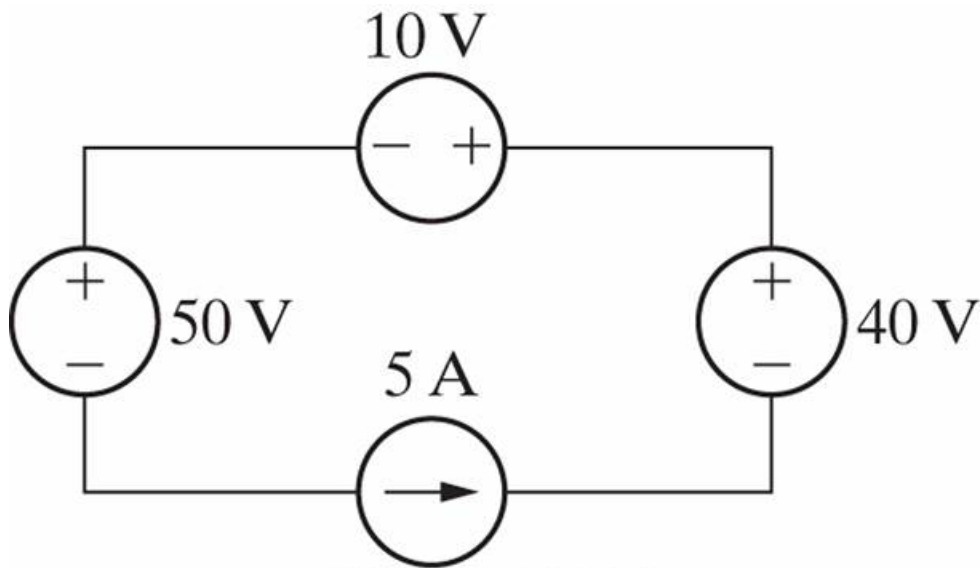

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P2.01b\_9ed

What is the total power developed by the following circuit?

Answer:



**Numeric Answer**

Power = -300 W

The correct answer is: -300

**Correct**

Marks for this submission: 10.00/10.00.

**Question 2**

Correct

Mark 10.00 out of 10.00

C1

An ideal current source is ....

Select one:

- ☒ A. defined as able to maintain a prescribed current regardless of the voltage across the device. ✓
- ☐ B. defined as able to maintain a prescribed voltage across the device regardless of the current through the device.
- ☐ C. only defined for independent current sources.
- ☐ D. only an abstraction and not useful in circuit analysis.

Your answer is correct.

An ideal current source is defined as able to maintain a prescribed current regardless of the voltage across the device.

The correct answer is: defined as able to maintain a prescribed current regardless of the voltage across the device.


**Correct**

Marks for this submission: 10.00/10.00.

**Question 3**

Correct

Mark 10.00 out of 10.00

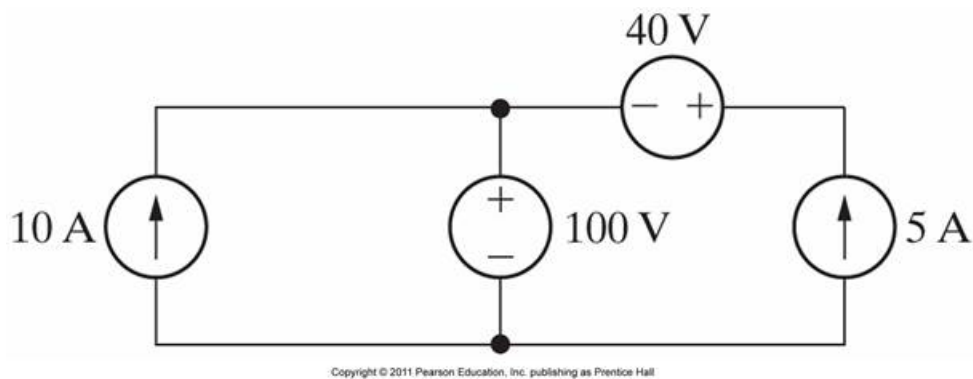

P2.04b\_9ed

What is the power in the 100 V source?

 $P_{100V} =$ 

Answer: 1500 ✓

**Numeric Answer** $P_{100V} = 1,500 \text{ W}$ 

The correct answer is: 1500

**Correct**

Marks for this submission: 10.00/10.00.

**Question 4**

Correct

Mark 10.00 out of  
10.00

C2

An ideal voltage source is ....

Select one:

- ☒ A. defined as able to maintain the prescribed voltage regardless of the current in the device. ✓
- ☐ B. defined as able to maintain the prescribed current regardless of the voltage in the device.
- ☐ C. only defined for independent current sources.
- ☐ D. only an abstraction and not useful in circuit analysis.

Your answer is correct.

An ideal voltage source is defined as able to maintain the prescribed voltage regardless of the current in the device.


The correct answer is: defined as able to maintain the prescribed voltage regardless of the current in the device.

**Correct**

Marks for this submission: 10.00/10.00.

**Question 5**

Correct

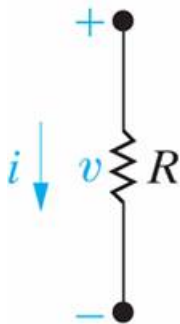Mark 10.00 out of  
10.00

CQ2.04

Given:  $v = 82$  Volts     $i = 50$  AmpsWhat is the conductance  $G$ ?     $G = ??$  S (siemens)Answer: 

Calculated question.

The correct answer is: 0.6098

**Correct**

Marks for this submission: 10.00/10.00.

**Question 6**

Correct

Mark 10.00 out of 10.00

C4

A resistor is a passive circuit element. Resistors can only (absorb/deliver) power.

Answer: Resistor can only absorb power.

The correct answer is: absorb


**Correct**

Marks for this submission: 10.00/10.00.

**Question 7**

Correct

Mark 10.00 out of 10.00

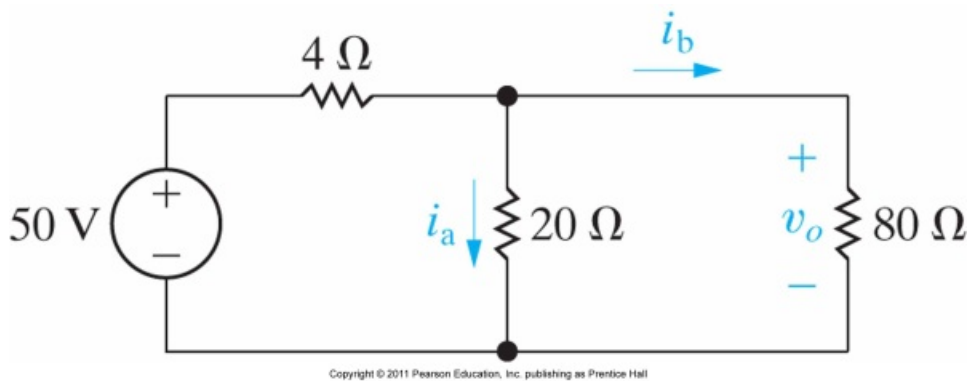

P2.19\_9ed

a) Find the value of  $i_a$ .  $i_a =$   Ab) Find the value of  $v_o$ .  $v_o =$   V

c) Find the power dissipated in each resistor.

 $P_{4\Omega} =$   W    $P_{20\Omega} =$   W    $P_{80\Omega} =$   W

d) Find the power delivered by the 50V source.


 $P_{50V} =$   W   “-” = Delivering   “+” = Absorbing**Numeric Answer** $i_a = 2$  A $v_o = 40$  V $P_{4\Omega} = 25$  W    $P_{20\Omega} = 80$  W    $P_{80\Omega} = 20$  W $P_{50V} = -125$  W**Correct**

Marks for this submission: 10.00/10.00.

**Question 8**

Correct

Mark 10.00 out of 10.00

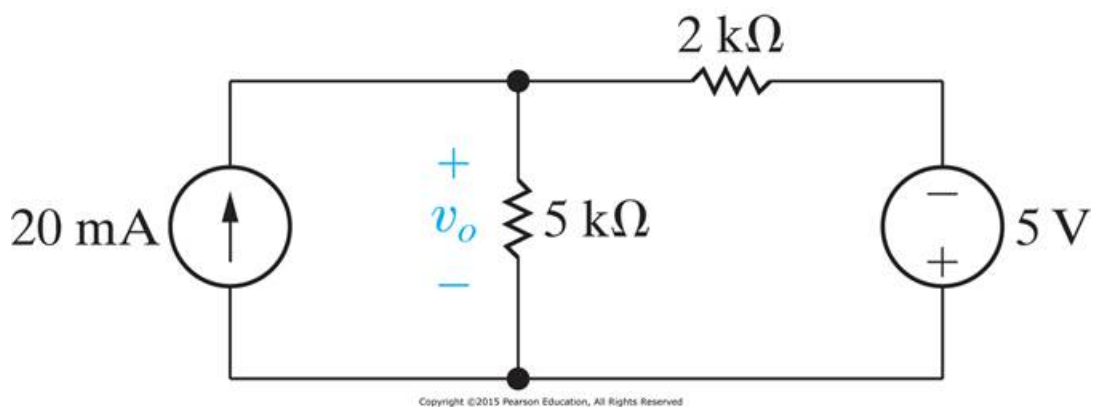

Copyright ©2015 Pearson Education, All Rights Reserved

P2.17\_10ed

Find  $v_o$  using Kirchhoff's Laws and Ohm's Law.  $v_o = ??$  V

Answer: 25

**Numeric Answer** $v_o = 25$  V

The correct answer is: 25


**Correct**

Marks for this submission: 10.00/10.00.

**Question 9**

Correct

Mark 10.00 out of 10.00

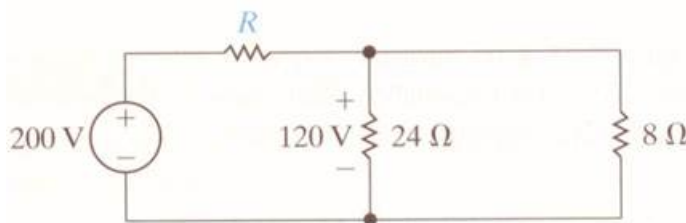

AP2.06\_9ed

Use Ohm's Law and Kirchhoff's laws to find the value of  $R$  in this circuit.  $R = ??$   $\Omega$  (Ohm)

Answer: 4

**Numeric Answer** $R = 4.0$   $\Omega$  (Ohm)


The correct answer is: 4

**Correct**

Marks for this submission: 10.00/10.00.

**Question 10**

Correct

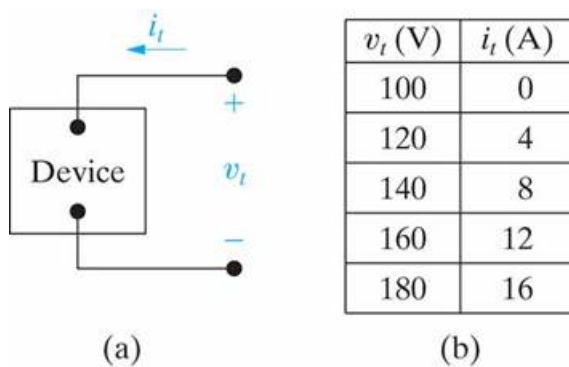Mark 10.00 out of  
10.00

P2.14\_9ed

The voltage and current were measured at the terminals of the device as shown in the table (b).

What is the value of the current source and resistor known to make up the device?

Current Source  $i =$   ✓ A

Resistor  $R =$   ✓  $\Omega$  (Ohm)

**Numeric Answer**

Current Source  $i = 20$  A

Resistor  $R = 5$   $\Omega$  (Ohm)

**Correct**

Marks for this submission: 10.00/10.00.