

CpE 151 and EEE 234 CMOS and VLSI Design

Quiz – 1

75
100

For CpE 151, 5 lowest grade questions will be dropped. For EEE234 2 questions will be dropped.

Metal Oxide Semi-Conductor Field Effect Transistor

1. MOSFET stands for metal oxide semi-conductor field effect transistor X
2. p-type semiconductor has holes (electrons/holes) as majority charge carriers. ✓
3. n-type semiconductor is built by doping intrinsic Silicon with group V (III/V) element. ✓
4. When a voltage of 5V (High) is applied to the Drain of a NMOS transistor, the transistor is:
(a) ON (b) OFF (c) Not enough information ✓
5. When a voltage of 0V (Low) is applied to the Gate of a PMOS transistor, the transistor is:
(a) ON (b) OFF (c) Not enough information ✓
6. Pick one option. A 3-input NAND gate has:
(a) 3 NMOS transistors in the Pull Up Network
(b) 3 PMOS transistors in the Pull Down Network
(c) 3 NMOS transistors in parallel and 3 PMOS transistors in series ✓
(d) 3 NMOS transistors in series and 3 PMOS transistors in parallel
7. If the NMOS and PMOS transistors switch places in an inverter, the resulting circuit is:
(a) Weak Inverter
(b) Strong Inverter
(c) Weak buffer ✓
(d) Strong buffer
8. Which of the following is true about NMOS transistor?
(a) It provides a good '1'
(b) It provides a good '0' ✓
(c) It uses p-well
(d) It uses n-well
9. To properly bias the Source-Bulk and Drain-Bulk diodes, the Bulk (B) terminal of the PMOS transistor should be connected to p-body High-Voltage X
10. Input dependent phase shift is brought about by which of the following transistor non-ideality?
a. Channel-charge injection
(b) Clock-feed through
(c) Non-zero ON-resistance X
d. Negative-bias Temperature Instability (NBTI)

11. Which of the following circuits uses 2-NMOS and 2-PMOS transistors, all in series?

- a. Inverter
- b. 2-input NAND gate
- c. Tri-state inverter
- d. 3-input NOR gate

12. In a transmission gate, when the PMOS is ON, then the NOMS is OFF (ON/OFF). X

13. The condition for NMOS transistor to be ON is $V_{gs} > V_t$. X

14. The condition for NMOS transistor to be in saturation is high drain voltage. X
 $V_{ds} \geq V_{gs} - V_t$

15. In the Figure – 2 shown below, plot the graph for the equivalent ON-resistance of a transmission gate. The On-resistance of NMOS and PMOS as a function of V_{in} .

 


Figure – 2. On-resistance of NMOS, PMOS and transmission gate

16. The mobility of electrons is equal than/to that of holes. (greater, smaller or equal). X

17. The relation between Q (charge), V (voltage) and C (capacitance) is given by $Q = V \cdot C$. ✓