

Home ► My courses ► [EEE117-2017S-Tatro](#) ► Exams and Quizzes ►  
Exam 3 (Final) - Bode Diagram, Chapters 14, 15, 16, and Bode Diagrams

---

<b>Started on</b>	Monday, 15 May 2017, 10:22 AM
-------------------	-------------------------------

---

<b>State</b>	Finished
--------------	----------

---

<b>Completed on</b>	Monday, 15 May 2017, 11:18 AM
---------------------	-------------------------------

---

<b>Time taken</b>	55 mins 35 secs
-------------------	-----------------

---


<b>Grade</b>	<b>91.50</b> out of 100.00
--------------	----------------------------

---

**Question 1**

Correct

Mark 10.00 out of 10.00

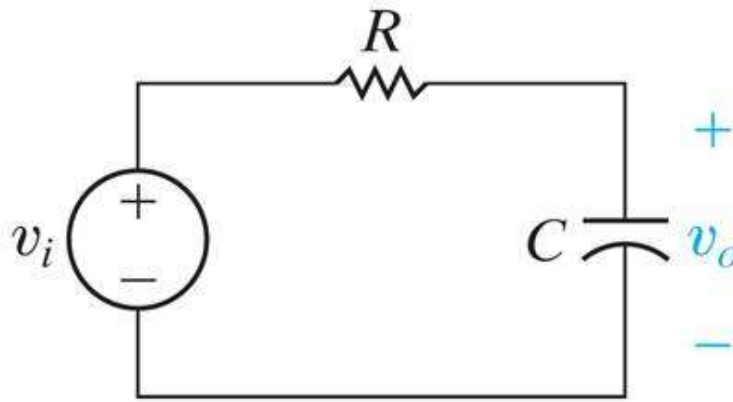

Q1c

Given:  $C = 347 \text{ nF}$  (nano F)     $R = 360 \Omega$  (Ohm)a) Write the parameters of the transfer function  $H(s)$ .

$$H(s) = V_o / V_i = \boxed{8005.5} \checkmark / (s + \boxed{8005.5} \checkmark)$$

b) Calculate the cutoff frequency  $\omega_c$  in rad/sec and  $f_c$  in Hz.

$$\omega_c = \boxed{8005.5} \checkmark \text{ rad/sec} \quad f_c = \boxed{1274.05} \checkmark \text{ Hz}$$

c) State the phase angle of the output voltage when fully in the passband region where  $\omega \ll \omega_c$ .

$$\theta(\text{pass band}) = \boxed{0} \checkmark ^\circ \text{ (Degrees)}$$

d) State the phase angle of the output voltage at the corner frequency  $\omega_c$ .

$$\theta(\omega_c) = \boxed{-45} \checkmark ^\circ \text{ (Degrees)}$$

e) State the phase angle of the output voltage when fully in the stopband region where  $\omega \gg \omega_c$ .

$$\theta(\text{stop band}) = \boxed{-90} \checkmark ^\circ \text{ (Degrees)}$$

f) Identify the filter type of this circuit.

$$\text{Filter Type} = \boxed{\text{Low Pass}} \checkmark$$

**Numeric Answer**

a)  $H(s) = 8,000.5123 / (s + 8,000.5123)$

b)  $\omega_c = 8,000.5123 \text{ rad/sec}$      $f_c = 1,274.0549 \text{ Hz}$

c)  $\theta(\text{pass band}) = 0^\circ$

d)  $\theta(\omega_c) = -45^\circ$

e)  $\theta(\text{stop band}) = -90^\circ$

f) Filter Type = Low Pass


**Correct**

Marks for this submission: 10.00/10.00.

**Question 2**

Correct

Mark 10.00 out of 10.00

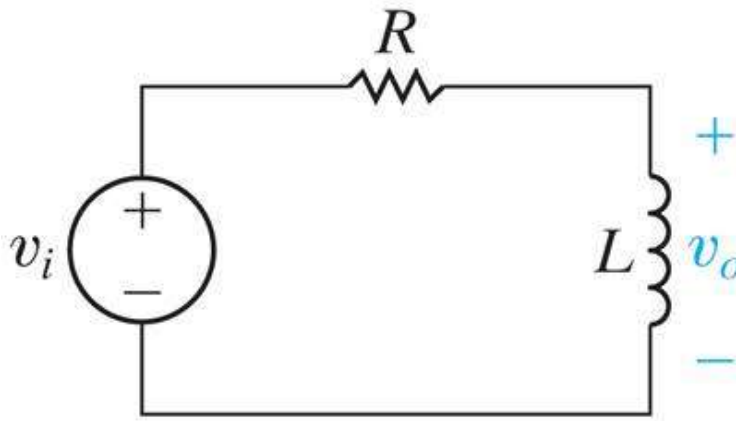

Q2e

Given:  $L = 67 \text{ mH}$  (milli H)       $R = 353 \Omega$  (Ohm)a) Write the parameters of the transfer function  $H(s)$ .

$$H(s) = V_o / V_i = s / (s + 5268) \quad \checkmark$$

b) Calculate the cutoff frequency  $\omega_c$  in rad/sec and  $f_c$  in Hz.

$$\omega_c = 5266 \quad \checkmark \text{ rad/sec} \quad f_c = 838.43 \quad \checkmark \text{ Hz}$$

c) State the phase angle of the output voltage when fully in the passband region where  $\omega \gg \omega_c$ .

$$\theta(\text{pass band}) = 0 \quad \checkmark \text{ }^\circ \text{ (Degrees)}$$

d) State the phase angle of the output voltage at the corner frequency  $\omega = \omega_c$ .

$$\theta(\omega_c) = 45 \quad \checkmark \text{ }^\circ \text{ (Degrees)}$$

e) State the phase angle of the output voltage when fully in the stopband region where  $\omega \ll \omega_c$ .

$$\theta(\text{stop band}) = 90 \quad \checkmark \text{ }^\circ \text{ (Degrees)}$$

f) Identify the filter type of this circuit.

Filter Type = High Pass    ☒**Numeric Answer**

a)  $H(s) = s / (s + 5,268.6567)$

b)  $\omega_c = 5,268.6567 \text{ rad/sec}$        $f_c = 838.5328 \text{ Hz}$

c)  $\theta(\text{pass band}) = 0^\circ$

d)  $\theta(\omega_c) = 45^\circ$

e)  $\theta(\text{stop band}) = 90^\circ$

f) Filter Type = High Pass


**Correct**

Marks for this submission: 10.00/10.00.

**Question 3**

Correct

Mark 10.00 out of 10.00

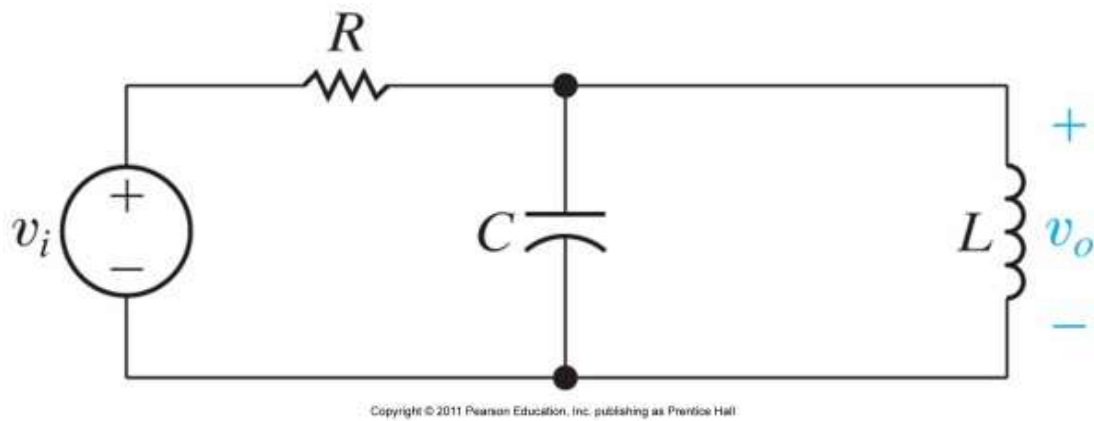

Q3Pa

Given:  $R = 160 \, \Omega$  (Ohm)    $C = 5 \, \mu\text{F}$  (micro F)    $L = 203 \, \mu\text{H}$  (micro H)a) Find the resonant frequency  $\omega_0$ .

$$\omega_0 = 31388 \, \checkmark \text{ rad/sec}$$

b) Find the lower half-power frequency  $\omega_{c1}$ .

$$\omega_{c1} = 30763 \, \checkmark \text{ rad/sec}$$

c) Find the upper half-power frequency  $\omega_{c2}$ .

$$\omega_{c2} = 32013 \, \checkmark \text{ rad/sec}$$

d) Find the bandwidth  $\beta$  (Beta).

$$\beta = 1250 \, \checkmark \text{ rad/sec}$$

e) Find the quality factor  $Q$ .

$$Q = 25.11 \, \checkmark$$

f) Identify the filter type of this circuit.

Filter Type = Band Pass ☒**Numeric Answer**a)  $\omega_0 = 31,388.2410 \text{ rad/sec}$ b)  $\omega_{c1} = 30,769.4629 \text{ rad/sec}$ c)  $\omega_{c2} = 32,019.4629 \text{ rad/sec}$ d)  $\beta = 1,250 \text{ rad/sec}$ e)  $Q = 25.1106$ 

f) Filter Type = Band Pass


**Correct**

Marks for this submission: 10.00/10.00.

**Question 4**

Correct

Mark 10.00 out of 10.00

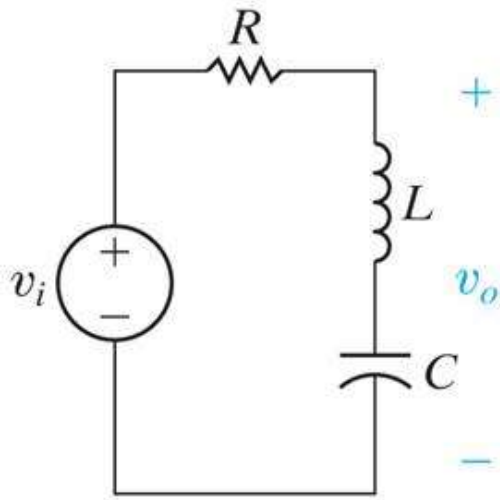

Q4Sc

Given:  $R = 1875 \, \Omega$  (Ohm)    $C = 20 \, \text{nF}$  (nano F)    $L = 200 \, \text{mH}$  (milli H)a) Calculate  $\omega_0$ .

$$\omega_0 = 15811.38 \, \checkmark \text{ rad/sec}$$

b) Calculate  $f_0$ .

$$f_0 = 2516.46 \, \checkmark \text{ Hz}$$

c) Find  $\omega_{c1}$ .

$$\omega_{c1} = 11804 \, \checkmark \text{ rad/sec}$$

d) Find  $\omega_{c2}$ .

$$\omega_{c2} = 21180 \, \checkmark \text{ rad/sec}$$

e) Find  $\beta$  (Beta).

$$\beta = 9378 \, \checkmark \text{ rad/sec}$$

f) Find  $Q$ .

$$Q = 1.68 \, \checkmark$$

g) Identify the filter type of this circuit.

Filter Type = Band Reject  $\checkmark$ **Numeric Answer**a)  $\omega_0 = 15,811.3883 \text{ rad/sec}$ b)  $f_0 = 2,516.4606 \text{ Hz}$ c)  $\omega_{c1} = 11,804.0935 \text{ rad/sec}$ d)  $\omega_{c2} = 21,179.0935 \text{ rad/sec}$ e)  $\beta = 9,375 \text{ rad/sec}$ f)  $Q = 1.6865$ 

g) Filter Type = Band Reject


**Correct**

Marks for this submission: 10.00/10.00.

**Question 5**

Correct

Mark 10.00 out of 10.00

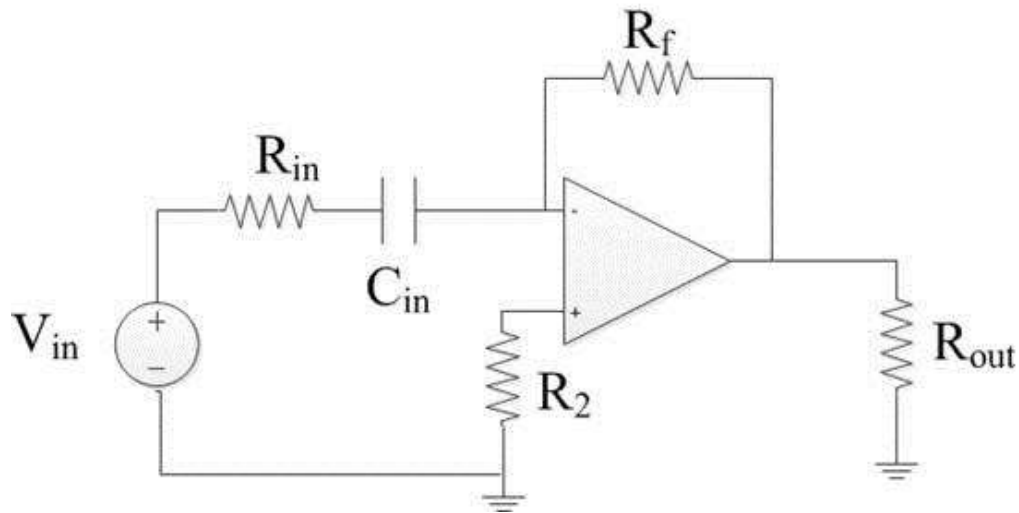

Q5e

Given:  $V_{in} = 25 \cos(4,000t)$  Volts $R_{in} = 40 \text{ k}\Omega$  (kilo Ohm)    $C_{in} = 0.1 \text{ }\mu\text{F}$  (micro F)    $R_f = 10 \text{ k}\Omega$  (kilo Ohm) $R_{out} = 1 \text{ k}\Omega$  (kilo Ohm)    $R_2 = 10 \text{ }\Omega$  (Ohm)

The opamp has power input rails at +15V and -15V.

Find the steady-state output voltage  $V_{out}$  which is the voltage across the resistor  $R_{out}$ .

$$v_{out} = 6.24 \cos(4,000 t + 183.6^\circ) \text{ (Degrees) Volts}$$

State the phase angle as a positive angle in the correct quadrant.

**Numeric Answer**

$$v_{out} = 6.2378 \cos(4,000 t + 183.5763^\circ) \text{ Volts}$$


**Correct**

Marks for this submission: 10.00/10.00.

**Question 6**

Correct

Mark 10.00 out of 10.00

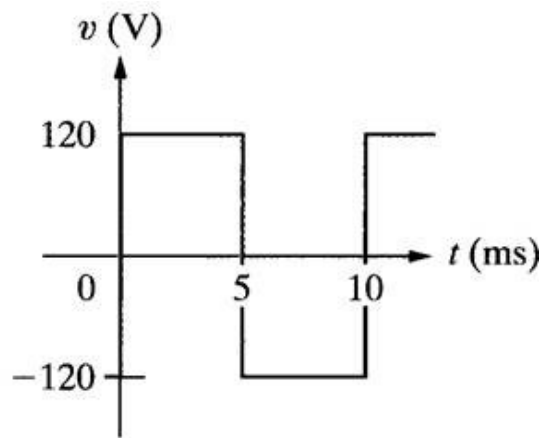

Q6a

Given: The Fourier coefficients for this waveform are

$$a_v = 0 \text{ V} \quad a_n = 0 \text{ V} \quad b_n = 480 / (n\pi) \text{ for } n \text{ odd}$$

Write the following terms of this waveform's Fourier series.

a) What is the average value?

$$\text{Avg} = \boxed{0} \text{ Volts}$$

Answers for the next two questions are in the order of magnitude, identify cosine or sine and the frequency of the sinusoid in radians/sec.

b) Find the Fourier Series term for  $n = 1$ .

$$v_1(t) = \boxed{152.8} \text{ sine } ( \boxed{628.3} \text{ t) Volts}$$

c) Find the Fourier Series term for  $n = 5$ .

$$v_5(t) = \boxed{30.6} \text{ sine } ( \boxed{3141.6} \text{ t) Volts}$$

**Numeric Answer**

a)  $a_v = 0 \text{ Volts}$

b) For  $n = 1$ ,  $v_1(t) = 480/\pi \sin(1 \cdot 200\pi) = 152.7887 \sin(628.3185 t) \text{ V}$

c) For  $n = 5$ ,  $v_5(t) = 96/\pi \sin(5 \cdot 200\pi) = 30.5577 \sin(3,141.5927 t) \text{ V}$

**Correct**

Marks for this submission: 10.00/10.00.

**Question 7**

Correct

Mark 10.00 out of  
10.00

Q7a

Given the “normal” trigonometric form of the Fourier series coefficients for a waveform are

$$a_{\text{avg}} = \text{zero} \quad a_n = -10/n^2 \quad b_n = 20/n$$

Determine the coefficients for the Alternative trigonometric form of the Fourier series in the polar form

$$a_n - jb_n = A_n \angle -\theta_n \quad (\text{Magnitude } A_n \text{ at angle } -\theta_n)$$

a) For the first term in the summation where  $n = 1$ :

$$A_1 = \boxed{22.38} \checkmark \text{ Volts}$$

$$-\theta_1 \text{ (Theta 1)} = \boxed{-116.57} \checkmark ^\circ \text{ (Degrees, angle CW from origin)}$$

b) For the second term in the summation where  $n = 2$ :

$$A_2 = \boxed{10.3} \checkmark \text{ Volts}$$

$$-\theta_2 \text{ (Theta 2)} = \boxed{-104.04} \checkmark ^\circ \text{ (Degrees, angle CW from origin)}$$

c) For the third term in the summation where  $n = 3$ :

$$A_3 = \boxed{6.76} \checkmark \text{ Volts}$$

$$-\theta_3 \text{ (Theta 3)} = \boxed{-99.463} \checkmark ^\circ \text{ (Degrees, angle CW from origin)}$$

CW = Clock-wise

Note that the angle also includes the “-” sign as shown in the polar form.

**Numeric Answer**

$$\text{a) } A_1 = 22.3607 \text{ Volts} \quad -\theta_1 = -116.5651^\circ$$

$$\text{b) } A_2 = 10.3078 \text{ Volts} \quad -\theta_2 = -104.0362^\circ$$

$$\text{c) } A_3 = 6.7586 \text{ Volts} \quad -\theta_3 = -99.4623^\circ$$

**Correct**


Marks for this submission: 10.00/10.00.



### Question 8

Correct

Mark 10.00 out of 10.00

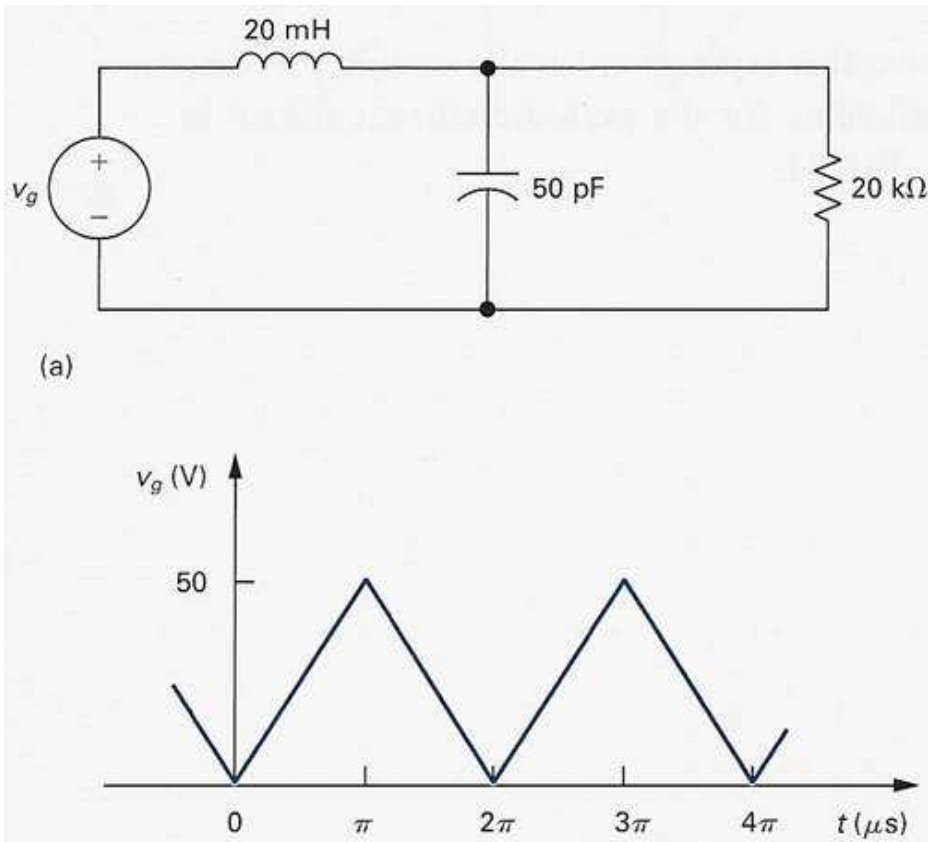

Q8

The triangular-wave voltage source is applied to this circuit.

The Fourier series of this input waveform is

$$v(t) = 25 - \frac{200}{\pi^2} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \cos(n\omega_0 t)$$

The s domain transfer function of the circuit is

$$H(s) = \frac{10^{12}}{s^2 + s10^6 + 10^{12}}$$

The desired output is the voltage across the  $20 \text{ k}\Omega$  (kilo Ohm) resistor.

a) Determine the steady-state output voltage for  $n = 1$  written as polar phasor.

$v_{1,20W,\text{steady-state}}(t) = \text{Magnitude } \boxed{-20.26} \checkmark \text{ at angle } \boxed{-90} \checkmark^\circ \text{ (Degrees) Volts}$   
(negative magnitude and negative angle)

b) Determine the steady-state output voltage for  $n = 5$  written as polar phasor.

$v_{5,20W,\text{steady-state}}(t) = \text{Magnitude } \boxed{-165} \checkmark \text{ at angle } \boxed{11.77} \checkmark^\circ \text{ (Degrees) Volts}$   
(negative magnitude and positive angle)

c) Determine an estimate of the time varying power across the  $20 \text{ k}\Omega$  (kilo Ohm) resistor based on the voltage from  $n = 1$  term only.

$P_{20W,\text{steady-state}} = \boxed{10.26} \checkmark \text{ mW (milli W)}$

### Numeric Answer

a)  $v_{1,20W,\text{steady-state}}(t) = -20.2642 \text{ at angle } -90^\circ \text{ V}$

b)  $v_{5,20W, \text{steady-state}}(t) = -0.1654$  at angle  $11.77^\circ$  V

c)  $P_{20W, \text{steady-state}} = 10.266$  mW


**Correct**

Marks for this submission: 10.00/10.00.

### Question 9

Correct

Mark 10.00 out of 10.00

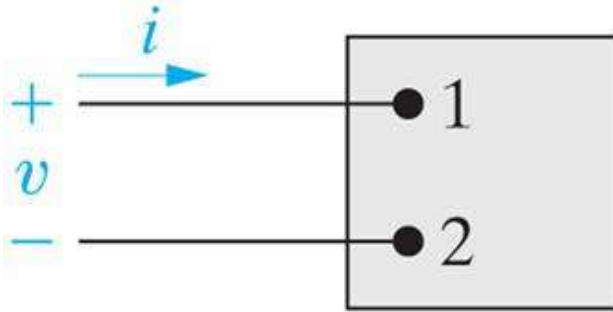

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Ltd.

Q9d

The voltage and current at terminals of this network are

$$v(t) = 150 + 120 \sin(300t + 45^\circ) + 40 \cos(900t) \text{ Volts}$$

$$i(t) = 45 + 18 \cos(300t + 75^\circ) + 8 \sin(900t - 15^\circ) \text{ Amps}$$

a) What is the average power at terminals?

$P =$    $\checkmark$  W

b) What is the rms value of the voltage of this truncated series?

$V_{\text{rms}} =$    $\checkmark$   $V_{\text{rms}}$

c) What is the rms value of the current of this truncated series?

$I_{\text{rms}} =$    $\checkmark$   $A_{\text{rms}}$

### Numeric Answer

a)  $P = 6,168.5890$  W

b)  $V_{\text{rms}} = 174.6425$   $V_{\text{rms}}$

c)  $I_{\text{rms}} = 47.1063$   $I_{\text{rms}}$

**Correct**

Marks for this submission: 10.00/10.00.

**Question 10**

Complete

Mark 1.50 out of  
10.00

You created a Bode Diagram of a given transfer function in-class on May 8th. That in-class work will be manually graded and the score entered here on your final exam.

**Comment:**

Please review Bode Diagrams. Your in-class work did not show understanding of the Bode concept.