

Home ► Electrical Engineering ► Engr17-2016F-Tatro ► Exams and Quizzes ►  
Exam 2 - Section 1 - Chapters 4, 5 and 6

---

|                   |                                      |
|-------------------|--------------------------------------|
| <b>Started on</b> | Wednesday, 2 November 2016, 11:55 AM |
|-------------------|--------------------------------------|

---

|              |          |
|--------------|----------|
| <b>State</b> | Finished |
|--------------|----------|

---

|                     |                                      |
|---------------------|--------------------------------------|
| <b>Completed on</b> | Wednesday, 2 November 2016, 12:55 PM |
|---------------------|--------------------------------------|

---

|                   |                 |
|-------------------|-----------------|
| <b>Time taken</b> | 59 mins 42 secs |
|-------------------|-----------------|

---


|              |                            |
|--------------|----------------------------|
| <b>Grade</b> | <b>82.50</b> out of 100.00 |
|--------------|----------------------------|

---

**Question 1**

Partially correct

Mark 7.50 out of 15.00

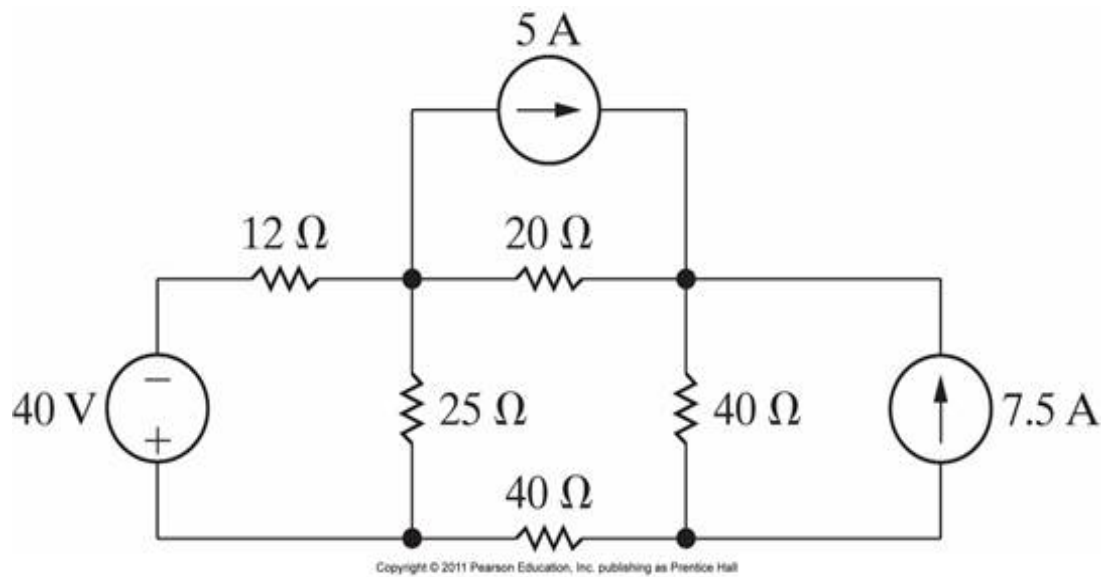

Q1d

a) Find the voltage across the 7.5A current source.

$$V_{7.5A} = -122 \text{ Volts}$$

b) Find the voltage across the 25 Ω (Ohm) resistor.

$$V_{25\Omega} = -10 \text{ Volts}$$

**Numeric Answer**

$$V_{7.5A} = 216V$$


$$V_{25\Omega} = -10V$$

**Partially correct**

Marks for this submission: 7.50/15.00.

**Question 2**

Correct

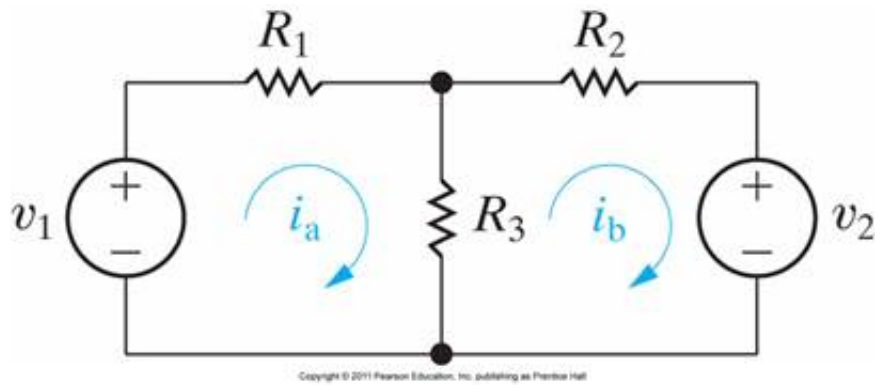Mark 15.00 out of  
15.00

Q2j

Given:

$v_1 = 21 \text{ Volts}$

$v_2 = 28 \text{ Volts}$

$R_1 = 10 \, \Omega \text{ (Ohms)}$

$R_2 = 40 \, \Omega \text{ (Ohms)}$

$R_3 = 80 \, \Omega \text{ (Ohms)}$

Find the currents  $i_a$  and  $i_b$ .

$i_a = 63.6 \text{ mA (milli Amp)}$

$i_b = -190.9 \text{ mA (milli Amp)}$

**Numeric Answer**

$i_a = 63.636 \text{ mA}$


$i_b = -190.909 \text{ mA}$

**Correct**

Marks for this submission: 15.00/15.00.

**Question 3**

Correct

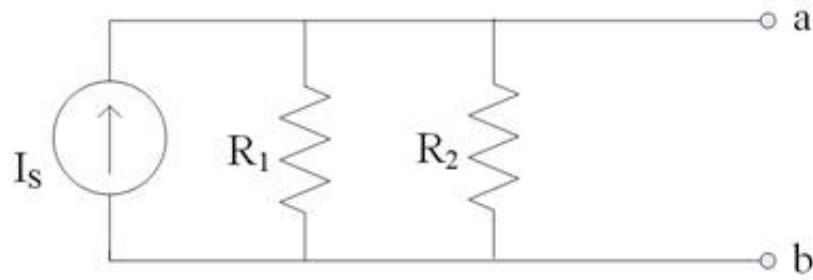Mark 10.00 out of  
10.00

Q3f

Given:  $I_s = 10 \text{ A}$      $R_1 = 10 \Omega$  (Ohms)     $R_2 = 40 \Omega$  (Ohms)

Perform a source transformation and find the voltage transform equivalent.

this circuit.

$$V_{transform} = 80 \text{ V}$$

$$R_{transform} = 8 \Omega \text{ (Ohm)}$$

**Numeric Answer**

$$V_{transform} = 80 \text{ V}$$


$$R_{transform} = 8 \Omega \text{ (Ohm)}$$

**Correct**

Marks for this submission: 10.00/10.00.

**Question 4**

Correct

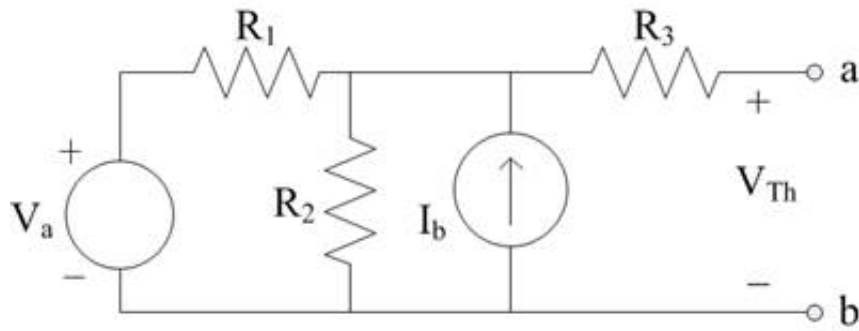Mark 15.00 out of  
15.00

Q4b

Given:

$V_a = 10 \text{ Volts}$

$I_b = 3 \text{ Amps}$

$R_1 = 20 \, \Omega \text{ (Ohm)}$

$R_2 = 20 \, \Omega \text{ (Ohm)}$

$R_3 = 10 \, \Omega \text{ (Ohm)}$

a) Find the Thévenin equivalent voltage  $V_{Th}$ .

$V_{Th} = 35 \text{ Volts}$

b) Find the Thévenin equivalent resistance  $R_{Th}$ .

$R_{Th} = 20 \, \Omega \text{ (Ohms)}$

**Numeric Answer**

a)  $V_{Th} = 35.0 \text{ Volts}$


b)  $R_{Th} = 20.0 \, \Omega \text{ (Ohms)}$

**Correct**

Marks for this submission: 15.00/15.00.

**Question 5**

Correct

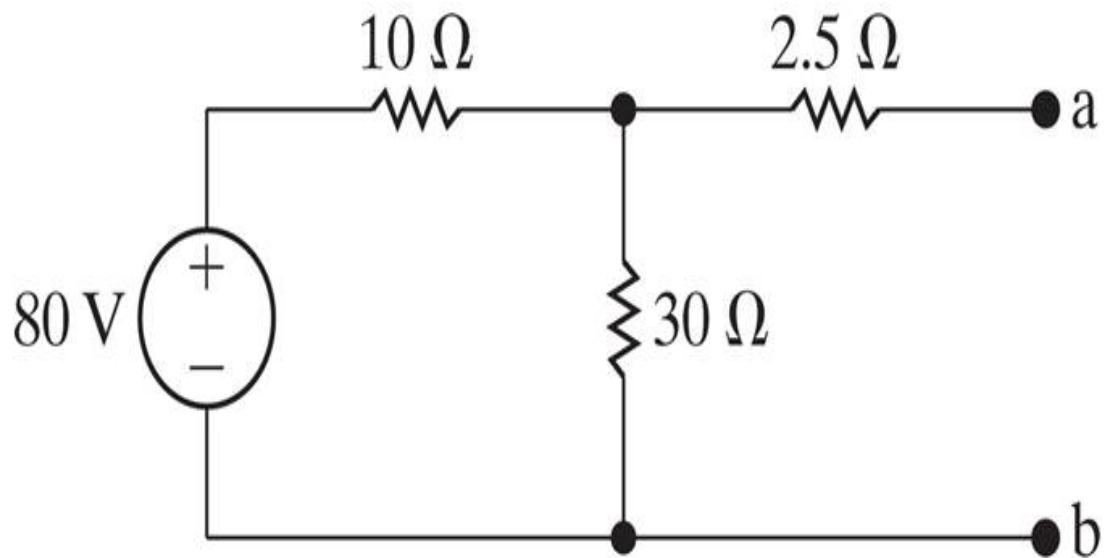Mark 15.00 out of  
15.00

Copyright ©2015 Pearson Education, All Rights Reserved

Q5b

Find the Norton equivalent circuit with respect to terminals ab.

$$I_N = 6 \text{ A}$$

$$R_{Th} = 10 \text{ } \Omega \text{ (Ohm)}$$

**Numeric Answer**

$$I_N = 6 \text{ A}$$

$$R_{Th} = 10 \text{ } \Omega \text{ (Ohm)}$$


**Correct**

Marks for this submission: 15.00/15.00.

**Question 6**

Correct

Mark 10.00 out of 10.00

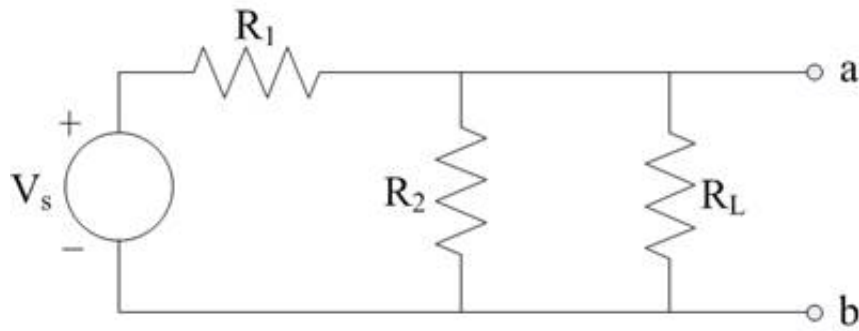

Q6j

Given:

$$V_s = 40 \text{ Volts} \quad R_1 = 140 \, \Omega \text{ (Ohm)} \quad R_2 = 84 \, \Omega \text{ (Ohm)}$$

a) Find the value of  $R_L$  that results in maximum power being transferred to  $R_L$ .

$$R_{L, \text{max power}} = 52.5 \, \Omega \text{ (Ohms)}$$

b) Find the maximum power that can be delivered to  $R_L$ .

$$P_{R_L, \text{max power}} = 1.07 \text{ Watts}$$

**Numeric Answer**

$$\text{a) } R_{L, \text{max power}} = 52.50 \, \Omega \text{ (Ohms)}$$


$$\text{b) } P_{R_L, \text{max power}} = 1.071 \text{ Watts}$$

**Correct**

Marks for this submission: 10.00/10.00.

**Question 7**

Not answered

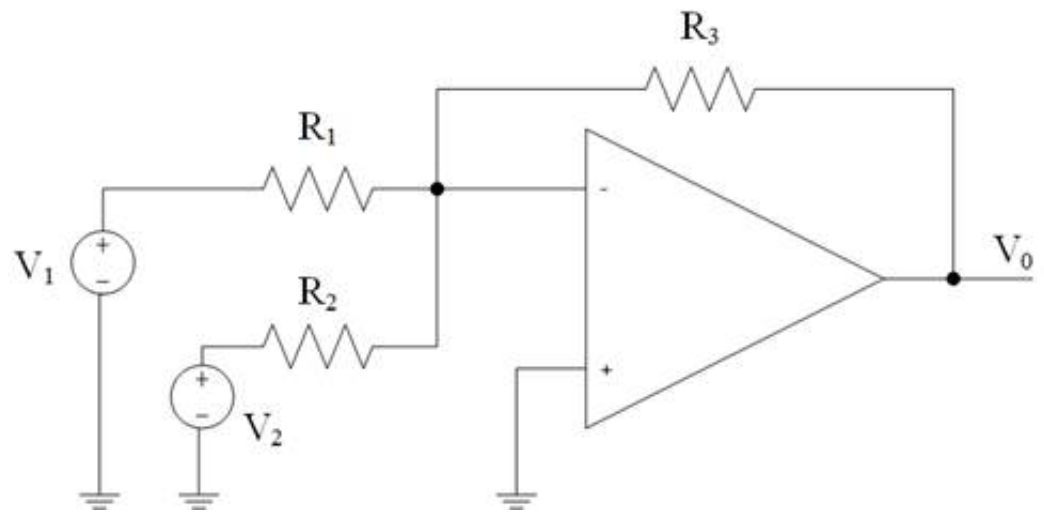Mark 0.00 out of  
5.00

Q7j


Assume that the operational amplifier is ideal.

The opamp has two power inputs (not shown) of  $+V_{cc} = +15V$  and  $-V_{cc} = -15V$ .Given:  $V_1 = 10$  Volts       $V_2 = 10$  Volts $R_1 = 2$  k $\Omega$  (kilo Ohm)       $R_2 = 3$  k $\Omega$  (kilo Ohm)       $R_3 = 1.5$  k $\Omega$  (kilo Ohm)Determine the voltage  $v_{out}$ . $v_{out} =$    $\times$  Volts**Numeric Answer** $v_{out} = -12.5$  Volts



**Question 8**

Incorrect

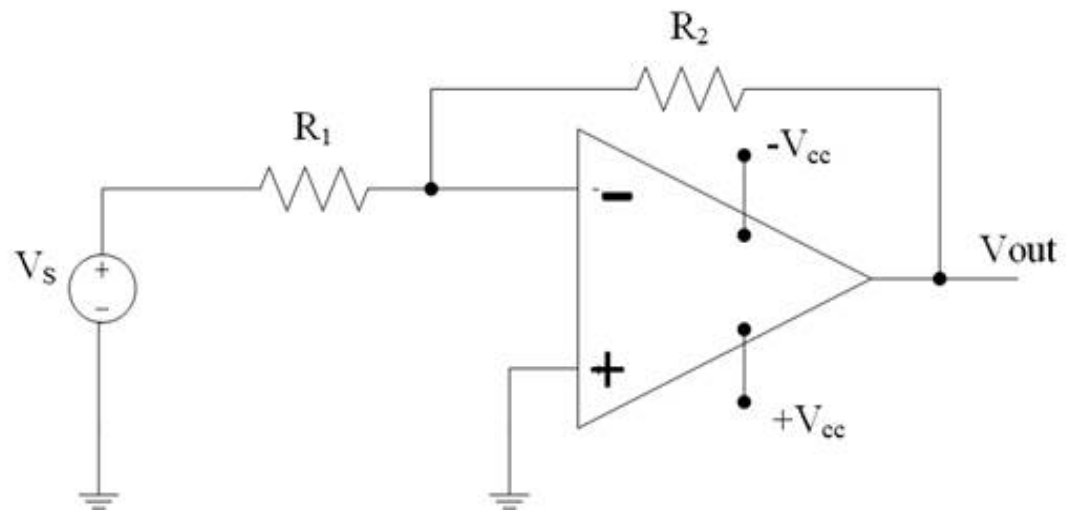Mark 0.00 out of  
5.00

Q8c


Assume that the operational amplifier is ideal.

The opamp has two power inputs  $+V_{cc} = +15\text{V}$  and  $-V_{cc} = -15\text{V}$ .Given:  $V_S = -3.0\text{ Volts}$   
(kilo Ohm) $R_1 = 47\text{ k}\Omega$  (kilo Ohm) $R_2 = 270\text{ k}\Omega$ Determine the voltage  $V_{out}$ . $V_{out} = -17.23$  ✗ Volts**Numeric Answer** $v_{out} = 15.0\text{ Volts}$ **Incorrect**

Marks for this submission: 0.00/5.00.

**Question 9**

Correct

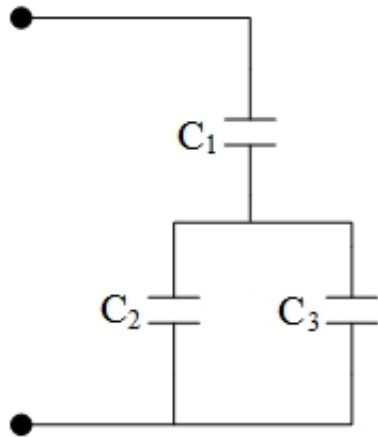Mark 5.00 out of  
5.00

Q9e

Given:

$$C_1 = 10 \mu\text{F (micro F)} \quad C_2 = 6 \mu\text{F (micro F)} \quad C_3 = 4 \mu\text{F (micro F)}$$

Find the equivalent capacitance  $C_{\text{Eq}}$ .

$$C_{\text{Eq}} = 5 \mu\text{F (micro F)}$$

**Numeric Answer**


$$C_{\text{Eq}} = 5.0 \mu\text{F (micro F)}$$

**Correct**

Marks for this submission: 5.00/5.00.

**Question 10**

Correct

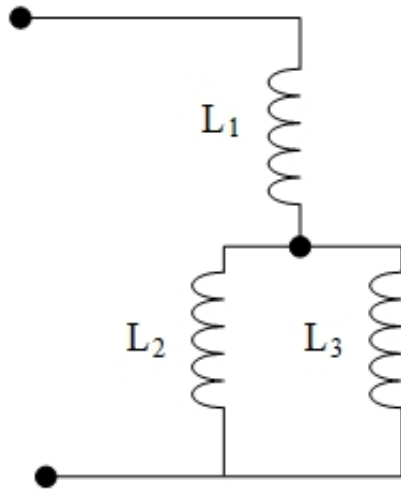Mark 5.00 out of  
5.00

Q10h

Given:

$$L_1 = 1 \text{ mH (milli H)} \quad L_2 = 4 \text{ mH (milli H)} \quad L_3 = 7 \text{ mH (milli H)}$$

Find the equivalent inductance  $L_{\text{Eq}}$ .

$$L_{\text{Eq}} = \boxed{3.55} \checkmark \text{ mH (milli H)}$$

**Numeric Answer**

$$L_{\text{Eq}} = 3.5455 \text{ mH}$$

**Correct**

Marks for this submission: 5.00/5.00.