

Started on Wednesday, 3 April 2019, 10:55 AM**State** Finished**Completed on** Wednesday, 3 April 2019, 11:37 AM**Time taken** 41 mins 55 secs**Grade** 100.00 out of 100.00**Question 1**

Correct

Mark 5.00 out of 5.00

Q1c

Find the Laplace Transform of $\left\{ \frac{d}{dt}[e^{-at} \sin(\omega t)] \right\} \Leftrightarrow$

Select one:

- ☒ a. $\frac{s\omega}{(s+a)^2 + \omega^2}$ ✓
- ☐ b. $\frac{-s^2}{(s+a)^2 + \omega^2}$
- ☐ c. $\frac{\omega^2}{(s+a)^2 + \omega^2}$
- ☐ d. $\frac{2sa}{(s+a)^2 + \omega^2}$

Correct

Marks for this submission: 5.00/5.00.

Question 2

Correct

Mark 15.00 out of 15.00

Q2a

Given $F(s) = \frac{100(s^2+69)}{(s+10)(s^2+10s+169)} = \frac{100(s^2+69)}{(s+10)(s+5-j12)(s+5+j12)}$

Find the partial fraction expansion of F(s) and then use the Laplace transform tables to find f(t).

$f(t) = [100 \checkmark e^{-10 \checkmark t} + 83.33 \checkmark e^{-5 \checkmark t} \cos(12 \checkmark t + 90 \checkmark^\circ)] u(t)$

Correct

Marks for this submission: 15.00/15.00.

Question 3

Correct

Mark 10.00 out of 10.00

Q3b

Given: $F(s) = \frac{10(s^2+40)}{(s+8)(s^2+12s+136)}$ which has an inverse transform f(t).

a) Find the initial value of f(t = 0).

$f(t=0) = 10 \checkmark$

b) Find the final value of f(t → ∞)

$f(t \rightarrow \infty) = 0 \checkmark$


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

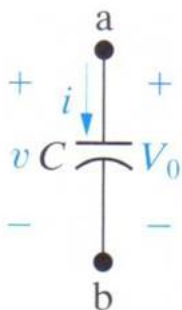

Q4b

Given: This capacitor has a value of $1\ \mu\text{F}$ (micro F) and has an initial voltage of $45\ \text{V}$ at $t = 0^-$.

Identify the Frequency Domain series form of the capacitor.

Select one:

- ☒ a. $V = \frac{1}{s(1 \times 10^{-6})} + \frac{45}{s}$ ✓
- ☐ b. $V = \frac{1}{s(1 \times 10^{-3})} + \frac{45}{s}$
- ☐ c. $I = s(1 \times 10^{-6})V - 45 \times 10^{-6}$
- ☐ d. $I = s(1 \times 10^{-3})V - 45 \times 10^{-3}$


Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 15.00 out of 15.00

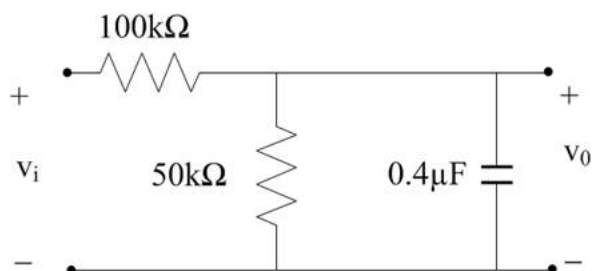

Q5c

Find the s domain transfer function $H(s) = V_0/V_i$ for this circuit.

$H(s) = 25 / (s + 75)$ ✓ ✓


Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 15.00 out of 15.00

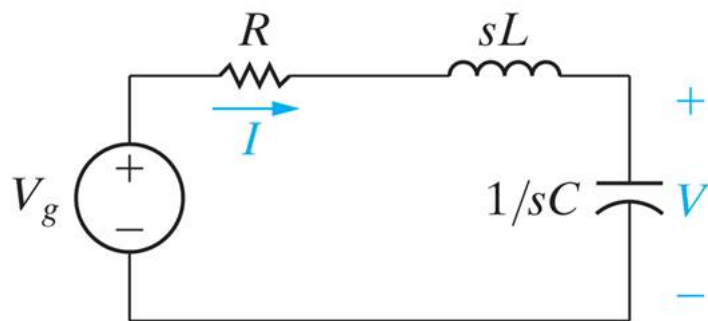

Q6a

Given: There is no energy stored in this circuit prior to $t = 0$.

The voltage source $V_g = 10\text{V}$ for $t \geq 0^+$.

$R = 125\ \Omega$ (Ohm)

$L = 1\text{ H}$

$C = 1\text{ mF}$ (milli F)

Find defined voltage V in the s domain.

$$V(s) = \boxed{10000} \checkmark / [s(s^2 + \boxed{125} \checkmark s + \boxed{1000} \checkmark)]$$

Correct

Marks for this submission: 15.00/15.00.

Question 7

Correct

Mark 15.00 out of 15.00

Q7d

Given: $F(s) = \frac{8(s^2 - 5s + 50)}{s(s + 10)}$

Find the partial fraction expansion of this transfer function.

$$F(s) = \boxed{40} \checkmark / s + \boxed{-160} \checkmark / (s + 10)$$


Correct

Marks for this submission: 15.00/15.00.

Question 8

Correct

Mark 15.00 out of 15.00

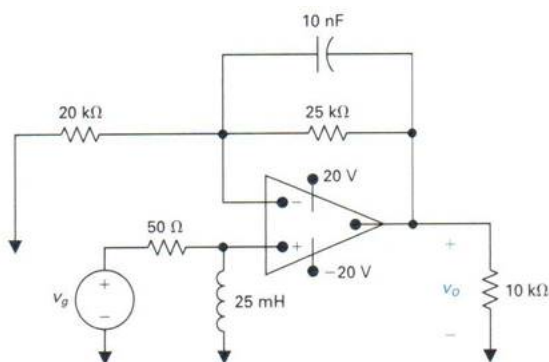

Q8c

Given: The opamp is ideal.

$$H(s) = \frac{V_o}{V_g} = \frac{s(s + 9,000)}{(s + 2,000)(s + 4,000)}$$

Find the steady-state response when the input $v_g(t) = 12 \cos(10,000 t)\text{ V}$.

$$v_o(t)_{\text{steady-state}} = [\boxed{14.69} \checkmark \cos(\boxed{10000} \checkmark t + \boxed{-8.88} \checkmark^\circ)] u(t)\text{ V}$$

Correct

Marks for this submission: 15.00/15.00.

