

Started on Sunday, 27 November 2016, 2:49 PM

State Finished

Completed on Sunday, 27 November 2016, 4:21 PM

Time taken 1 hour 32 mins

Grade 93.33 out of 100.00

Question 1

Correct

Mark 10.00 out of
10.00

CQ6.13

Given two inductors are magnetically coupled.

The coefficient of coupling $k = 0.56$

The self-inductances are:

$$L_1 = 1.4 \text{ H} \quad L_2 = 4.4 \text{ H}$$

Find the mutual inductance.

$$M = ?? \text{ H}$$

Answer:



Calculated Question

The correct answer is: 1.390

Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of
10.00



P6.39_10ed

Given: $L_1 = 5 \text{ H}$ $L_2 = 0.2 \text{ H}$ $M = 0.5 \text{ H}$ $R_0 = 10 \Omega$ (Ohm)
 $i_g = -10 + e^{-10t} \text{ A}$ for $t \geq 0$ $i_2 = 0.625e^{-10t} - 0.250e^{-50t} \text{ A}$ for $t \geq 0$

There is no energy stored in this circuit at the time the switch is opened.

a) Find the voltage $v_1(t)$ at $t = 0^+$ sec just as the switch opens.

$$v_1(t = 0^+ \text{ sec}) = -46.875 \text{ V}$$

b) Find the voltage $v_1(t)$ at $t = 0.2$ sec after the switch opens.

$$v_1(t = 0.2 \text{ sec}) = -7.189 \text{ V}$$

Numeric Answer

a) $v_1(t = 0^+ \text{ sec}) = -46.875 \text{ V}$

b) $v_1(t = 0.2 \text{ sec}) = -7.190 \text{ V}$

Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00



P6.39_6ed

Two magnetically coupled coils which have

$$L_1 = 196 \text{ mH} \quad L_2 = 4 \text{ mH} \quad M = 23.8 \text{ mH}$$

a) What is the coefficient of coupling k ?

$$k = 0.85 \quad \checkmark$$

b) What is the largest possible value of M if the coupling was perfect?

$$M = 28 \quad \checkmark \text{ mH}$$

c) Given that in this circuit $P_1 = P_2$, what is the turns ratio N_1/N_2 ?

$$N_1/N_2 = 7 \quad \checkmark$$

Numeric Answera) $k = 0.850$ b) $M = 28.0 \text{ mH}$ c) $N_1/N_2 = 7$ **Correct**

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of
10.00

P9.76_9ed

The sinusoidal source is operating at 200 krad/sec (kilo rad/sec).

The coefficient of coupling k is adjusted until the peak amplitude of i_1 is maximum.

Given $v_g = 560 \cos(200,000t)$ V.

a) What is the value of k ? [Hint: Use reflected impedance which includes k and determine when Z_{in} is minimum which yields the max current]

$$k = \boxed{.3536} \checkmark$$

b) What is the peak amplitude of i_1 ?

$$|i_1| = \boxed{2} \checkmark \text{ A}$$

Numeric Answer

$$k = 0.3536$$

$$i_1 = 2 \text{ A (peak) the phasor current is 2 at angle } -36.87^\circ \text{ A}$$

Correct

Marks for this submission: 10.00/10.00.

Question 5

Partially correct

Mark 5.00 out of
10.00

P9.60_6ed

Given $v_g = 369 \cos(50,000t)$ V.The coefficient of coupling k is adjusted until the peak amplitude of i_1 is maximum.a) What is the value of k ? [Hint: Use reflected impedance which includes k and determine when Z_{in} is minimum which yields the max current] $k =$ b) What is the peak amplitude of i_1 ? $|i_1| =$ A**Numeric Answer** $k = 0.566$ $i_1 = 1.5$ A (peak) the phasor current is $1.50 \angle -36.87^\circ$ A**Partially correct**

Marks for this submission: 5.00/10.00.

Question 6

Correct

Mark 10.00 out of
10.00

P9.63_6ed

Given driving source frequency = 25 krad/sec.

The coefficient of coupling k is adjusted so that Z_{ab} is purely resistive.Find Z_{ab} for this condition. $Z_{ab} =$ ✓ Ω (Ohm)**Numeric Answer** $Z_{ab} = 30.0 \Omega$ (Ohm)**Correct**

Marks for this submission: 10.00/10.00.

Question 7

Partially correct

Mark 8.33 out of
10.00



AP9.14_9ed

A linear transformer couples a load $Z_L = 360 \, \Omega$ (Ohm) resistor in series with a 0.25 H inductor to a sinusoidal voltage source.

The voltage source V_S has an internal impedance $Z_S = 184 + j 0 \, \Omega$ (Ohm) and a maximum voltage of 245.20 V.

The frequency of the source V_S is 800 rad/sec.

$R_1 = 100 \, \Omega$ (Ohm) $L_1 = 0.5 \, \text{H}$

$R_2 = 40 \, \Omega$ (Ohm) $L_2 = 0.125 \, \text{H}$ $k = 0.4$

a) Calculate the reflected impedance.

$Z_r =$ ✓ $+ j$ ✗ $\, \Omega$ (Ohm) (real + j imaginary)

b) Calculate the time domain primary side current. Use the form $i_1(t) = I_m \cos(\omega t + \phi^\circ)$ Amps

$i_1(t) =$ ✓ $\cos(800 t +$ ✓ $^\circ)$ (Degrees) Amps

c) Calculate the secondary side current. Use the form $i_2(t) = I_m \cos(\omega t + \phi^\circ)$ Amps

$i_2(t) =$ ✓ $\cos(800 t +$ ✓ $^\circ)$ (Degrees) Amps

Numeric answer

a) $Z_r = 10.24 - j 7.68 \, \Omega$

b) $i_1(t) = 0.5 \cos(800t - 53.13^\circ)$ Amps

c) $i_2(t) = 0.08 \cos(800t)$ Amps

Partially correct

Marks for this submission: 8.33/10.00. Accounting for previous tries, this gives **8.33/10.00**.

Question 8

Correct

Mark 10.00 out of
10.00



P9.83_6ed

Find the impedance Z_{ab} if $Z_L = 80$ at angle $60^\circ \Omega$ (Ohms).

$|Z_{ab}| =$ ✓ k Ω (kilo Ohm)

Z_{ab} angle = ✓ $^\circ$ (Degrees)

Numeric Answer

$Z_{ab} = 512$ at angle 60° k Ω (kilo Ohm)

Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of
10.00

P9.77_8ed

Given: $Z_L = 200 + j 150 \, \Omega$.Find the impedance Z_{ab} $Z_{ab} =$ Magnitude ✓ at Angle ✓ ° (Degrees) Ω (Ohm)**Numeric Answer** $Z_{ab} = 1,000$ at angle $36.87^\circ \, \Omega$ **Correct**

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of
10.00

AP9.15_9ed

The source voltage is 25 at angle 0° kV (kilo Volts).Find the amplitude and phase angle of \mathbf{V}_2 and \mathbf{I}_2 . $|\mathbf{V}_2| =$ ✓ VoltsPhase angle $\mathbf{V}_2 =$ ✓ $^\circ$ (Degrees) $|\mathbf{I}_2| =$ ✓ APhase angle $\mathbf{I}_2 =$ ✓ $^\circ$ (Degrees)**Numeric Answer** $\mathbf{V}_2 = 1868.16$ at angle 142.4° Volts $\mathbf{I}_2 = 125$ at angle 216.88° A**Correct**

Marks for this submission: 10.00/10.00.