


Home ► My courses ► EEE117-2017S-Tatro ► Exams and Quizzes ►
Exam 3 (Final) - Bode Diagram, Chapters 14, 15, 16, and Bode Diagrams

Started on	Monday, 15 May 2017, 10:10 AM
State	Finished
Completed on	Monday, 15 May 2017, 11:29 AM
Time taken	1 hour 18 mins
Grade	94.50 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

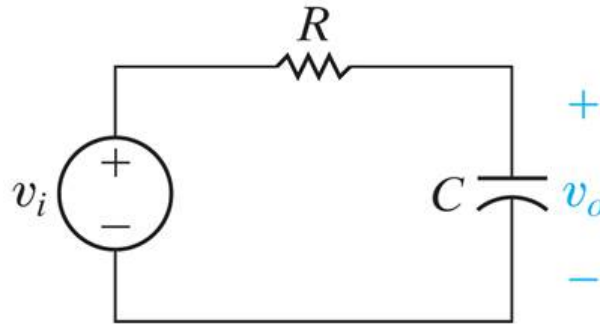

Q1c

Given: $C = 347 \text{ nF}$ (nano F) $R = 360 \Omega$ (Ohm)a) Write the parameters of the transfer function $H(s)$.

$$H(s) = V_o / V_i = \boxed{8005.12} \checkmark$$

$$/ (s + \boxed{8005.12} \checkmark)$$

b) Calculate the cutoff frequency ω_c in rad/sec and f_c in Hz.

$$\omega_c = \boxed{8005.12} \checkmark$$

$$\text{rad/sec} \quad f_c = \boxed{1274.05} \checkmark \text{ Hz}$$

c) State the phase angle of the output voltage when fully in the passband region where $\omega \ll \omega_c$.

$$\theta(\text{pass band}) = \boxed{0} \checkmark$$

° (Degrees)

d) State the phase angle of the output voltage at the corner frequency ω_c .

$$\theta(\omega_c) = \boxed{-45} \checkmark$$

° (Degrees)

e) State the phase angle of the output voltage when fully in the stopband region where $\omega \gg \omega_c$.

$$\theta(\text{stop band}) = \boxed{-90} \checkmark$$

° (Degrees)

f) Identify the filter type of this circuit.

$$\text{Filter Type} = \boxed{\text{Low Pass}} \checkmark$$

Numeric Answer

$$\text{a) } H(s) = 8,000.5123 / (s + 8,000.5123)$$

$$\text{b) } \omega_c = 8,000.5123 \text{ rad/sec} \quad f_c = 1,274.0549 \text{ Hz}$$

$$\text{c) } \theta(\text{pass band}) = 0^\circ$$

$$\text{d) } \theta(\omega_c) = -45^\circ$$

$$\text{e) } \theta(\text{stop band}) = -90^\circ$$

$$\text{f) } \text{Filter Type} = \text{Low Pass}$$


Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

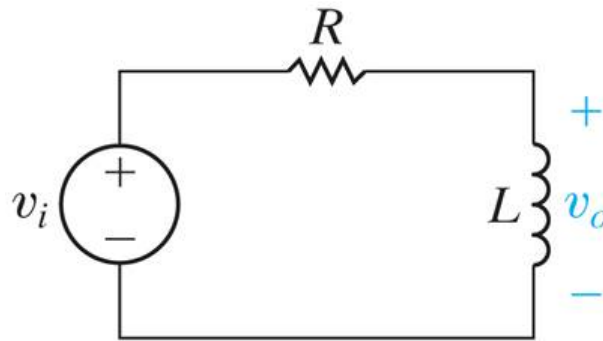

Q2c

Given: $L = 140 \text{ mH}$ (milli H) $R = 3.5 \text{ k}\Omega$ (kilo Ohm)a) Write the parameters of the transfer function $H(s)$.

$$H(s) = V_o / V_i = s / (s + 25000) \quad \checkmark$$

)

b) Calculate the cutoff frequency ω_c in rad/sec and f_c in Hz.

$$\omega_c = 25000 \quad \checkmark$$

$$\text{rad/sec} \quad f_c = 3980.9 \quad \checkmark \quad \text{Hz}$$

c) State the phase angle of the output voltage when fully in the passband region where $\omega \gg \omega_c$.

$$\theta(\text{pass band}) = 0 \quad \checkmark$$

° (Degrees)

d) State the phase angle of the output voltage at the corner frequency $\omega = \omega_c$.

$$\theta(\omega_c) = 45 \quad \checkmark$$

° (Degrees)

e) State the phase angle of the output voltage when fully in the stopband region where $\omega \ll \omega_c$.

$$\theta(\text{stop band}) = 90 \quad \checkmark$$

° (Degrees)

f) Identify the filter type of this circuit.

$$\text{Filter Type} = \text{High Pass} \quad \checkmark$$

Numeric Answer

a) $H(s) = s / (s + 25,000)$

b) $\omega_c = 25,000 \text{ rad/sec}$ $f_c = 3,978.8736 \text{ Hz}$

c) $\theta(\text{pass band}) = 0^\circ$

d) $\theta(\omega_c) = 45^\circ$


e) $\theta(\text{stop band}) = 90^\circ$

f) Filter Type = High Pass

Correct

Marks for this submission: 10.00/10.00.

Mark 10.00 out of 10.00

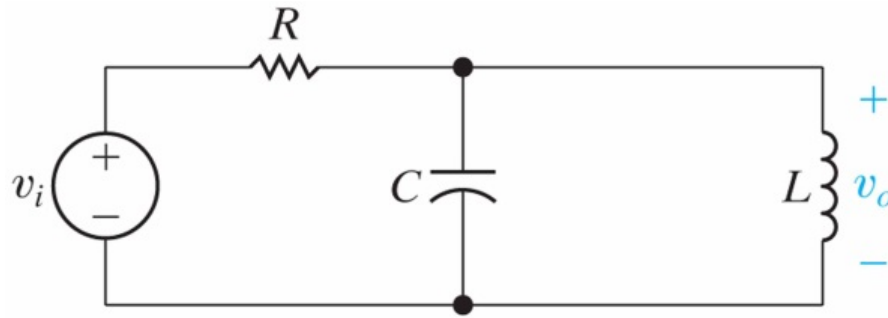

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

g) Filter Type = Band Reject


Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

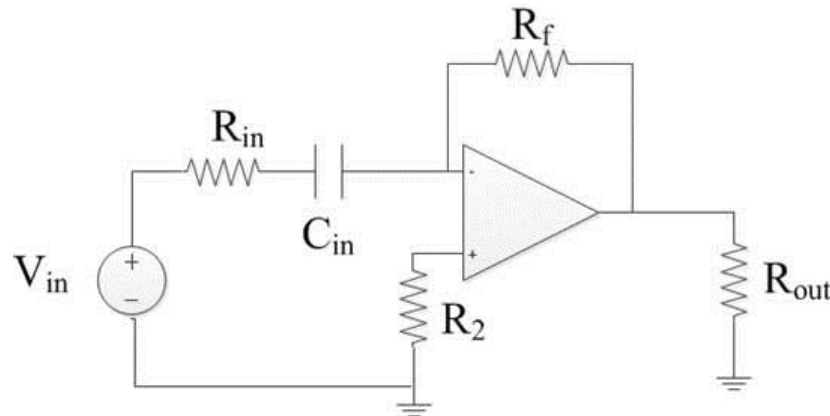

Q5d

Given: $V_{in} = 15 \cos(5,000t)$ Volts

$R_{in} = 10 \text{ k}\Omega$ (kilo Ohm) $C_{in} = 0.1 \text{ }\mu\text{F}$ (micro F) $R_f = 10 \text{ k}\Omega$ (kilo Ohm)

$R_{out} = 1 \text{ k}\Omega$ (kilo Ohm) $R_2 = 10 \text{ }\Omega$ (Ohm)

The opamp has power input rails at +15V and -15V.

Find the steady-state output voltage v_{out} which is the voltage across the resistor R_{out} .

$v_{out} =$ ✓

$\cos(5,000 t +$ ✓ $^\circ$ (Degrees) Volts

State the phase angle as a positive angle in the correct quadrant.

Numeric Answer

$v_{out} = 14.7087 \cos(5,000 t + 191.3099^\circ)$ Volts


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

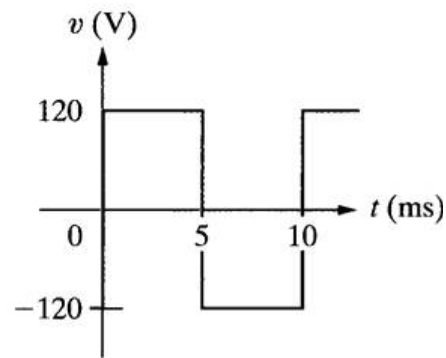

Q6a

Given: The Fourier coefficients for this waveform are

$$a_v = 0 \text{ V} \quad a_n = 0 \text{ V} \quad b_n = 480 / (n\pi) \text{ for } n \text{ odd}$$

Write the following terms of this waveform's Fourier series.

a) What is the average value?

$$\text{Avg} = \boxed{0} \checkmark$$

Volts

Answers for the next two questions are in the order of magnitude, identify cosine or sine and the frequency of the sinusoid in radians/sec.

b) Find the Fourier Series term for $n = 1$.

$$v_1(t) = \boxed{152.8} \checkmark$$

$$\text{sine } \boxed{\text{sin}} \checkmark (\boxed{628.3} \checkmark t) \text{ Volts}$$

c) Find the Fourier Series term for $n = 5$.

$$v_5(t) = \boxed{30.6} \checkmark$$

$$\text{sine } \boxed{\text{sin}} \checkmark (\boxed{3141.6} \checkmark t) \text{ Volts}$$

Numeric Answera) $a_v = 0$ Voltsb) For $n = 1$, $v_1(t) = 480/\pi \sin(1 \cdot 200\pi) = 152.7887 \sin(623.3185 t) \text{ V}$ c) For $n = 5$, $v_5(t) = 96/\pi \sin(5 \cdot 200\pi) = 30.5577 \sin(3,141.5927 t) \text{ V}$ **Correct**

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

Q7b

Given the “normal” trigonometric form of the Fourier series coefficients for a waveform are

$$a_{\text{avg}} = \text{zero} \quad a_n = -5/n^2 \quad b_n = 15/n$$

Determine the coefficients for the Alternative trigonometric form of the Fourier series in the polar form

$$a_n - jb_n = A_n \angle -\theta_n \quad (\text{Magnitude } A_n \text{ at angle } -\theta_n)$$

a) For the first term in the summation where $n = 1$:

$$A_1 = 15.8 \quad \checkmark$$

Volts

$$-\theta_1 (\text{Theta } 1) = -108.4 \quad \checkmark$$

° (Degrees, angle CW from origin)

b) For the second term in the summation where $n = 2$:

$$A_2 = 7.6 \quad \checkmark$$

Volts

$$-\theta_2 (\text{Theta } 2) = -99.5 \quad \checkmark$$

° (Degrees, angle CW from origin)

c) For the third term in the summation where $n = 3$:

$$A_3 = 5.03 \quad \checkmark$$

Volts

$$-\theta_3 (\text{Theta } 3) = -96.4 \quad \checkmark$$

° (Degrees, angle CW from origin)

CW = Clock-wise

Note that the angle also includes the “-” sign as shown in the polar form.

Numeric Answer

a) $A_1 = 15.8114$ Volts $-\theta_1 = -108.4349^\circ$

b) $A_2 = 7.6035$ Volts $-\theta_2 = -99.4623^\circ$

c) $A_3 = 5.0308$ Volts $-\theta_3 = -96.3402^\circ$


Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

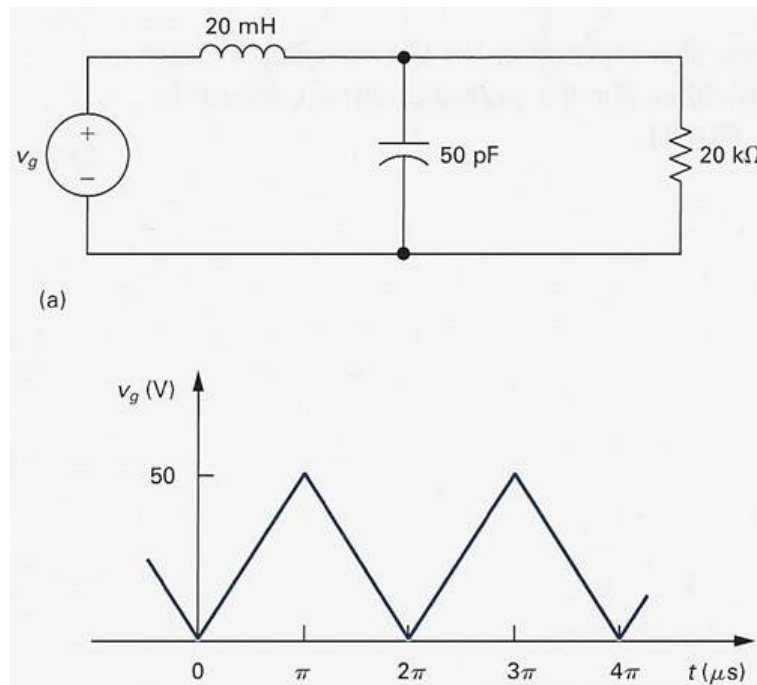

Q8

The triangular-wave voltage source is applied to this circuit.

The Fourier series of this input waveform is

$$v(t) = 25 - \frac{200}{\pi^2} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \cos(n\omega_0 t)$$

The s domain transfer function of the circuit is

$$H(s) = \frac{10^{12}}{s^2 + s10^6 + 10^{12}}$$

The desired output is the voltage across the $20\text{ k}\Omega$ (kilo Ohm) resistor.a) Determine the steady-state output voltage for $n = 1$ written as polar phasor.

$$v_{1,20W,\text{steady-state}}(t) = \text{Magnitude } \boxed{-20.26} \checkmark$$

at angle $\boxed{-90} \checkmark$ ° (Degrees) Volts (negative magnitude and negative angle)b) Determine the steady-state output voltage for $n = 5$ written as polar phasor.

$$v_{5,20W,\text{steady-state}}(t) = \text{Magnitude } \boxed{-0.165} \checkmark$$

at angle $\boxed{11.77} \checkmark$ ° (Degrees) Volts (negative magnitude and positive angle)c) Determine an estimate of the time varying power across the $20\text{ k}\Omega$ (kilo Ohm) resistor based on the voltage from $n = 1$ term only.

$$P_{20W,\text{steady-state}} = \boxed{10.26} \checkmark$$

mW (milli W)

Numeric Answer

a) $v_{1,20W,\text{steady-state}}(t) = -20.2642$ at angle -90° V

b) $v_{5,20W,\text{steady-state}}(t) = -0.1654$ at angle 11.77° V

c) $P_{20W,\text{steady-state}} = 10.266$ mW


Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

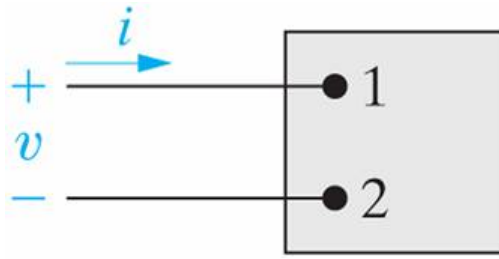

Q9e

The voltage and current at terminals of this network are

$$v(t) = 55 + 120 \cos(300t + 45^\circ) + 40 \sin(900t) \text{ Volts}$$

$$i(t) = 35 + 18 \sin(300t + 75^\circ) + 8 \cos(900t - 15^\circ) \text{ Amps}$$

a) What is the average power at terminals?

$$P = 2506.4 \checkmark$$

W

b) What is the rms value of the voltage of this truncated series?

$$V_{\text{rms}} = 105 \checkmark$$

 V_{rms}

c) What is the rms value of the current of this truncated series?

$$I_{\text{rms}} = 37.67 \checkmark$$

 A_{rms} **Numeric Answer**

a) $P = 2,506.4110 \text{ W}$

b) $V_{\text{rms}} = 105.00 \text{ V}_{\text{rms}}$

c) $I_{\text{rms}} = 37.6696 \text{ I}_{\text{rms}}$

Correct

Marks for this submission: 10.00/10.00.

Question 10

Complete

Mark 4.50 out of 10.00

You created a Bode Diagram of a given transfer function in-class on May 8th. That in-class work will be manually graded and the score entered here on your final exam.

Manual Grading

Comment:

Please review Bode Diagrams. Your in-class work showed some understanding of the Bode concept but with significant conceptual errors.