

Started on Monday, 30 January 2017, 11:21 AM

State Finished

Completed on Friday, 3 February 2017, 1:09 PM


Time taken 4 days 1 hour

Grade 98.75 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

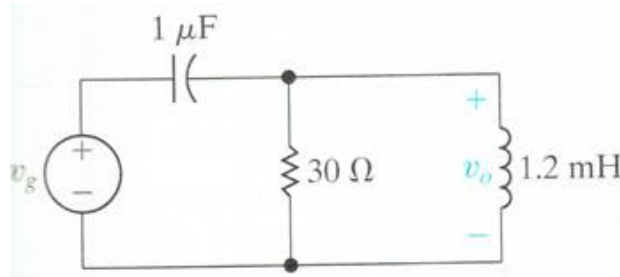

P9.20_7ed

Given: $v_g(t) = 40 \cos(50,000 t)$ Volts

Find the steady-state expression for $v_o(t)$.

$v_{0,\text{steady-state}}(t) =$ ☒ $\cos(50,000 t +$ ☒ $^\circ) \text{ Volts}$

Numeric Answer

$v_{0,\text{steady-state}}(t) = 42.426 \cos(50,000 t + 45^\circ) \text{ Volts}$


Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

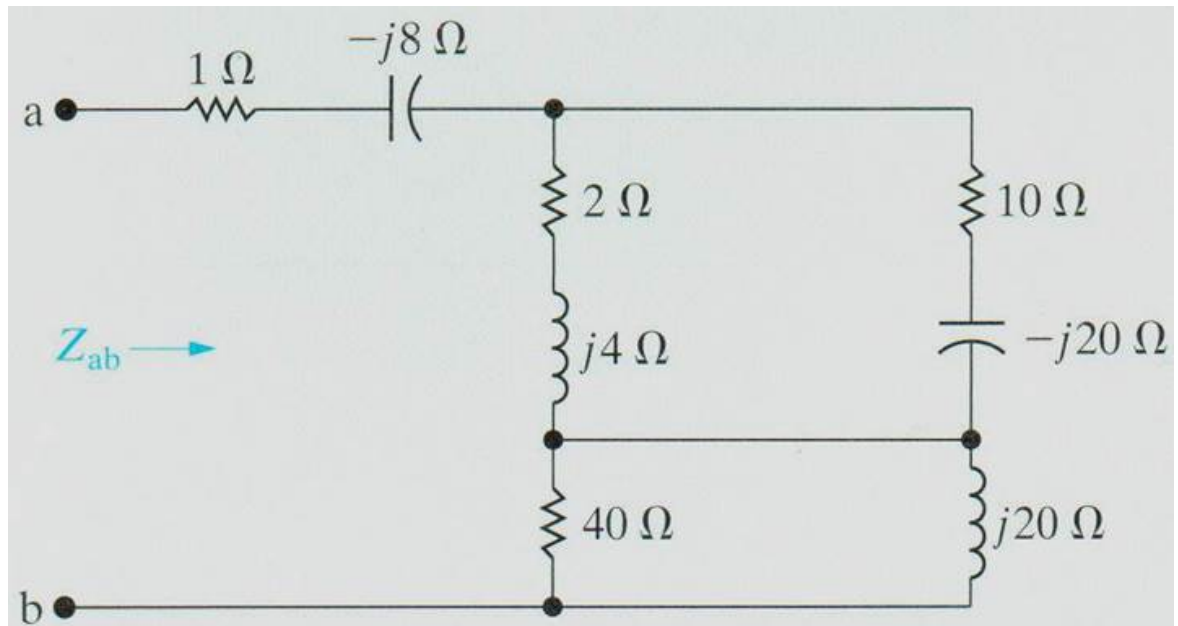

P9.33_7ed


Find the equivalent impedance Z_{ab} at the terminals a,b. $Z_{ab} =$ ✓ $+ j$ ✓ Ω (Ohm)**Numeric Answer** $Z_{ab} = 12.0 + j\ 12.0\ \Omega$ (Ohm)**Correct**

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

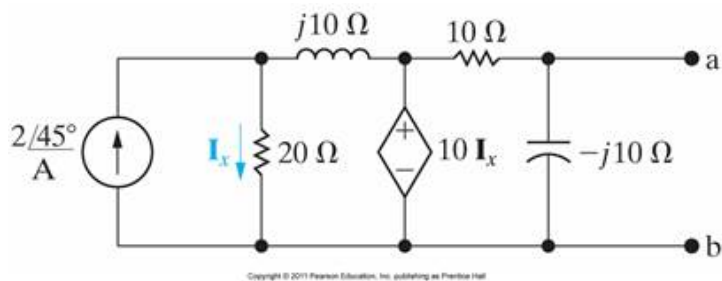

AP9.11_9ed

Find the Thévenin equivalent with respect to terminals a,b.


 V_{Th} = Magnitude ✓ with Angle ✓° (Degrees) Volts Z_{Th} = Magnitude ✓ with Angle ✓° (Degrees) W (Ohm)**Numeric Answer** $V_{Th} = 10\angle 45^\circ$ Volts $Z_{Th} = 7.071\angle -45^\circ$ Ohms**Correct**

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

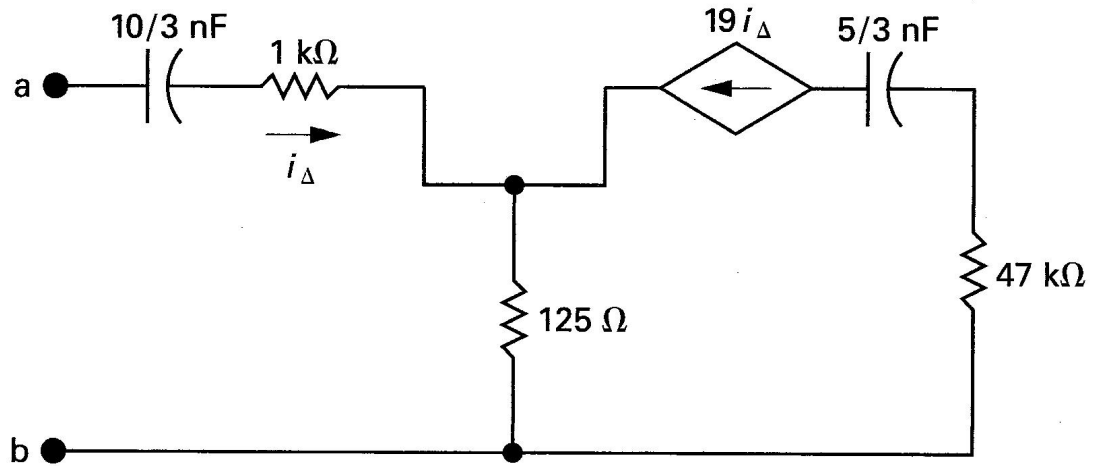

P9.36_6ed

Find the Thévenin impedance seen looking into the terminals ab of this circuit.

The frequency of operation is 25 krad/sec.


 $Z_{Th} =$ ✓ + j ✓ W (Ohm) in rectangular form**Numeric Answer** $Z_{Th} = 3,500 - j 12,000 \text{ W}$ **Correct**

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

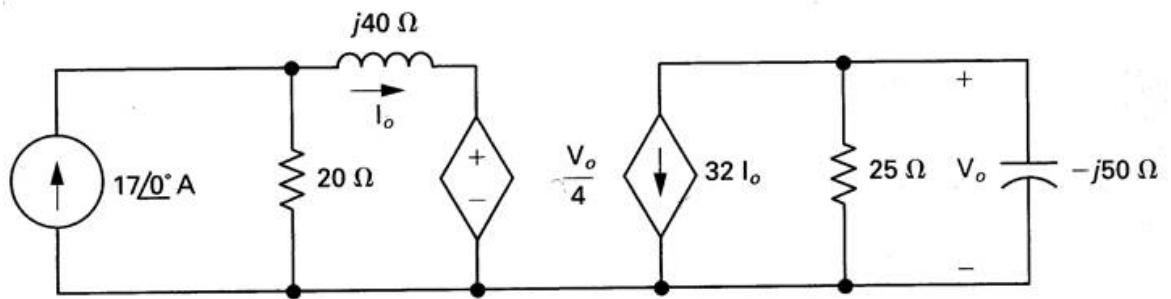

P9.56_6ed

Use the node-voltage method to find the following phasor values.

$$\mathbf{V}_o = \boxed{1280} \checkmark + j \boxed{320} \checkmark \text{ Volts}$$

$$\mathbf{I}_o = \boxed{-1.4} \checkmark + j \boxed{-1.2} \checkmark \text{ Amps}$$

Numeric answer

$$\mathbf{V}_o = 1,280 + j 320 \text{ V} = 1319.394 \angle 14.04^\circ \text{ V}$$

$$\mathbf{I}_o = -1.40 - j 1.20 \text{ A} = 1.844 \angle -139.40^\circ \text{ A}$$


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

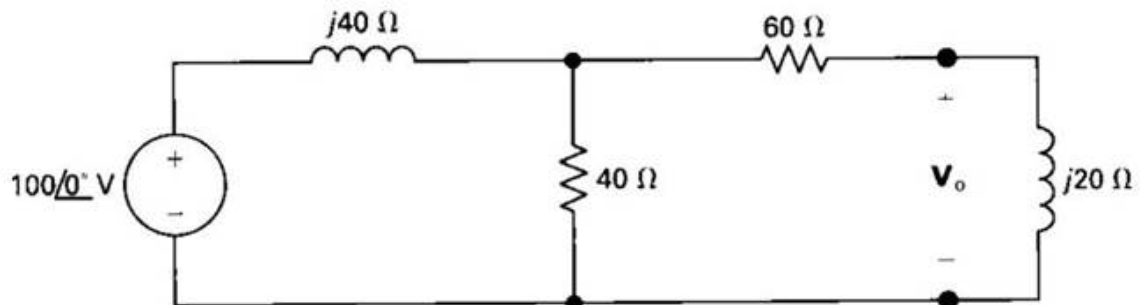

P9.47_6ed

Find \mathbf{V}_o in this circuit.

$$\mathbf{V}_o = \text{Mag } \boxed{15.81} \checkmark \text{ with Angle } \boxed{18.4} \checkmark \text{ Degrees Volts}$$

Numeric answer

$$\mathbf{V}_o = 15.811 \angle 18.43^\circ \text{ Volts}$$


Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

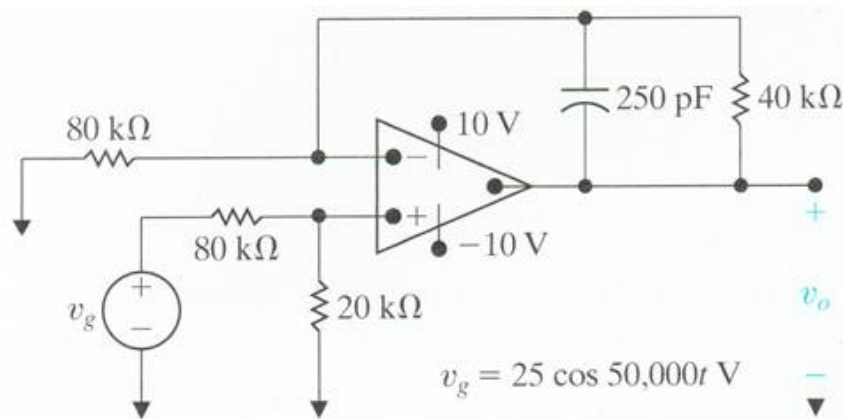

P9.81_7ed

The operational amplifier is ideal.

Given $v_g(t) = 25 \cos(50,000 t)$ Va) Find the steady-state output $v_o(t)$.

$$v_o(t) = 7.054 \cos(50,000 t + -8.14^\circ) \text{ (Degrees) Volts}$$

b) How large can the amplitude of $v_g(t)$ be before the amplifier saturates?

$$|v_o(t)_{\max}| \leq 35.46 \text{ Volts (less than or equal to)}$$


Numeric answera) $v_o(t) = 7.07 \cos(50,000 t - 8.13^\circ)$ Voltsb) $|v_o(t)_{\max}| \leq 35.3557$ Volts**Correct**

Marks for this submission: 10.00/10.00.

Question 8

Partially correct

Mark 8.75 out of 10.00

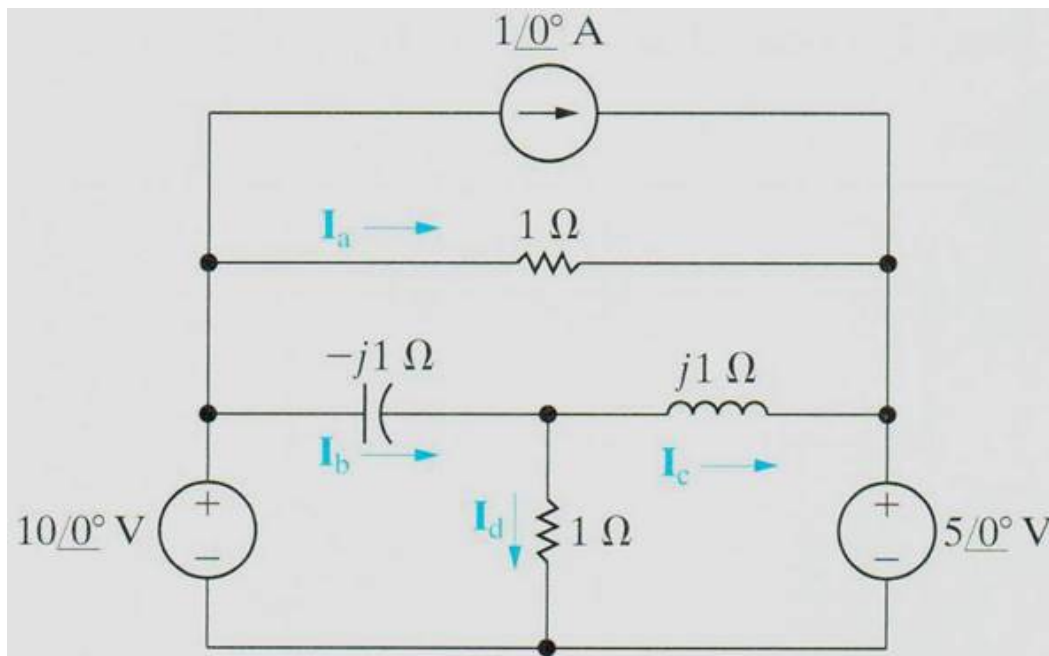

P9.62_7ed

Use the Mesh method and find the following currents:

 I_a = Magnitude ✓ with Angle ✓° (Degrees) Amps I_b = Magnitude ✗ with Angle ✓° (Degrees) Amps I_c = Magnitude ✓ with Angle ✓° (Degrees) Amps I_d = Magnitude ✓ with Angle ✓° (Degrees) Amps**Numeric Answer**

$$I_a = 5 \angle 0^\circ \text{ A}$$

$$I_b = 5 + j 10 \text{ A} = 11.180 \angle 63.43^\circ \text{ A}$$

$$I_c = 5 + j 5 \text{ A} = 7.071 \angle 45.0^\circ \text{ A}$$

$$I_d = 0 + j 5 \text{ A} = 5 \angle 90^\circ \text{ A}$$


Partially correct

Marks for this submission: 8.75/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

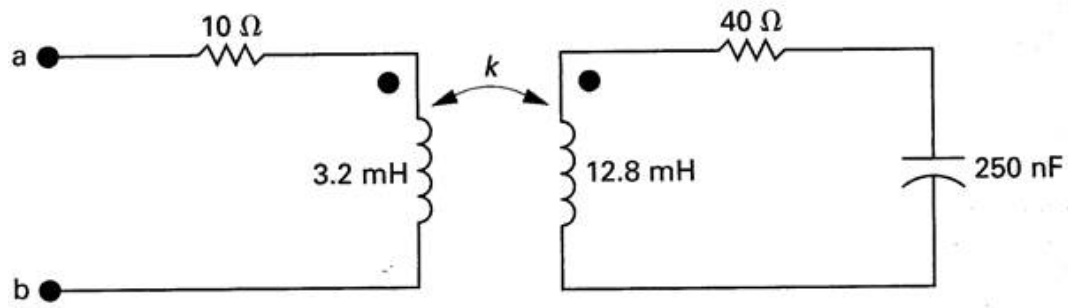

P9.63_6ed

Given driving source frequency = 25 krad/sec.

The coefficient of coupling k is adjusted so that Z_{ab} is purely resistive.Find Z_{ab} for this condition.

$$Z_{ab} = \boxed{30} \text{ } \checkmark \text{ W (Ohm)}$$

Numeric Answer

$$Z_{ab} = 30.0 \text{ W (Ohm)}$$


Correct

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of 10.00

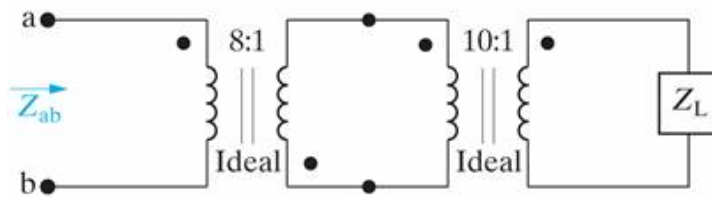Find the impedance Z_{ab} if $Z_L = 80 \angle 60^\circ \text{ W (Ohms)}$.

$$|Z_{ab}| = \boxed{512} \text{ } \checkmark \text{ kW (kilo Ohm)}$$

$$Z_{ab} \text{ angle} = \boxed{60} \text{ } \checkmark \text{ }^\circ \text{ (Degrees)}$$

Numeric Answer

$$Z_{ab} = 512 \angle 60^\circ \text{ kW (kilo Ohm)}$$

Correct

Marks for this submission: 10.00/10.00.