

Started on Sunday, 19 February 2017, 3:40 PM

State Finished

Completed on Sunday, 19 February 2017, 3:54 PM

Time taken 13 mins 28 secs

Grade 94.17 out of 100.00

Question 1



Correct

Mark 10.00 out of
10.00



P11.1_10ed

What is the phase sequence of each of the following sets of voltages?

a) $v_a = 137 \cos(\omega t + 63^\circ) \text{ V}$ $v_b = 137 \cos(\omega t - 57^\circ) \text{ V}$ $v_c = 137 \cos(\omega t + 183^\circ) \text{ V}$

abc – Positive Phase Sequence:  

b) $v_a = 820 \cos(\omega t - 36^\circ) \text{ V}$ $v_b = 820 \cos(\omega t + 84^\circ) \text{ V}$ $v_c = 820 \sin(\omega t - 66^\circ) \text{ V}$

acb – Negative Phase Sequence:  

a) abc – Positive Phase Sequence

b) acb – Negative Phase Sequence


Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

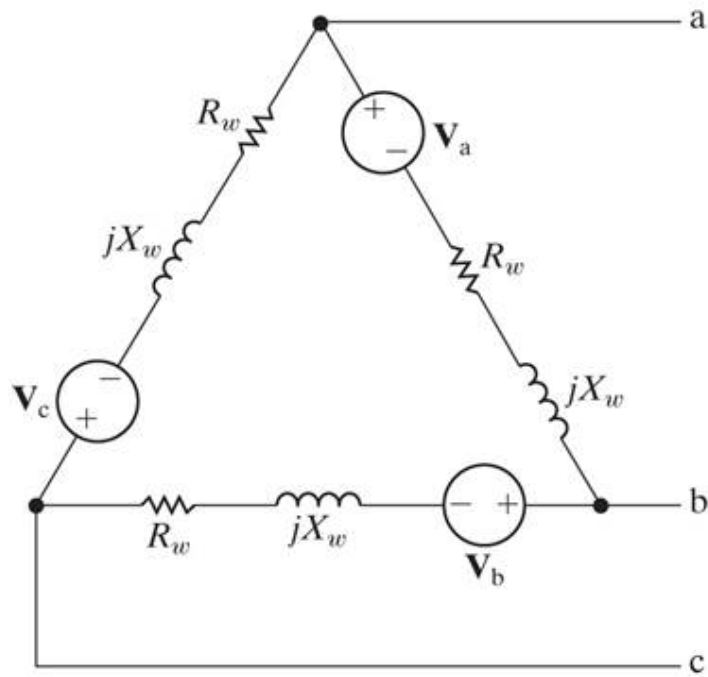

P11.4_10ed

Assume that nodes a,b,c are “open circuited” with no external connections.

Given: $v_a = 188 \cos(\omega t + 60^\circ) \text{ V}$ $v_b = -188 \cos(\omega t) \text{ V}$ $v_c = 188 \cos(\omega t - 60^\circ) \text{ V}$

Determine the current circulating in this Δ -connected generator.

$$I_{\Delta} = \boxed{0} \text{ A}$$

$I_{\Delta} = \text{zero A}$


Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

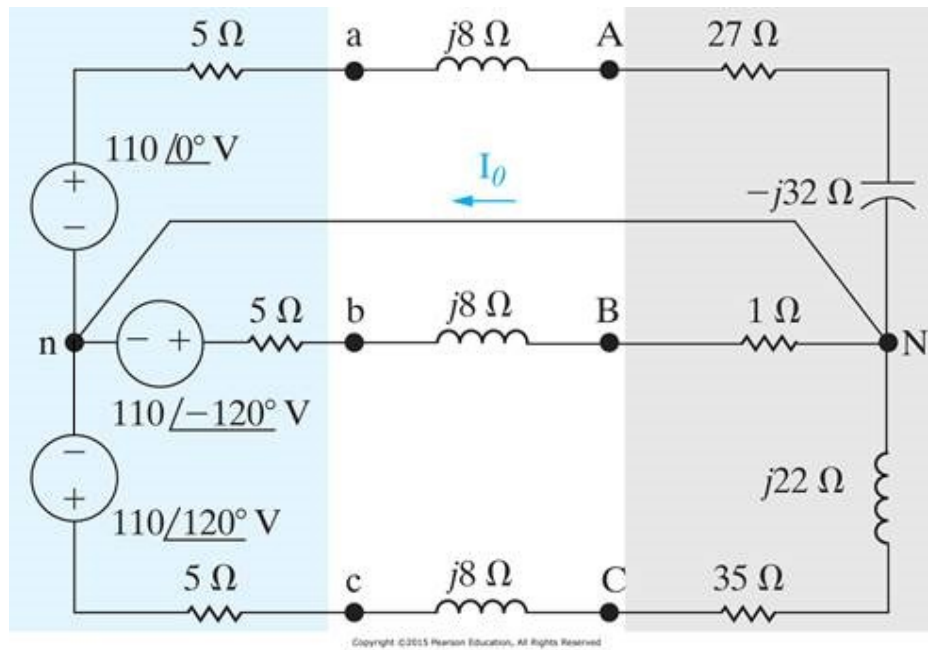

P11.6_10ed

Given that all voltages are rms values.

a) Find the current I_{aA} .

$$I_{aA} = 2.2 + j 1.65 \text{ A}_{\text{rms}}$$

b) Find the current I_{bB} .

$$I_{bB} = -10.92 + j -1.3 \text{ A}_{\text{rms}}$$

c) Find the current I_{cC} .

$$I_{cC} = 0.26 + j 2.18 \text{ A}_{\text{rms}}$$

d) Find the current I_0 as shown in the circuit.

$$I_0 = -8.46 + j 2.52 \text{ A}_{\text{rms}}$$

e) Is this circuit a balanced or unbalanced three-phase system?

Balanced/Unbalanced? **Unbalanced**

a) $I_{aA} = 2.20 + j 1.650 \text{ A}_{\text{rms}}$

b) $I_{bB} = -10.9210 - j 1.3158 \text{ A}_{\text{rms}}$

c) $I_{cC} = 0.2632 + j 2.1842 \text{ A}_{\text{rms}}$

d) $I_0 = -8.4579 + j 2.5184 \text{ A}_{\text{rms}}$

e) The system is unbalanced since the current I_0 does not equal zero.


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

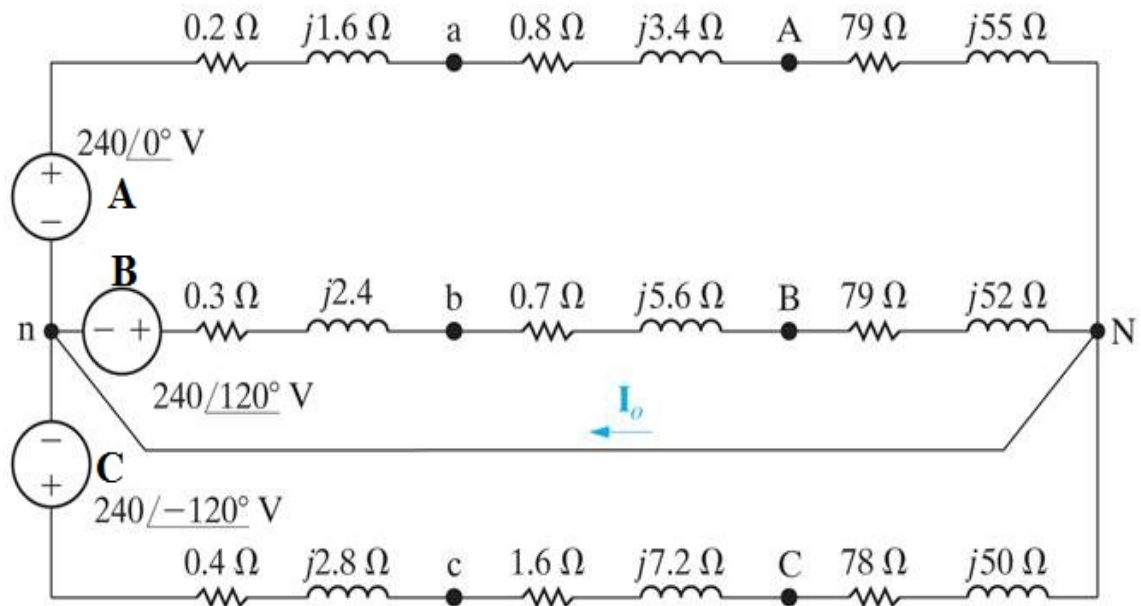

P11.6_8ed

- a) Find the current I_o as shown in the circuit.

$$I_o = 0 \text{ A}$$

- b) Find the voltage V_{AN} .

$$V_{AN} = 230.88 + j -8.14 \text{ V}$$

- c) Find the voltage V_{AB} .

$$V_{AB} = 332.08 + j -211.32 \text{ V}$$

- d) Is this circuit a balanced or unbalanced three-phase system?

Balanced/Unbalanced? **Unbalanced**

Numeric Answer

- a) $I_o = 0 \text{ A}$
 b) $V_{AN} = 230.8804 - j 8.1432 \text{ V}$
 c) $V_{AB} = 332.0867 - j 211.317 \text{ V}$
 d) The system is unbalanced since the voltages V_{AN} , V_{BN} and V_{CN} will not equal zero.


Correct

Marks for this submission: 10.00/10.00.

Question 5

Partially correct

Mark 9.44 out of 10.00

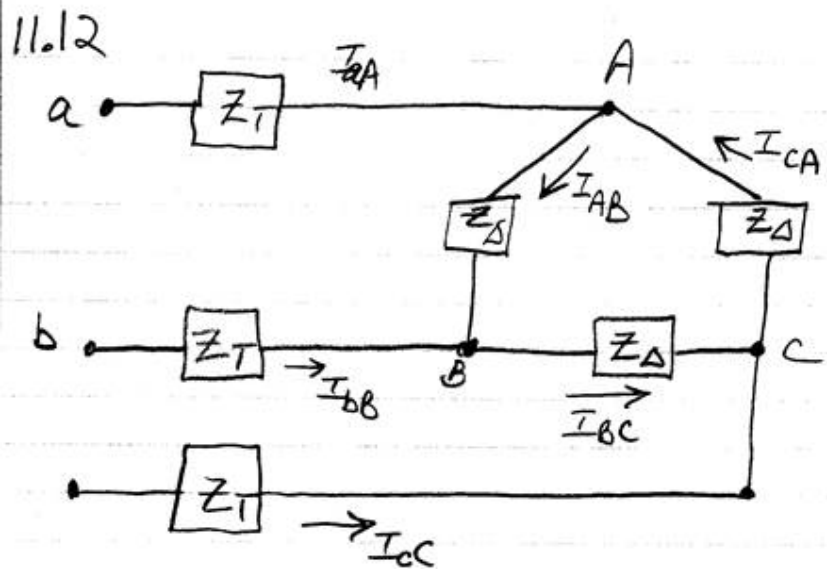

P11.12_8ed

A balanced Δ -connected load has an impedance of $Z_{\Delta} = 360 + j 105 \text{ W/f}$.

The load is fed through a line have an impedance $Z_T = 0.1 + j 1 \text{ W/f}$.

The phase voltage at the terminals of the load is 33 kV.

The phase sequence is positive.

Use \mathbf{V}_{AB} as the zero angle reference.

a) Calculate the three phase currents in the load.

$$\mathbf{I}_{AB} = 84.48 + j -24.64 \text{ A}$$

$$\mathbf{I}_{BC} = -63.58 + j -60.84 \text{ A}$$

$$\mathbf{I}_{CA} = -20.9 + j 85.48 \text{ A}$$

b) Calculate the three line currents.

$$\mathbf{I}_{aA} = 105.38 + j -110.12 \text{ A}$$

$$\mathbf{I}_{bB} = -148.06 + j -36.2 \text{ A}$$

$$\mathbf{I}_{cC} = 42.68 + j 146.32 \text{ A}$$

c) Calculate the three line voltages at the sending end of the line.

$$\mathbf{V}_{ab} = 33120.66 + j -104.22 \text{ V}$$

$$\mathbf{V}_{bc} = -16478.73 + j -28730.44 \text{ V}$$

$$\mathbf{V}_{ca} = -16641.93 + j 28636.22 \text{ V}$$

Numeric Answer

a) $\mathbf{I}_{AB} = 84.48 - j 24.64 \text{ A}$

$$\mathbf{I}_{BC} = -63.5789 - j 60.8418 \text{ A}$$

$$\mathbf{I}_{CA} = -20.9011 + j 85.4818 \text{ A}$$

- b) $I_{aA} = 105.3812 - j 110.1218 \text{ A}$
 $I_{bB} = -148.0589 - j 36.2018 \text{ A}$
 $I_{cC} = 42.6777 + j 146.3237 \text{ A}$
- c) $V_{ab} = 33099.2073 + j 246.0432 \text{ V}$
 $V_{bc} = -16336.563 - j 28787.8438 \text{ V}$
 $V_{ca} = -16762.7226 + j 28541.8004 \text{ V}$


Partially correct

Marks for this submission: 9.44/10.00. Accounting for previous tries, this gives **9.44/10.00**.

Question 6

Partially correct

Mark 7.22 out of 10.00

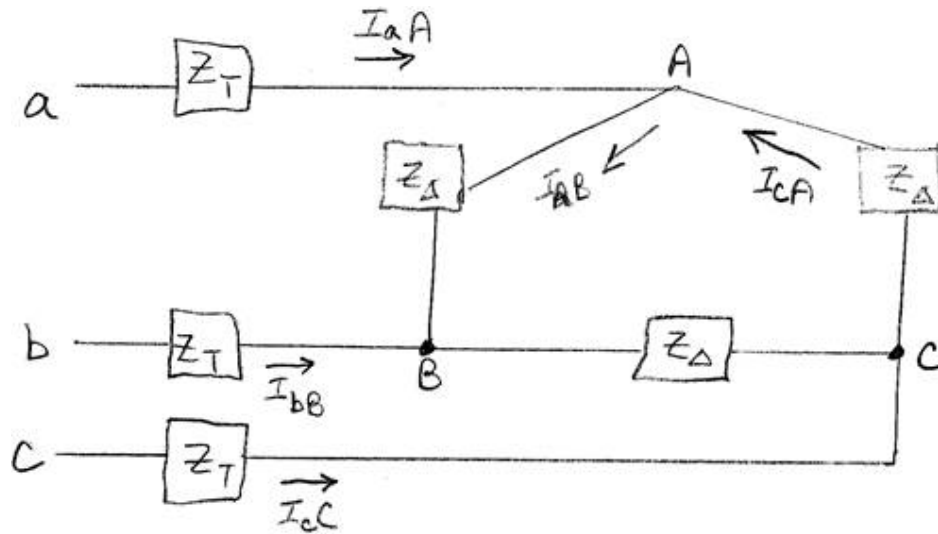

P11.11_7ed

A balanced Δ -connected load has an impedance of $Z_{\Delta} = 60 + j 45 \Omega/\Phi$.

The load is fed through a line have an impedance $Z_T = 0.8 + j 0.6 \Omega/\Phi$.

The phase voltage at the terminals of the load is $|V_{AB}| = 480 \text{ V}_{\text{rms}}$.

The phase sequence is positive.

Use V_{AB} as the zero angle reference.

a) Calculate the three phase currents in the load.

$I_{AB} =$ $+ j$ A_{rms}

$I_{BC} =$ $+ j$ A_{rms}

$I_{CA} =$ $+ j$ A_{rms}

b) Calculate the three line currents.

$I_{aA} =$ $+ j$ A_{rms}

$I_{bB} =$ $+ j$ A_{rms}

$I_{cC} =$ $+ j$ A_{rms}

c) Calculate the three line voltages at the sending end of the line.

$$\mathbf{V}_{ab} = 480 \times + j 0 \checkmark V_{rms}$$

$$\mathbf{V}_{bc} = -480 \times + j 0 \times V_{rms}$$

$$\mathbf{V}_{ca} = 480 \times + j 0 \times V_{rms}$$

a) $\mathbf{I}_{AB} = 5.120 - j 3.840 A_{rms}$

$$\mathbf{I}_{BC} = -5.8855 - j 2.514 A_{rms}$$

$$\mathbf{I}_{CA} = 0.7655 + j 6.3541 A_{rms}$$

b) $\mathbf{I}_{aA} = 4.3545 - j 10.1941 A_{rms}$

$$\mathbf{I}_{bB} = -11.0055 + j 1.3260 A_{rms}$$

$$\mathbf{I}_{cC} = 6.6511 + j 8.8681 A_{rms}$$

c) $\mathbf{V}_{ab} = 499.2001 + j 0 V_{rms}$

$$\mathbf{V}_{bc} = -249.60 - j 432.320 V_{rms}$$

$$\mathbf{V}_{ca} = -249.60 + j 432.320 V_{rms}$$


Partially correct

Marks for this submission: 7.22/10.00. Accounting for previous tries, this gives **7.22/10.00**.

Question 7

Partially correct

Mark 7.50 out of 10.00

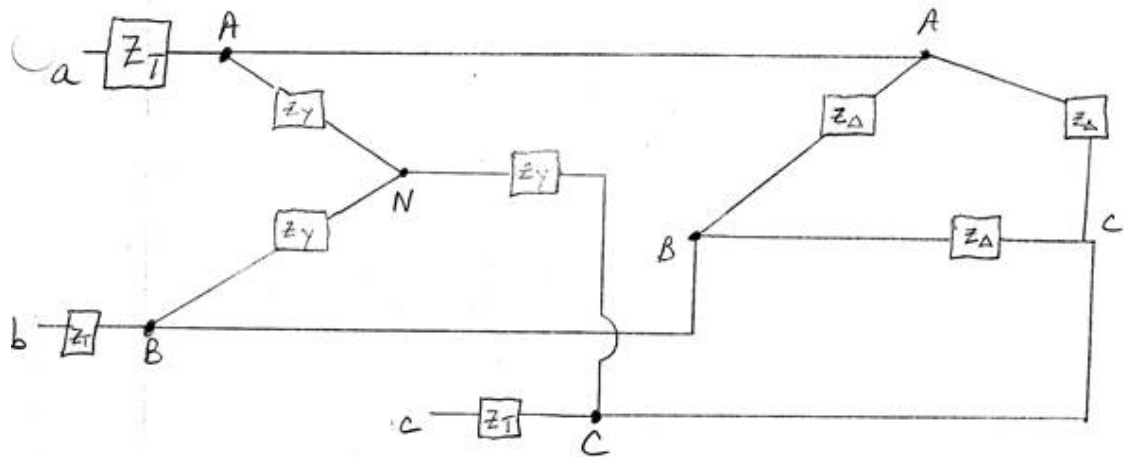

P11.12_7ed

A balanced Y-connected load having an impedance of $Z_Y = 72 + j 21 \Omega/\Phi$ is connected in parallel with a balanced Δ -connected load having an impedance of $Z_{\Delta} = 150 + j 0 \Omega/\Phi$. The parallel loads are fed from a line having an impedance of $Z_T = 0 + j 1 \Omega/\Phi$. The magnitude of the line-to-neutral voltage of the Y-connected load is $7,650 \text{ V}_{\text{rms}}$.

a) Calculate the magnitude of the current in the line feeding the loads.

$$|I_{aA}| = |I_{bB}| = |I_{cC}| = \boxed{252.54} \checkmark \text{ A}_{\text{rms}}$$

b) Calculate the magnitude of the phase current in the Δ -connected load.

$$|I_{AB}| = |I_{BC}| = |I_{CA}| = \boxed{-51} \times \text{ A}_{\text{rms}}$$

c) Calculate the magnitude of the phase current in the Y-connected load.

$$|I_{AN}| = |I_{BN}| = |I_{CN}| = \boxed{102} \checkmark \text{ A}_{\text{rms}}$$

d) Calculate the magnitude of the line-to-line voltages at the sending end of the line.

$$|V_{AB}| = |V_{BC}| = |V_{CA}| = \boxed{13264.38} \checkmark \text{ V}_{\text{rms}}$$

a) $|I_{aA}| = |I_{bB}| = |I_{cC}| = 252.5403 \text{ A}_{\text{rms}}$

b) $|I_{AB}| = |I_{BC}| = |I_{CA}| = 88.3346 \text{ A}_{\text{rms}}$

c) $|I_{AN}| = |I_{BN}| = |I_{CN}| = 102 \text{ A}_{\text{rms}}$

d) $|V_{AB}| = |V_{BC}| = |V_{CA}| = 13306.755 \text{ V}_{\text{rms}}$

Partially correct

Marks for this submission: 7.50/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

P11.13_8ed

A balanced Y-connected load has an impedance of $Z_Y = 96 - j 28 \Omega/\Phi$ is connected in parallel with a balanced Δ -connected load which has an impedance of $Z_\Delta = 144 + j 42 \Omega/\Phi$.

The parallel loads are fed from a (transmission) line having an impedance of $Z_T = 0 + j 1.5 \Omega$ (Ohm).

The magnitude of the line-to-neutral voltage of the Y-connected load is $V_{AN} = 7500$ at angle 0° Volts.

a) Calculate the magnitude of the current in the line feeding the loads.

$$|I_{aA}| = |I_{bB}| = |I_{cC}| = \boxed{217.02} \checkmark \text{ A}$$

b) Calculate the magnitude of the phase current in the D-connected load.

$$|I_{AB}| = |I_{BC}| = |I_{CA}| = \boxed{86.6} \checkmark \text{ A}$$

c) Calculate the magnitude of the phase current in the Wye-connected load.

$$|I_{AN}| = |I_{BN}| = |I_{CN}| = \boxed{75} \checkmark \text{ A}$$

d) Calculate the magnitude of the line voltage at the sending end of the line.

$$|V_{AB}| = |V_{BC}| = |V_{CA}| = \boxed{13057} \checkmark \text{ V}$$

$$a) |I_{aA}| = |I_{bB}| = |I_{cC}| = 217.0184 \text{ A}$$

$$b) |I_{AB}| = |I_{BC}| = |I_{CA}| = 86.6025 \text{ A}$$

$$c) |I_{AN}| = |I_{BN}| = |I_{CN}| = 75.0 \text{ A}$$

$$d) |V_{AB}| = |V_{BC}| = |V_{CA}| = 13,0571.0059 \text{ V}$$

Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

P11.23_8ed

The total apparent power supplied in a balanced three-phase Y- Δ system is 3,600 VA. The load line-to-line voltage is $208 V_{rms}$. If the line impedance is negligible and the power factor angle of the load is 25° , determine the impedance of the load.

$$Z_{load,\Delta} = \boxed{32.67} \checkmark + j \boxed{15.23} \checkmark \Omega \text{ (Ohms)}$$

$$Z_{load,\Delta} = 32.6754 + j 15.2367 \Omega \text{ (Ohms)}$$

Correct

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of
10.00

P11.22_8ed

A balanced three-phase source is supplying 90 kVA at 0.8 lagging to two balanced Y-connected parallel loads. The distribution line connecting the source to the load has negligible impedance. Load 1 is purely resistive and absorbs 60 kW. Find the per-phase impedance of load 2 if the line voltage is 415.69 V_{rms} and the impedance components are in series.

$$Z_{\text{load},2} = 0.678 + j 3.05 \text{ W (Ohms)}$$

$$Z_{\text{load},2} = 0.6776 + j 3.0494 \text{ W (Ohms)}$$

Correct

Marks for this submission: 10.00/10.00.