

Started on Monday, 15 May 2017, 10:11 AM

State Finished

Completed on Monday, 15 May 2017, 11:18 AM


Time taken 1 hour 6 mins

Grade 90.00 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

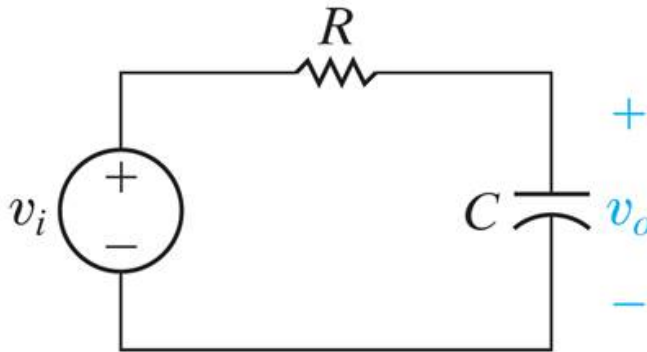

Q1b

Given: $C = 347 \text{ nF}$ (nano F) $R = 2.4 \text{ k}\Omega$ (kilo Ohm)

a) Write the parameters of the transfer function $H(s)$.

$$H(s) = V_o / V_i = \boxed{1200.76} \checkmark / (s + \boxed{1200.76} \checkmark)$$

b) Calculate the cutoff frequency ω_c in rad/sec and f_c in Hz.

$$\omega_c = \boxed{1200.76} \checkmark \text{ rad/sec} \quad f_c = \boxed{191.205} \checkmark \text{ Hz}$$

c) State the phase angle of the output voltage when fully in the passband region where $\omega \ll \omega_c$.

$$\theta(\text{pass band}) = \boxed{0} \checkmark^\circ \text{ (Degrees)}$$

d) State the phase angle of the output voltage at the corner frequency ω_c .

$$\theta(\omega_c) = \boxed{-45} \checkmark^\circ \text{ (Degrees)}$$

e) State the phase angle of the output voltage when fully in the stopband region where $\omega \gg \omega_c$.

$$\theta(\text{stop band}) = \boxed{-90} \checkmark^\circ \text{ (Degrees)}$$

f) Identify the filter type of this circuit.

Filter Type = Low Pass ↕ ✓


Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

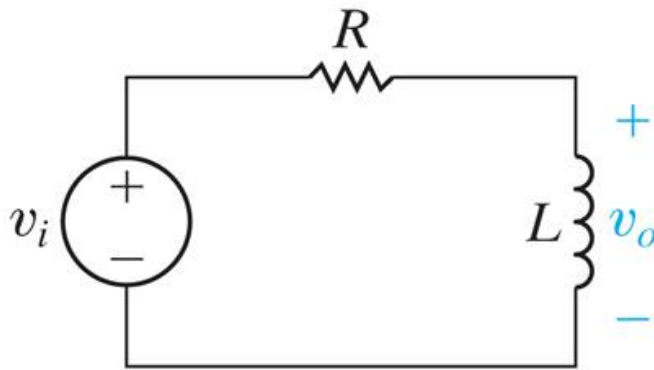

Q2a

Given: $L = 1 \text{ mH}$ (milli H) $R = 10 \Omega$ (Ohm)a) Write the parameters of the transfer function $H(s)$.

$$H(s) = V_o / V_i = s / (s + \boxed{10000}) \checkmark$$

b) Calculate the cutoff frequency ω_c in rad/sec and f_c in Hz.

$$\omega_c = \boxed{10000} \checkmark \text{ rad/sec} \quad f_c = \boxed{1592.35} \checkmark \text{ Hz}$$

c) State the phase angle of the output voltage when fully in the passband region where $\omega \gg \omega_c$.

$$\theta(\text{pass band}) = \boxed{0} \checkmark^\circ \text{ (Degrees)}$$

d) State the phase angle of the output voltage at the corner frequency $\omega = \omega_c$.

$$\theta(\omega_c) = \boxed{45} \checkmark^\circ \text{ (Degrees)}$$

e) State the phase angle of the output voltage when fully in the stopband region where $\omega \ll \omega_c$.

$$\theta(\text{stop band}) = \boxed{90} \checkmark^\circ \text{ (Degrees)}$$

f) Identify the filter type of this circuit.


Filter Type = High Pass ↕ ✓**Correct**

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

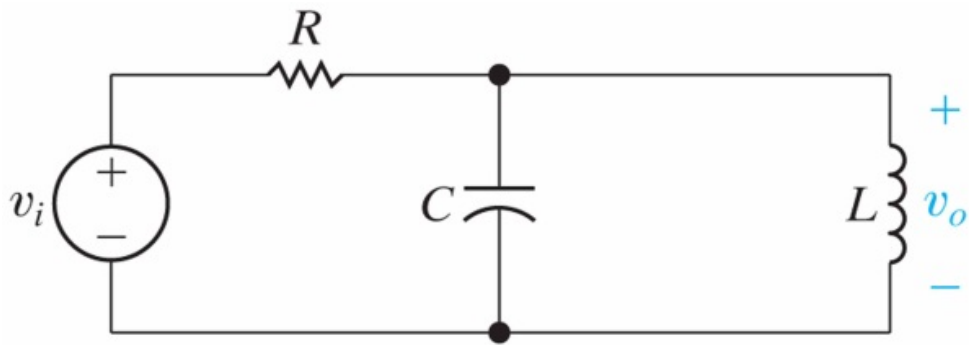

Q3Pa

Given: $R = 160 \, \Omega$ (Ohm) $C = 5 \, \mu\text{F}$ (micro F) $L = 203 \, \mu\text{H}$ (micro H)a) Find the resonant frequency ω_0 .

$$\omega_0 = 31388 \, \checkmark \text{ rad/sec}$$

b) Find the lower half-power frequency ω_{c1} .

$$\omega_{c1} = 30763 \, \checkmark \text{ rad/sec}$$

c) Find the upper half-power frequency ω_{c2} .

$$\omega_{c2} = 32013 \, \checkmark \text{ rad/sec}$$

d) Find the bandwidth β (Beta).

$$\beta = 1250 \, \checkmark \text{ rad/sec}$$

e) Find the quality factor Q .

$$Q = 25.11 \, \checkmark$$

f) Identify the filter type of this circuit.


Filter Type = Band Pass \checkmark **Correct**

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

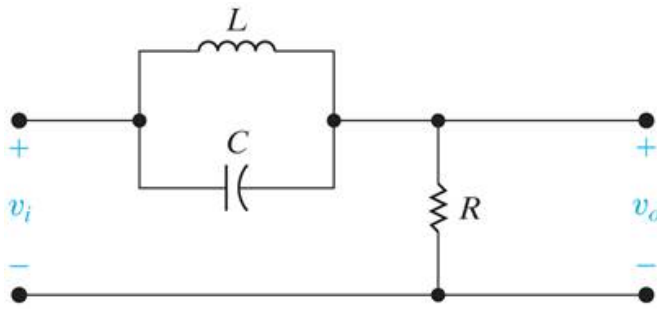

Q4Pc

Given: $R = 750 \, \Omega$ (Ohm) $C = 40 \, \text{nF}$ (nano F) $L = 150 \, \mu\text{H}$ (micro H)a) Calculate ω_0 .

$$\omega_0 = 408 \, \checkmark \text{ krad/sec (kilo rad/sec)}$$

b) Calculate f_0 .

$$f_0 = 65 \, \checkmark \text{ kHz (kilo Hz)}$$

c) Find ω_{c1} .

$$\omega_{c1} = 392 \, \checkmark \text{ krad/sec (kilo rad/sec)}$$

d) Find ω_{c2} .

$$\omega_{c2} = 425 \, \checkmark \text{ krad/sec (kilo rad/sec)}$$

e) Find β (Beta).

$$\beta = 33 \, \checkmark \text{ krad/sec (kilo rad/sec)}$$

f) Find Q .

$$Q = 12.36 \, \checkmark$$


g) Identify the filter type of this circuit.

Filter Type = **Band Reject** \checkmark **Correct**

Marks for this submission: 10.00/10.00.

Question 5

Correct

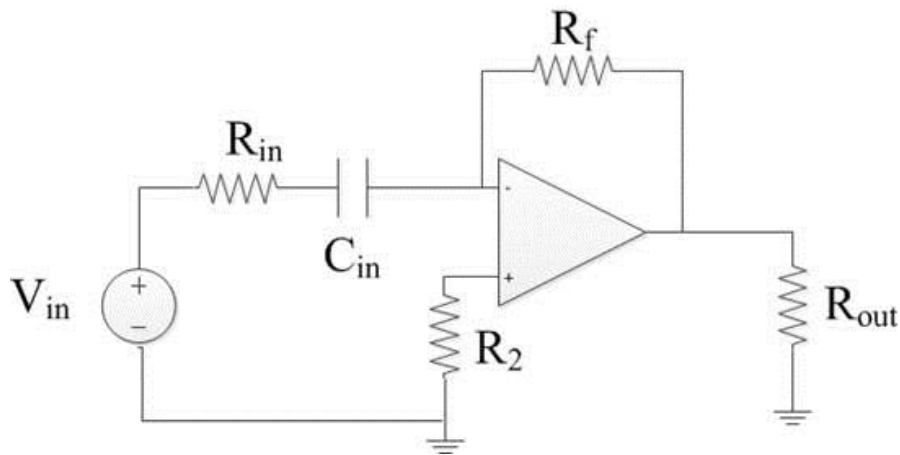Mark 10.00 out of
10.00

Q5b

Given: $V_{in} = 20 \cos(2,000t)$ Volts $R_{in} = 20 \text{ k}\Omega$ (kilo Ohm) $C_{in} = 0.1 \text{ }\mu\text{F}$ (micro F) $R_f = 10 \text{ k}\Omega$ (kilo Ohm) $R_{out} = 1 \text{ k}\Omega$ (kilo Ohm) $R_2 = 10 \text{ }\Omega$ (Ohm)

The opamp has power input rails at +15V and -15V.

Find the steady-state output voltage v_{out} which is the voltage across the resistor R_{out} .

$$v_{out} = 9.7 \checkmark \cos(2,000t + 194 \checkmark^\circ \text{ (Degrees) Volts}$$

State the phase angle as a positive angle (counterclockwise from the origin) in the correct quadrant.


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

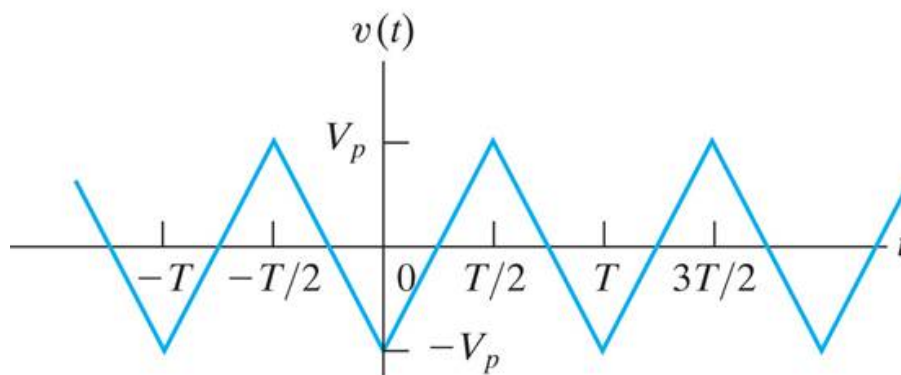

Q6b

Given: The Fourier coefficients for this waveform are

$$a_v = 0 \text{ V} \quad a_n = -8V_p / (n\pi)^2 \text{ Volts for } n \text{ odd} \quad b_n = 0 \text{ V}$$

$$V_p = 50 \text{ V} \quad T = 5 \text{ ms (milli sec)}$$

Write the following terms of this waveform's Fourier series.

a) What is the average value?

$$\text{Avg} = 0 \text{ Volts}$$

Answers for the next two questions are in the order of magnitude, identify cosine or sine and the frequency of the sinusoid in radians/sec.

b) Write the expression for $n = 1$.

$$v_1(t) = 40.53 \text{ cosine } (1256.64 \text{ t) Volts}$$

c) Write the expression for $n = 5$.

$$v_5(t) = 1.62 \text{ cosine } (6283.9 \text{ t) Volts}$$

Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

Q7c

Given the “normal” trigonometric form of the Fourier series coefficients for a waveform are

$$a_{\text{avg}} = \text{zero} \quad a_n = -20/n^2 \quad b_n = 15/n$$

Determine the coefficients for the Alternative trigonometric form of the Fourier series in the polar form

$$a_n - jb_n = A_n \angle -\theta_n \quad (\text{Magnitude } A_n \text{ at angle } -\theta_n)$$

a) For the first term in the summation where $n = 1$:

$$A_1 = 25 \text{ Volts}$$

$$-\theta_1 (\text{Theta } 1) = -143.13^\circ \text{ (Degrees, angle CW from origin)}$$

b) For the second term in the summation where $n = 2$:

$$A_2 = 9 \text{ Volts}$$

$$-\theta_2 (\text{Theta } 2) = -123.69^\circ \text{ (Degrees, angle CW from origin)}$$

c) For the second term in the summation where $n = 3$:

$$A_3 = 5.5 \text{ Volts}$$

$$-\theta_3 (\text{Theta } 3) = -114^\circ \text{ (Degrees, angle CW from origin)}$$

CW = Clock-wise

Note that the angle also includes the “-” sign as shown in the polar form.


Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

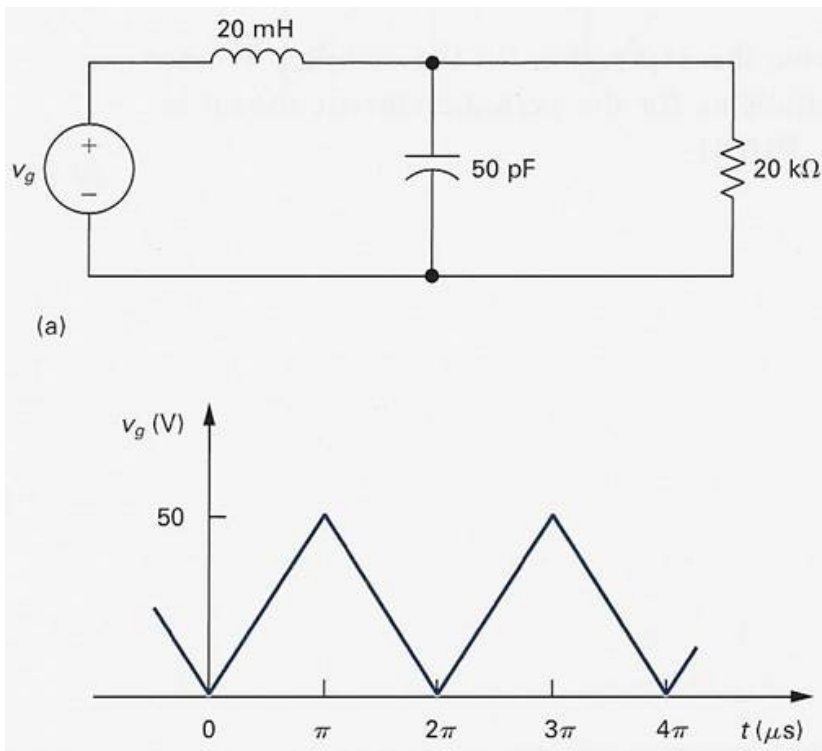

Q8

The triangular-wave voltage source is applied to this circuit.

The Fourier series of this input waveform is

$$v(t) = 25 - \frac{200}{\pi^2} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \cos(n\omega_0 t)$$

The s domain transfer function of the circuit is

$$H(s) = \frac{10^{12}}{s^2 + s10^6 + 10^{12}}$$

The desired output is the voltage across the $20\text{ k}\Omega$ (kilo Ohm) resistor.

a) Determine the steady-state output voltage for $n = 1$ written as polar phasor.

$v_{1,20W,\text{steady-state}}(t)$ = Magnitude ✓ at angle ✓ ° (Degrees) Volts (negative magnitude and negative angle)

b) Determine the steady-state output voltage for $n = 5$ written as polar phasor.

$v_{5,20W,\text{steady-state}}(t)$ = Magnitude ✓ at angle ✓ ° (Degrees) Volts (negative magnitude and positive angle)

c) Determine an estimate of the time varying power across the $20\text{ k}\Omega$ (kilo Ohm) resistor based on the voltage from $n = 1$ term only.


$P_{20W,\text{steady-state}}$ = ✓ mW (milli W)

Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

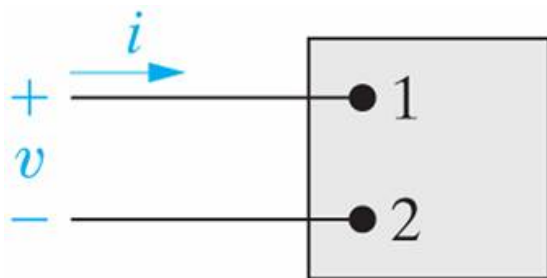Mark 10.00 out of
10.00

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

Q9b

The voltage and current at terminals of this network are

$$v(t) = 70 + 200 \sin(500t + 45^\circ) + 60 \cos(1,500t) \text{ Volts}$$

$$i(t) = 8 + 6 \cos(500t + 75^\circ) + 3 \sin(1,500t - 30^\circ) \text{ Amps}$$

a) What is the average power at terminals?

$$P = 215 \checkmark \text{ W}$$

b) What is the rms value of the voltage of this truncated series?

$$V_{\text{rms}} = 163.4 \checkmark \text{ V}_{\text{rms}}$$

c) What is the rms value of the current of this truncated series?

$$I_{\text{rms}} = 9.298 \checkmark \text{ A}_{\text{rms}}$$

Correct

Marks for this submission: 10.00/10.00.

Question 10

Not answered

Marked out of
10.00

You created a Bode Diagram of a given transfer function in-class on May 8th. That in-class work will be manually graded and the score entered here on your final exam.