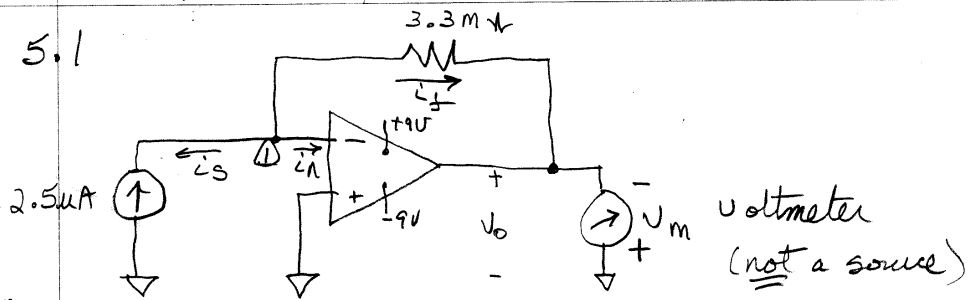


Chapter 5 The Operational Amplifier – Homework SolutionsJames W. Nilsson and Susan A. Riedel, *Electric Circuits*, 6th Edition, 2001

Problems 1, 2, 3, 10 part a only, 16 and 21

- 1 $V_m = 8.25 \text{ V}$
- 2 $i_L = -200 \text{ } \mu\text{A}$
- 3 a) $V_o = -12 \text{ V}$
 b) $V_o = -18 \text{ V}$
 c) $V_o = 10 \text{ V}$
 d) $V_o = -14 \text{ V}$
 e) $V_o = 18 \text{ V}$
 f) $2.8 \text{ V} \leq V_a \leq 7.3 \text{ V}$
- 10 a) $V_o = -2.4 \text{ V}$
- 16 a) $i_L = 2 \text{ mA}$
 b) $R_L = 3 \text{ k}\Omega \text{ max}$
 c) Hint – is the op-amp in saturation?
- 21 a) $V_o = V_s [(R_2 + R_1)/R_1]$
 b) $V_o = V_s$
 c) No hint

5.1



① Assume ideal op-amp

$$i_p = i_n = 0 \quad \text{and} \quad v_p = v_n$$

② note $v_o = -v_m$ (look at references on circuit)find v_m

I have drawn all currents away from node ①

$$i_s + i_n + \frac{v_n - v_o}{R_f} = 0$$

 i_s reference was away from node but indep

$$i_s - \frac{v_o}{R_f} = 0$$

current source is "into"


thus $i_s = -2.5 \mu A$

$$v_o = i_s R_f = (-2.5 \mu A)(3.3 M\Omega) = -8.25 V$$

$$v_m = -v_o = \underline{\underline{8.25 V}}$$

less than negative power supply

5.2

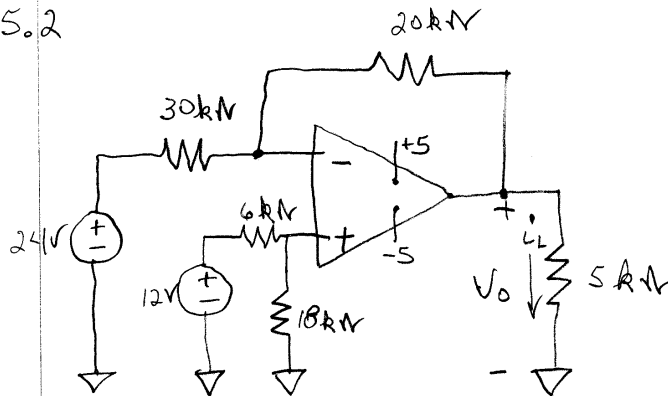

① V_o is not dependent on R_L , thus op-amp sets V_o and then R_L determines i_L

② $v_p = v_n$ but $v_p \neq 0$ it is set by voltage divider.

$$v_p = \frac{18k\Omega}{(6k + 18k)\Omega} 12V = 9.0V = v_n$$

at inverting node ($v_n \neq 0$!)


$$\frac{v_n - 24V}{30k\Omega} + \frac{v_n - V_o}{20k\Omega} = 0$$

$$\frac{9V - 24V}{30k\Omega} + \frac{9V - V_o}{20k\Omega} \Rightarrow V_o = 20k\Omega \left(\frac{-18V}{30k\Omega} + \frac{9V}{20k\Omega} \right)$$

$$V_o = -1V = i_L R_L = i_L (5k\Omega)$$

$$i_L = \frac{-1V}{5k\Omega} = -0.2 \times 10^{-3} A = \underline{\underline{-200\mu A}}$$

5.3

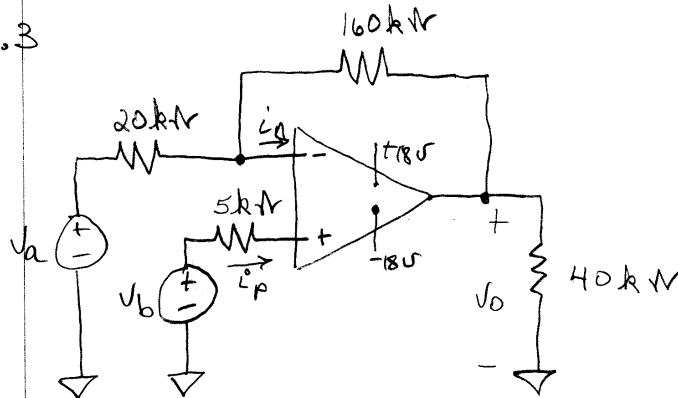

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS

Note $i_p = i_n = 0$ thus $V_p = V_b = V_n$

a) find V_o for $V_a = 1.5\text{ V}$ & $V_b = 0\text{ V}$ (solution is general form of inverting op-amp)

$$V_o = -\frac{R_f}{R_s} V_s = -\frac{160\text{ k}\Omega}{20\text{ k}\Omega} (1.5\text{ V}) = \underline{\underline{-12\text{ V}}}$$

b) find V_o for $V_a = 3.0\text{ V}$ & $V_b = 0$

$V_o = -8(3\text{ V}) = -24\text{ V}$ but outside linear region!
so op-amp in saturation

$$\underline{\underline{V_o = -18\text{ V}}}$$

c) find V_o for $V_a = 1.0\text{ V}$ & $V_b = 2.0\text{ V} = V_n$

$$\frac{V_n - V_a}{20\text{ k}\Omega} + i_n + \frac{V_n - V_o}{160\text{ k}\Omega} = 0 \Rightarrow V_o = +160\text{ k}\Omega \left(\frac{V_n - V_a}{20\text{ k}\Omega} + \frac{V_n}{160\text{ k}\Omega} \right)$$

$$V_o = +160\text{ k}\Omega \left(\frac{2\text{ V} - 1\text{ V}}{20\text{ k}\Omega} + \frac{2\text{ V}}{160\text{ k}\Omega} \right) = \underline{\underline{+10\text{ V}}}$$

5.3 continued

d) find V_o for $V_a = 4V$ & $V_b = 2V$ $= V_n$
use eqn from part c)

$$V_o = 160k\Omega \left(\frac{2V - 4V}{20k\Omega} + \frac{2V}{160k\Omega} \right) = \underline{\underline{-14V}}$$

e) find V_o for $V_a = 6V$ & $V_b = 8V$

$$V_o = 160k\Omega \left(\frac{8V - 6V}{20k\Omega} + \frac{8V}{160k\Omega} \right) = 24V \quad \text{not possible!}$$

op-amp in saturation

so

$$\underline{\underline{V_o = 18V}}$$

f) Given $V_b = 4.5V$ find V_a for linear operation of op-amp
again note $V_b = V_n$

$$\frac{V_b - V_a}{20k\Omega} + \frac{V_b - V_o}{160k\Omega} = 0 \Rightarrow V_o = 9V_b - 8V_a$$

limits of V_o are $\pm 18V$

so

$$-18V \leq 9V_b - 8V_a \leq 18V$$

$$-18V \leq 9(4.5V) - 8V_a \leq 18V$$


$$-18V \leq 40.5V - 8V_a \leq 18V$$

$$-58.5 \leq -8V_a \leq -22.5$$

$$7.3125 \leq V_a \leq 2.8125$$

thus
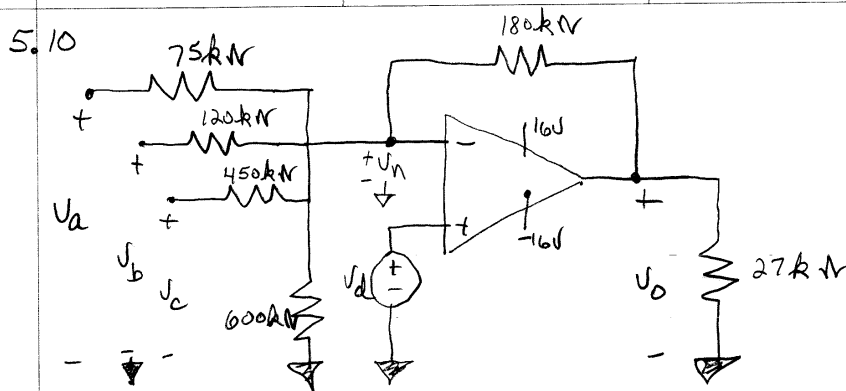
$$\underline{\underline{2.8125V \leq V_a \leq 7.3125V}}$$



a) find V_o for $V_a = 18V$

$$V_b = 6V$$

$$V_c = -15V$$

$$V_d = 8V = V_p = V_n$$

Treat $600k\Omega$ branch as
a 4th summing at zero
volts


$$\frac{V_n - V_a}{75k\Omega} + \frac{V_n - V_b}{120k\Omega} + \frac{V_n - V_c}{450k\Omega} + \frac{V_n - 0}{600k\Omega} + \frac{V_n - V_o}{180k\Omega} = 0$$

in the above eqn - the only unknown is V_o

$$V_o = 180k\Omega \left(\frac{8V - 18V}{75k\Omega} + \frac{8V - 6V}{120k\Omega} + \frac{8V - (-15V)}{450k\Omega} + \frac{8V}{600k\Omega} + \frac{8V}{180k\Omega} \right)$$

$$V_o = -2.4V$$

5.16

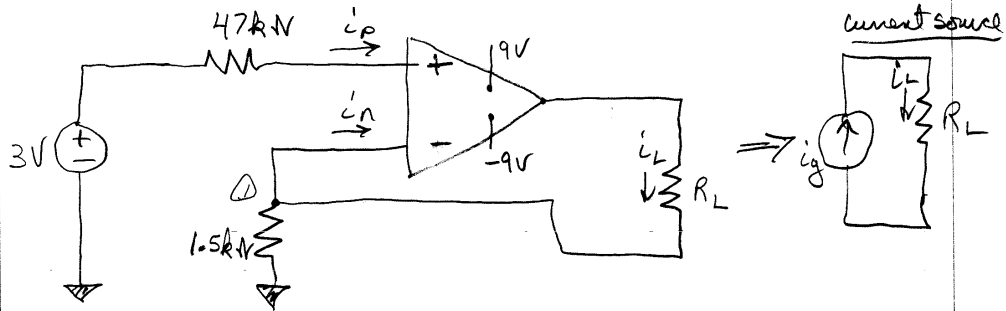

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



a) find i_L for $R_L = 2.5k\Omega$

$$V_P = 3V = V_N$$

at node ①

$$\frac{V_N - 0}{1.5k\Omega} + i_N + (-i_L) = 0$$

$$i_L = \frac{V_N}{1.5k\Omega} = \frac{3V}{1.5k\Omega} = \underline{\underline{2mA}}$$

b) if $i_L = 2mA$ then find max R_L

$$V_O = i_L (R_L + 1.5k\Omega) \quad \text{where } V_O \leq 9V$$

$$R_L = \frac{V_O}{i_L} - 1.5k\Omega = \frac{9V}{2mA} - 1.5k\Omega = 4.5k\Omega - 1.5k\Omega$$

$$\underline{\underline{R_L = 3.0k\Omega \text{ max}}}$$

5.16 continued

c) given $R_L = 6.5 \text{ k}\Omega$. Explain the operation of the circuit.

since $R_L > 3 \text{ k}\Omega$ op-amp is in saturation $\rightarrow \underline{V_O = 9 \text{ V}}$

$$i_L = \frac{V_O}{(1.5 + 6.5) \text{ k}\Omega} = \frac{9 \text{ V}}{8 \text{ k}\Omega} = \underline{\underline{1.125 \text{ mA}}}$$

Note The following discussion is to show the "ideal op-amp" model is quite good.

The above results are valid only if $i_P = i_N = 0$.

or equivalently $i_P = i_N \ll i_L$

if we assume ① $i_P \rightarrow 0$ is current thru $47 \text{ k}\Omega$ resistor is negligible.

and ② $R_{in} \geq 500 \text{ k}\Omega$ (Typically $R_{in} \geq 1 \text{ M}\Omega$ for real op-amps)

$$V_N = i_L (1.5 \text{ k}\Omega) = (1.125 \text{ mA}) (1.5 \text{ k}\Omega) = 1.6875 \text{ V}$$


$$\text{thus } i_P = i_N = \left(\frac{V_P - V_N}{R_{in}} \right) = \frac{3 \text{ V} - 1.6875 \text{ V}}{500 \text{ k}\Omega}$$

$$= 2.6 \mu\text{A} = 2.6 \times 10^{-6} \text{ A} \quad \begin{array}{l} V_P = 3 \text{ V} - (2.6 \mu\text{A}) (47 \text{ k}\Omega) \\ = 2.9 \text{ V} \end{array}$$

thus our assumption $i_P = i_N = 0$ is quite good!!

or equally $\underline{\underline{i_P = i_N \ll i_L}}$

5.21

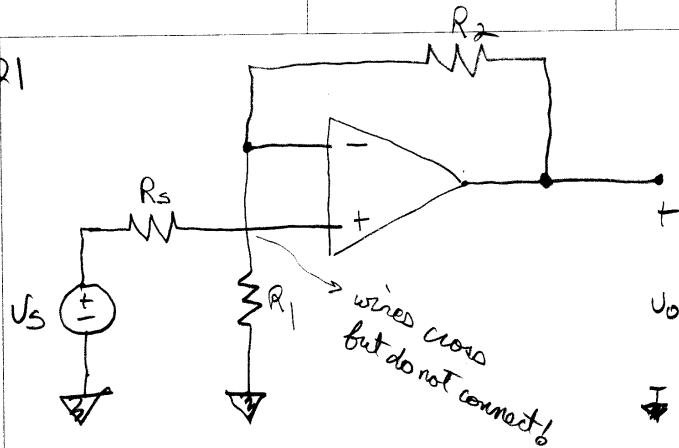

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS
ANTPAD

a) Show $V_o = \frac{R_1 + R_2}{R_1} V_s$

at node U_n

$$I_n + \frac{U_n - 0}{R_1} + \frac{U_n - V_o}{R_2} = 0 \quad \text{but } U_n = U_p = V_s$$

$$\frac{V_s - 0}{R_1} + \frac{V_s - V_o}{R_2} = 0 \Rightarrow V_s \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_o}{R_2}$$

$$V_o = V_s \left(\frac{R_2 + R_1}{R_1 R_2} \right) R_2 = \underline{\underline{V_s \left(\frac{R_2 + R_1}{R_1} \right)}}$$


b) What happens as $R_1 \rightarrow \infty$ & $R_2 \rightarrow 0$

$$\frac{R_2 + R_1}{R_1} \rightarrow 1$$

thus $V_o = V_s$ ie voltage follower

5.21 continued

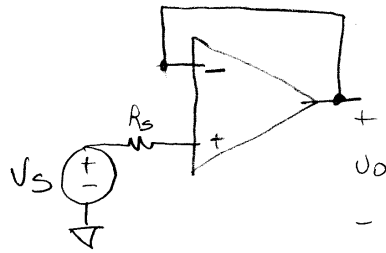
- c) when $R_1 = \infty$ & $R_2 = 0$
we have this circuit



$$\left. \begin{array}{l} \text{thus } V_n = V_p = V_s \\ \& V_n = V_o \end{array} \right\} V_o = V_s \text{ as found in part b)}$$

So up to the limit of the positive power supply voltage
 V_{out} will "follow" V_s .

5.25

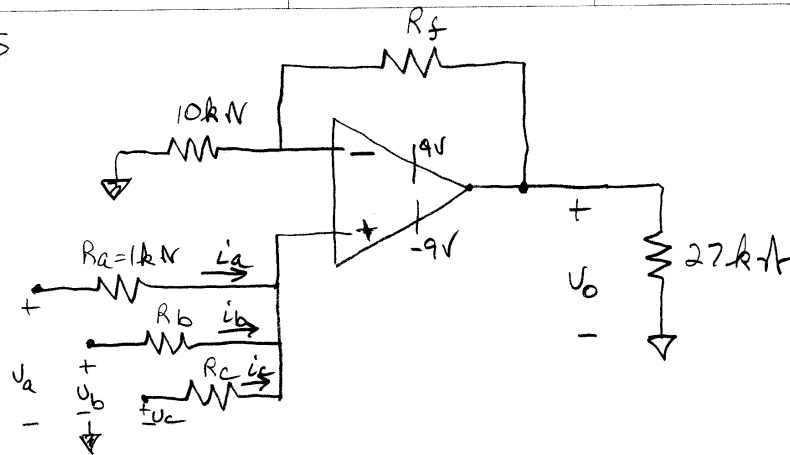

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



Design the circuit so that $U_o = 5U_a + 4U_b + U_c$

a) find R_b , R_c & R_f

start by writing the node equations at U_p and then at U_n

$$\frac{U_p - U_a}{R_a} + \frac{U_p - U_b}{R_b} + \frac{U_p - U_c}{R_c} = 0$$

$$U_p \left(\frac{1}{R_a} + \frac{1}{R_b} + \frac{1}{R_c} \right) = \frac{U_a}{R_a} + \frac{U_b}{R_b} + \frac{U_c}{R_c}$$

$$U_p = \left(\frac{U_a}{R_a} + \frac{U_b}{R_b} + \frac{U_c}{R_c} \right) \left(\frac{R_a R_b R_c}{R_b R_c + R_a R_c + R_a R_b} \right)$$

now at U_n

$$\frac{U_n - 0}{10kN} + \cancel{i_p^0} + \frac{U_n - U_o}{R_f} \Rightarrow U_n \left(\frac{1}{10kN} + \frac{1}{R_f} \right) = \frac{U_o}{R_f}$$

$$U_o = U_n \left(\frac{R_f}{10kN} + 1 \right)$$

$$= U_p \left(\frac{R_f}{10kN} + 1 \right) \quad \begin{array}{l} \text{by ideal op-amp} \\ U_n = U_p \end{array}$$

5.25 cont

so we found 2 eqns for V_o now combine those with the given constraint $V_o = 5V_a + 4V_b + V_c$

first let us gather up some common terms so we can see them clearly.

rewrite

$$V_p = \frac{R_b R_c}{D} V_a + \frac{R_a R_c}{D} V_b + \frac{R_a R_b}{D} V_c$$

$$\text{where } D = R_b R_c + R_a R_c + R_a R_b$$

$$\text{and let } k = \frac{R_s}{10k\Omega} + 1$$

thus

$$V_o = k V_p = \frac{k}{D} (R_b R_c V_a + R_a R_c V_b + R_a R_b V_c)$$

now equate common coefficients

$$\frac{k}{D} R_b R_c = 5 \quad \Rightarrow R_b = 5 \frac{D}{k R_c}$$

$$\frac{k}{D} R_a R_c = 4 \quad \Rightarrow R_a = 4 \frac{D}{k R_c}$$

$$\frac{k}{D} R_a R_b = 1 \quad \Rightarrow R_a = \frac{D}{k R_b} \Rightarrow \frac{1}{R_a} = \frac{k}{D} R_b$$

$$\text{or also} \quad \frac{1}{R_b} = \frac{k}{D} R_a$$



5.25 cont

Plug relationships & find a ratio to R_a (= 1 kN remember)

$$\frac{k}{D} R_b R_c = \frac{R_c}{R_a} = 5 \quad \text{thus } R_c = 5 R_a = \underline{\underline{5 \text{ kN} = R_c}}$$

$$\frac{k}{D} R_a R_c = \frac{R_c}{R_b} = 4 \Rightarrow R_b = \frac{R_c}{4} = \underline{\underline{1.25 \text{ kN} = R_b}}$$

Now all that is left is R_f .

$$\frac{k}{D} R_b R_c = 5 \Rightarrow k = \frac{5D}{R_b R_c}$$

where

$$D = [1.25(5) + 1(5) + 1.25(1)] \text{ m}^2 = 12.5 \text{ m}^2$$

$$k = \frac{5(12.5 \text{ m}^2)}{(1.25 \text{ kN})(5 \text{ kN})} = 10 = \frac{R_f}{10 \text{ kN}} + 1$$

$$\frac{R_f}{10 \text{ kN}} = 9 \Rightarrow \underline{\underline{R_f = 90 \text{ kN}}}$$

thus $R_a = 1 \text{ kN}$ (given)

$$R_b = 1.25 \text{ kN}$$

$$R_c = 5 \text{ kN}$$

$$R_f = 90 \text{ kN}$$



5.25 cont.

b) find i_a , i_b & i_c in μA

$$\text{for } U_a = 0.5V$$

$$U_b = 1.0V$$

$$U_c = 1.5V$$

$$U_o = 5(0.5V) + 4(1.0V) + 1.5V = 8V$$

$$\frac{U_n - 0}{10k\Omega} + \overset{0}{i_n} + \frac{U_n - U_o}{90k\Omega} = 0 \Rightarrow U_n \left(\frac{1}{10k\Omega} + \frac{1}{90k\Omega} \right) = \frac{U_o}{90k\Omega}$$

$$U_n \left(\frac{90k\Omega}{10k\Omega} + \frac{90k\Omega}{90k\Omega} \right) = U_o$$

$$U_n (9+1) = U_o \Rightarrow U_n = \frac{U_o}{10} = \frac{8V}{10} = 0.8V = U_p$$

(you could have found U_p from the non-inverting amp solution $U_o = (1 + \frac{R_f}{R_s}) U_p \Rightarrow U_p = \frac{U_o}{1 + \frac{90k}{10k}} = \frac{U_o}{1+9} = \frac{U_o}{10}$)

now we can find the currents

$$i_a = \frac{U_a - U_p}{1k\Omega} = \frac{(0.5 - 0.8)V}{1k\Omega} = \frac{-0.3V}{1k\Omega} = \underline{\underline{-300\mu A}}$$

$$i_b = \frac{U_b - U_p}{1.25k\Omega} = \frac{(1.0 - 0.8)V}{1.25k\Omega} = \underline{\underline{160\mu A}}$$

$$i_c = \frac{U_c - U_p}{5k\Omega} = \frac{(1.5 - 0.8)V}{5k\Omega} = \underline{\underline{140\mu A}}$$