

**Started on** Wednesday, 7 December 2016, 11:03 AM

**State** Finished

**Completed on** Wednesday, 7 December 2016, 11:53 AM


**Time taken** 50 mins 38 secs

**Grade** 100.00 out of 100.00

### Question 1

Correct

Mark 100.00 out of 100.00

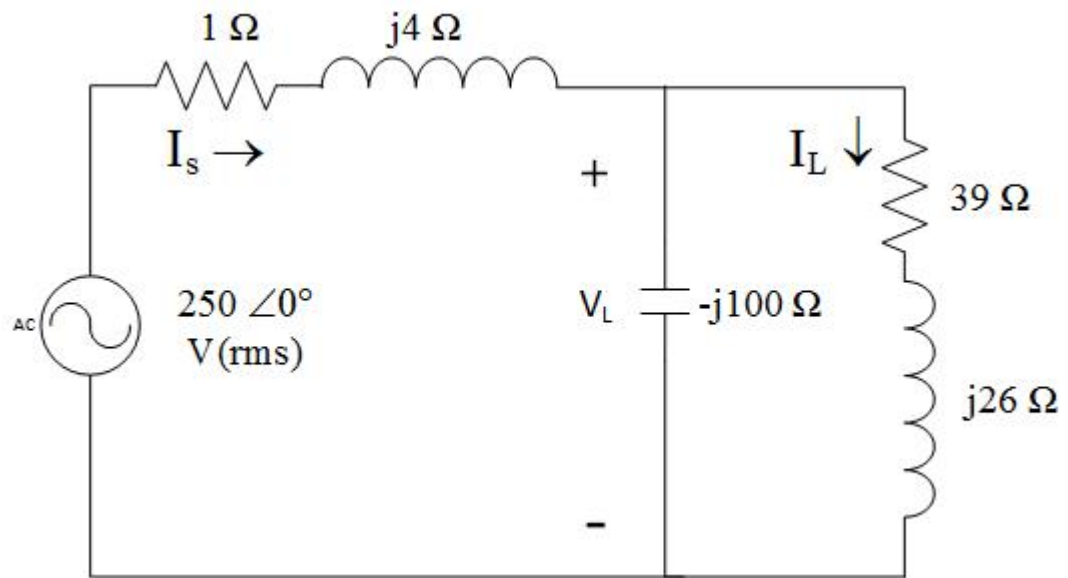

### Quiz 12a

The load  $L$  is the series resistor and inductor in parallel with the capacitor.

a) Calculate the rms phasors  $V_L$  and  $I_L$ .

$|V_L| =$    $✓ V_{rms}$

Phase angle  $V_L =$    $✓ ^\circ$  (Degrees)

$|I_L| =$    $✓ A_{rms}$

Phase angle  $I_L =$    $✓ ^\circ$  (Degrees)

b) Calculate the average power and magnetizing reactive power absorbed by the  $(39 + j 26) \Omega$  (Ohm) elements.

$$P_{\text{avg}} = 1050.74 \checkmark \checkmark \text{ W}$$

$$Q = 700.5 \checkmark \text{ VAR}$$

c) Calculate the power factor and the power factor angle seen by the voltage source.

$$\text{pf} = 0.985 \checkmark \checkmark$$

$$\text{pf angle } \theta = 9.78 \checkmark \text{ Degrees}$$

### Numeric Answer

a)  $V_L = 243.3$  at angle  $-3.86^\circ$  Vrms       $I_L = 5.191$  at angle  $-37.55^\circ$  Arms

b)  $P_{\text{avg}} = 1,051.04 \text{ W}$        $Q = 700.7 \text{ VAR}$

c)  $\text{pf} = 0.986$        $\text{pf angle } \theta = 9.76 \text{ Degrees}$

**Correct**

Marks for this submission: 100.00/100.00.