

Started on Wednesday, 3 April 2019, 10:56 AM

State Finished

Completed on Wednesday, 3 April 2019, 11:36 AM

Time taken 39 mins 32 secs

Grade 96.67 out of 100.00

Question 1

Correct

Mark 5.00 out of 5.00

Q1b

Find the Laplace Transform of $\left\{ \frac{d}{dt} \sin \omega t \right\}$

Select one:

- ☒ a. $\frac{s\omega}{s^2 + \omega^2}$ ✓
- ☐ b. $\frac{-s^2}{s^2 + \omega^2}$
- ☐ c. $\frac{1}{s^2 + \omega^2}$
- ☐ d. $\frac{\omega}{s^2 + \omega^2}$

Your answer is correct.

$$\frac{s\omega}{s^2 + \omega^2}$$

The correct answer is: $\frac{s\omega}{s^2 + \omega^2}$

Correct

Marks for this submission: 5.00/5.00.

Question 2

Correct

Mark 15.00 out of
15.00

Q2a

Given

$$F(s) = \frac{100(s^2 + 69)}{(s+10)(s^2 + 10s + 169)} = \frac{100(s^2 + 69)}{(s+10)(s+5-j12)(s+5+j12)}$$

Find the partial fraction expansion of F(s) and then use the Laplace transform tables to find f(t).

$$f(t) = \left[100 e^{-10t} + 83.33 e^{-5t} \cos(12t + 90^\circ) \right] u(t)$$

$$f(t) = \left[100e^{-10t} + 83.33e^{-5t} \cos(12t + 90^\circ) \right] u(t)$$

Correct

Marks for this submission: 15.00/15.00.

Question 3

Correct

Mark 10.00 out of
10.00

Q3d

Given: $F(s) = \frac{40(s+4)}{(s+1)(s+5)}$ which has an inverse transform f(t).

a) Find the initial value of f(t = 0).

$$f(t = 0) = 40$$

b) Find the final value of f(t → ∞)

$$f(t \rightarrow \infty) = 0$$

Numeric Answer

a) f(t = 0) = 40


b) f(t → ∞) = 0

Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

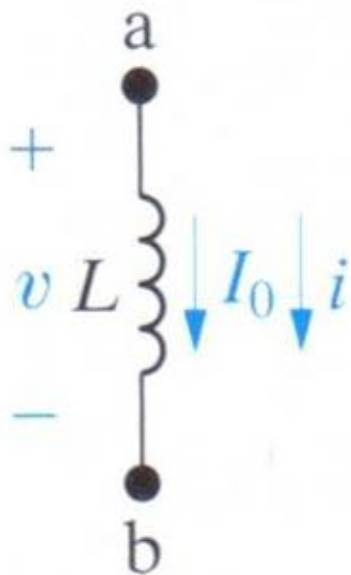Mark 6.67 out of
10.00

Q4d

Given: This inductor has a value of 10 mH (milli H) and has an initial current of 15 A at $t = 0^-$. Identify the Frequency Domain series form of the inductor.

Select one:

- ☒ a. $V = s(10 \times 10^{-3})I - 0.15$ ✓
- ☐ b. $V = s(10 \times 10^{-6})I - 0.00015$
- ☐ c. $I = \frac{V}{s(10 \times 10^{-3})} + \frac{15}{s}$
- ☐ d. $I = \frac{V}{s(10 \times 10^{-6})} + \frac{15}{s}$

Your answer is correct.


$$V = s(10 \times 10^{-3})I - 0.15$$

The correct answer is: $V = s(10 \times 10^{-3})I - 0.15$

CorrectMarks for this submission: 10.00/10.00. Accounting for previous tries, this gives **6.67/10.00**.

Question 5

Correct

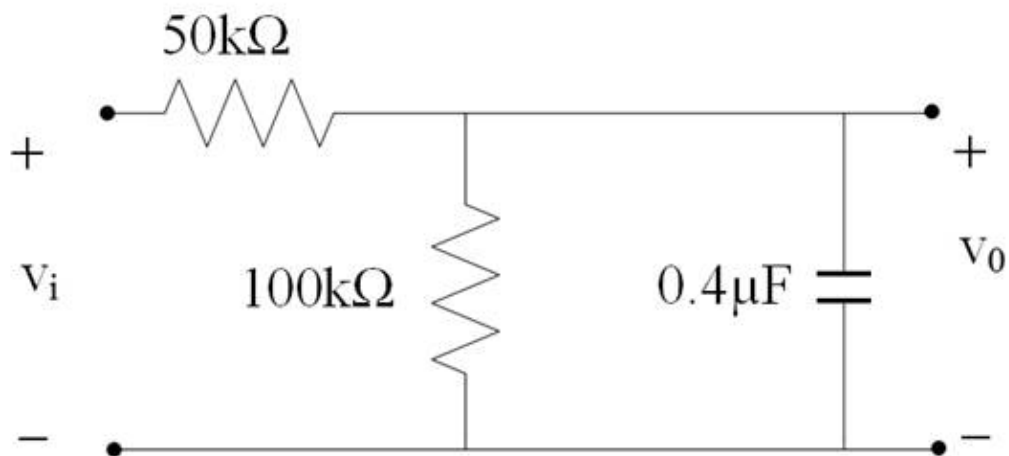Mark 15.00 out of
15.00

Q5a

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = \boxed{50} \checkmark / (s + \boxed{75} \checkmark)$$

$$H(s) = \frac{50}{s+75}$$


Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 15.00 out of 15.00

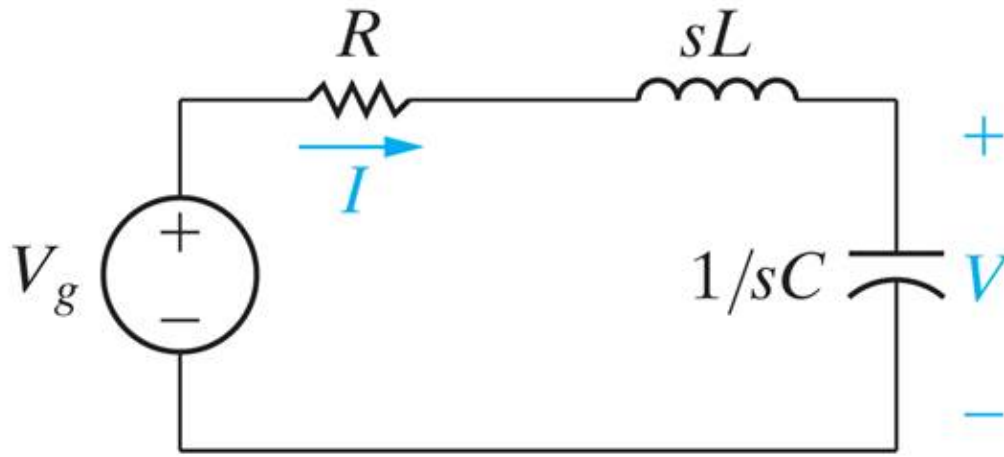

Q6c

Given: There is no energy stored in this circuit prior to $t = 0$.The voltage source $V_g = 10\text{V}$ for $t \geq 0^+$. $R = 125\ \Omega$ (Ohm) $L = 1\text{ H}$ $C = 1\text{ mF}$ (milli F)Find the defined current I in the s domain.

$$I(s) = \boxed{10} \checkmark / (s^2 + \boxed{125} \checkmark s + \boxed{1000} \checkmark)$$

$$H(s) = \frac{V}{V_g} = \frac{10,000}{s(s^2 + s125 + 1,000)}$$

Correct

Marks for this submission: 15.00/15.00.

Question 7

Correct

Mark 15.00 out of 15.00

Q7e

$$\text{Given: } F(s) = \frac{2(5s+11)}{s^2+14s+625} = \frac{2(5s+11)}{(s+7-j24)(s+7+j24)}$$

Find the partial fraction expansion of this transfer function.

$$F(s) = \boxed{5.09} \checkmark \text{ at Angle } \boxed{11.3} \checkmark / (s + 7 - j24)$$

$$+ \boxed{5.09} \checkmark \text{ at Angle } \boxed{-11.3} \checkmark / (s + 7 + j24)$$

State the angle in each case as a positive angle.


$$F(s) = \frac{2(5s+11)}{s^2+14s+625} = \frac{5.0990 \angle 11.31^\circ}{s+7-j24} + \frac{5.0990 \angle [?][?]-11.31^\circ}{s+7+j24}$$

Correct

Marks for this submission: 15.00/15.00.

Question 8

Correct

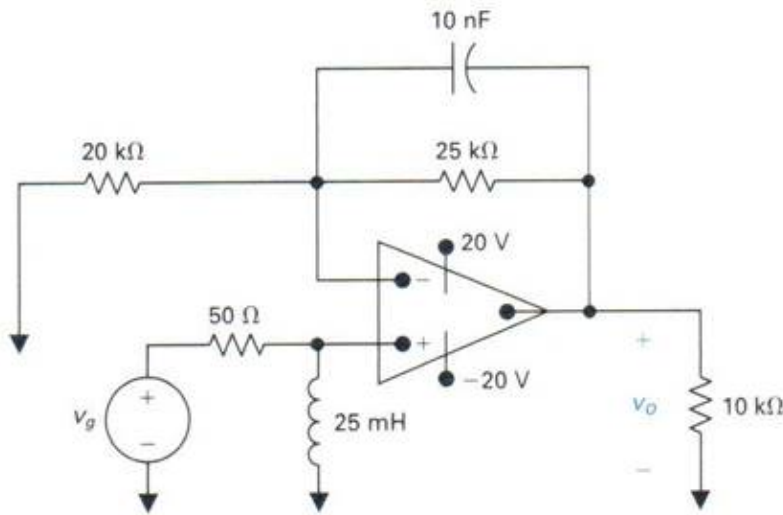Mark 15.00 out of
15.00

Q8c

Given: The opamp is ideal.

$$H(s) = \frac{V_o}{V_g} = \frac{s(s+9,000)}{(s+2,000)(s+4,000)}$$

Find the steady-state response when the input $v_g(t) = 12 \cos(10,000 t) \text{ V}$.

$$v_o(t)_{\text{steady-state}} = [14.69 \checkmark \cos(10000 \checkmark t + -8.88 \checkmark ^\circ)] u(t) \text{ V}$$

Numeric Answer

$$v_o(t)_{\text{steady-state}} = 14.6980 \cos(10,000 t - 8.86^\circ) u(t) \text{ V}$$

Correct

Marks for this submission: 15.00/15.00.

◀ Quiz 7 - Chapter 13

Jump to... ▼

Quiz 8 - Bode Diagrams ►