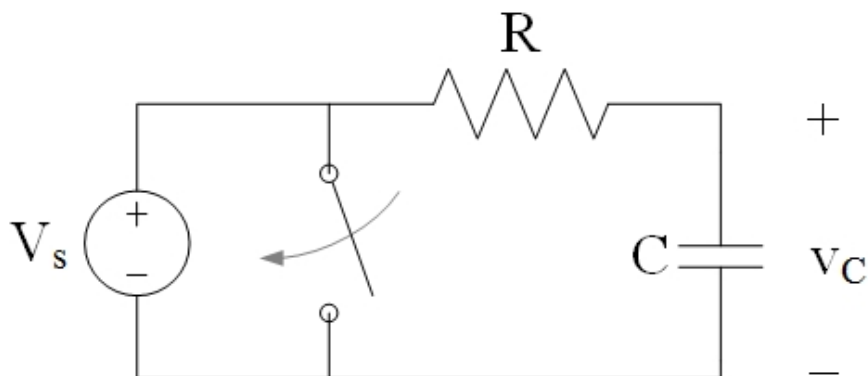


**Started on** Wednesday, 13 March 2019, 8:58 AM**State** Finished**Completed on** Wednesday, 13 March 2019, 9:22 AM**Time taken** 24 mins 31 secs**Grade** 100.00 out of 100.00**Question 1**

Correct

Mark 100.00 out of 100.00



Quiz 6f

Given: After a long time the switch closes at  $t = 0$ . $V_s = 12 \text{ V}$      $R = 1 \text{ k}\Omega$  (kilo Ohm)     $C = 5 \text{ nF}$  (nano F)

a) Determine the initial voltage across the capacitor.

$$v_C(t = 0) = \boxed{12} \checkmark \text{ V}$$

b) Find the time domain voltage  $v_C(t)$  across the capacitor for  $t \geq 0^+$ .

$$v_C(t \geq 0) = \boxed{12} \checkmark \exp(\boxed{-200000} \checkmark t) \text{ Volts}$$

**Correct**

Marks for this submission: 100.00/100.00.

◀ Quiz 5 - Chapter 12

Jump to...



Quiz 7 - Chapter 13 ►