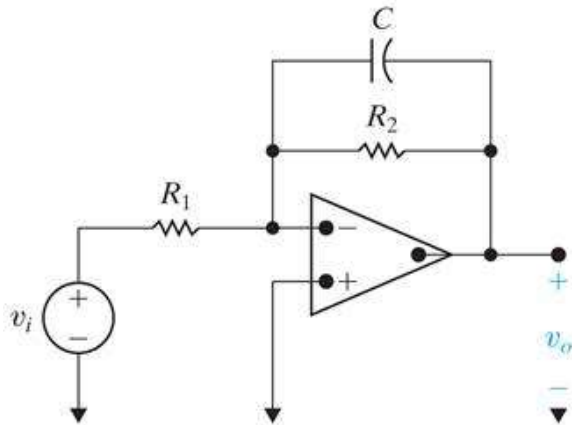


**Started on** Monday, 24 April 2017, 3:14 PM**State** Finished**Completed on** Monday, 1 May 2017, 5:15 AM**Time taken** 6 days 14 hours**Grade** 27.00 out of 100.00**Question 1**

Correct

Mark 13.00 out of 13.00



P15.1\_10ed

Given:  $R_1 = ?? \, \Omega$  (Ohm)  $C_{in} = 750 \, \text{nF}$  (nano F)  $R_2 = ?? \, \Omega$  (Ohm)

Assume the opamp is ideal.

Design a low-pass filter with a passband gain of 10 dB and a cutoff frequency of 1 kHz.

 $R_1 =$    $\checkmark \, \Omega$  (Ohm) $R_2 =$    $\checkmark \, \Omega$  (Ohm)


After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.

 $R_1 = 212.2066 \, \Omega$  $R_2 = 67.1056 \, \Omega$ **Correct**

Marks for this submission: 13.00/13.00.

**Question 2**

Not answered

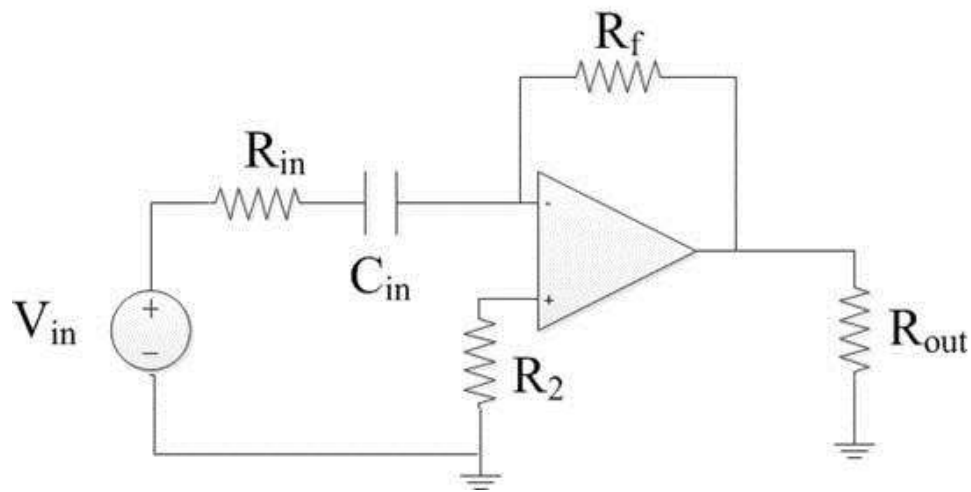Mark 0.00 out of  
14.00

P15.1T

Given:  $R_{in} = 10 \text{ k}\Omega$  (kilo Ohm)  $C_{in} = 0.1 \text{ }\mu\text{F}$  (micro F)  $R_2 = 10 \text{ }\Omega$  (Ohm) $R_{out} = 1 \text{ k}\Omega$  (kilo Ohm)  $R_f = 10 \text{ k}\Omega$  (kilo Ohm) $V_{in} = 20 \cos(\omega t)$  Volts

The opamp is not ideal and can only deliver up to 15 mA at the output.

The opamp has power input rails at +15V and -15V.

Determine the radian frequency  $\omega$  where the opamp just begins saturation. $\omega_{\text{saturation}} =$    $\times \text{ rad/sec}$ 


After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.

 $\omega_{\text{saturation}} = 1,133.8934 \text{ rad/sec}$

### Question 3

Partially correct

Mark 4.67 out of 14.00

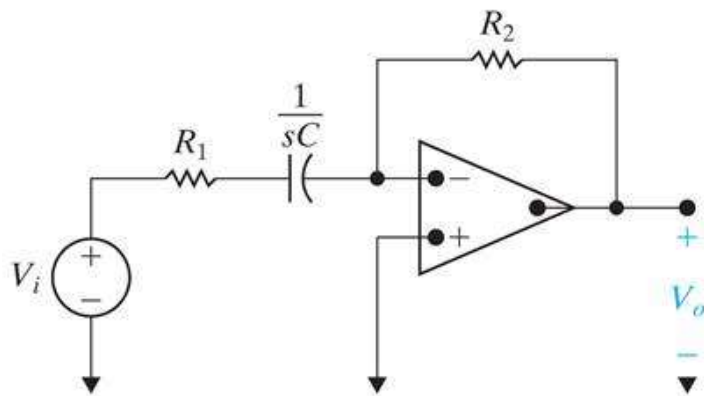

P15.11\_10ed

Given:  $R_1 = 159 \, \Omega$  (Ohm)  $C_{in} = 250 \, \text{nF}$  (nano F)  $R_2 = 1,273 \, \Omega$  (Ohm)

Assume the opamp is ideal.

The input to this high-pass filter is  $v_i(t) = 2.5 \cos(\omega t)$  Volts.

The opamp has power input rails at +20V and -20V.

For the steady-state condition and letting the output voltage magnitude be negative:

a) Find the output voltage when the input frequency  $\omega = \omega_c$ . ( $\omega = \text{omega}$ )

$v_o(t) =$   ☒  $\cos($   ☒  $\pi t +$   ☒  $^\circ)$  (Degrees) Volts

b) Find the output voltage when the input frequency  $\omega = 0.125 \, \omega_c$ .

$v_o(t) =$   ☒  $\cos($   ☒  $\pi t +$   ☒  $^\circ)$  (Degrees) Volts

c) Find the output voltage when the input frequency  $\omega = 8 \, \omega_c$ .

$v_o(t) =$   ☒  $\cos($   ☒  $\pi t +$   ☒  $^\circ)$  (Degrees) Volts

After you get a numeric answer, create a PSpice simulation and compare your answer with the simulation results.

a)  $v_o(t) = -14.1533 \cos(8,008\pi t + 45^\circ) \, \text{V}$

b)  $v_o(t) = -2.4827 \cos(1,001\pi t + 82.87^\circ) \, \text{V}$

c)  $v_o(t) = -19.8612 \cos(64,062.3670\pi t + 7.13^\circ) \, \text{V}$


**Partially correct**

Marks for this submission: 4.67/14.00. Accounting for previous tries, this gives **4.67/14.00**.

**Question 4**

Correct

Mark 9.33 out of 14.00

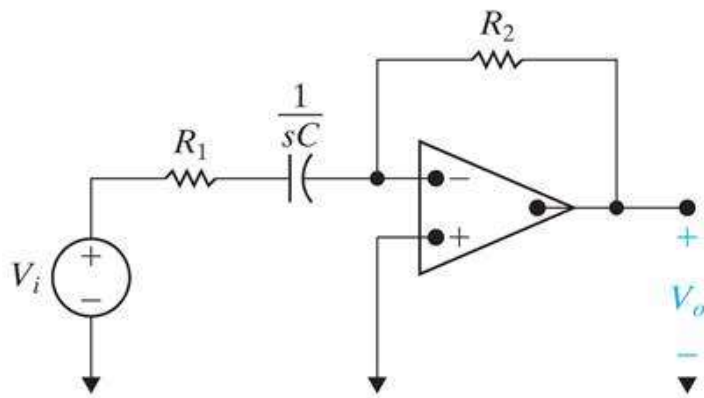

P15.8\_10ed

Given:  $R_1 = ?? \, \Omega$  (Ohm)  $C_{in} = 3.9 \, \text{nF}$  (nano F)  $R_2 = ?? \, \Omega$  (Ohm)

Assume the opamp is ideal.

Design a high-pass filter with a passband gain of 14 dB and a cutoff frequency of 8 kHz.

 $R_1 =$    $\checkmark \, \Omega$  (Ohm) $R_2 =$    $\checkmark \, \Omega$  (Ohm)


After you get a numeric answer, consider creating a PSpice simulation and compare your answer with the simulation results.

 $R_1 = 5,101.120 \, \Omega$  $R_2 = 25,566.1621 \, \Omega$ **Correct**Marks for this submission: 14.00/14.00. Accounting for previous tries, this gives **9.33/14.00**.

### Question 5

Not answered

Mark 0.00 out of  
15.00

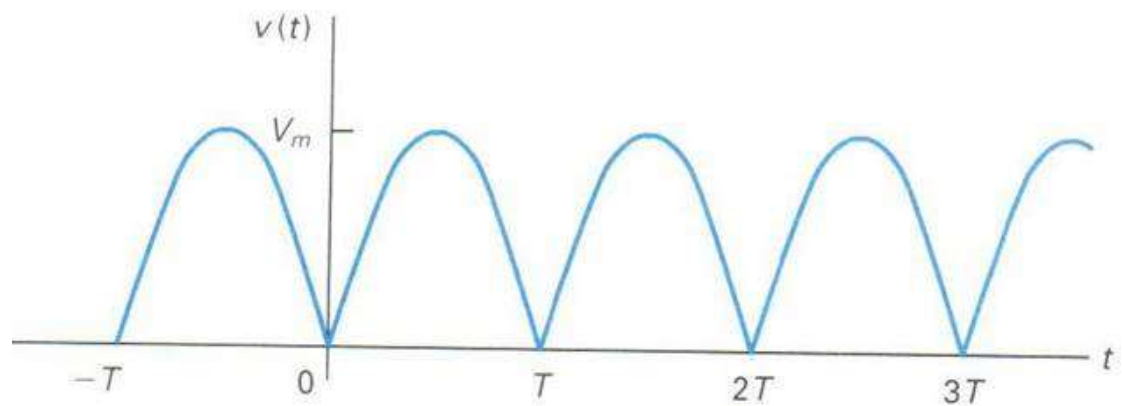

P16.03b\_6ed

Find the Fourier series coefficients for this periodic waveform which is a full-wave rectified sine wave where  $v(t) = V_m \sin(\pi t/T)$  for  $0 \leq t \leq T$ .

a) Find  $a_v$ .

$$a_v = \boxed{\phantom{000}} \times V_m / \pi$$

b) Find  $a_k$ .

$$a_k = \boxed{\phantom{000}} \times V_m / [\pi (1 - \boxed{\phantom{000}} \times k^2)] \text{ for all } k$$

c) Find  $b_k$ .

$$b_k = \boxed{\phantom{000}} \times$$

$$a) a_v = 2 V_m / \pi$$


$$b) a_k = \frac{4 V_m}{\pi (1 - 4 k^2)}$$

$$c) b_k = 0$$

### Question 6

Not answered

Mark 0.00 out of  
15.00

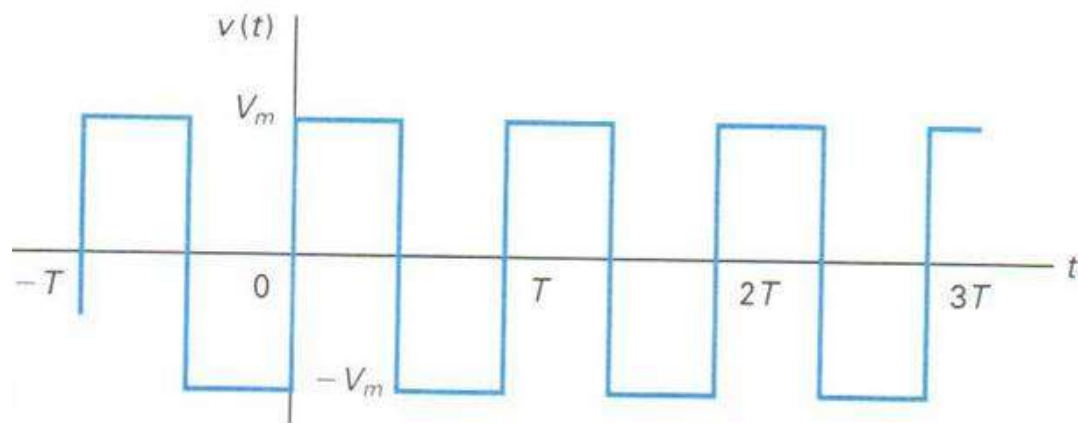

AP16.5\_10ed

Find the Fourier series coefficients for this periodic waveform.

a) Find  $a_v$ .

$$a_v = \boxed{\phantom{0}} \times$$

b) Find  $a_k$ .

$$a_k = \boxed{\phantom{0}} \times$$

c) Find  $b_k$ .

$$b_k = \boxed{\phantom{0}} \times V_m / \pi k \quad \text{for } k \boxed{\phantom{0}} \times$$


a)  $a_v = 0$

b)  $a_k = 0$

c)  $b_k = \frac{4V_m}{\pi k}$  for k odd

**Question 7**

Not answered

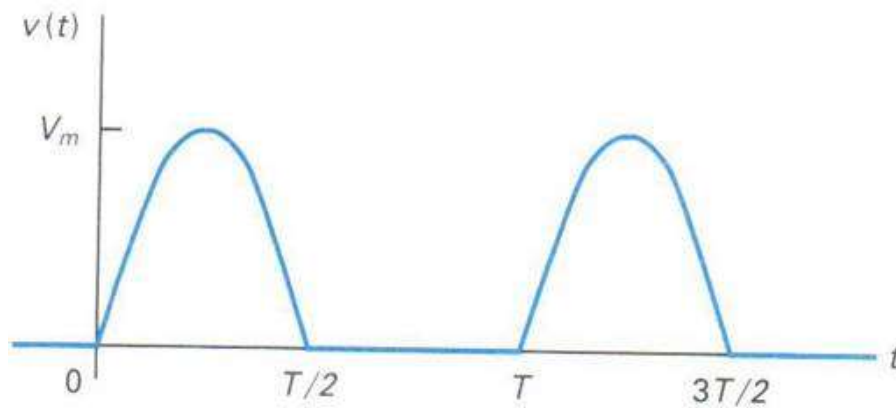Mark 0.00 out of  
15.00

P16.03c\_6ed

Find the Fourier series coefficients for this periodic waveform which is a half-wave rectified sine wave where  $v(t) = V_m \sin(2\pi t/T)$  for  $0 \leq t \leq T/2$ .

Also given  $V_m = 12$  V.

a) Find  $a_v$ .

$a_v =$   ✗ Volts

b) Find  $a_k$ .

$a_k =$   ✗ /  $(1 - k^2)$  Volts for all even

c) Find  $b_k$ .

$b_k =$   ✗ for k even and for k odd  $> 1$ .

$b_1 =$   ✗  $\sin(\omega_0 t)$  Volts

a)  $a_v = 3.8197$  V

$$b) a_{k, \text{even}} = \frac{2V_m}{\pi} \left[ \frac{1}{1-k^2} \right] = 7.6394 \left[ \frac{1}{1-k^2} \right] V$$

c)  $b_k = 0$  for k even and odd (for  $k > 1$ )

$$b_1 = (12V/2) \sin(\omega_0 t) = 6 \sin(\omega_0 t) \text{ Volts}$$