

Home ► My courses ► **EEE117-2019S-Sec1** ► Exams and Quizzes ►
Exam 1 - Chapters 9, 10 and 11

Started on	Wednesday, 20 February 2019, 10:55 AM
-------------------	---------------------------------------

State	Finished
--------------	----------

Completed on	Wednesday, 20 February 2019, 11:40 AM
---------------------	---------------------------------------

Time taken	45 mins 47 secs
-------------------	-----------------

Grade	100.00 out of 100.00
--------------	-----------------------------

Question 1

Correct

Mark 10.00 out of 10.00

Q1e

Consider the sinusoidal voltage $v(t) = 460 \cos(880 \pi t + 75^\circ) V_{\text{rms}}$.

a) What is the maximum amplitude of the voltage?

$$V_m = \boxed{650.54} \checkmark \text{ V}$$

b) What is the frequency of $v(t)$ in hertz?

$$f = \boxed{440} \checkmark \text{ Hz}$$

c) What is the frequency of $v(t)$ in radians per second?

$$\omega = \boxed{2764.6} \checkmark \text{ rad/sec}$$

d) What is the phase angle in radians?

$$\phi \text{ (phi)} = \boxed{1.31} \checkmark \text{ radians}$$

e) What is the period in milliseconds?

$$T = \boxed{2.27} \checkmark \text{ ms (milli sec)}$$

Numeric Answer

a) $V_m = 650.5382 \text{ V}$

b) $f = 440 \text{ Hz}$

c) $\omega = 2,764.602 \text{ rad/sec}$

d) $\phi \text{ (phi)} = 1.3090 \text{ radians}$

e) $T = 2.2727 \text{ ms (milli sec)}$

Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

Q2c

Given: $x(t) = 250 \cos(300 t + 30^\circ) + 350 \cos(300 t - 50^\circ)$

Use the concept of the phasor to combine this sinusoidal function into a single trigonometric expression in the form similar to $x(t) = A \cos(\omega t + \theta^\circ)$.

Magnitude A of $x(t)$ = ✓

Angle θ of $x(t)$ = ✓ ° (Degree)

$$x(t) = 464.0996 \cos(300 t - 17.9612^\circ)$$


Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 15.00 out of 15.00

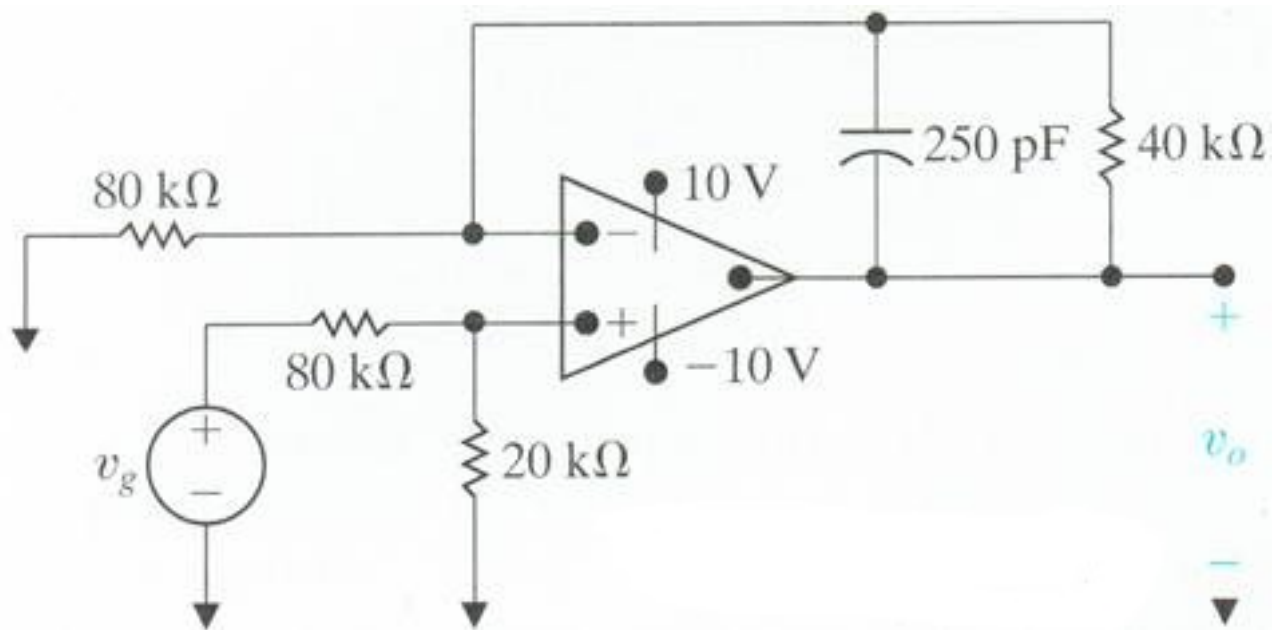

Q3a

Assume the operational amplifier is ideal.

Given $v_g(t) = 34.50 \text{ V}$ (a constant voltage)

Find the steady-state output $v_o(t)$.

$$v_o(t) = \boxed{10} \checkmark \text{ Volts}$$

Numeric Answer

$v_o(t) = 10 \text{ V}$ since the opamp is in saturation at the positive power supply rail.


Correct

Marks for this submission: 15.00/15.00.

Question 4

Correct

Mark 15.00 out of 15.00

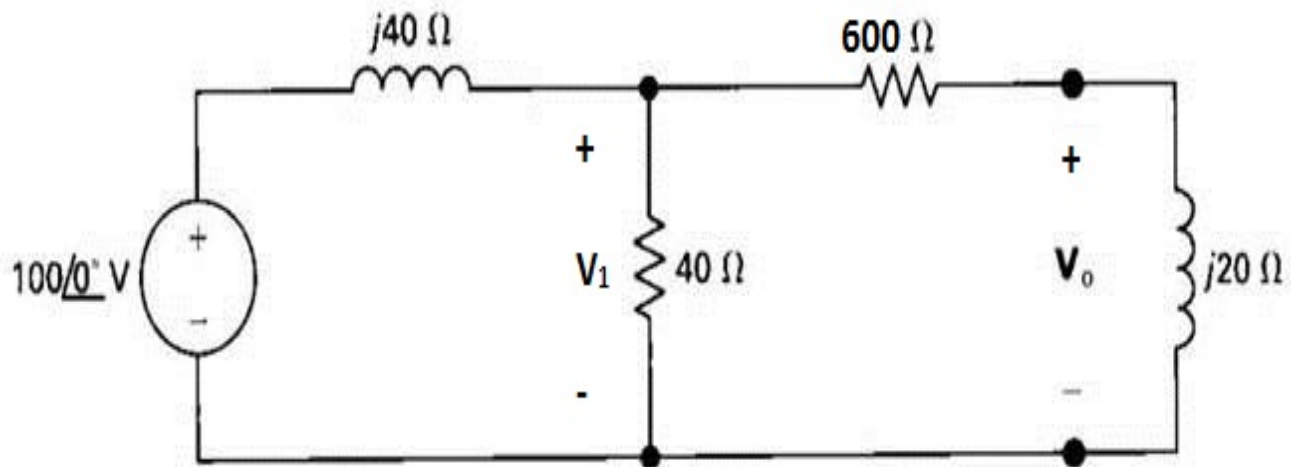

Q4c

Find the phasor voltages V_0 and V_1 . I suggest you use the Node Method.

$V_0 =$ ✓ at angle ✓ ° (Degrees) Volts

$V_1 =$ ✓ at angle ✓ ° (Degrees) Volts

Express your answer as a positive magnitude and then the angle in the appropriate quadrant.

Numeric Answer

$V_0 = 2.2763$ at angle 41.31° Volts

$V_1 = 68.3256$ at angle -46.78° Volts


Correct

Marks for this submission: 15.00/15.00.

Question 5

Correct

Mark 15.00 out of 15.00

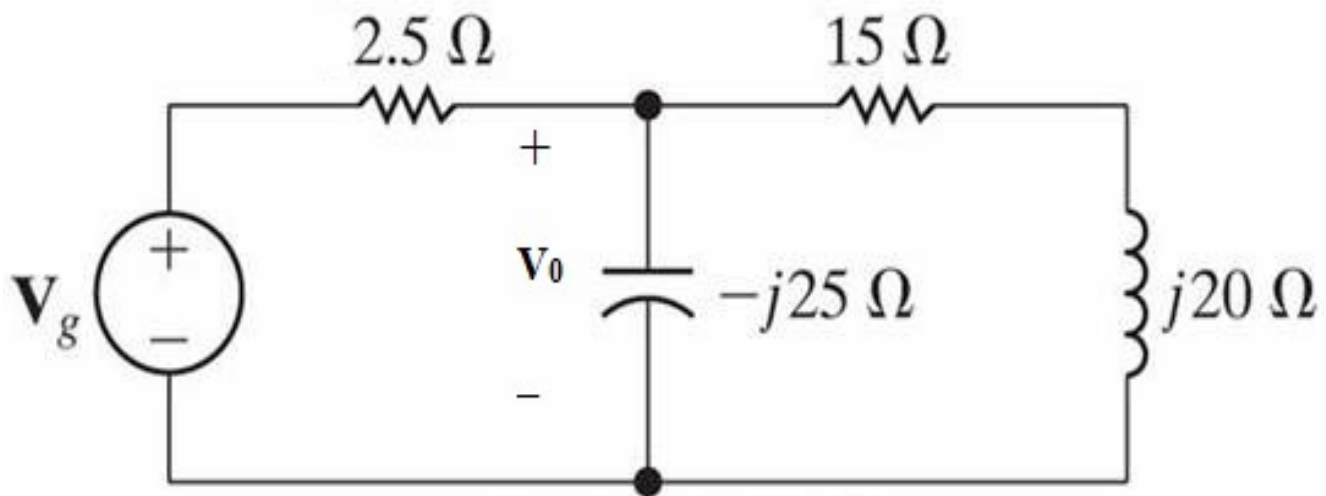

Q5c

Given:

The voltage source $V_g = 160$ at angle 0° V_{rms}
and the voltage $V_0 = 150.9165$ at angle -1.08° V_{rms} .

Find the average and reactive power for the voltage source V_g .

$$S_g = \boxed{-583} \checkmark + j \boxed{182} \checkmark \text{ VA}$$

“+” = absorbed and “-” = delivered

Numeric Answer

$$S_g = -583.0605 + j 182.2064 \text{ VA}$$

Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 5.00 out of 5.00

Q6b

What is the phase sequence of each of the following sets of voltages?

$$v_a = 820 \cos(\omega t - 46^\circ) \text{ V} \quad v_b = 820 \cos(\omega t + 74^\circ) \text{ V} \quad v_c = 820 \sin(\omega t - 76^\circ) \text{ V}$$

acb – Negative Phase Sequence: ▼ 

Correct answer is acb – Negative Phase Sequence


Correct

Marks for this submission: 5.00/5.00.

Question 7

Correct

Mark 15.00 out of 15.00

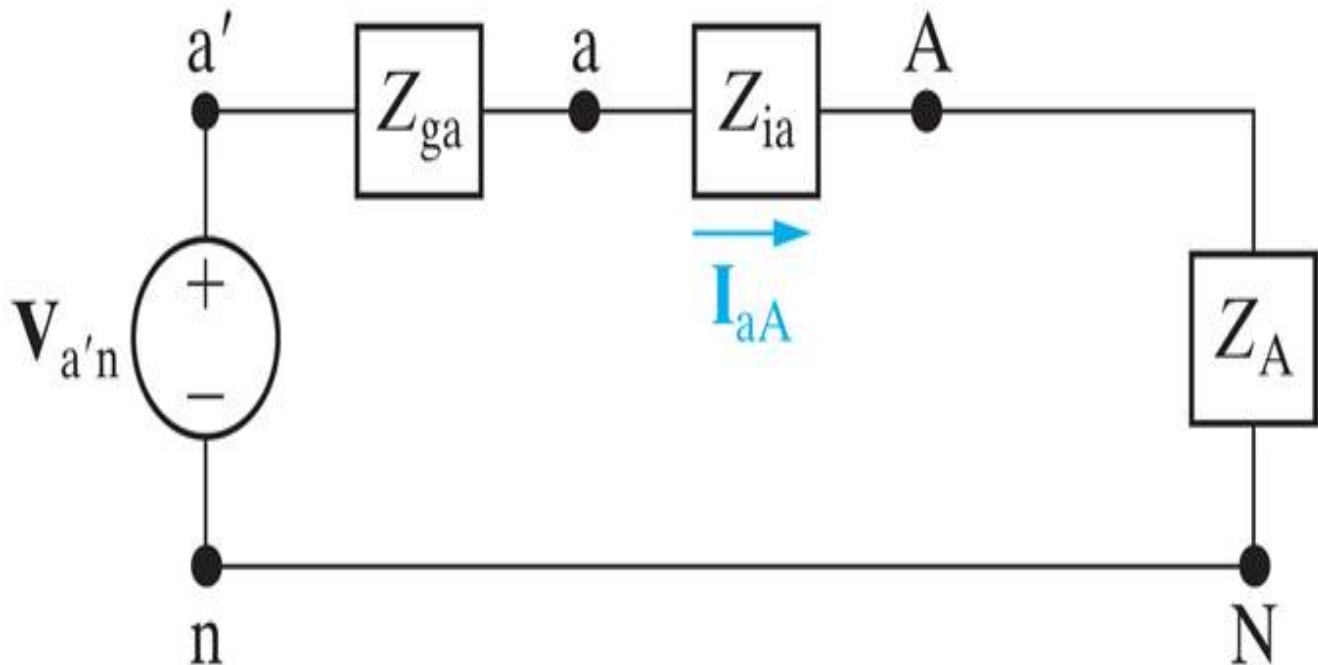

Q7a

Given: $V_{a'n} = 120$ at angle 0° V_{rms} in a balanced three phase system with a positive phase sequence.

The source and load are Y connected.

$$Z_{ga} = 1 + j15 \, \Omega \quad Z_{ia} = 19 + j5 \, \Omega \quad Z_A = 20 + j20 \, \Omega$$

Calculate the single phase equivalent line currents I_{aA} , I_{bB} and I_{cC} .

$$I_{aA} = 2.12 \text{ at angle } -45^\circ \text{ (Degrees) } A_{rms}$$

$$I_{bB} = 2.12 \text{ at angle } -165^\circ \text{ (Degrees) } A_{rms}$$

$$I_{cC} = 2.12 \text{ at angle } 75^\circ \text{ (Degrees) } A_{rms}$$

Calculate the line to line voltages V_{AB} , V_{BC} , and V_{CA} .

$$V_{AB} = 103.9 \text{ at angle } 30^\circ \text{ (Degrees) } V_{rms}$$

$V_{BC} = 103.9$ ✓ at angle -90 ✓ ° (Degrees) V_{rms}

$V_{CA} = 103.9$ ✓ at angle 150 ✓ ° (Degrees) V_{rms}

$I_{aA} = 2.1213$ at angle -45° A_{rms}

$I_{bB} = 2.1213$ at angle -165° A_{rms}

$I_{cC} = 2.1213$ at angle 75° A_{rms}

$V_{AB} = 103.923$ at angle 30° V_{rms}

$V_{BC} = 103.923$ at angle -90° V_{rms}

$V_{CA} = 103.923$ at angle 150° V_{rms}

Correct

Marks for this submission: 15.00/15.00.

Question 8

Correct

Mark 15.00 out of 15.00

Q8c

The total apparent power supplied in a balanced three-phase Y- Δ (wye to delta) system is 3,600 VA. The source line to neutral voltage is 240 V_{rms}. The line impedance is negligible and the power factor angle of the load is 25° leading.

Determine the impedance of each phase of the delta-connected load.

$$Z_{\Delta, \text{load}} = \boxed{130.5} \checkmark + j \boxed{-60.9} \checkmark \Omega \text{ (Ohms)}$$

$$Z_{\Delta, \text{load}} = 130.5083 - j 60.8570 \Omega \text{ (Ohms)}$$

Correct

Marks for this submission: 15.00/15.00.

◀ Quiz 3 - Chapter 10

Jump to...



Quiz 4 - Chapter 12 ▶