

Started on Saturday, 3 December 2016, 9:01 PM

State Finished

Completed on Sunday, 4 December 2016, 1:42 AM


Time taken 4 hours 41 mins

Grade 100.00 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

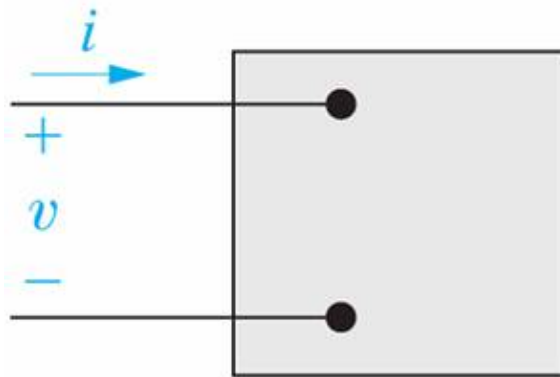

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P10.01b_9ed

For the following set of values, calculate P, Q and state whether the circuit inside the box is absorbing or delivering (1) average power and (2) magnetizing vars.

b) $v = 40 \cos(\omega t - 15^\circ) \text{ V}$ $i = 20 \cos(\omega t + 60^\circ) \text{ A}$

P = 103.53 ✓ W Absorbing ✓ Watts

Q = -386.37 ✓ VAR Delivering ✓ VARs

Numeric Answer


b) P = 103.53W abs Q = -386.37 VAR del

Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

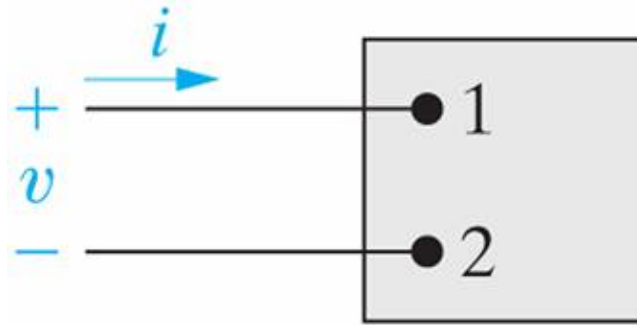Mark 10.00 out of
10.00Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P10.01b_6ed

Calculate P and Q of the following voltage and current. State whether the element is absorbing or delivering average power and magnetizing VARs.

$$v = 75 \cos(\omega t - 15^\circ) \text{ V}$$

$$i = 16 \cos(\omega t + 60^\circ) \text{ A}$$

$P =$ ✓ W ✓ Watts

$Q =$ ✓ VAR ✓ VARs

Numeric Answer


$P = 155.3 \text{ W abs}$ $Q = -579.6 \text{ VAR del}$

Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

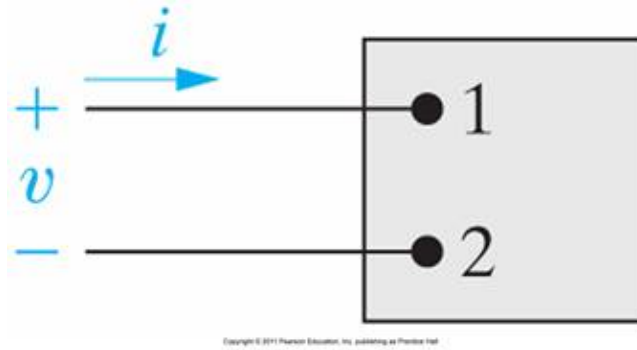Mark 10.00 out of
10.00

P10.01a_6ed

Calculate P and Q of the following voltage and current. State whether the element is absorbing or delivering average power and magnetizing VARs.

$$v = 340 \cos(\omega t + 60^\circ) \text{ V} \quad i = 20 \cos(\omega t + 15^\circ) \text{ A}$$

$P =$ ✓ W ✓ Watts

$Q =$ ✓ VAR ✓ VARS

Numeric Answer


$P = 2,404.16 \text{ abs}$ $Q = 2404.16 \text{ VAR abs}$

Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

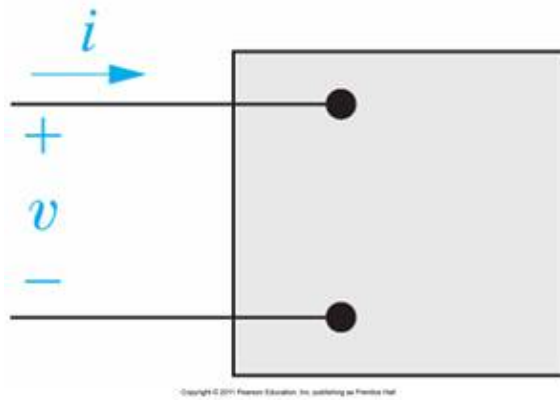Mark 10.00 out of
10.00Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P10.01d_9ed

For the following set of values, calculate P, Q and state whether the circuit inside the box is absorbing or delivering (1) average power and (2) magnetizing vars.

d) $v = 200 \sin(\omega t + 250^\circ) \text{ V}$ $i = 5 \cos(\omega t + 40^\circ) \text{ A}$

P = ✓ W ✓ Watts

Q = ✓ VAR ✓ VARs

Numeric Answer


d) P = -250W del Q = 433.01 VAR abs

Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

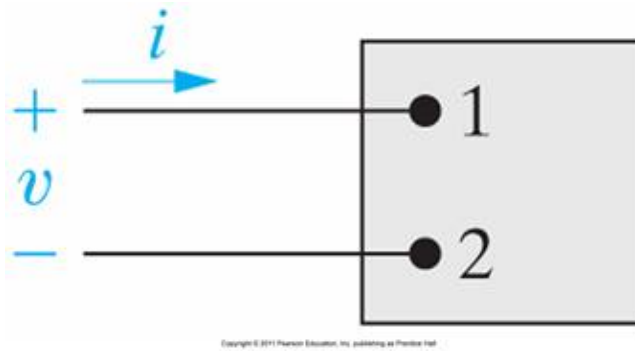Mark 10.00 out of
10.00

P10.01d_6ed

Calculate P and Q of the following voltage and current. State whether the element is absorbing or delivering average power and magnetizing VARs.

$$v = 180 \sin(\omega t + 220^\circ) \text{ V}$$

$$i = 10 \cos(\omega t + 20^\circ) \text{ A}$$

P = ✓ W ✓ Watts

Q = ✓ VAR ✓ VARs

Numeric Answer

P = -307.8 W delivering

Q = 845.7 VAR absorbing


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

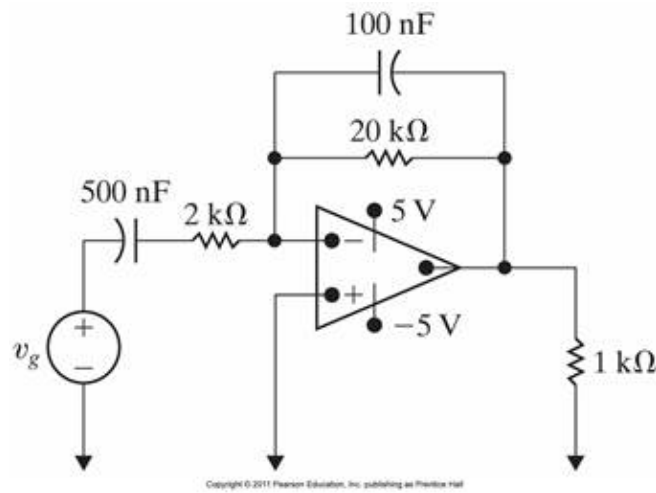

P10.07_9ed

The opamp is ideal. $v_g = \cos(1,000t)$ V

Calculate the average power dissipated by the 1 kΩ (kilo Ohm) resistor.

$$P_{\text{avg}, 1\text{k}\Omega} = \boxed{5} \checkmark \text{ mW (milli Watt) ("+" = absorbed, "-" = delivered)}$$

Numeric Answer

$$P_{\text{avg}, 1\text{k}\Omega} = 5 \text{ mW (milli Watt)}$$

Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

$$p_{\text{max}} = P_{\text{avg}} + \sqrt{P^2 + Q^2}$$

$$p_{\text{min}} = P_{\text{avg}} - \sqrt{P^2 + Q^2}$$

P10.04_9ed

A load consisting of a 480 Ω (Ohm) resistor in parallel with a $(5/9)$ μF (micro Farad) capacitor is connected across the terminals of a sinusoidal voltage source $v_g = 240 \cos(5,000t)$ V.

a) What is the average power absorbed/delivered by the load?

$$P_{\text{avg}} = \boxed{60} \checkmark \text{ W}$$

b) What is the reactive power absorbed/delivered by the load?

$$Q = \boxed{-80} \checkmark \text{ VAR}$$

c) What is the peak value of the instantaneous power delivered by the source?The figure shows the result of a derivation for p_{max} .

$$p_{\max} = -160 \text{ W} \quad (\text{"+" = absorbed, "-" = delivered})$$

d) What is the peak value of the instantaneous power absorbed by the source?

The figure shows the result of a derivation for p_{\min} .

$$p_{\min} = 40 \text{ W} \quad (\text{"+" = absorbed, "-" = delivered})$$

e) What is the power factor of the load?

$$\text{pf} = .6$$

f) What is the reactive factor of the load?

$$\text{rf} = -0.8 \quad (\text{"+" = inductive, "-" = capacitive})$$

Numeric Answer

a) $P_{\text{avg}} = 60 \text{ W}$

b) $Q = -80 \text{ VAR}$

c) $P_{\text{peak}} = -160 \text{ W delivered}$

d) $P_{\text{source}} = 40 \text{ W absorbed}$

e) $\text{pf} = 0.6 \text{ leading}$

f) $\text{rf} = -0.8$

Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

P10.11b_9ed

A laser printer is rated at 90 W at $115 \text{ V}_{\text{rms}}$.

a) Calculate the rms value of the current drawn by the laser printer.

$$i_{\text{printer,rms}} = .78 \text{ Arms}$$

b) Calculate the peak magnitude of the voltage fed to the laser printer.

$$V_{\text{peak}} = 162.6 \text{ V}$$

Numeric Answer

a) $i_{\text{printer,rms}} = 0.7826 \text{ A}_{\text{rms}}$

b) $V_{\text{peak}} = 162.6346 \text{ V}$

Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

P10.11a_9ed

A personal computer with a monitor and keyboard voltage and current are:

$$v(t) = 115 \cos(2\pi 60 + 0^\circ) \text{ V}_{\text{rms}} \quad i(t) = 0.5 \cos(2\pi 60 - 25^\circ) \text{ Arms}$$

Calculate the real power absorbed by the computer system.

$$P_{\text{computer}} = 52.11 \text{ W} \quad (\text{"+" = absorbed, "-" = delivered})$$

Numeric Answer

$$P_{\text{computer}} = 52.1127 \text{ W}$$


Correct

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of 10.00

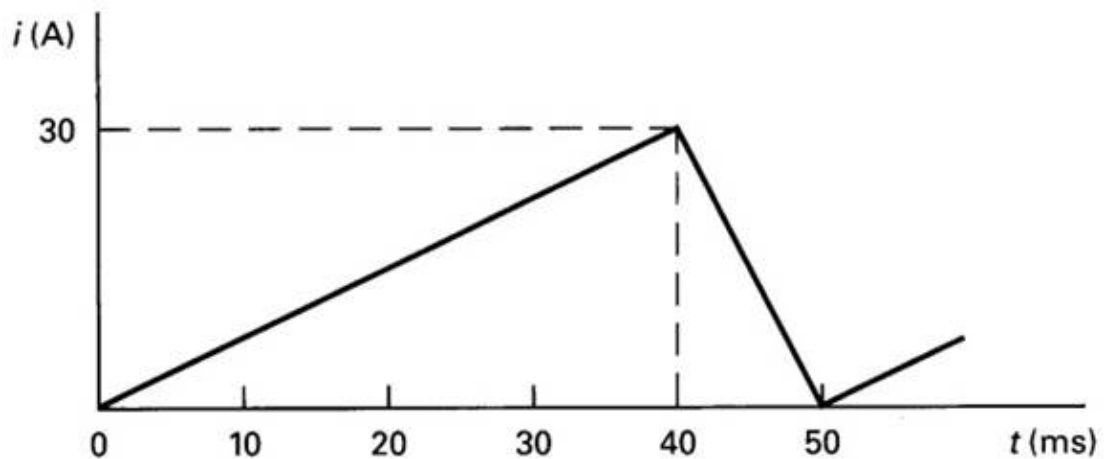

P10.5_6ed

Given: The period of the waveform is 50 ms (milli sec).

a) Find the rms value of the periodic current shown in the figure.

$$i_{\text{rms}} = 17.32 \text{ A}_{\text{rms}}$$

b) Given that the periodic waveform dissipates an average power of 24 kW in a resistor. What is the value of the resistor?

$$R = 80 \text{ } \Omega \text{ (Ohm)}$$

Numeric Answer

$$\text{a) } i_{\text{rms}} = 17.321 \text{ A}_{\text{rms}}$$

$$\text{b) } R = 80.0 \text{ } \Omega \text{ (Ohm)}$$

Correct

Marks for this submission: 10.00/10.00.

