

Started on Thursday, 10 November 2016, 1:05 PM

State Finished

Completed on Thursday, 10 November 2016, 1:05 PM

Time taken 6 secs

Grade 79.67 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

P9.06_6ed

Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric express.

The time domain form is assumed to be similar to $x(t) = \cos(\omega t + \phi^\circ)$

a) $x(t) = 100 \cos(300 t + 45^\circ) + 500 \cos(300 t - 60^\circ)$

$x(t) =$ ✓ $\cos (300t +$ ✓ $^\circ)$

b) $y(t) = 250 \cos(377 t + 30^\circ) - 150 \sin(377 t + 140^\circ)$

$y(t) =$ ✓ $\cos (377 t +$ ✓ $^\circ)$

c) $v(t) = 60 \cos(100 t + 60^\circ) - 120 \sin(100 t - 125^\circ) + 100 \cos(100 t + 90^\circ)$

$v(t) =$ ✓ $\cos (100 t +$ ✓ $^\circ)$

d) $w(t) = 100 \cos(\omega t + 40^\circ) + 100 \cos(\omega t + 160^\circ) + 100 \cos(\omega t - 80^\circ)$

$w(t) =$ ✓ $\cos (\omega t +$ ✓ $^\circ)$

Numeric Answer

a) $x(t) = 483.858 \cos (300 t - 48.48^\circ)$

b) $y(t) = 120.512 \cos (377 t + 4.80^\circ)$

c) $v(t) = 152.877 \cos (100 t + 32.94^\circ)$


d) $w(t) = 0 \cos (\omega t + 0^\circ)$

Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

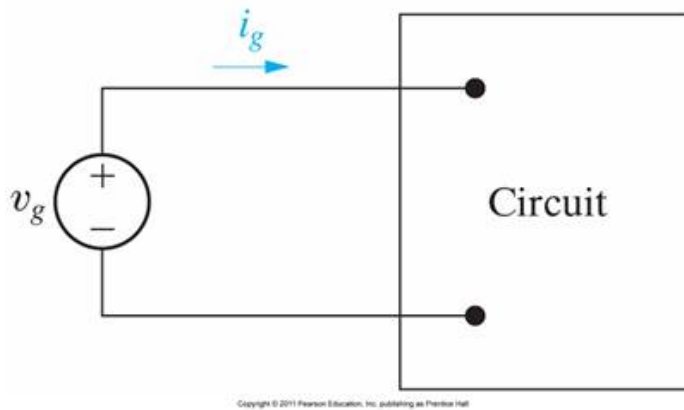Mark 10.00 out of
10.00

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

P9.12_9ed

The expressions for the steady-state voltage and current at the terminals of the circuit are

$$v_g = 300 \cos(5,000 \pi t + 78^\circ) \text{ V}$$

$$i_g = 6 \sin(5,000 \pi t + 123^\circ) \text{ A}$$

a) What is the impedance seen by the source? Write in rectangular form.

$$Z = 35.36 \checkmark + j 35.36 \checkmark \Omega \text{ (Ohm)}$$

b) By how much time t in microseconds is the current out of phase with the voltage?

$$i_g \text{ lags } v_g \text{ by } 50 \checkmark \mu\text{s (micro sec)}$$

Numeric Answer

$$\text{a) } Z = 35.355 + j 35.355 \Omega$$


$$\text{b) } t_{\text{lag}} = 50 \mu\text{s}$$

Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

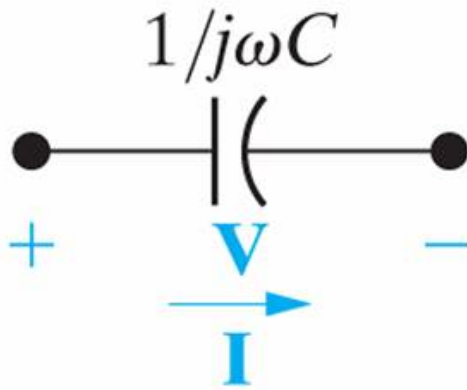Mark 10.00 out of
10.00

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

AP9.04_9ed

The voltage across the terminals of the 5 μF (micro F) capacitor is $30 \cos(4,000t + 25^\circ)$ V.

a) Calculate the capacitive reactance.

$$X_C = \boxed{-50} \checkmark \text{ Ohms}$$

b) Calculate the impedance of the capacitor.

$$Z_C = j \boxed{-50} \checkmark \text{ Ohms}$$

c) Calculate the phasor current **I**.

$$I = \text{Magnitude } \boxed{0.6} \checkmark \text{ with Angle } \boxed{115} \checkmark \text{ Degrees Amps}$$

d) Write the steady-state expression for $i(t)$.

$$i(t) = \boxed{0.6} \checkmark \cos(\boxed{4000} \checkmark t + \boxed{115} \checkmark^\circ) \text{ Amps}$$

Numeric Answer

a) $X_C = -50 \, \Omega$ (Ohm)

b) $Z_C = -j50 \, \Omega$ (Ohm)

c) $I = 0.6 \angle 115^\circ$ Volts

d) $i(t) = 0.6 \cos(4,000t + 115^\circ)$ Volts


Correct

Marks for this submission: 10.00/10.00.

Question 4

Partially correct

Mark 1.67 out of 10.00

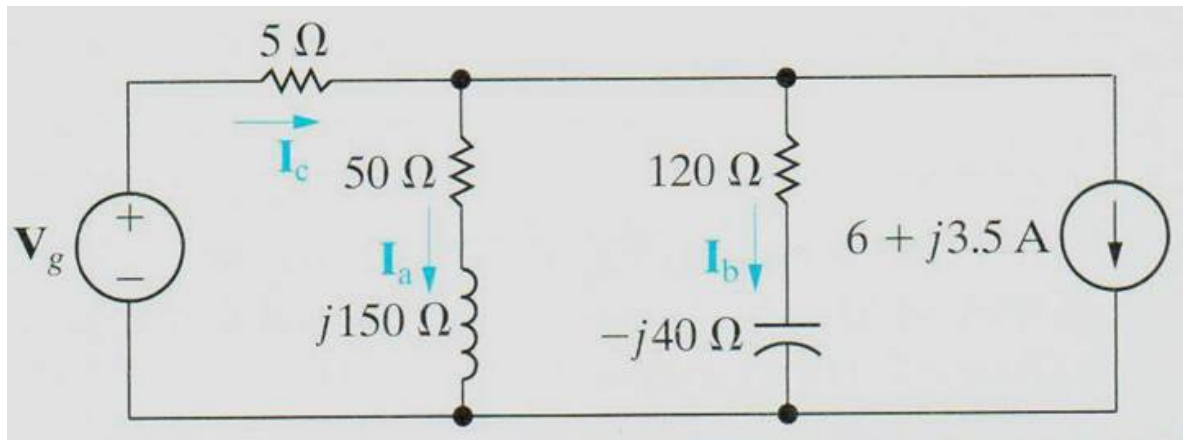

P9.40_7ed

Given the phasor current $\mathbf{I}_a = 2$ at angle 0° A (magnitude 2 with angle 0 degrees Amps).

Find the following phasor values:

\mathbf{I}_b = Magnitude ✓ with Angle ✗° (Degrees) Amps

\mathbf{I}_c = Magnitude ✗ with Angle ✗° (Degrees) Amps

\mathbf{V}_g = Magnitude ✗ with Angle ✗° (Degrees) Volts

Numeric Answer

$\mathbf{I}_b = 2.5$ at angle 90° A

$\mathbf{I}_c = 10.0$ at angle 36.87° A


$\mathbf{V}_g = 358.469$ at angle 67.01° V

Partially correct

Marks for this submission: 1.67/10.00. Accounting for previous tries, this gives **1.67/10.00**.

Question 5

Correct

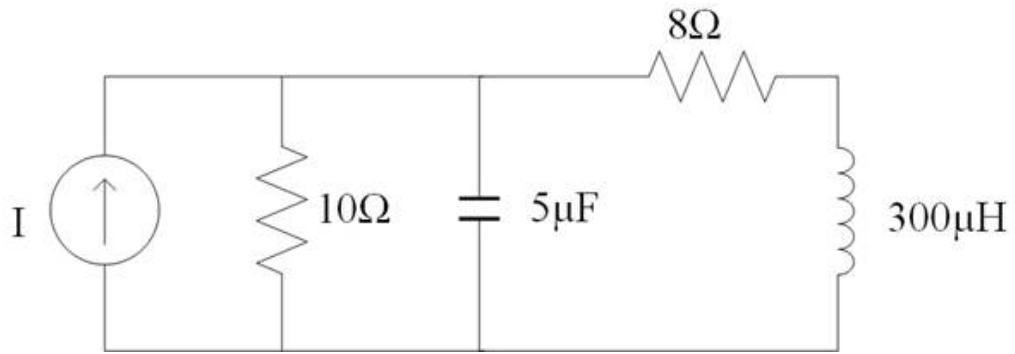Mark 10.00 out of
10.00

P9.16_9ed

Given: $I = 922 \cos(20,000 t + 30^\circ) \text{ A}$.

What is the phasor voltage in polar form across the current source? Use the polarity of “top” equals positive voltage and “bottom” equals the reference node.

 $|V| =$ ✓ VAngle = ✓° (Degrees)**Numeric Answer** $|V| = 5,000.25 \text{ V}$

Angle = 17.47 Degrees


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

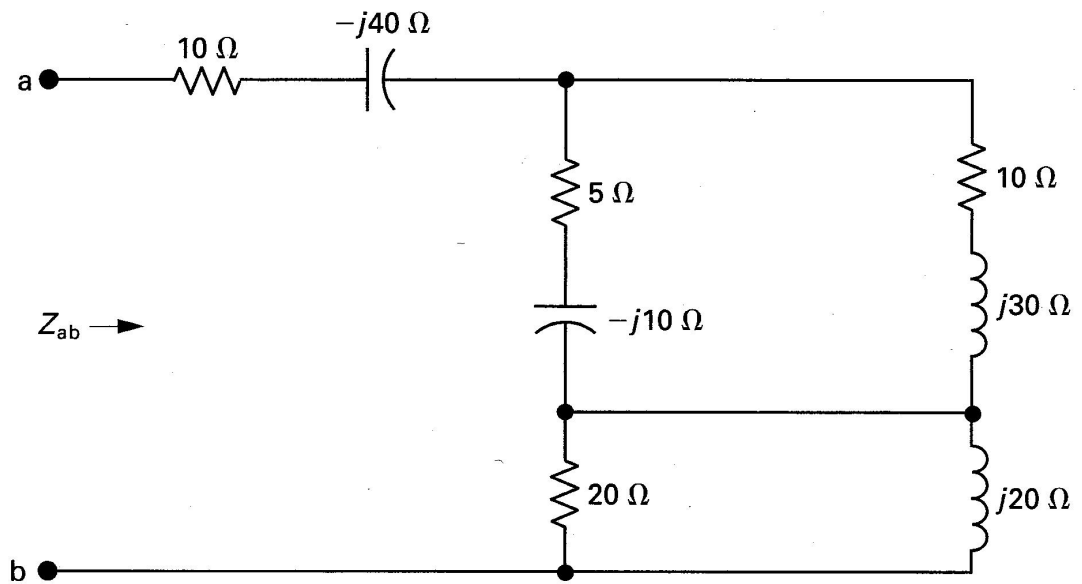


P9.23_6ed

Find the impedance Z_{ab} in this circuit. $Z_{ab} =$ \checkmark $+ j$ \checkmark Ω (Ohms) in rectangular form $Z_{ab} =$ Mag \checkmark and Angle \checkmark $^\circ$ (Degrees) Ω (Ohms) in polar form**Numeric Answer** $Z_{ab} = 30 - j 40\ \Omega$ (Ohms) in rectangular form $Z_{ab} = 50$ at angle $-53.13^\circ\ \Omega$ (Ohms) in polar form**Correct**

Marks for this submission: 10.00/10.00.

Question 7

Correct

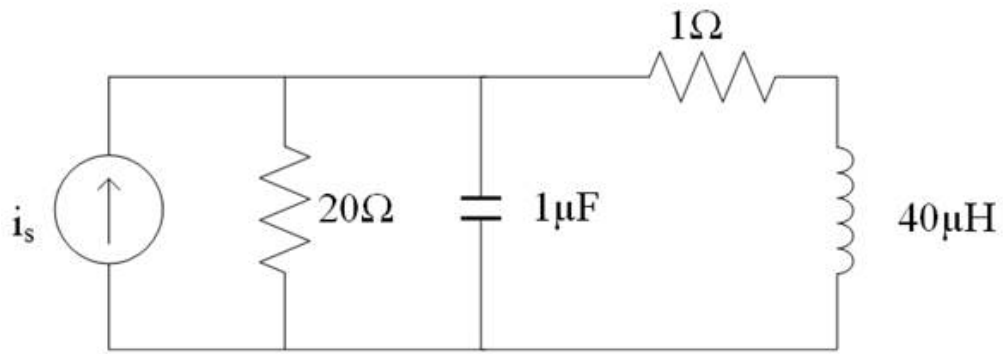Mark 10.00 out of
10.00

P9.09_6ed

Given: $i_s = 20 \cos(50,000t - 20^\circ)$ A.Find the time domain voltage across the 20Ω (Ohm) resistor.

$$v_{20\Omega}(t) = 46.5 \checkmark \cos(50,000 t + 34.46 \checkmark^\circ) \text{ V}$$

Numeric Answer


$$v_{20\Omega}(t) = 46.5 \cos(50,000 t + 34.46^\circ) \text{ Volts}$$

Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

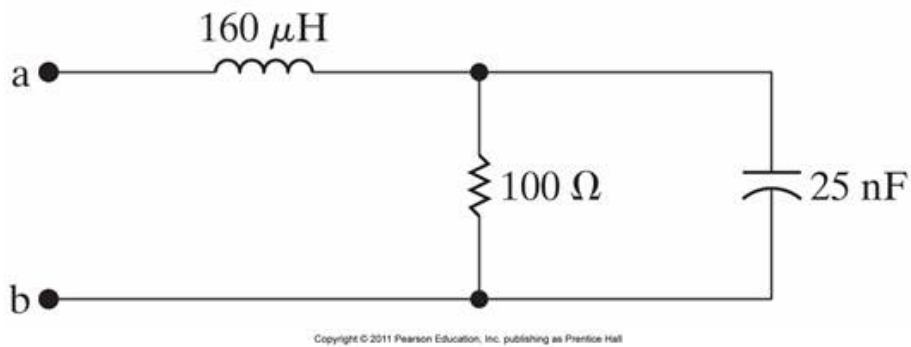Mark 10.00 out of
10.00

P9.25_9ed

a) Find the frequency (in radians per second) at which the impedance Z_{ab} of this circuit appears purely resistive.

$$\omega \text{ (omega)} = \boxed{300} \checkmark \text{ k rad/sec (kilo rad/sec)}$$

b) Find the value of Z_{ab} at the frequency of a).

$$Z_{ab} = \boxed{64} \checkmark \Omega \text{ (Ohm)}$$


Numeric Answer $\omega \text{ (omega)} = 300 \text{ krad/sec (kilo rad/sec)}$ $Z_{ab} = 64 \Omega \text{ (Ohm)}$ **Correct**

Marks for this submission: 10.00/10.00.

Question 9

Partially correct

Mark 8.00 out of 10.00

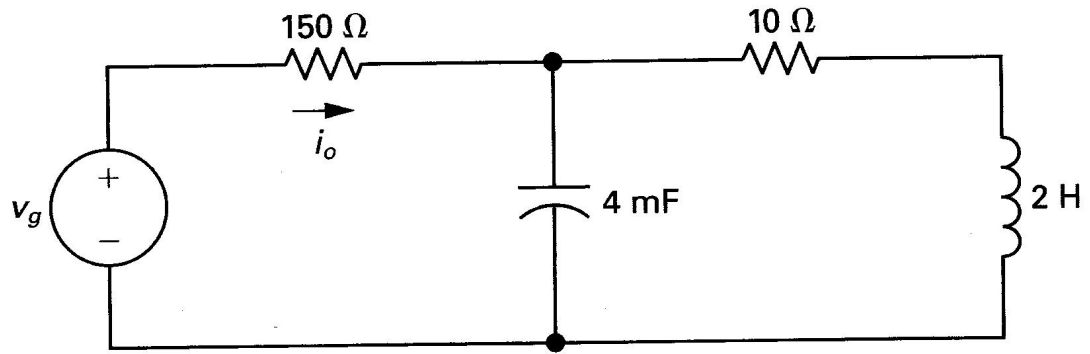

P9.16_6ed

Given: $v_g = 10 \cos(\omega t)\text{ V}$.The frequency ω (Omega) of the input voltage sinusoid is adjusted until the current i_o is in phase with v_g .

a) Find this frequency in Hz.

$$f = 1.59 \text{ Hz}$$

b) Find the equivalent impedance at this frequency.

$$Z_{\text{Eq}} = 50 \ \Omega \text{ (Ohm)}$$

c) Find the time domain current $i_o(t)$ at this frequency.


$$i_o(t) = 50 \cos(10 t + 0^\circ) \text{ mA (milli A)}$$

Numeric Answera) $f = 1.592\text{ Hz}$ b) $Z_{\text{Eq}} = 200\ \Omega \text{ (Ohm)}$ c) $i_o(t) = 50 \cos(10 t) \text{ mA}$ **Partially correct**

Marks for this submission: 8.00/10.00.

Question 10

Incorrect

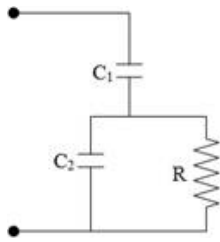Mark 0.00 out of
10.00

Given:

$$C_1 = 2.5 \text{ } \mu\text{F (micro F)} \quad C_2 = 14.2 \text{ } \mu\text{F (micro F)} \quad R = 12.4 \text{ } \Omega \text{ (Ohms)}$$

The radian frequency of the driving source is 3,000 rad/sec

Find the equivalent impedance of this circuit.

$$Z_{\text{Eq}} = 12.35 \text{ } \Omega \text{ (Ohms)} + j -0.00015649452 \text{ } \Omega \text{ (Ohms)}$$

Numeric Answer

$$\text{Real}\{Z_{\text{Eq}}\} = 9.6948 \text{ } \Omega \text{ (Ohms)}$$

$$\text{Imag}\{Z_{\text{Eq}}\} = -j 138.4545 \text{ } \Omega \text{ (Ohms)}$$

Incorrect

Marks for this submission: 0.00/10.00.