

Started on Wednesday, 7 December 2016, 11:03 AM

State Finished

Completed on Wednesday, 7 December 2016, 11:53 AM


Time taken 50 mins

Grade 25.00 out of 100.00

Question 1

Partially correct

Mark 25.00 out of 100.00

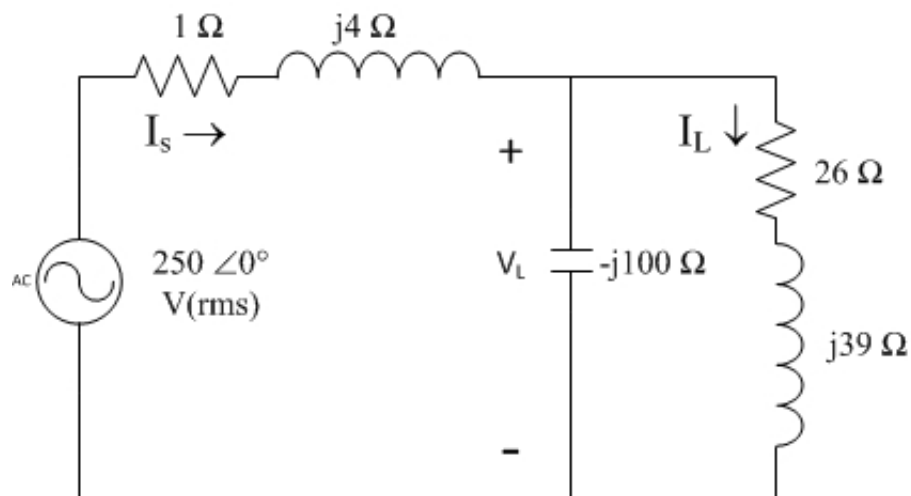

Quiz 12b

The load L is the series resistor and inductor in parallel with the capacitor.

a) Calculate the rms phasors \mathbf{V}_L and \mathbf{I}_L .

$|\mathbf{V}_L| =$ \checkmark V_{rms}

Phase angle $\mathbf{V}_L =$ \times° (Degrees) (smallest negative angle)

$|\mathbf{I}_L| =$ \checkmark A_{rms}

Phase angle $\mathbf{I}_L =$ \times° (Degrees) (smallest negative angle)

b) Calculate the average power and magnetizing reactive power absorbed by the $(26 + j 39) \Omega$ (Ohm) elements.

$P_{\text{avg}} =$ \times W

$$Q = \boxed{} \times \text{VAR}$$

c) Calculate the power factor and the power factor angle seen by the voltage source.

$$\text{pf} = \boxed{} \times$$

$$\text{pf angle } \theta = \boxed{} \times^\circ \text{ (Degrees)}$$

Numeric Answer

a) $V_L = 239.5574$ at angle -2.17° (Degrees) Vrms $I_L = 5.1109$ at angle -58.48° (Degrees) Arms

b) $P_{\text{avg}} = 679.1448$ W $Q = 1,018.7173$ VAR

c) $\text{pf} = 0.815$ $\text{pf angle } \theta = 35.40^\circ$ (Degrees)

Partially correct

Marks for this submission: 25.00/100.00.