

Started on	Thursday, 3 November 2016, 10:25 AM
State	Finished
Completed on	Thursday, 3 November 2016, 11:21 AM
Time taken	55 mins 56 secs
Grade	100.00 out of 100.00

Question 1

Complete

Mark 20.00 out of 20.00

Q1

You have already completed a Bode Diagram in-class.

The instructor will manually grade your Bode Diagram and enter your score here.

Enter nothing here.


Move along to the next question.

Comment:

Question 2

Correct

Mark 10.00 out of 10.00

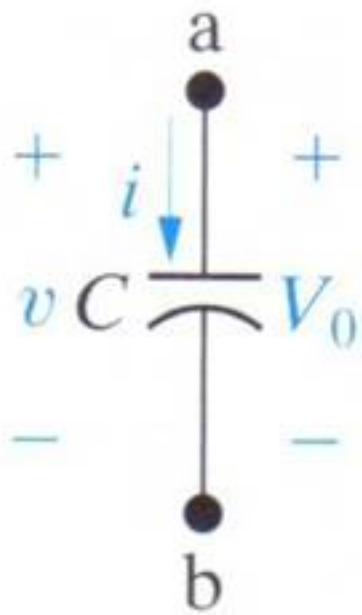

Q2b

Given: This capacitor has a value of 1 μF (micro F) and has an initial voltage of 45 V at t = 0⁻.

Identify the Frequency Domain series form of the capacitor.

Select one:

- ☒ a. $V = \frac{1}{s(1 \times 10^{-6})} + \frac{45}{s}$ ✓
- ☐ b. $V = \frac{1}{s(1 \times 10^{-3})} + \frac{45}{s}$
- ☐ c. $I = s(1 \times 10^{-6})V - 45 \times 10^{-6}$
- ☐ d. $I = s(1 \times 10^{-3})V - 45 \times 10^{-3}$

Your answer is correct.

$$V = \frac{1}{s(1 \times 10^{-6})} + \frac{45}{s}$$

The correct answer is: $V = \frac{1}{s(1 \times 10^{-6})} + \frac{45}{s}$


Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

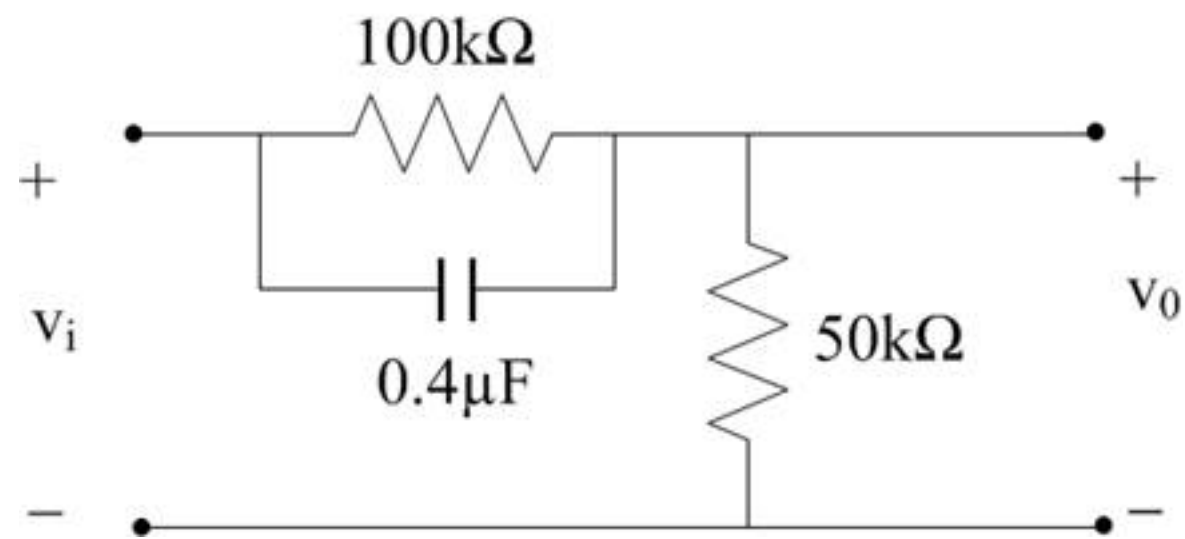

Q3b

Find the s domain transfer function $H(s) = V_0/V_i$ for this circuit.

$H(s) = (s + 25)$ ✓
 $) / (s + 75)$ ✓)

$$H(s) = \frac{s+25}{s+75}$$


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 15.00 out of 15.00

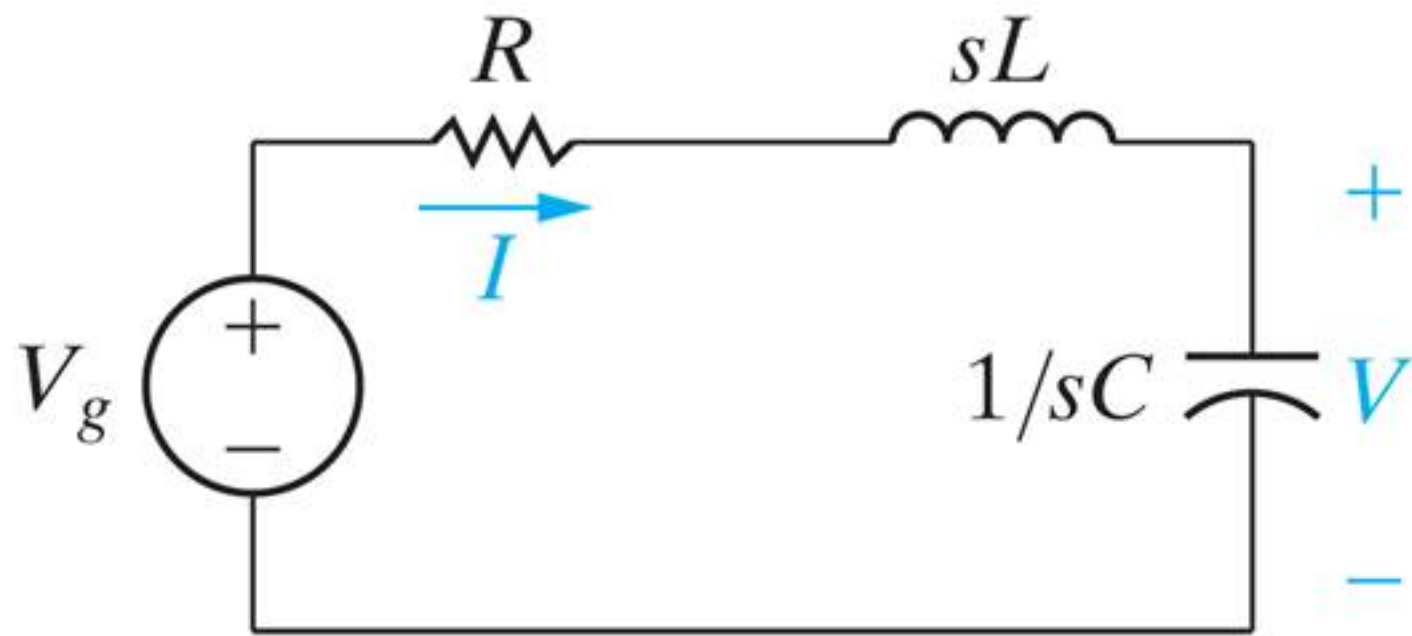

Q4b

Given: There is no energy stored in this circuit prior to $t = 0$.

The voltage source $V_g = 25 \text{ V}$ for $t \geq 0^+$.

$R = 250 \text{ } \Omega$ (Ohm) $L = 1 \text{ H}$ $C = 2 \text{ mF}$ (milli F)

Find defined voltage V in the s domain.

$V(s) =$ ✓
/ $[s (s^2 +$ ✓ $s +$ ✓ $)]$

$$V(s) = \frac{12,500}{s(s^2 + 250s + 500)}$$

Correct

Marks for this submission: 15.00/15.00.

Question **5**

Correct

Mark 15.00 out of 15.00

Q5c

Given: $F(s) = \frac{25s+40}{s(s+10)}$

Find the partial fraction expansion of this transfer function.

F(s) = ✓
/ s + ✓ / (s + 10)

$$F(s) = \frac{25s+40}{s(s+10)} = \frac{4}{s} + \frac{21}{s+10}$$


Correct

Marks for this submission: 15.00/15.00.

Question 6

Correct

Mark 15.00 out of 15.00

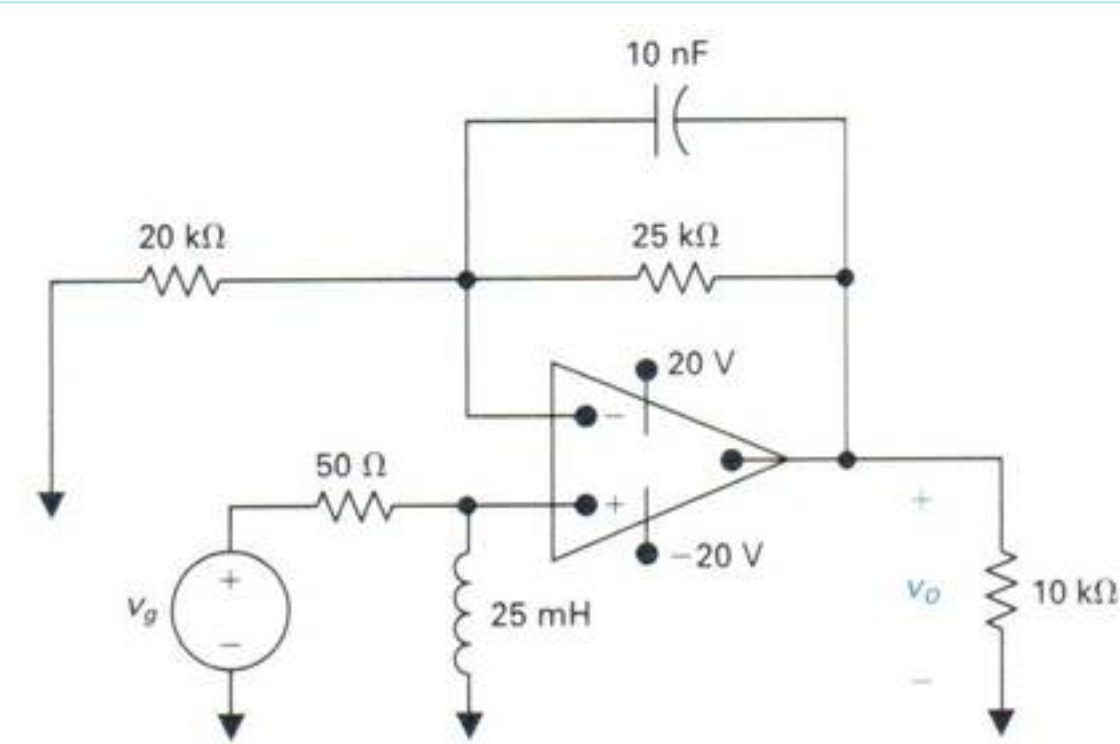

Q6d

Given: The opamp is ideal.

$$H(s) = \frac{V_o}{V_g} = \frac{s(s+9,000)}{(s+2,000)(s+4,000)}$$

Find the steady-state response when the input $v_g(t) = 11 \cos(5,000 t) \text{ V}$.

$v_o(t)_{\text{steady-state}} = [\text{16.4} \checkmark$
 $\cos (\text{5000} \checkmark t + \text{-0.48} \checkmark^\circ)] u(t) \text{ V}$

Numeric Answer

$v_o(t)_{\text{steady-state}} = 16.4219 \cos (5,000 t - 0.484^\circ) u(t) \text{ V}$

Correct

Marks for this submission: 10.00/15.00. Accounting for previous tries, this gives **10.00/15.00**.

Comment:
Your answer is correct. Answer guide was rounded incorrectly. Score adjusted.

Question 7

Correct

Mark 15.00 out of 15.00

Q7c

Given
$$H(s) = \frac{(45,000)(s+200)}{(s+2,000)(s+9,000)}$$

a) What is the zero of this function in the form $s + z_1$?

$z_1 =$ ✓

b) What are the two poles of this function in the form $s + p_{1,2}$?

$p_1 =$ ✓

(positive lower value)

$p_2 =$ ✓

(positive higher value)

c) What is the *gain* K in dB after putting this function in *Standard Form*?

$K =$ ✓

dB

For the following use the Bode diagram straight-line approximation conventions (do not plot the function)

d) Find the magnitude of this transfer function at $\omega = 2,000$ rad/sec.

$| H(j\omega = 2,000 \text{ rad/sec}) | =$ ✓

dB

e) Find the phase angle at $\omega = 2,000$ rad/sec

$\theta(j\omega = 2,000 \text{ rad/sec}) =$ ✓

° (Degrees)

Numeric Answer

a) $z_1 = 200$

b) $p_1 = 2,000$ $p_2 = 9,000$

c) K in dB = -6.0206 dB

d) $| H(j\omega = 2,000 \text{ rad/sec}) | = 14$ dB

e) $\theta(j\omega = 200 \text{ rad/sec}) = 45^\circ$

Correct

Marks for this submission: 15.00/15.00.