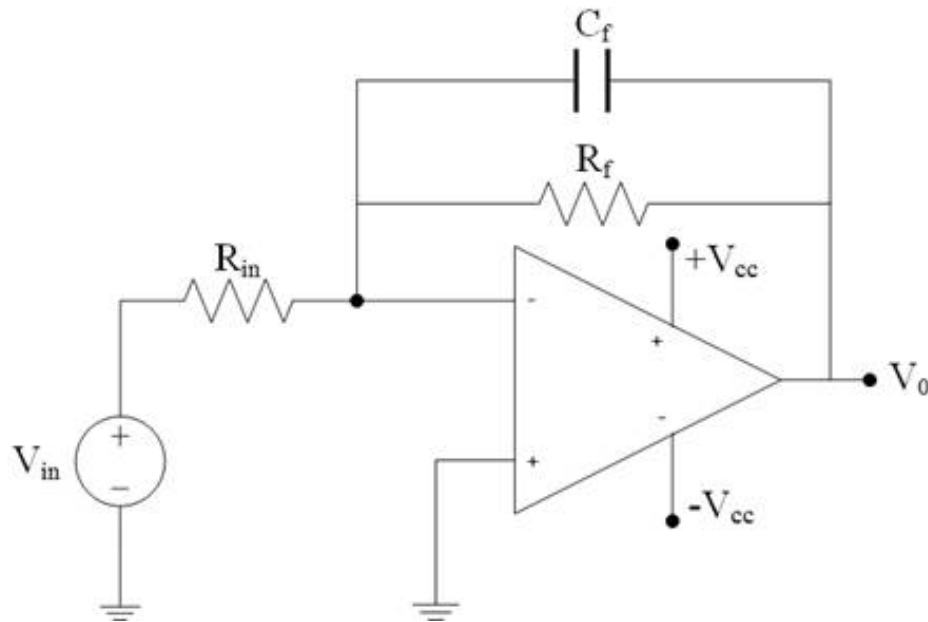


Started on	Wednesday, 8 February 2017, 11:55 AM
State	Finished
Completed on	Wednesday, 8 February 2017, 12:55 PM
Time taken	1 hour
Grade	33.33 out of 100.00

Question 1

Partially correct

Mark 33.33 out of 100.00



Quiz 2b

The operational amplifier is ideal.

Given:

$$R_{in} = 10 \text{ k}\Omega \text{ (kilo Ohm)} \quad R_f = 14 \text{ k}\Omega \text{ (kilo Ohm)} \quad C_f = 0.1 \text{ }\mu\text{F (micro F)}$$

$$+V_{cc} = 15 \text{ V} \quad -V_{cc} = -15 \text{ V}$$

For each question below, report your answer in the form of real + j imaginary

a) Find the steady-state phasor output \mathbf{V}_0 when $V_{in}(t) = 5 \text{ V}$.

$$\mathbf{V}_0 = \boxed{-7} \checkmark + j \boxed{0} \checkmark \text{ Volts}$$

b) Find the steady-state phasor output \mathbf{V}_0 when $V_{in}(t) = 5 \cos(500t) \text{ V}$.

$$\mathbf{V}_0 = \boxed{-3.54} \times = j \boxed{3.54} \times \text{ Volts}$$

c) Find the magnitude of the steady-state phase output \mathbf{V}_0 when $V_{in}(t) = 5 \cos(5,000t) \text{ V}$.

$$\mathbf{V}_0 = \boxed{-0.2} \times + j \boxed{3.54} \times \text{ Volts}$$

a) $\mathbf{V}_0 = -7.0 + j 0 \text{ V} = 7.0 \text{ at angle } 180^\circ \text{ V}$ b) $\mathbf{V}_0 = -4.6980 + j 3.2886 \text{ V} = 5.7346 \text{ at angle } 145.01^\circ \text{ V}$ c) $\mathbf{V}_0 = -0.1400 + j 0.9800 \text{ V} = 0.9899 \text{ at angle } 98.13^\circ \text{ V}$ **Partially correct**

Marks for this submission: 33.33/100.00. Accounting for previous tries, this gives

33.33/100.00.