

Started on Wednesday, 14 December 2016, 10:11 AM

State Finished

Completed on Wednesday, 14 December 2016, 12:11 PM


Time taken 1 hour 59 mins

Grade 95.00 out of 100.00

Question 1

Correct

Mark 10.00 out of 10.00

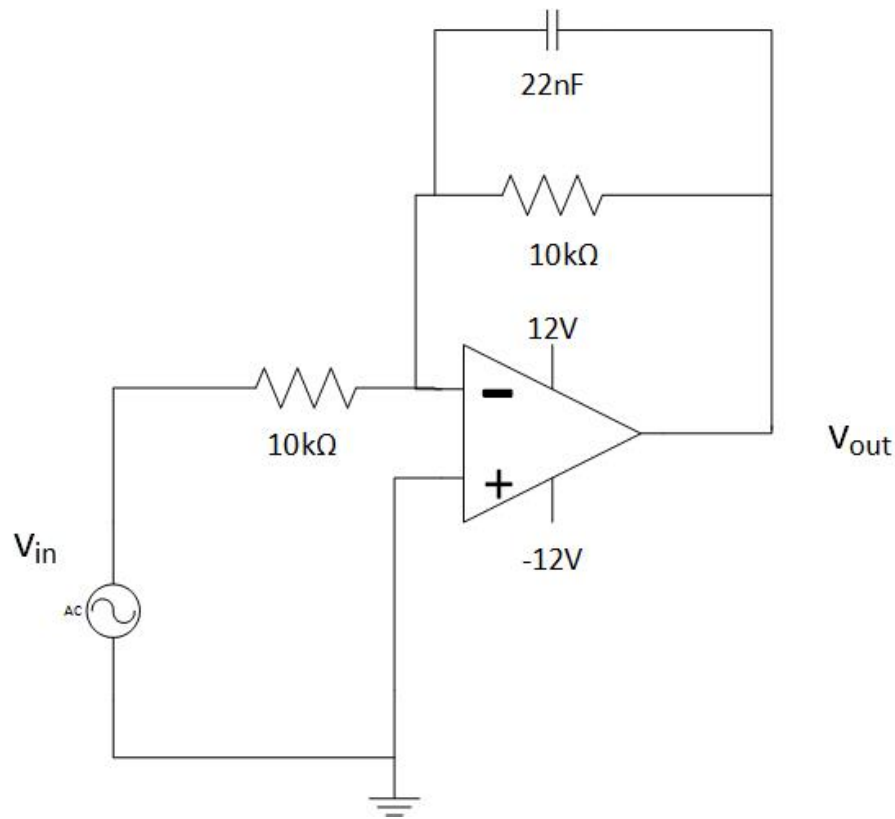

Q1b

Given $V_{in} = 10 \cos(200t)$.

What is the steady state output V_{out} ?

State your answer in the rectangular form Real + j Imaginary.

$V_{out} =$ ✓ + j ✓ V


Correct

Marks for this submission: 10.00/10.00.

Question 2

Partially correct

Mark 10.00 out of 15.00

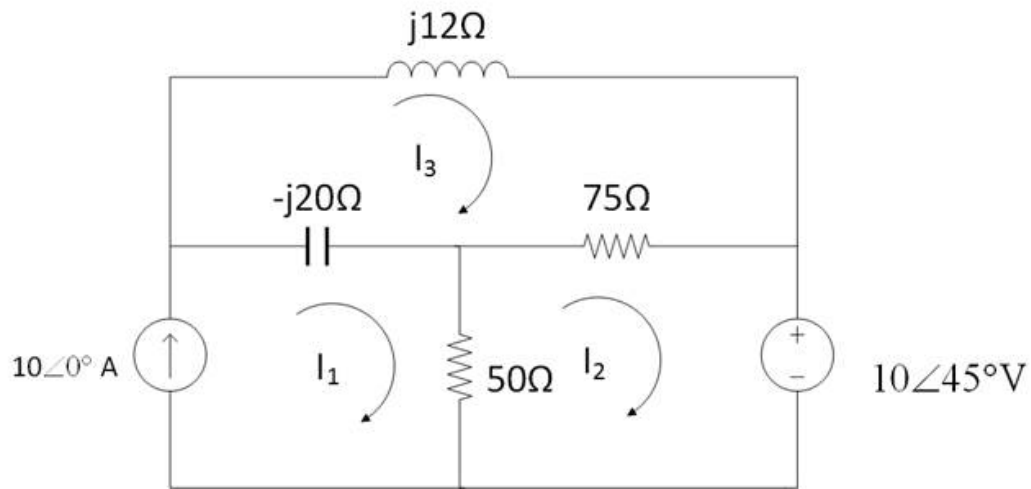

Q2e

Find the three mesh currents.

State your answer in the rectangular form Real + j Imaginary.

$$I_1 = 10 + j 0 \text{ Amps}$$


$$I_2 = 10.3 + j 0 \text{ Amps}$$

$$I_3 = 10.7 + j 0 \text{ Amps}$$

Partially correctMarks for this submission: 10.00/15.00. Accounting for previous tries, this gives **10.00/15.00**.**Question 3**

Correct

Mark 15.00 out of 15.00

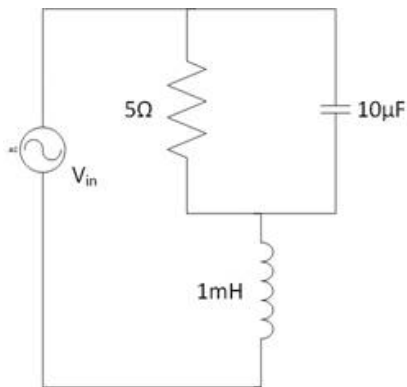

Q3d

$$\text{Given } V_{in} = 22 \cos(10,000 t)$$

Find the steady state phasor current through the 5 W (Ohm) resistor.

State your answer with the smallest appropriate negative angle.


$$I_{5W} \text{ (polar form) Magnitude } 2.24 \text{ Phase } -90^\circ \text{ (Degree) Amps}$$

Correct

Marks for this submission: 15.00/15.00.

Question 4

Correct

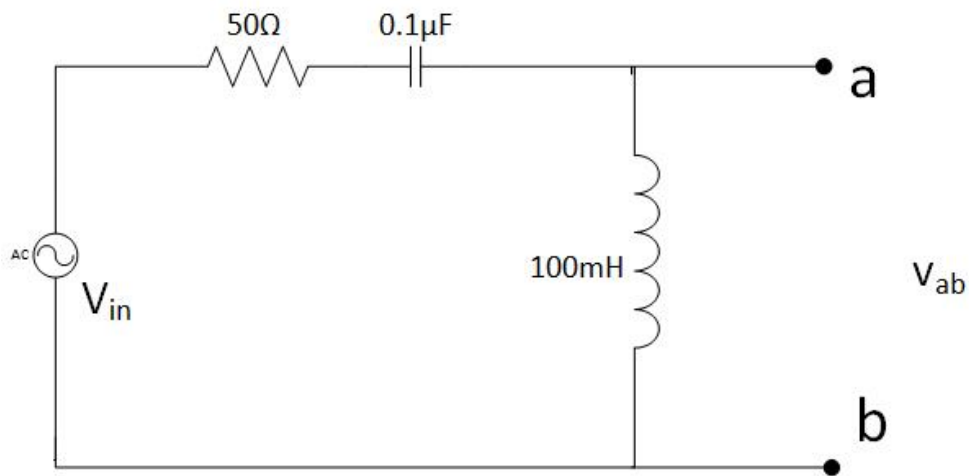Mark 15.00 out of
15.00

Q4c

Given $V_{in} = 12 \cos(10,000 t)$

Find the Thévenin phasor equivalent of this circuit.


 Z_{Th} (rectangular form) = ✓ + j ✓ Ω (Ohm) V_{Th} (rectangular form) = ✓ + j ✓ V**Correct**

Marks for this submission: 15.00/15.00.

Question 5

Correct

Mark 10.00 out of 10.00

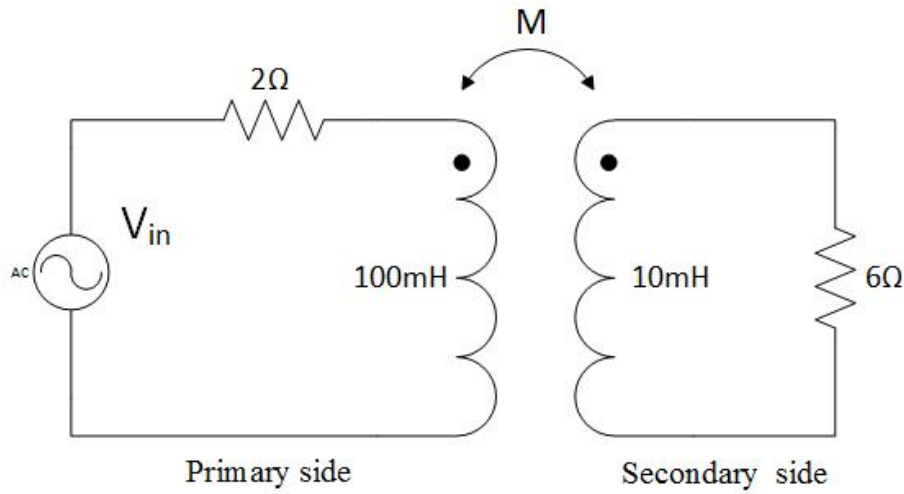

Q5a

Given $V_{in} = 120 \cos(377t) \text{ V}_{\text{rms}}$ and coefficient of coupling $k = 0.9$

a) Find the mutual inductance between the two windings.

$M =$ \checkmark mH (milli H)

b) Find the magnitude of the reflected impedance from the secondary side to the primary (source) side.

$|Z_r| =$ \checkmark Ω (Ohm)

c) Find the current in the primary side.

State as positive current magnitude and smallest appropriate negative angle.

$|I_1| =$ \checkmark A_{rms} Angle $I_1 =$ \checkmark $^\circ$ (Degree)


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

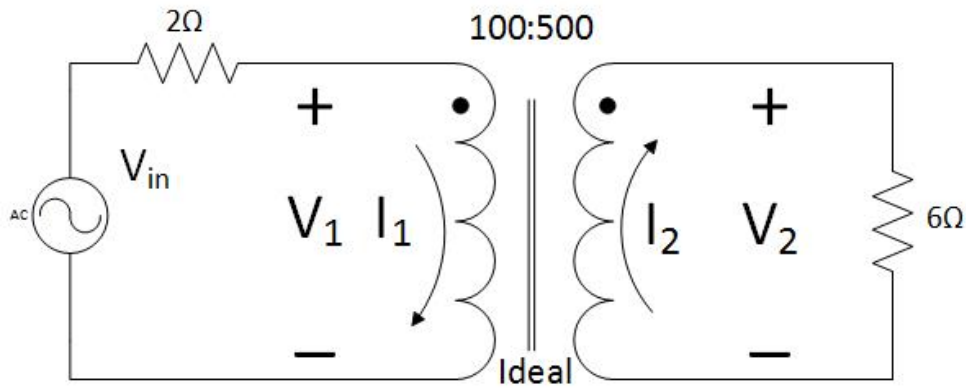

Q6a

Given: The transformer is ideal.

$$V_{in} = 120 \cos(377 t) \text{ V}$$

a) Find the magnitude of the current I_1 . $|I_1| =$ \checkmark A

b) Find the magnitude of the voltage V_1 . $|V_1| =$ \checkmark V

Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

Q7c

A circuit has the following input voltage with the resulting current:

$$v = 240 \sin(377 t) \text{ V}_{\text{rms}}$$

$$i = 13 \cos(377 t - 125^\circ) \text{ A}_{\text{rms}}$$

a) Find the average power absorbed by the circuit. $P =$ \checkmark W

b) Find the reactive power. $Q =$ \checkmark VAR

c) Find the apparent power. $|S| =$ \checkmark VA

Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 5.00 out of 5.00

Q8f

A circuit has the following input voltage with the resulting current:

$$v = 120 \cos(377t - 45^\circ) \text{ V}_{\text{rms}}$$

$$i = 7 \cos(377t + 10^\circ) \text{ A}_{\text{rms}}$$

a) Find the power factor of this circuit. pf = ✓

b) Is this a lagging or leading power factor?


 ✓**Correct**

Marks for this submission: 5.00/5.00.

Question 9

Correct

Mark 10.00 out of 10.00

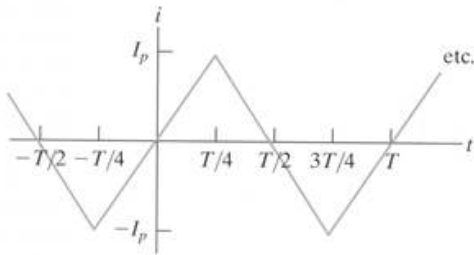

Q9d

The periodic triangular current has a peak value of 200 mA (milli Amp).

a) Find the rms value of the current.

$$I_{p,\text{rms}} = \text{115.47} \text{ mA}_{\text{rms}} \text{ (milli A}_{\text{rms}})$$

b) Find the average power that this current delivers to a 5 k Ω (kilo Ohm) resistor.

$$P_{\text{avg}} = \text{66.67} \text{ W}$$

Correct

Marks for this submission: 10.00/10.00.