
 


 1. The following reset signal is asynchronous



Complete the following waveform:



```
Library ieee;
Use ieee.std_logic_1164.all;
entity prob1 (a, b, reset: in std_logic;
q1, q2: out std_logic);
end prob1;
architecture circuit of prob1 is
signal clk, m, d1, t1, t2: std_logic;
begin
clk <= a nand m;
m <= b nand clk;
d1 <= not t2;
process (clk, reset)
begin
if (reset = '1') then
t1 <= '0';
elsif (rising_edge(clk)) then
t1 <= d1;
end if;
end process;
process (clk, reset)
begin
if (reset = '1') then
t2 <= '0';
elsif (falling_edge(clk)) then
t2 <= t1;
end if;
end process;
q1 <= t1;
q2 <= t2;
end circuit;
```

3. Draw the synthesized schematic for the VHDL code


```
process(a, b, sel)
begin
if (sel = '1') then
c <= a;
else
c <= b;
end if;
end process;
```

TESTBENCH

```
Library ieee;
Use ieee.std_logic_1164.all;
entity prob1_tb
end prob1_tb;
architecture beh of prob1_tb is
signal a, b, reset: std_logic;
signal q1, q2: std_logic;
component prob1 (a, b, reset: in std_logic;
q1, q2: out std_logic);
end component;
begin
uut: prob1 port map (a, b, reset, q1, q2);
-- Method 2:
-- uut: prob1 port map (a => a, b => b, reset => reset, q1 => q1, q2 => q2);
-- port mapping rule: lower level entity pin name => top level testing signal name
process
begin
reset <= '1';
wait for 5 ns;
reset <= '0';
wait for 100 ns;
wait;
end process;
b <= not a;
process
begin
a <= '1';
wait for 10 ns;
a <= '0';
wait for 5 ns;
a <= '1';
wait for 5 ns;
a <= '0';
wait for 5 ns;
a <= '1';
wait for 5 ns;
a <= '0';
wait for 5 ns;
a <= '1';
wait for 5 ns;
a <= '0';
wait for 5 ns;
wait;
end process;
end beh;
```

Draw the synthesized schematic for the VHDL code.


Solution:

 

```
process (a, b, sel)
begin
case (sel) is
when '0' => c <= ~b;
when '1' => c <= a;
end case;
end process;
```

Draw the synthesized schematic for the VHDL code.


Solution:

 

```
process ((s1, s0, a, b, c))
begin
if (s1 = '1') then
d <= a;
elsif (s0 = '0') then
d <= b;
else
d <= c;
end if;
end process;
```

Draw the synthesized schematic for the VHDL code.


Solution:

 

```
process (clock)
begin
if (rising_edge(clock)) then
m1 <= din;
m2 <= m1;
m3 <= m2;
end if;
end process;
```

Draw the synthesized schematic for the VHDL code.


Solution:

 

```
process (clock)
begin
if (rising_edge(clock)) then
if (sel = '1') then
c <= a;
else
c <= b;
end if;
end if;
end process;
```

Draw the synthesized schematic for the VHDL code.

Solution:

 


2. Write testbench for the finite state machine and complete the waveform


```
Library ieee;
Use ieee.std_logic_1164.all;
entity prob2_fsm (w, Reset, Clk: in std_logic;
M, N: out std_logic);
end prob2_fsm;
Architecture beh of prob2_fsm is
type st is ( SA, SB, SC );
signal cs, ns: st;
begin
process (w, cs)
begin
case (cs)
when SA => if (w = '0') then
ns <= SA;
else
ns <= SB;
end if;
when SB => if (w = '0') then
ns <= SA;
else
ns <= SC;
end if;
when SC => if (w = '0') then
ns <= SA;
else
ns <= SC;
end if;
when others => ns <= SA;
end case;
end process;
process (Clk, Reset)
begin
if (Reset = '1') then
cs <= SA;
elsif (rising_edge(Clk)) then
cs <= ns;
end if;
end process;
M <= '1' when (cs = SC) else '0';
N <= w when (cs = SB) else '0';
end beh;
```

Draw state diagram for the finite state machine.

Solution:

 


 Complete the following waveform for signals cs, ns, M, and N.



```
Library ieee;
Use ieee.std_logic_1164.all;
entity prob2_fsm_tb
end prob2_fsm_tb;
architecture beh of prob2_fsm_tb is
signal w, Reset, Clk: std_logic;
signal M, N: std_logic;
component prob2_fsm (w, Reset, Clk: in std_logic;
M, N: out std_logic);
end component;
begin
uut: prob2_fsm port map (w, Reset, Clk, M, N);
reset <= '1', '0' after 15 ns;
w <= '0', '1' after 35 ns;
process
begin
Clk <= '1'; wait for 10 ns;
Clk <= '0'; wait for 10 ns;
end process;
end beh;
```

 Complete the following waveform for signals cs, ns, M, and N.



1. [28 points] Fill out the blanks shown below.

[1]. Given the following VHDL statement,
rst <= '0', '1' after 100 ns, '0' after 200 ns;
rst is 0 at time zero, 1 at time 50 ns, 0 at time 100 ns, 1 at time 150 ns, 0 at time 200 ns, 0 at time 300 ns;

[2]. Each of the D2, D1, D0 signals is std_logic type,
signal D2, D1, D0: std_logic;
signal D3: std_logic_vector(2 downto 1);

Given the following codes:
D2 <= '0'; D1 <= '1'; D0 <= '1';
D3 <= (D2 xor D1) & (D1 nor D0);

What is binary value for D3? D3 010

[3]. (7,4) hamming code construction diagram is shown below.
If d4 d3 d2 d1 = "1100", the constructed 7-bit hamming code is:
Bit 7: 0 Bit 6: 1 Bit 5: 1 Bit 4: 0 Bit 3: 0 Bit 2: 0 Bit 1: 0
1100001

Complete the following waveform:

INPUTS		A	B	AND	NAND	OR	NOR	EXOR	EXNOR
		0	0	0	1	0	1	0	1
		0	1	0	1	1	0	1	0
		1	0	0	1	1	0	1	0
		1	1	1	0	0	1	0	1
NOT gate		A	A'						
		0	1						
		1	0						

Data bits				parity		
D3	D2	D1	D0	P3	P2	P1
0	0	0	0	0	0	0
1	0	0	0	1	0	1
2	0	0	1	0	1	0
3	0	0	1	1	1	0
4	0	1	0	0	1	1
5	0	1	0	1	1	0
6	0	1	1	0	0	1
7	0	1	1	1	0	0
8	1	0	0	0	1	1
9	1	0	0	1	1	0
A	1	0	1	0	0	1
B	1	0	1	1	0	0
C	1	1	0	0	0	1
D	1	1	0	1	0	1
E	1	1	1	0	1	0
F	1	1	1	1	1	1

Table 1

Data bits and Hamming code.

5. CRC Error Detection	
Message 110101	
Generating Polynomial = 101	
110101	111011
101	
111	
101	
100	
101	
011	
000	
110	
101	
110	
101	
11	
Message with CRC = 11010111	


Quotient (has no function in CRC calculation)

Remainder = CRC checksum

Description	CKT Diagram	VHDL Model
Typical logic circuit		<pre> entity my_ckt is Port (A,B,C,D : in std_logic; F : out std_logic); end my_ckt; architecture ckt1 of my_ckt is begin F <= (A AND B) OR (C AND (NOT D)); end ckt1; architecture ckt2 of my_ckt is begin F <= '1' when (A = '1' AND B = '1') else '1' when (C = '1' AND D = '0') else '0'; end ckt2; </pre>
4:1 Multiplexor		<pre> entity MUX_4T1 is Port (SEL : in std_logic_vector(1 downto 0); D_IN : in std_logic_vector(3 downto 0); F : out std_logic); end MUX_4T1; architecture my_mux of MUX_4T1 is begin F <= D_IN(0) when (SEL = "00") else D_IN(1) when (SEL = "01") else D_IN(2) when (SEL = "10") else D_IN(3) when (SEL = "11") else '0'; end my_mux; </pre>
2:4 Decoder		<pre> entity DECODER is Port (SEL : in std_logic_vector(1 downto 0); F : out std_logic_vector(3 downto 0)); end DECODER; architecture my_dec of DECODER is begin with SEL select F <= "0001" when "00", "0010" when "01", "0100" when "10", "1000" when "11", "0000" when others; end my_dec; </pre>
8-bit register with chip load enable		<pre> entity REG is port (LD,CLK : in std_logic; D_IN : in std_logic_vector (7 downto 0); D_OUT : out std_logic_vector (7 downto 0)); end REG; architecture my_reg of REG is begin process (CLK,LD) begin if (LD = '1' and rising_edge(CLK)) then D_OUT <= D_IN; end if; end process; end my_reg; </pre>
8-bit up/down counter with asynchronous reset		<pre> entity COUNT_8B is port (RESET,CLK,LD,UP : in std_logic; DIN : in std_logic_vector (7 downto 0); COUNT : out std_logic_vector (7 downto 0)); end COUNT_8B; architecture my_count of COUNT_8B is signal t_cnt : std_logic_vector(7 downto 0); begin process (CLK, RESET) begin if (RESET = '1') then t_cnt <= "00000000"; elsif (rising_edge(CLK)) then if (LD = '1') then t_cnt <= DIN; else if (UP = '1') then t_cnt <= t_cnt + 1; else t_cnt <= t_cnt - 1; end if; end if; end if; end process; COUNT <= t_cnt; end my_count; </pre>

a, b & c are 3 input signals. clk is also an input signal. a & b is given to 2 i/p nand gate and its output is f1. f1 & not c is given as input to 2 to 1 MUX. When clk is at rising edge and select line is 1 the output of MUX f2 is f1 else if S=0 then f2 is not of c (c). Then f2 is given as input to D flip flop and at rising edge of clock its output f3 is f2.

The RTL Schematic of VHDL code

 

Count Value	Output Frequency
1	25MHz
25	1MHz
50	500KHz
1000	25KHz
25000000	1Hz

VHDL Code for Clock Divider

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.numeric_std.ALL;
4
5 entity Clock_Divider is
6 port ( clk,reset: in std_logic;
7       clock_out: out std_logic);
8 end Clock_Divider;
9
10 architecture bhv of Clock_Divider is
11
12 signal count: integer:=1;
13 signal tmp : std_logic := '0';
14
15 begin
16
17 process(clk,reset)
18 begin
19   if(reset='1') then
20     count<=1;
21     tmp<='0';
22   elsif(clk'event and clk='1') then
23     count <=count+1;
24     if (count = 25000) then
25       tmp <= NOT tmp;
26       count <= 1;
27     end if;
28   end if;
29   clock_out <= tmp;
30 end process;
31
32 end bhv;

```

VHDL Testbench code for Clock Divider

```

1 LIBRARY ieee;
2 USE ieee.std_logic_1164.ALL;
3
4 ENTITY Tb_clock_divider IS
5 END Tb_clock_divider;
6
7 ARCHITECTURE behavior OF Tb_clock_divider IS
8
9 -- Component Declaration for the Unit Under Test (UUT)
10
11 COMPONENT Clock_Divider
12 PORT(
13   clk : IN std_logic;
14   reset : IN std_logic;
15   clock_out : OUT std_logic
16 );
17 END COMPONENT;
18
19 --Inputs
20 signal clk : std_logic := '0';
21 signal reset : std_logic := '0';
22
23 --Outputs
24 signal clock_out : std_logic;
25
26 -- Clock period definitions
27 constant clk_period : time := 20 ns;
28
29 BEGIN
30
31 -- Instantiate the Unit Under Test (UUT)
32 uut: Clock_Divider PORT MAP (
33   clk => clk,
34   reset => reset,
35   clock_out => clock_out
36 );
37
38 -- Clock process definitions
39 clk_process:process
40 begin
41   clk <= '0';
42   wait for clk_period/2;
43   clk <= '1';
44   wait for clk_period/2;
45 end process;
46
47 -- Stimulus process
48 stim_proc: process
49 begin
50   wait for 100 ns;
51   reset <= '1';
52   wait for 100 ns;
53   reset <= '0';
54   wait;
55 end process;
56
57 END;

```

[16 points] Draw the synthesized schematic for the VHDL code.

signal a, b, c, d, sel: std_logic;
...
...

```

process (a , b , c, d, sel)
begin
  case (sel) is
    when '0' => y <= a or b;
    when '1' => y <= c and d;
  end case;
end process;

```

signal a, b, c: std_logic;
signal f1, f2, f3;
...
...


f1 <= a nand b;

```


process (clock)
begin
  if (rising_edge(clock)) then
    if (s = '1') then
      f2 <= f1;
    else
      f2 <= not c;
    end if;
    f3 <= f2;
  end if;
end process;

```

 
Draw the synthesized schematic for the VHDL code.



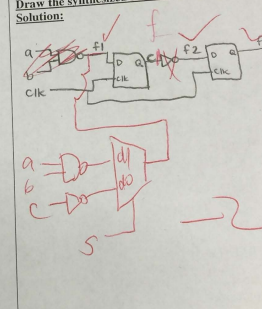Draw the synthesized schematic for the VHDL code.



 [32 points]
 Design the following circuit in VHDL. This circuit is required to be loaded with value Q4 Q3 Q2 Q1 = "1100" if the asynchronous reset control signal is logic '1'.



```

library ieee;
use ieee.std_logic_1164.all;
entity flop is port(
  clk, reset: in std_logic;
  Q4, Q3, Q2, Q1: out std_logic);
end flop;

architecture archi of flop is
  signal clk, t1, D2, Q3, t2, t3, t4: std_logic;
begin
  t1 <= xor(Q3, Q4);
  D2 <= t1;
  process (reset, clk)
  begin
    if (reset = '1') then
      Q4 <= '1';
      Q3 <= '1';
      Q2 <= '0';
      Q1 <= '0';
    elsif (rising_edge(clk)) then
      Q4 <= t4;
      Q3 <= t3;
      Q2 <= t2;
      Q1 <= t1;
    end if;
  end process;
end archi;
  
```

t2? X
 t3? X
 t4? X

```

8 //Answer Question 2
9 Q: out std_logic_vector(4downto1);
10 end flop;
11
12 architecture whatever of flop is //MAKE SURE YOU CHANGE THE NAME OF whatever TO SOMETHING DIFFERENT
13 signal t: std_logic_vector(4downto1);
14 process (clk, reset)
15 begin
16   if (reset='1') then
17     t<="1100";
18   elsif (rising_edge(clk)) then
19     t(1) <= t(2);
20     t(2) <= t(3) xor t(1);
21     t(3) <= t(4);
22     t(4) <= t(1);
23   end if;
24 end process;
25
26 Q<=t;
27 end whatever; //MAKE SURE YOU CHANGE THE NAME OF whatever TO SOMETHING DIFFERENT
28
29 //Testbench, flop_tb can be renamed
30
31 library ieee;
32 use ieee.std_logic_1164.all;
33 entity flop_tb
34 entity flop_tb
35 architecture beh of flop_tb is
36 component flop (
37   clk, reset: in std_logic;
38   Q: out std_logic_vector(4downto1);
39 end component;
40 signal clk, D, reset: std_logic;
41 signal Q: std_logic_vector(4downto1);
42 constant clk2: time := 100 ns;
43
44 begin
45   uut: flop port map (clk, reset, Q);
46
47   clk process :process
48   begin
49     clk <= '0';
50     wait for clk2/2;
51     clk <= '1';
52     wait for clk2/2;
53     end process;
54
55   process
56   begin
57     reset <='1';
58     wait 5ns;
59     reset <='0'
60     wait 5ns;
61     wait;
62   end process;
63 end beh;
64
  
```

