

Home ► My courses ► EEE117-2017S-Tatro ► Homework ► Homework 14 - Chapter 16

Started on Sunday, 7 May 2017, 11:58 AM

State Finished

Completed on Sunday, 7 May 2017, 9:41 PM


Time taken 9 hours 43 mins

Grade 100.00 out of 100.00

Question 1

Correct

Mark 11.00 out of 11.00

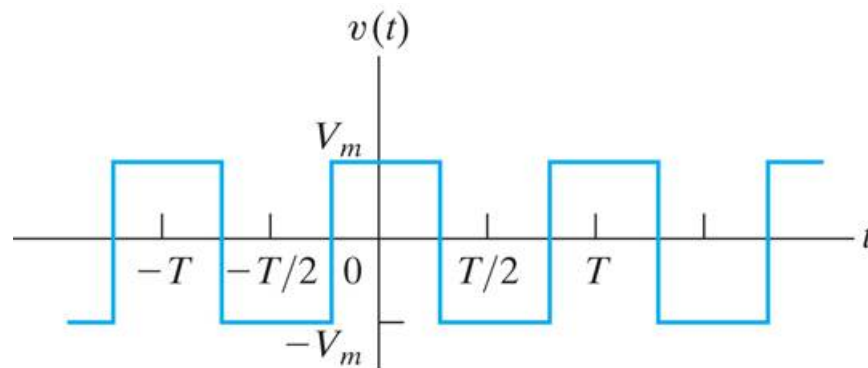

P16.13a_10ed

Use waveform symmetry and find the Fourier series coefficients for this periodic waveform.

a) Find a_v .

$a_v =$ ✓

Volts

b) Find a_k .

$a_k = ($ ✓

$V_m/\pi) \sin(k\pi/$ ✓ $)$ Volts for k odd

c) Find b_k .

$b_k =$ ✓

for all k

a) $a_v = 0$ V

b) $a_k = (4V_m/\pi) \sin(k\pi/2)$ Volts for k odd

c) $b_k = 0$ for all k


Correct

Marks for this submission: 11.00/11.00.

Question 2

Correct

Mark 11.00 out of 11.00

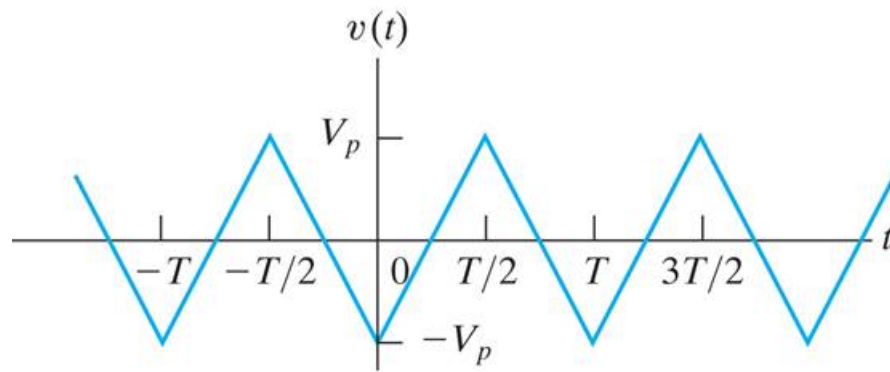

P16.13b_10ed

Use waveform symmetry and find the Fourier series coefficients for this periodic waveform.

Given over the time range zero to $T/2$.a) Find a_v .

$$a_v = \boxed{0} \checkmark$$

Volts

b) Find a_k .

$$a_k = \boxed{-8} \checkmark$$

 $V_m / (k\pi)^2$ Volts for k oddc) Find b_k .

$$b_k = \boxed{0} \checkmark$$

for all k


a) $a_v = 0$ Vb) $a_k = -8V_p / (k\pi)^2$ Volts for k oddc) $b_k = 0$ for all k**Correct**

Marks for this submission: 11.00/11.00.

Question 3

Correct

Mark 11.00 out of 11.00

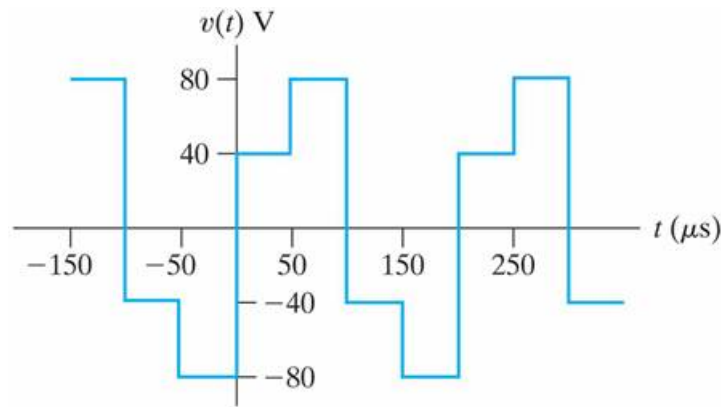

P16.19a_9ed

Given:

$$v(t) = -\frac{80}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin\left(\frac{\pi n}{2}\right) \cos(n\omega_0 t) + \frac{240}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin(n\omega_0 t)$$

Rewrite the Fourier Series for this waveform using the Alternative Trigonometric Form given by

$$f(t) = a_v + \sum_{n=1}^{\infty} A_n \cos(n\omega_0 t - \theta_n)$$

The alternate form is

For $n = 1, 5, 9, \dots$ $A_n =$ ✓/ $n\pi$ angle $\theta_n =$ ✓

° (Degrees, CW from the origin)

For $n = 3, 7, 11, \dots$ $A_n =$ ✓/ $n\pi$ and angle $\theta_n =$ ✓

° (Degrees, CW from the origin)

CW = Clock-wise

$$v(t) = -\frac{80}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin\left(\frac{\pi n}{2}\right) \cos(n\omega_0 t) + \frac{240}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin(n\omega_0 t)$$


Correct

Marks for this submission: 11.00/11.00.

Question 4

Correct

Mark 11.00 out of 11.00

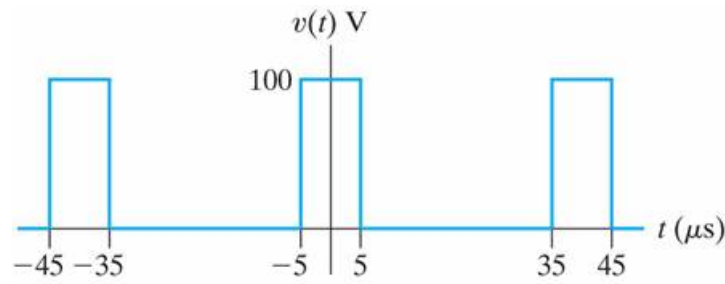

P16.19b_9ed

Given:

$$v(t) = 25 + \frac{200}{\pi} \sum_{n=1}^{\infty} \frac{1}{n} \sin\left(\frac{\pi n}{4}\right) \cos(n\omega_0 t) \text{ Volts}$$

The Fourier Series for this waveform using the Alternative Trigonometric Form given by

$$f(t) = a_v + \sum_{n=1}^{\infty} A_n \cos(n\omega_0 t - \theta_n)$$

Determine:

The average value $a_v =$ ✓

Volts

 $A_1 =$ ✓Volts and $\theta_1 =$ ✓ ° (Degrees) $A_2 =$ ✓Volts and $\theta_2 =$ ✓ ° (Degrees) $A_3 =$ ✓Volts and $\theta_3 =$ ✓ ° (Degrees) $A_4 =$ ✓Volts and $\theta_4 =$ ✓ ° (Degrees) $A_5 =$ ✓Volts and $\theta_5 =$ ✓ ° (Degrees)

$$v(t) = 25 + \frac{200}{\pi} \sum_{n=1}^{\infty} \frac{1}{n} \sin\left(\frac{\pi n}{4}\right) \cos(n\omega_0 t - 0^\circ) \text{ Volts}$$

 $A_1 = 45.0158$ Volts and $\theta_1 = 0^\circ$ $A_2 = 31.8310$ Volts and $\theta_2 = 0^\circ$ $A_3 = 15.0053$ Volts and $\theta_3 = 0^\circ$ $A_4 = 0$ (zero) Volts and $\theta_4 = 0^\circ$ $A_5 = -9.0032$ Volts and $\theta_5 = 0^\circ$


Correct

Marks for this submission: 11.00/11.00.

Question 5

Correct

Mark 11.00 out of 11.00

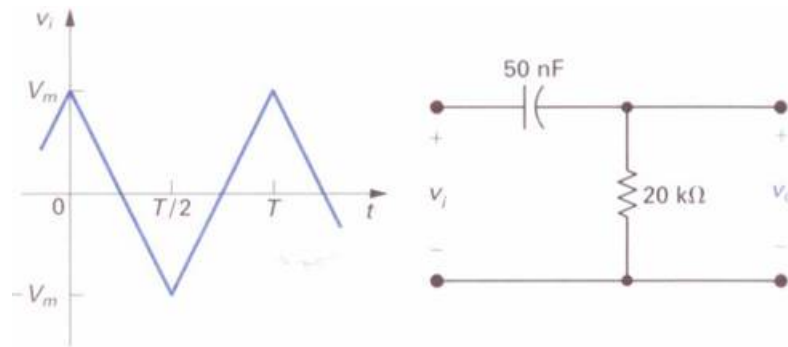

P16.23_6ed

Given: $v(t) = 450 \pi^2$ mV (milli V) with a period $T = 2\pi$ ms (milli sec) ($\pi = \text{pi}$).

The periodic triangular-wave voltage is applied to the circuit shown.

Find the circuit's response $v_o(t)$ by using the first three nonzero Fourier series terms.

You should be able to simplify the Fourier series to

$$v_{o,1}(t) = 2.545 \checkmark$$

$$\cos(1000 \checkmark t + 45 \checkmark^\circ) \text{ Volts}$$

$$v_{o,3}(t) = .38 \checkmark$$

$$\cos(3000 \checkmark t + 18.43 \checkmark^\circ) \text{ Volts}$$

$$v_{o,5}(t) = .141 \checkmark$$

$$\cos(5000 \checkmark t + 11.31 \checkmark^\circ) \text{ Volts}$$

$$v_{o,1}(t) = 2.5456\cos(1,000t + 45.0^\circ)$$

$$v_{o,3}(t) = 0.3795\cos(3,000t + 18.43^\circ) \text{ Volts}$$

$$v_{o,5}(t) = 0.1412\cos(5,000t + 11.31^\circ) \text{ Volts}$$

$$v(t) = 2.5456\cos(1,000t + 45.0^\circ) + 0.3795\cos(3,000t + 18.43^\circ) + 0.1412\cos(5,000t + 11.31^\circ) \text{ Volts}$$



Correct

Marks for this submission: 11.00/11.00.

Question 6

Correct

Mark 11.00 out of 11.00

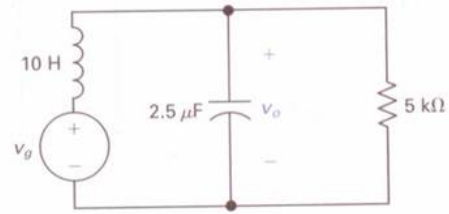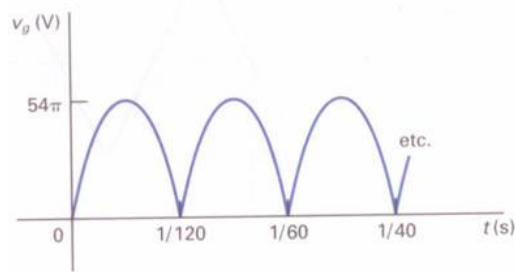

P16.27_6ed

The full-wave rectified sine-wave voltage is applied to the circuit shown.

Find the circuit's response $v_o(t)$ by using the first four nonzero Fourier series terms.

$$v_{0,avg}(t) = 108 \quad \checkmark$$

Volts

$$v_{0,1}(t) = 5.41 \quad \checkmark$$

$$\cos(240 \quad \checkmark \pi t + 6.51 \quad \checkmark ^\circ) \text{ Volts}$$

$$v_{0,2}(t) = .257 \quad \checkmark$$

$$\cos(480 \quad \checkmark \pi t + 3.08 \quad \checkmark ^\circ) \text{ Volts}$$

$$v_{0,3}(t) = .049 \quad \checkmark$$

$$\cos(720 \quad \checkmark \pi t + 2 \quad \checkmark ^\circ) \text{ Volts}$$

$$v_{0,avg}(t) = 108 \text{ Volts}$$

$$v_{0,1}(t) = 5.4143 \cos(240\pi t + 6.51^\circ) \text{ Volts}$$

$$v_{0,2}(t) = 0.2575 \cos(480\pi t + 3.09^\circ) \text{ Volts}$$

$$v_{0,3}(t) = 0.0486 \cos(720\pi t + 2.04^\circ) \text{ Volts}$$

$$v(t) = 108 + 5.4143 \cos(240\pi t + 6.51^\circ) + 0.2575 \cos(480\pi t + 3.09^\circ) + 0.0486 \cos(720\pi t + 2.04^\circ) \text{ Volts}$$


Correct

Marks for this submission: 11.00/11.00.

Question 7

Correct

Mark 11.00 out of 11.00

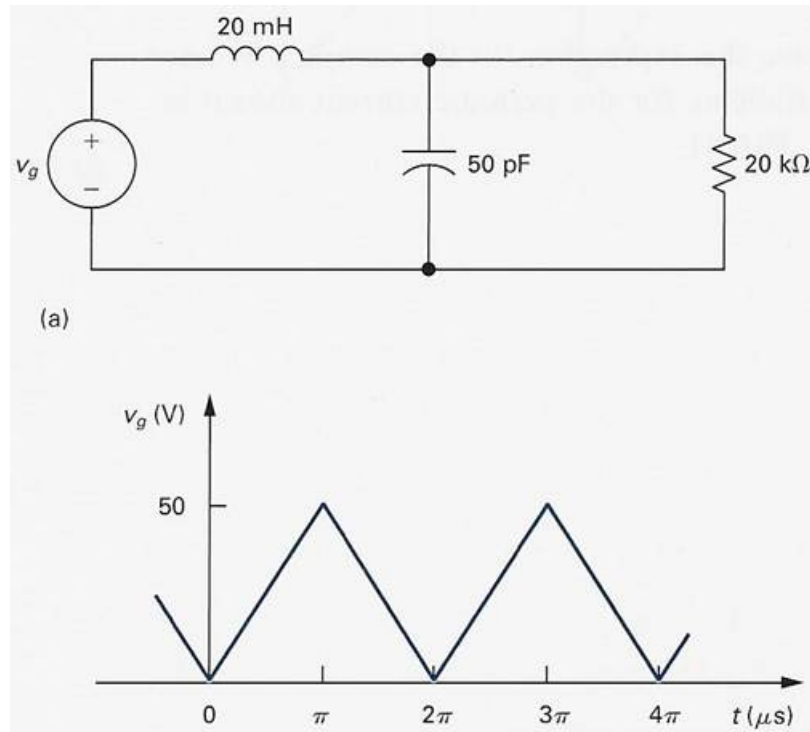

P16.38_6ed

The triangular-wave voltage source is applied to this circuit.

The equation for the function $= 50 \times 10^6 t / \pi$ for $0 \leq t \leq \pi\text{ }\mu\text{s}$ (micro sec)Estimate the average power delivered to the $20\text{ k}\Omega$ (kilo (Ohm) resistor) when the circuit is in steady-state operation.

$$P_{20\Omega, \text{steady-state}} = 41.64 \quad \checkmark$$

mW (milli W)

$$P_{20\Omega, \text{steady-state}} = 41.532\text{ mW}$$


Correct

Marks for this submission: 11.00/11.00.

Question 8

Correct

Mark 11.00 out of 11.00

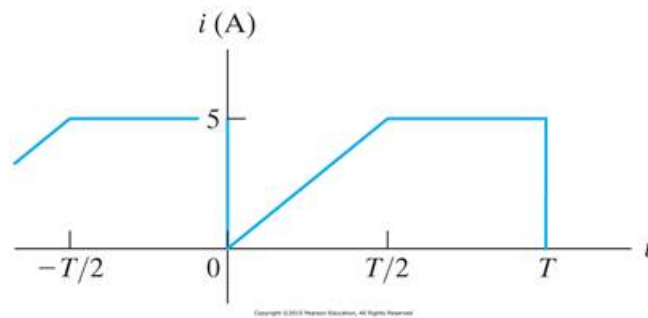

P16.33_10ed

The periodic current waveform is applied to a 2.5 k Ω (kilo Ohm) resistor.

Given: $i(t) = \frac{I_m}{T/2} t$ for $0 \leq t \leq T/2$ and $i(t) = I_m$ for $T/2 \leq t \leq T$ where $I_m = 5$ A

a) Use the first three nonzero terms in the Fourier Series representation of $i(t)$ to estimate the average power dissipated in the 2.5 k Ω (kilo Ohm) resistor.

$P_{2.5 \text{ k}\Omega, \text{estimate}} = 40.4$ ✓

kW (kilo Watt)

b) Calculate the exact value of the average power dissipated in the 2.5 k Ω (kilo Ohm) resistor. Hint: You must use the rms integral for the current waveform.

$P_{2.5 \text{ k}\Omega, \text{exact}} = 41.67$ ✓

kW (kilo Watt)

b) Calculate the exact value of the average power dissipated in the 2.5 k Ω (kilo Ohm) resistor.

% Error = -3.05 ✓

"-" under estimate "+" = over estimate

a) $P_{2.5 \text{ kW, estimate}} = 40.3974 \text{ kW}$

b) $P_{2.5 \text{ kW, exact}} = 41.6667 \text{ kW}$

c) % error = -3.046%


Correct

Marks for this submission: 11.00/11.00.

Question 9

Correct

Mark 12.00 out of 12.00

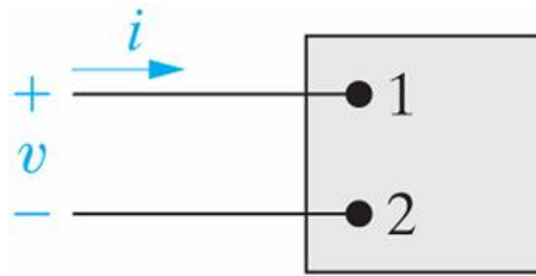

P16.35_6ed

The voltage and current at the terminals of this network are

$$v(t) = 80 + 200 \cos(500t + 45^\circ) + 60 \sin(1,500t) \text{ Volts}$$

$$i(t) = 10 + 6 \sin(500t + 75^\circ) + 3 \cos(1,500t - 30^\circ) \text{ Amps}$$

a) What is the average power at element's terminals?

$$P = 1145 \checkmark$$

W

b) What is the rms value of the voltage?

$$V_{\text{rms}} = 167.93 \checkmark$$

 V_{rms}

c) What is the rms value of the current?

$$I_{\text{rms}} = 11.06 \checkmark$$

 A_{rms} a) $P = 1,145 \text{ W}$ b) $V_{\text{rms}} = 167.9286 \text{ V}_{\text{rms}}$ c) $I_{\text{rms}} = 11.0680 \text{ I}_{\text{rms}}$ **Correct**

Marks for this submission: 12.00/12.00.